

ECE 523

Symmetrical Components

Session 27

$$Y_{\text{bus1_alt}} - Y_{\text{bus1}} = \begin{pmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{pmatrix}$$

$$Y_{\text{bus2}} := Y_{\text{bus1}}$$

- Now for zero sequence matrix. Now we need to include the zero sequence mutual coupling
 - It will be put into the Z_{pr0} matrix as off-diagonal terms
 - The sign of the off-diagonal terms depends on the sign of the associated links in the digraph (positive signs if the arrows point the same way and negative otherwise).

Mapping to digraph

$$Z_{\text{pr0M}} := \begin{pmatrix} Z_{\text{S0}} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Z_{\text{R0}} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{\text{0L1}} & Z_{\text{0M12}} & 0 & 0 & 0 \\ 0 & 0 & Z_{\text{0M12}} & Z_{\text{0L2}} & -Z_{\text{0M23}} & 0 & 0 \\ 0 & 0 & 0 & -Z_{\text{0M23}} & Z_{\text{0L3}} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & Z_{\text{0L4}} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Z_{\text{0L5}} \end{pmatrix} \begin{matrix} \text{a} \\ \text{b} \\ \text{c} \\ \text{d} \\ \text{e} \\ \text{f} \\ \text{g} \end{matrix}$$

The resulting screen with the data entered looks like this:

Mutual Impedances

Filter: Advanced ~ Mutual Impedance ~ Find... Remove Quick Filter ~ Options ~

Records ~ Set ~ Columns ~ f(x) ~ SORT ASCD

	L1 From Bus	L1 To Bus	L1 Ckt ID	L2 From Bus	L2 To Bus	L2 Ckt ID	Mutual R	Mutual X	L1 Mut. Start	L1 Mut. End	L2 Mut. Start	L2 Mut. End
1	1	2 1		1	5 1		0.06000	0.25580	0.000	1.000	0.000	0.800
2	2	3 1		1	5 1		0.01500	0.06390	0.000	0.333	0.800	1.000

per unit

- L1 From Bus, L1 To Bus, and L1 Ckt ID are the "From Bus" number, "To Bus" number, and circuit identifier for the first mutually coupled line
- L2 From Bus, L2 To Bus, and L2 Ckt ID are the "From Bus" number, "To Bus" number, and circuit identifier for the second mutually coupled line
- Mutual R and Mutual X are the per unit values from Z0M for the two lines in question, they were calculated in the other handout from last time.
 - Polarity dot is assumed to be at the From Bus for each line, so designate the lines based on this
- L1 Mutual Start and L1 Mutual End are the starting and end points for line 1, where 1.000 represents 100% of the line length
 - Program uses these for analyzing faults within the line section
- L2 Mutual Start and L2 Mutual End are the starting and end points for line 2, where 1.000 represents 100% of the line length
 - Program uses these for analyzing faults within the line section

127 3/18

and for later comparisons, the same matrix, with no mutual terms.

$$Z_{\text{pr0_noM}} := \begin{pmatrix} Z_{S0} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Z_{R0} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{0L1} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & Z_{0L2} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & Z_{0L3} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & Z_{0L4} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Z_{0L5} \end{pmatrix}$$

$$Y_{\text{bus0_M}} := A_{\text{incid}} \cdot Z_{\text{pr0M}}^{-1} \cdot A_{\text{incid}}^T$$

$$Y_{\text{bus0_NoM}} := A_{\text{incid}} \cdot Z_{\text{pr0_noM}}^{-1} \cdot A_{\text{incid}}^T$$

$$Y_{\text{bus0_M}} = \begin{pmatrix} 0.46 - 3.17i & -0.29 + 1.37i & 0.03 - 0.14i & 0 & -0.2 + 0.93i \\ -0.29 + 1.37i & 0.8 - 4i & -0.44 + 2.13i & 0 & -0.08 + 0.5i \\ 0.03 - 0.14i & -0.44 + 2.13i & 0.9 - 4.44i & -0.45 + 2.2i & -0.04 + 0.25i \\ 0 & 0 & -0.45 + 2.2i & 0.73 - 4.41i & -0.28 + 1.38i \\ -0.2 + 0.93i & -0.08 + 0.5i & -0.04 + 0.25i & -0.28 + 1.38i & 0.6 - 3.05i \end{pmatrix}$$

Matches Powerworld Matrix:

Name	Bus 1	Bus 2	Bus 3	Bus 4	Bus 5
BUS1	0.46 - j3.17	-0.29 + j1.37	0.03 - j0.14		-0.20 + j0.93
BUS2	-0.29 + j1.37	0.80 - j4.00	-0.44 + j2.13		-0.08 + j0.50
BUS3	0.03 - j0.14	-0.44 + j2.13	0.90 - j4.44	-0.45 + j2.20	-0.04 + j0.25
BUS4			-0.45 + j2.20	0.73 - j4.41	-0.28 + j1.38
BUS5	-0.20 + j0.93	-0.08 + j0.50	-0.04 + j0.25	-0.28 + j1.38	0.60 - j3.05

Case 2: With mutual coupling:

$$I_{0_M} := \frac{V_f}{Z_{Bus1_{4,4}} + Z_{Bus2_{4,4}} + Z_{0_M_{4,4}}}$$

$$I_{1_M} := I_{0_M} \quad I_{2_M} := I_{1_M}$$

$$I_{ABC_SLG_M} := A_{012} \cdot \begin{pmatrix} I_{0_M} \\ I_{1_M} \\ I_{2_M} \end{pmatrix}$$

$$|I_{0_M}| = 0.694 \text{ pu} \quad \arg(I_{0_M}) = -84.48 \cdot \text{deg}$$

$$\overrightarrow{|I_{ABC_SLG_M}|} = \begin{pmatrix} 2.081 \\ 0 \\ 0 \end{pmatrix} \quad \overrightarrow{\arg(I_{ABC_SLG_M})} = \begin{pmatrix} -84.48 \\ 13.173 \\ 13.173 \end{pmatrix} \cdot \text{deg}$$

- Very close match to Powerworld results

$$\Delta V_{1_M} := Z_{Bus1} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{1_M} \end{pmatrix}$$

$$V_{1_M} := \begin{pmatrix} 1.0 \\ 1.0 \\ 1.0 \\ 1.0 \\ 1.0 \end{pmatrix} + \Delta V_{1_M}$$

$$\overrightarrow{|V_{1_M}|} = \begin{pmatrix} 0.885 \\ 0.882 \\ 0.879 \\ 0.877 \\ 0.809 \end{pmatrix}$$

$$\overrightarrow{\arg(V_{1_M})} = \begin{pmatrix} -0.777 \\ -0.746 \\ -0.722 \\ -0.699 \\ 0.431 \end{pmatrix} \cdot \text{deg}$$

Same as usual

127 5/18

$$\begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{2_M} \end{pmatrix}$$

$$\Delta V_{2M} := Z_{Bus2} \cdot$$

$$V_{2M} := \Delta V_{2M}$$

$$\begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{0_M} \end{pmatrix}$$

$$\Delta V_{0M} := Z_{0_M} \cdot$$

$$V_{0M} := \Delta V_{0M}$$

$$\begin{pmatrix} V_{0M_0} \\ V_{1M_0} \\ V_{2M_0} \end{pmatrix}$$

$$V_{ABC_B1_M} := A_{012} \cdot$$

$$\overrightarrow{|V_{ABC_B1_M}|} = \begin{pmatrix} 0.4253 \\ 1.1558 \\ 1.1159 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(V_{ABC_B1_M})} = \begin{pmatrix} -8.412 \\ -129.471 \\ 131.182 \end{pmatrix} \cdot \text{deg}$$

$$\begin{pmatrix} V_{0M_1} \\ V_{1M_1} \\ V_{2M_1} \end{pmatrix}$$

$$V_{ABC_B2_M} := A_{012} \cdot$$

$$\overrightarrow{|V_{ABC_B2_M}|} = \begin{pmatrix} 0.3423 \\ 1.1973 \\ 1.1708 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(V_{ABC_B2_M})} = \begin{pmatrix} -8.838 \\ -132.399 \\ 133.597 \end{pmatrix} \cdot \text{deg}$$

approach
same

L27 6/18

Compare to Powerworld

Voltage match

Name	Phase Volt A	Phase Volt B	Phase Volt C	Phase Ang A	Phase Ang B	Phase Ang C
BUS1	0.4253	1.15581	1.11585	-8.41	-129.47	131.18
BUS2	0.34229	1.19733	1.17075	-8.84	-132.4	133.6
BUS3	0.33257	1.19963	1.17171	-9.06	-132.45	133.71
BUS4	0.3491	1.18713	1.15225	-9.17	-131.47	133.02
BUS5	0	1.28049	1.25553	0	-136.32	137.53

- First get the positive and negative sequence currents in each of the three branches involved in the mutual coupled lines

$$I_{1_L1_M} := \frac{V1_{M0} - V1_{M1}}{Z_{1L1}}$$

$$|I_{1_L1_M}| = 0.019 \quad \arg(I_{1_L1_M}) = -79.972 \cdot \text{deg}$$

$$I_{2_L1_M} := \frac{V2_{M0} - V2_{M1}}{Z_{1L1}}$$

$$|I_{2_L1_M}| = 0.019 \quad \arg(I_{2_L1_M}) = -79.972 \cdot \text{deg}$$

$$I_{1_L2_M} := \frac{V1_{M0} - V1_{M4}}{Z_{1L2}}$$

$$|I_{1_L2_M}| = 0.366 \quad \arg(I_{1_L2_M}) = -84.241 \cdot \text{deg}$$

$$I_{2_L2_M} := \frac{V2_{M0} - V2_{M4}}{Z_{1L2}}$$

$$|I_{2_L2_M}| = 0.366 \quad \arg(I_{2_L2_M}) = -84.241 \cdot \text{deg}$$

pos sequence
neg sequence
same
approx
equal

ECE 523:
Symmetrical Components

$$I_{1_L3_M} := \frac{V1_{M1} - V1_{M2}}{Z_{1L3}}$$

$$|I_{1_L3_M}| = 0.019 \cdot \text{pu} \quad \arg(I_{1_L3_M}) = -79.972 \cdot \text{deg}$$

$$I_{2_L3_M} := \frac{V2_{M1} - V2_{M2}}{Z_{1L3}}$$

$$|I_{2_L3_M}| = 0.019 \cdot \text{pu} \quad \arg(I_{2_L3_M}) = -79.972 \cdot \text{deg}$$

- The zero sequence calculation is little more tricky. This is based on equation 12.19 in the text book
- We need terms from the matrix of impedance primitives, recall:

$$Z_{\text{pr0M}} := \begin{pmatrix} Z_{S0} & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Z_{R0} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{0L1} & Z_{0M12} & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{0M12} & Z_{0L2} & -Z_{0M23} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -Z_{0M23} & Z_{0L3} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Z_{0L4} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & Z_{0L5} \end{pmatrix}$$

We need the 3x3 block in the middle of the matrix.

$$Z_{\text{mutual0}} := \text{submatrix}(Z_{\text{pr0M}}, 2, 4, 2, 4) \quad Z_{\text{mutual0}} = \begin{pmatrix} 0.118 + 0.582i & 0.06 + 0.256i & 0 \\ 0.06 + 0.256i & 0.142 + 0.698i & -0.015 - 0.064i \\ 0 & -0.015 - 0.064i & 0.089 + 0.436i \end{pmatrix}$$

Mutual Coupling in Fault Analysis

$$\text{MVA} := 1000\text{kW}$$

$$j \cdot \frac{2 \cdot \pi}{3}$$

$$\text{pu} := 1$$


$$a := 1 \cdot e$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

$$S_{\text{base}} := 100\text{MVA} \quad V_{\text{base}} := 138\text{kV}$$

$$Z_{\text{base}} := \frac{V_{\text{base}}^2}{S_{\text{base}}} = 190.44 \Omega$$
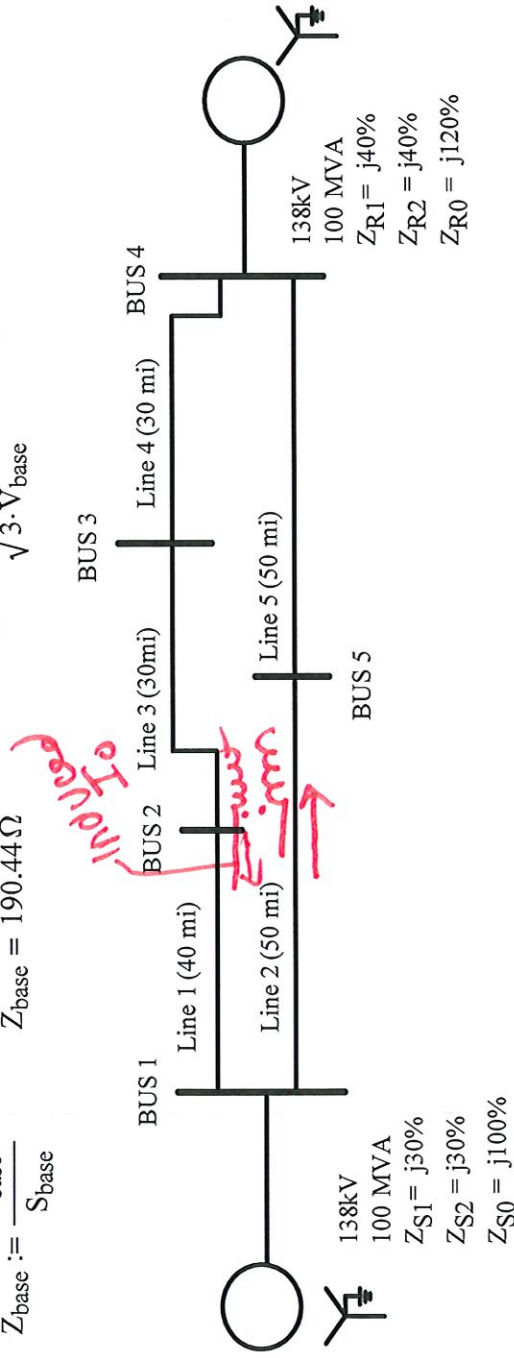
$$I_{\text{base}} := \frac{S_{\text{base}}}{\sqrt{3} \cdot V_{\text{base}}} = 418.37\text{A}$$



- Source impedances:
 - $Z_{S1} := j \cdot 0.3\text{pu}$
 - $Z_{S0} := j \cdot 1.0\text{pu}$
 - $Z_{R1} := j \cdot 0.4\text{pu}$
 - $Z_{R0} := j \cdot 1.2\text{pu}$
- Line impedances from lecture 32 handout:
 - Line 1, 40 mile length

$$\begin{pmatrix} I_{0_L1_M} \\ I_{0_L2_M} \\ I_{0_L3_M} \end{pmatrix} := Z_{\text{mutual0}}^{-1} \cdot \begin{pmatrix} V0_{M0} - V0_{M1} \\ V0_{M0} - V0_{M4} \\ V0_{M2} - V0_{M1} \end{pmatrix}$$

Back to the graph...

- Note sign on $I_{0_L3_M}$, dot polarity

$$I_{ABC_L1_M} := A_{012} \cdot \begin{pmatrix} I_{0_L1_M} \\ I_{1_L1_M} \\ I_{2_L1_M} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L1_M}|} = \begin{pmatrix} 0.013 \\ 0.0669 \cdot \text{pu} \\ 0.0669 \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L1_NoM}|} = \begin{pmatrix} 0.0487 \\ 0.007 \cdot \text{pu} \\ 0.007 \end{pmatrix}$$

$$I_{ABC_L2_M} := A_{012} \cdot \begin{pmatrix} I_{0_L2_M} \\ I_{1_L2_M} \\ I_{2_L2_M} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L2_M}|} = \begin{pmatrix} 1.1325 \\ 0.0336 \cdot \text{pu} \\ 0.0336 \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L2_NoM}|} = \begin{pmatrix} 1.0853 \\ 0.0073 \cdot \text{pu} \\ 0.0073 \end{pmatrix}$$

$$\arg(I_{0_L1_M}) = 90.677 \cdot \text{deg}$$

$$\arg(I_{0_L2_M}) = -84.435 \cdot \text{deg}$$

$$\arg(-I_{0_L3_M}) = 90.677 \cdot \text{deg}$$

$$\overrightarrow{\arg(I_{ABC_L1_M})} = \begin{pmatrix} 62.941 \\ 93.277 \cdot \text{deg} \\ 93.277 \end{pmatrix}$$

$$\overrightarrow{\arg(I_{ABC_L1_NoM})} = \begin{pmatrix} -80.275 \\ 102.864 \cdot \text{deg} \\ 102.864 \end{pmatrix}$$

$$\overrightarrow{\arg(I_{ABC_L2_M})} = \begin{pmatrix} -84.309 \\ -86.547 \cdot \text{deg} \\ -86.547 \end{pmatrix}$$

$$\overrightarrow{\arg(I_{ABC_L3_NoM})} = \begin{pmatrix} -80.275 \\ 102.864 \cdot \text{deg} \\ 102.864 \end{pmatrix}$$

*200 separate the with
current for each phase
three mutually coupled
lines*

un-faulted

faulted line

L27 9/18

Underground/Undersea Cables

Built from single core cables

• circuit model for fault analysis --



→ use standard 60Hz/50Hz models

~~polyethylene~~
polyethylene

insulating
cable
2-2-2-5



"short line"

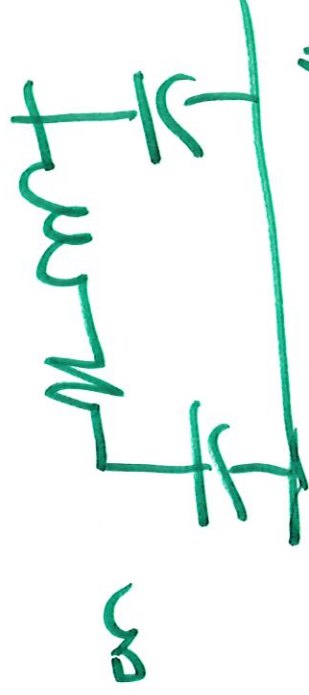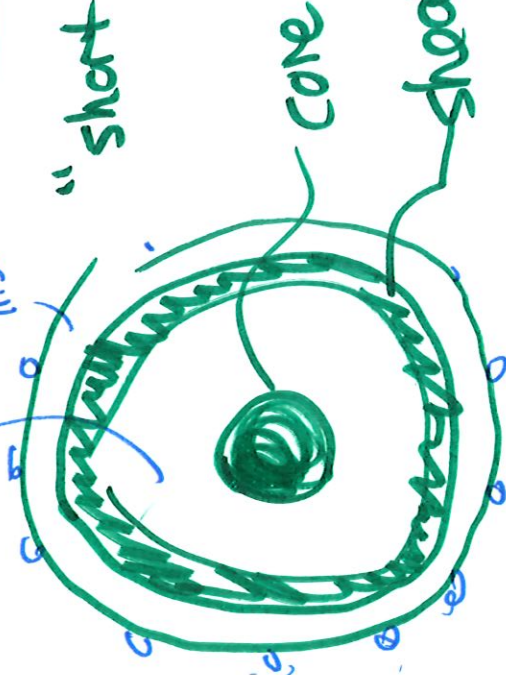


"medium line"


- for power flow, use
for lines over
15 km

cross linked polyethylene


XLPE

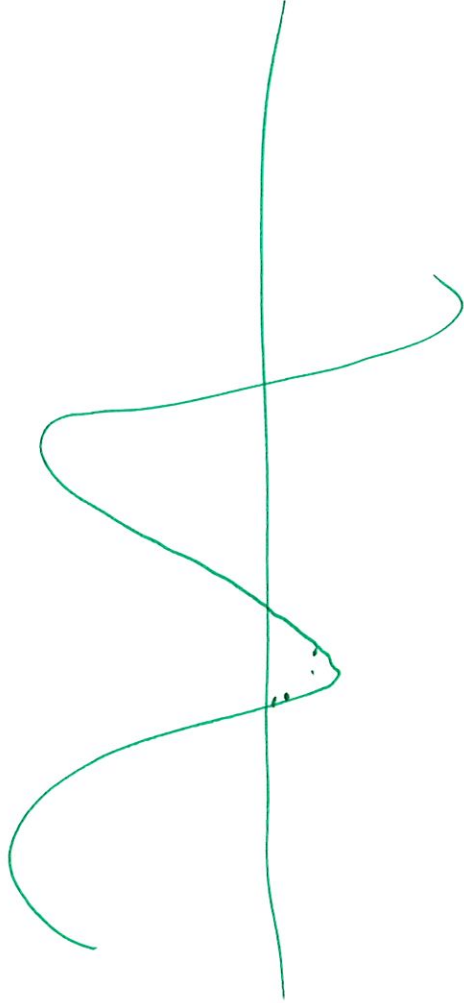


3Q Designs

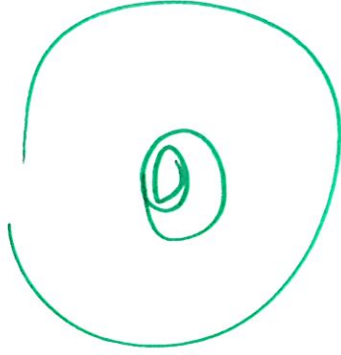


A

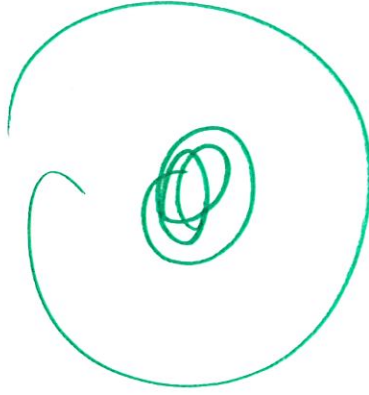



B

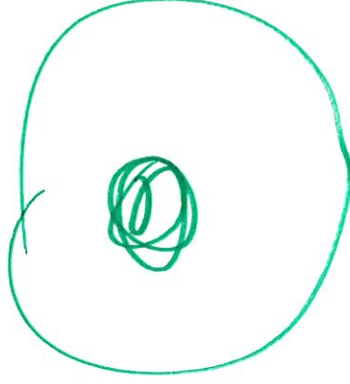

C

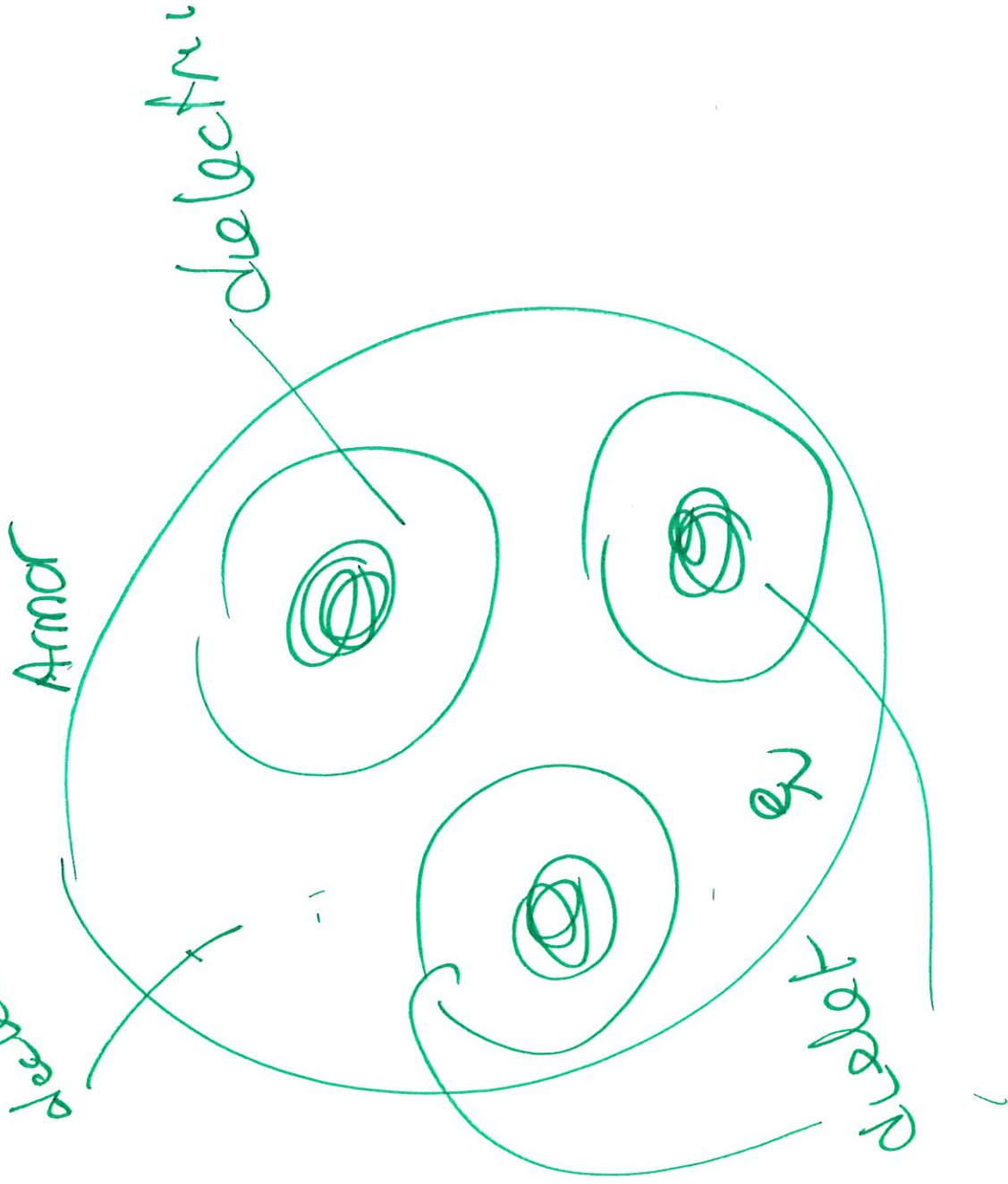


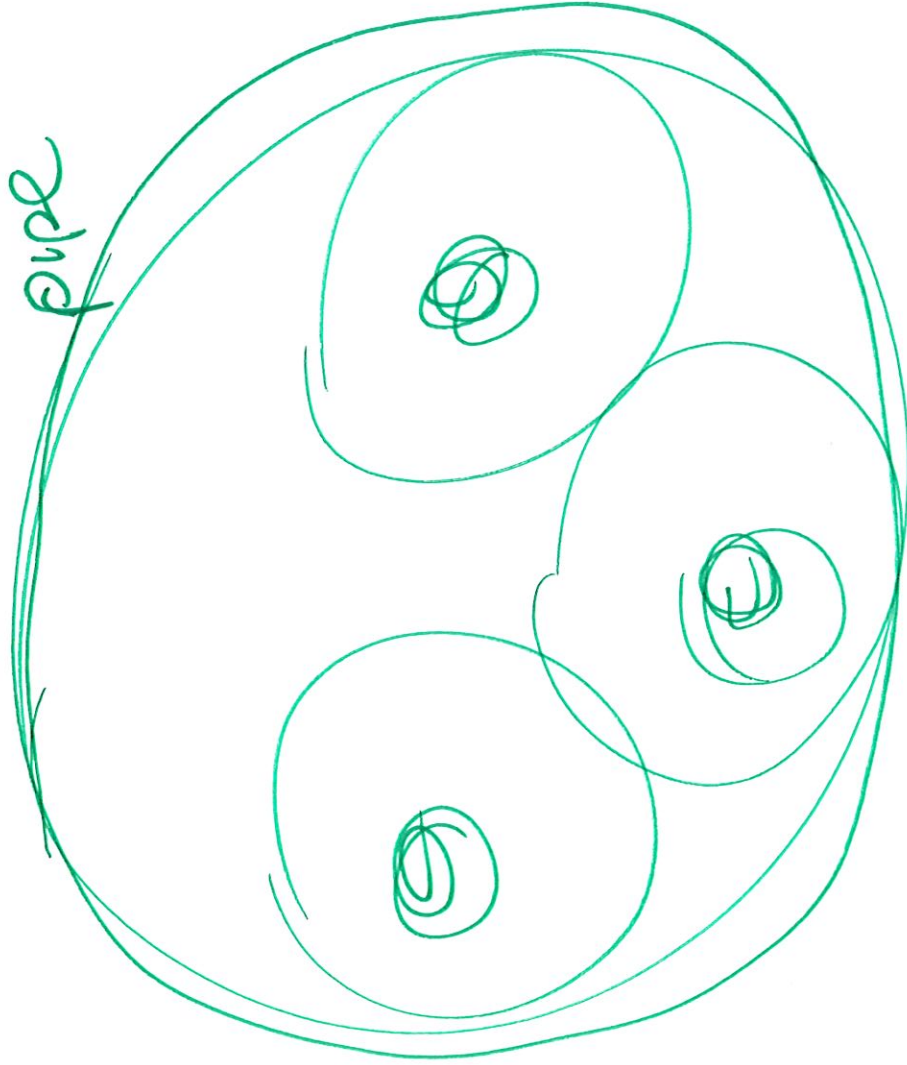

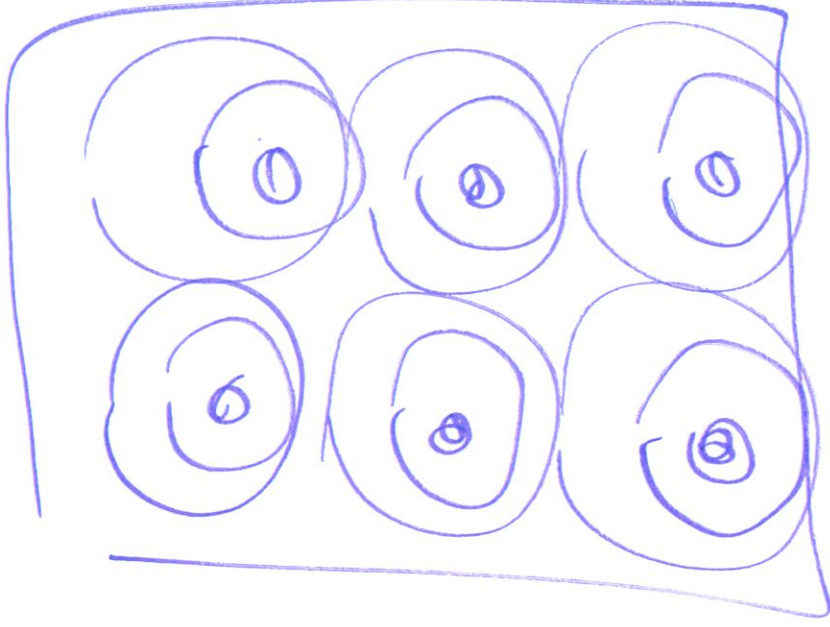

Sheath - cross bonding

sheath A

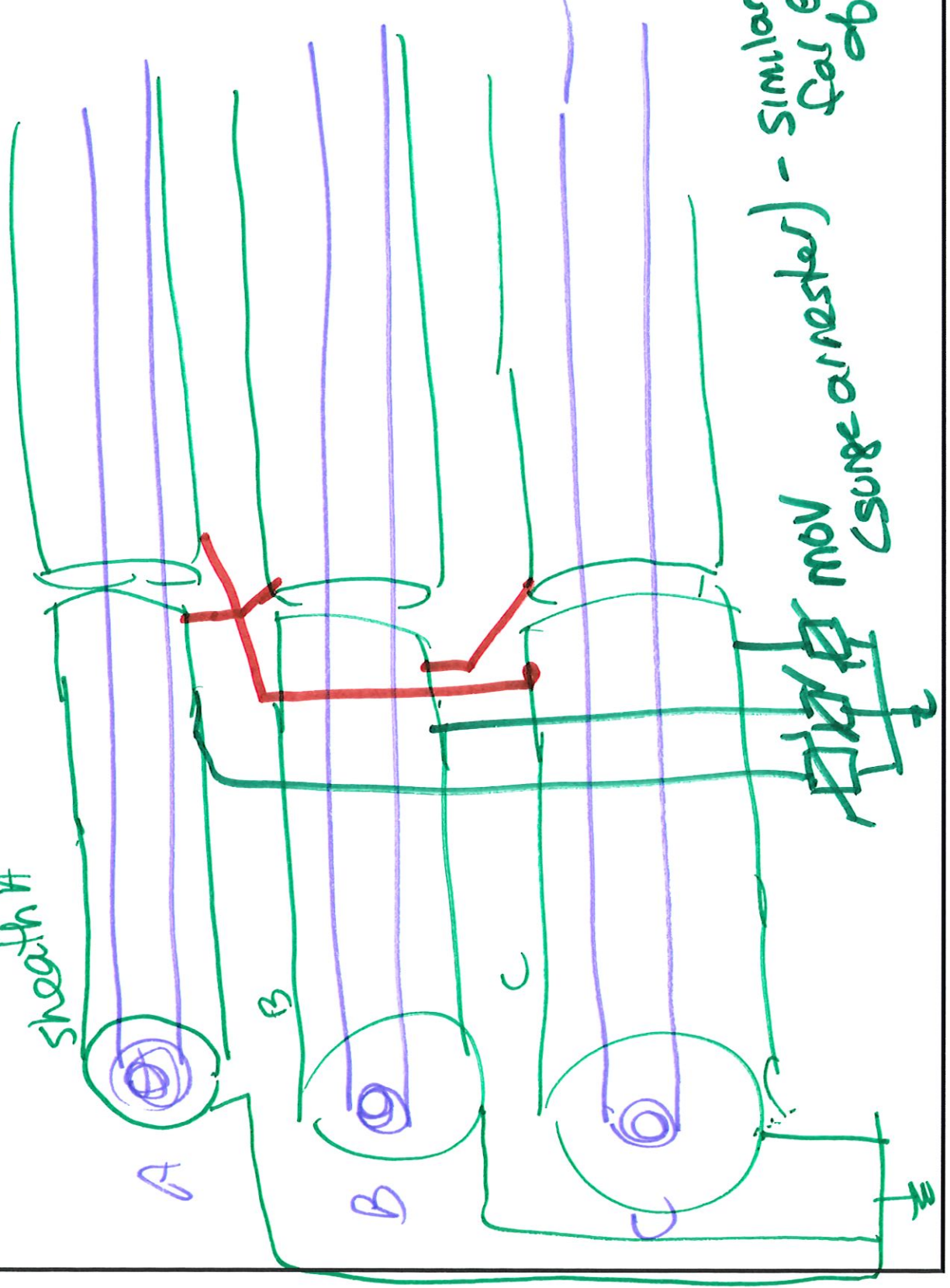

Cable sequence impedances

- Best option - if available

→ get data from
manufacturer

→ ABC


→ OIZ

Calculating L, C, R per unit length

R → from data sheets

RAC
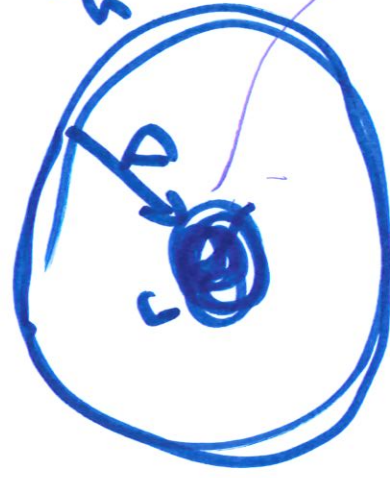
$$L_{\text{core}} = \frac{20}{2\pi} \ln \left(\frac{D}{GMR} \right)$$



sheath

Geometric

mean radius

outer radius of core

$$D = R_2 - R_1$$

inner radius of sheath

