

Winding Impedance calculations for three winding autotransformer

$$\text{MVA} := 1000\text{kW} \quad \text{pu} := 1$$

Useful Constants V_1 is l-l since will be in Delta

$$V_h := \frac{525 \cdot \text{kV}}{\sqrt{3}} \quad V_m := \frac{241.5 \cdot \text{kV}}{\sqrt{3}} \quad V_1 := 34.5 \cdot \text{kV} \quad S_b := 100 \cdot \text{MVA}$$

Test Impedances, found at bases listed next to numbers (in percent), Note Z_{hm} and Z_{hl} are reversed from the other cases

$$X_{hm} := 7.94\% \quad 448 \text{ MVA}$$

$$X_{hl} := 3.46\% \quad 25 \text{ MVA}$$

$$X_{ml} := 2.98\% \quad 25 \text{ MVA}$$

Convert test impedances to 100 MVA Base (answers still in percent), based on the data from data sheets regarding H/L and H/M

$$X_{hl\text{new}} := \frac{100}{25} \cdot X_{hl} \quad X_{hl\text{new}} = 0.138 \cdot \text{pu}$$

$$X_{hm\text{new}} := \frac{100}{448} \cdot X_{hm} \quad X_{hm\text{new}} = 0.018 \cdot \text{pu}$$

$$X_{ml\text{new}} := \frac{100}{25} \cdot X_{ml} \quad X_{ml\text{new}} = 0.119 \cdot \text{pu}$$

Find X_h , X_m , and X_l

$$X_h := (0.5) \cdot (X_{hl\text{new}} + X_{hm\text{new}} - X_{ml\text{new}}) \quad X_h = 1.846\%$$

$$X_m := (0.5) \cdot (X_{hm\text{new}} + X_{ml\text{new}} - X_{hl\text{new}}) \quad X_m = -0.074\%$$

$$X_l := (0.5) \cdot (X_{ml\text{new}} + X_{hl\text{new}} - X_{hm\text{new}}) \quad X_l = 11.994\%$$

- Autotransformer specific extension:

$$\text{Define a constant: } r := \frac{(V_h - V_m)}{V_h} \quad r = 0.54$$

- Given X_h , X_m and X_l , find the physical transformer winding reactances

$$X_s := \left(\frac{1}{r}\right)^2 \cdot X_h + \frac{(1-r)}{r^2} \cdot X_m \quad X_s = 6.215\%$$

$$X_c := \left(\frac{1}{r}\right) \cdot X_m \quad X_c = -0.137\%$$

$$X_t := X_l - \frac{1-r}{r} \cdot X_m \quad X_t = 12.057\%$$

- Alternate conversion:

$$X_{s_c} := X_{hmnew} \cdot \left(\frac{V_h}{V_h - V_m}\right)^2 \quad X_{s_c} = 6.078\%$$

$$X_{c_t} := X_{mlnew} \quad X_{c_t} = 11.92\%$$

$$X_{s_t} := X_{hmnew} \cdot \left[\frac{V_h \cdot V_m}{(V_h - V_m)^2}\right] + X_{hlnew} \cdot \left(\frac{V_h}{V_h - V_m}\right) - X_{mlnew} \cdot \left(\frac{V_m}{V_h - V_m}\right)$$

$$X_{s_t} = 18.271\%$$

$$X_s := 0.5 \cdot (X_{s_c} + X_{s_t} - X_{c_t}) \quad X_s = 6.215\%$$

$$X_c := 0.5 \cdot (X_{s_c} + X_{c_t} - X_{s_t}) \quad X_c = -0.137\%$$

$$X_t := 0.5 \cdot (X_{c_t} + X_{s_t} - X_{s_c}) \quad X_t = 12.057\%$$

- If instead you are given the physical transformer reactances, you can do the following to find X_h , X_m and X_l .

$$n := \left(\frac{V_h}{V_m} \right) \quad \bullet \quad \text{Note that this is the voltage ratio of the autotransformer}$$

$$X_{m_auto} := \left(\frac{n-1}{n} \right) \cdot X_c \quad X_{m_auto} = -0.074\%$$

above we had: $X_m = -0.074\%$

$$X_{l_auto} := X_t + \frac{X_c}{n} \quad X_{l_auto} = 11.994\%$$

above we had $X_l = 11.994\%$

$$X_{h_auto} := \left(\frac{n-1}{n} \right)^2 \cdot X_s - \left(\frac{n-1}{n^2} \right) \cdot X_c \quad X_{h_auto} = 1.846\%$$


above we had $X_h = 1.846\%$

- Suppose this 3 winding transformer is grounded through an impedance of 0.1 pu (on the MVA base used for X_{hl}), calculate the new zero sequence equivalent circuit

$$X_{n_new} := 0.1 \text{ pu} \cdot \frac{100}{25} \quad X_{n_new} = 40\%$$

as above: $n := \left(\frac{V_h}{V_m} \right)$
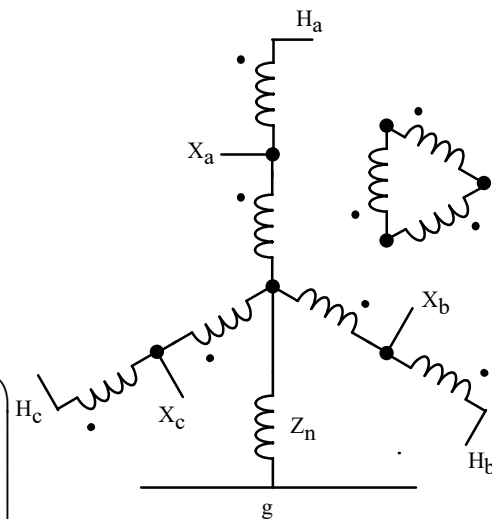
$$X_{hmn0}(Z_n) := \frac{1}{2} \cdot \begin{bmatrix} 1 & 1 & -1 & \frac{-(n-1)}{n^2} \\ 1 & -1 & 1 & \frac{(n-1)}{n} \\ -1 & 1 & 1 & \frac{1}{n} \end{bmatrix} \cdot \begin{pmatrix} X_{hmnew} \\ X_{hlnew} \\ X_{mlnew} \\ 6 \cdot Z_n \end{pmatrix}$$



$$X_{hmn0}(X_{n_new}) = \begin{pmatrix} -27.962 \\ 64.726 \\ 67.194 \end{pmatrix} \cdot \%$$


Note that if $X_n=0$, this gives the identical results to part (a)

$$X_{hmn0}(0) = \begin{pmatrix} 1.846 \\ -0.074 \\ 11.994 \end{pmatrix} \cdot \%$$

And if X_n is infinity (ungrounded)

$$X_{hmn0}(10^{10}) = \begin{pmatrix} -7.452 \times 10^9 \\ 1.62 \times 10^{10} \\ 1.38 \times 10^{10} \end{pmatrix}$$

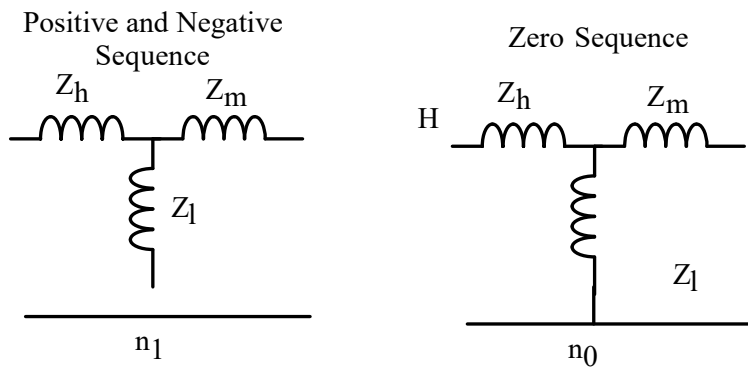- Symmetrical Components Equivalent Circuits for $X_n=0$



Zero sequence circuit with X_n non-zero

