


ECE 523  
Symmetrical Components

Session 30

# Synch machine

Pos Sequence fault response

# is time varying

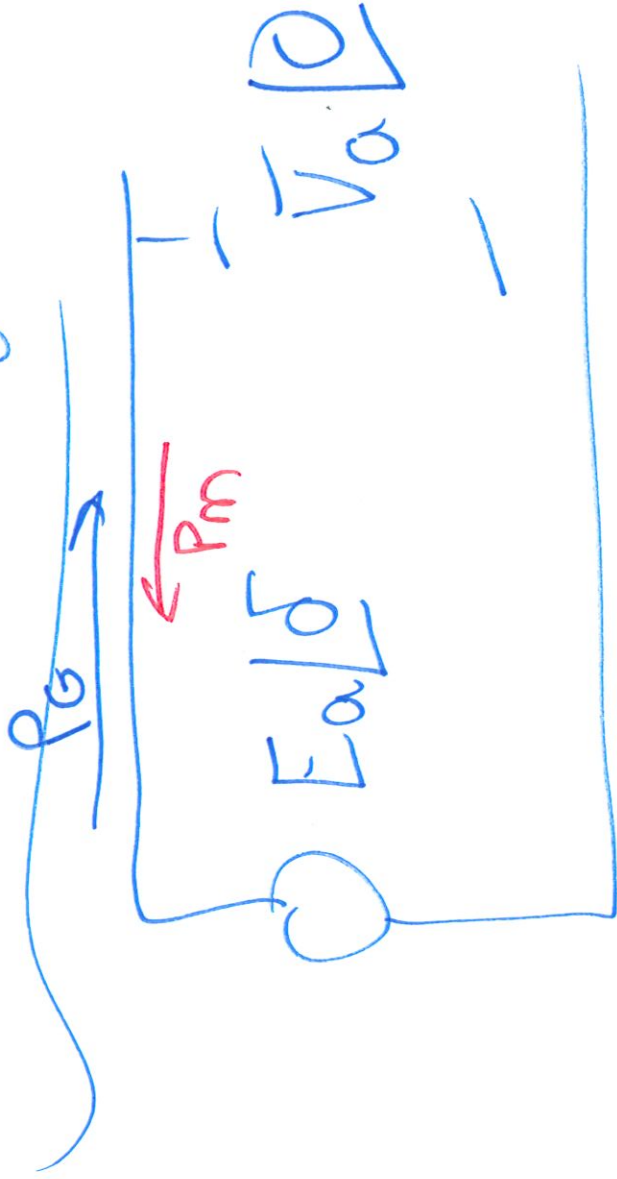


# Induction Machines

## fault studies

positive seq


$$jX_d'' \leq I_{motor}$$

$X_{locked Rotor}$

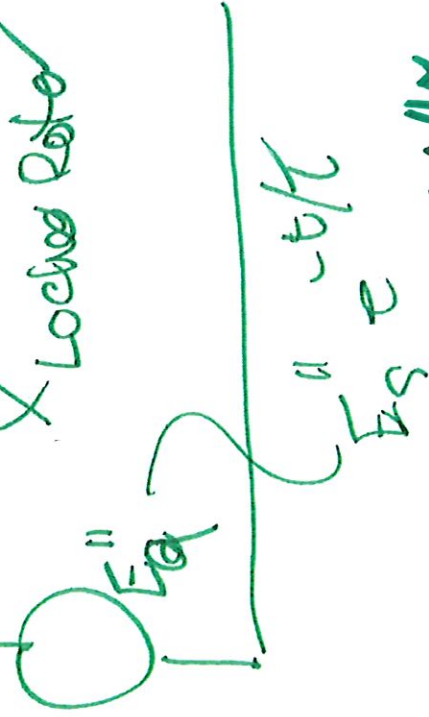


$$X_d'' = X_s + X_r$$

Steinmetz mode

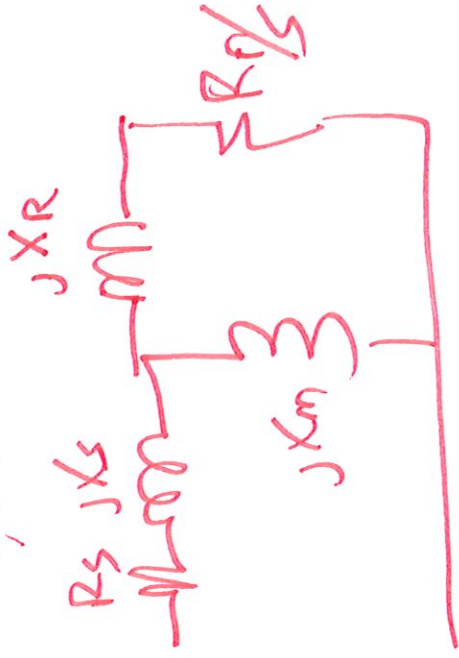

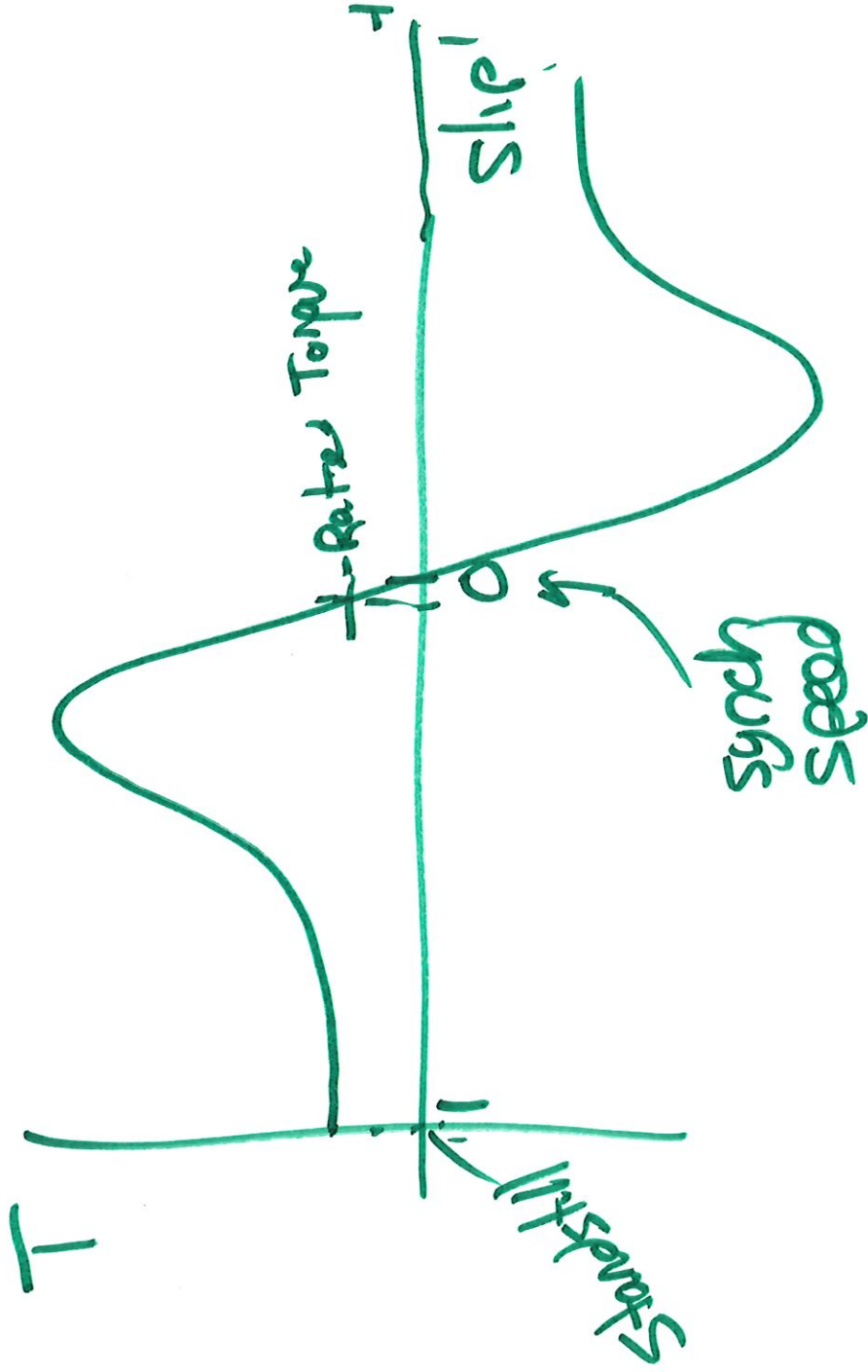- motor operation  
- slip is positive
- generator  
- slip negative



# Negative sequence

approx.

$$\frac{jX_d''}{s} \left[ X_s + jX_r \right]$$

more accurate  
- calculate pre-fault

slip

$$\frac{jX_d''}{s} \left[ \frac{Pr}{2-s} \right]$$

$$\left[ \frac{Pr}{2-s} \right]$$



Pre-fault current

$P_{out} \rightarrow$  shaft power  
HP

$$\eta = 95\%$$

rated pf 0.85 lagging  
rated speed or rated slip

$$P = T \cdot \omega_r$$

~~Shaft~~ Power HP  $\rightarrow \omega$

$$114P \approx 74600$$

$$\approx \underline{1214A}$$

$$S_{\text{rated}} = \frac{\text{Power}(\omega)}{\text{PF} - \gamma} \left\langle \cos^{-1}(\text{PF}) \right\rangle$$


$$S_{\text{pu}} = \overline{V}_{\text{pu}} \cdot \overline{I}_{\text{pu}}^* \quad \text{on system base}$$

→ can find current



# Adjustable Speed motor drives


most common type

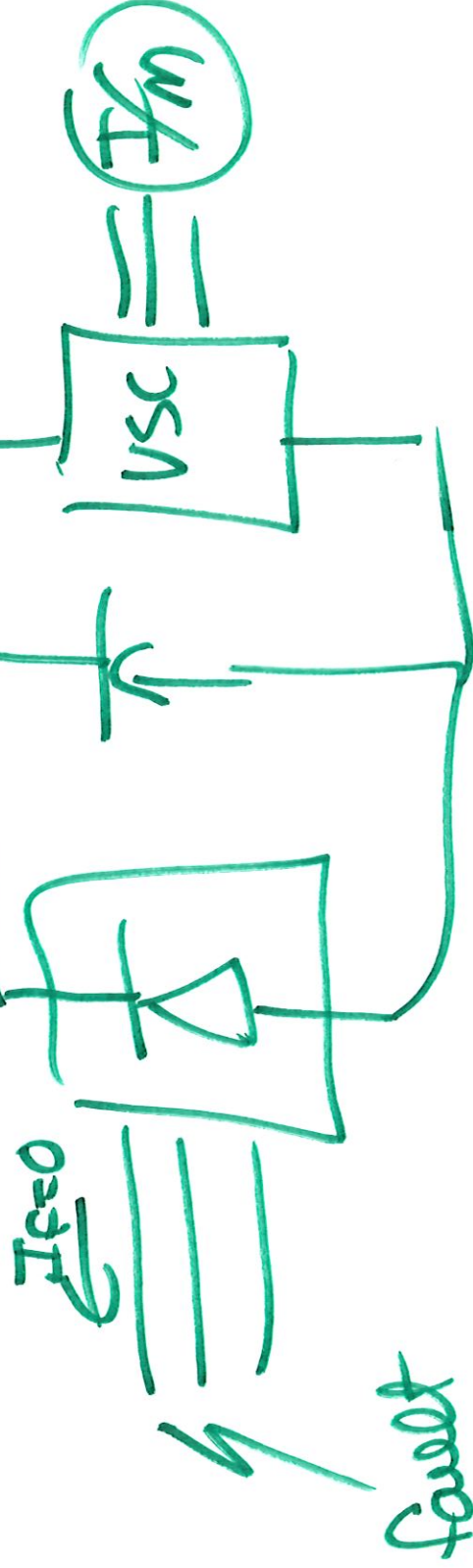



# Regenerative Motor drives

- newer types

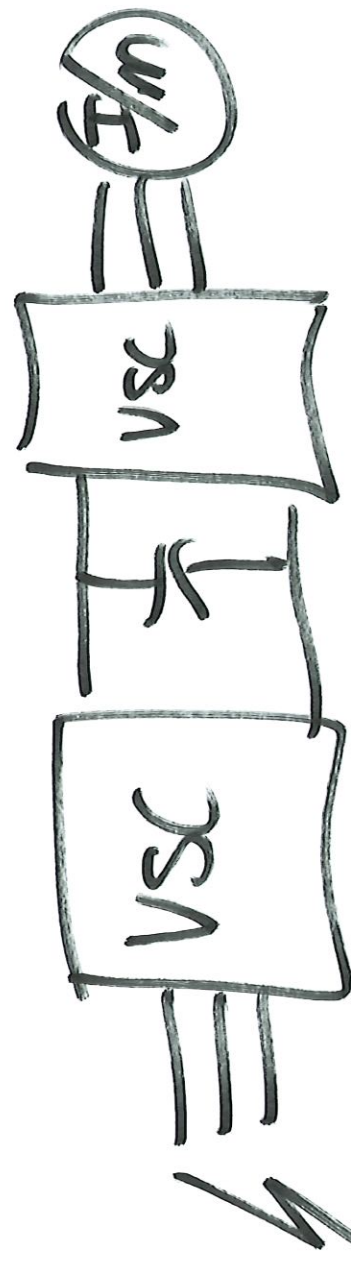

Fault  $\leftarrow$  supplies controlled fault current } some programmed to only draw current  
 }

some can supply limited current  
 - limited to  $\approx I_{rated}$

# - Inverter Based Grid Following Generation & Storage

- Type 3 & Type 4 wind turbine

- Photovoltaic Inverters

- Batteries, ultracapacitors, Flywheel ---

↳ controlled as grid forms converter (increasing trend)

→ All controlled to track grid frequency/angle with fast time

constant

↳ good for getting maximum power from resource

# Grid Following

- fault response?

(disturbance response)

- track change in angle with time  
consistent of a few ms.

→ fast current control

→ limit max SS to 1.1 → 1.4 pu

→ many calculate  $|I_{ref}| = \frac{P}{|V|}$

current reference limit ← on  $\frac{Q}{|V|}$

→ about 1 → 2 cycles to settle to steady state

fault current angle?

- $\cos$  like  $S/m$
- angle depends on controls
- Initially pre-fault  $\text{pf}$ 
  - If  $\cos$   $\text{pf}$  pre-fault, will be  $\cos$   $\text{pf}$  in steady-state faulted case
- For low voltage ride through requirement
  - may provide  $\text{Q}$  to improve performance
  - $I$  leads  $V$



# Zero sequence

open in converter

→ transformer dominates





# Negative Sequence

→ Older converters

→ Either regulated phase

current → don't control  $I_2$

but stays essentially 0

→ Intentionally regulate  $I_2 = 0$

→ New cases - especially at transmission level.

IEEE 2800, or Grid Codes (Europe especially)

require supply  $|I_2|$  as percentage of  $|I_1|$  and angle relative to  $V_2$

Summary: Grd Follow. M

pos sequence  $\rightarrow$  current source  
with regulated  
magnitude & angle

Negative sequence  
 $\rightarrow$  either (1)  $\bar{I}_2 = 0$   
(open)

(2) current source  
with regulated  
 $|I_2|$  & angle

Zero  $\rightarrow$  converter open  
 $\rightarrow$  transformer connection


# Fault analysis

→ need superposition  
of voltage source driven  
currents (what we've done  
all semester) & current sources

→ Section 7.6 - simple circuits

Section 7.2 → matrix. ✓

# 3 winding transformers

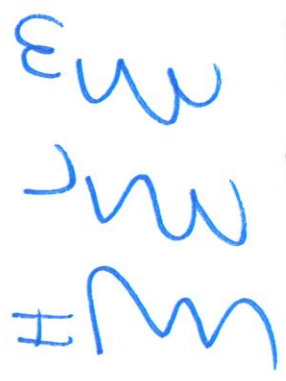

Primary  
Secondary

Short circuit data  
on XFMR model


$X_{HM}$  → voltage applied "at H, M shorted"  
L open

$X_{HL}$   
 $X_{ML}$


per unit

- L winding on MVA base of that winding



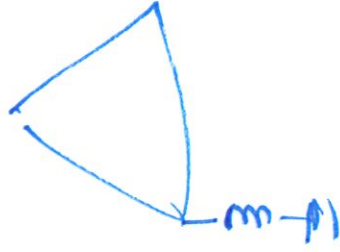

Pos & negative

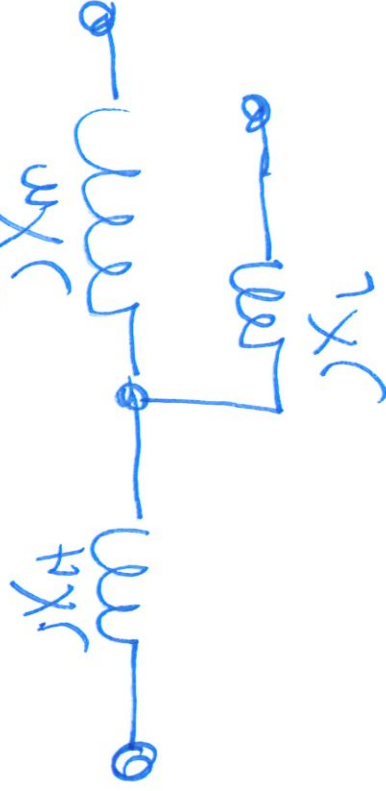

Zero (depends on connection)

