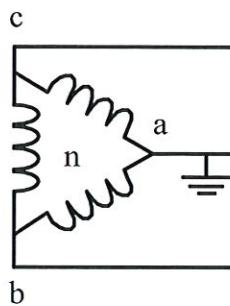


ECE 523
Symmetrical Components
Session 6

1/16
LG


5. The ungrounded system below has a phase to ground fault on phase "a". Assume that the line to ground (and line to neutral voltages) were balanced three phase set before the fault occurred. Do the following:

- Find the symmetrical components of the phase a line-to-neutral voltages when a ground fault is applied (V_{an0} , V_{an1} , V_{an2}).
- Repeat part (a) using line to ground voltages instead of the line to neutral voltages and find (V_{ag0} , V_{ag1} , V_{ag2}).



6. Do the following:

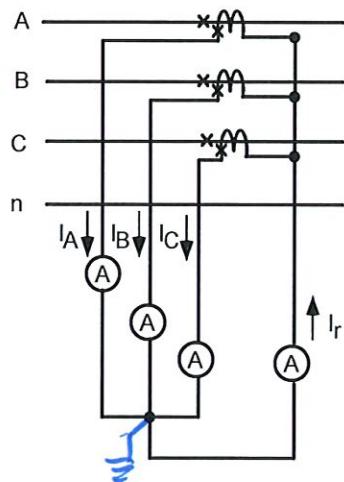- (a) A set of current transformers reads the following currents (in Amperes). If the current transformers each have a turns ratio of 5:500 (usually referred to as a current transformation ratio or CTR of 500:5) calculate the primary currents in amps.



Note that the symbol: is equivalent to:
 SOURCE LINE
 SPA SECONDARY


$$I_A := 12e^{-j \cdot 87\text{deg}}$$

$$I_B := 4 \cdot e^{-j \cdot 120\text{deg}}$$

$$I_C := 4 \cdot e^{j \cdot 120\text{deg}}$$





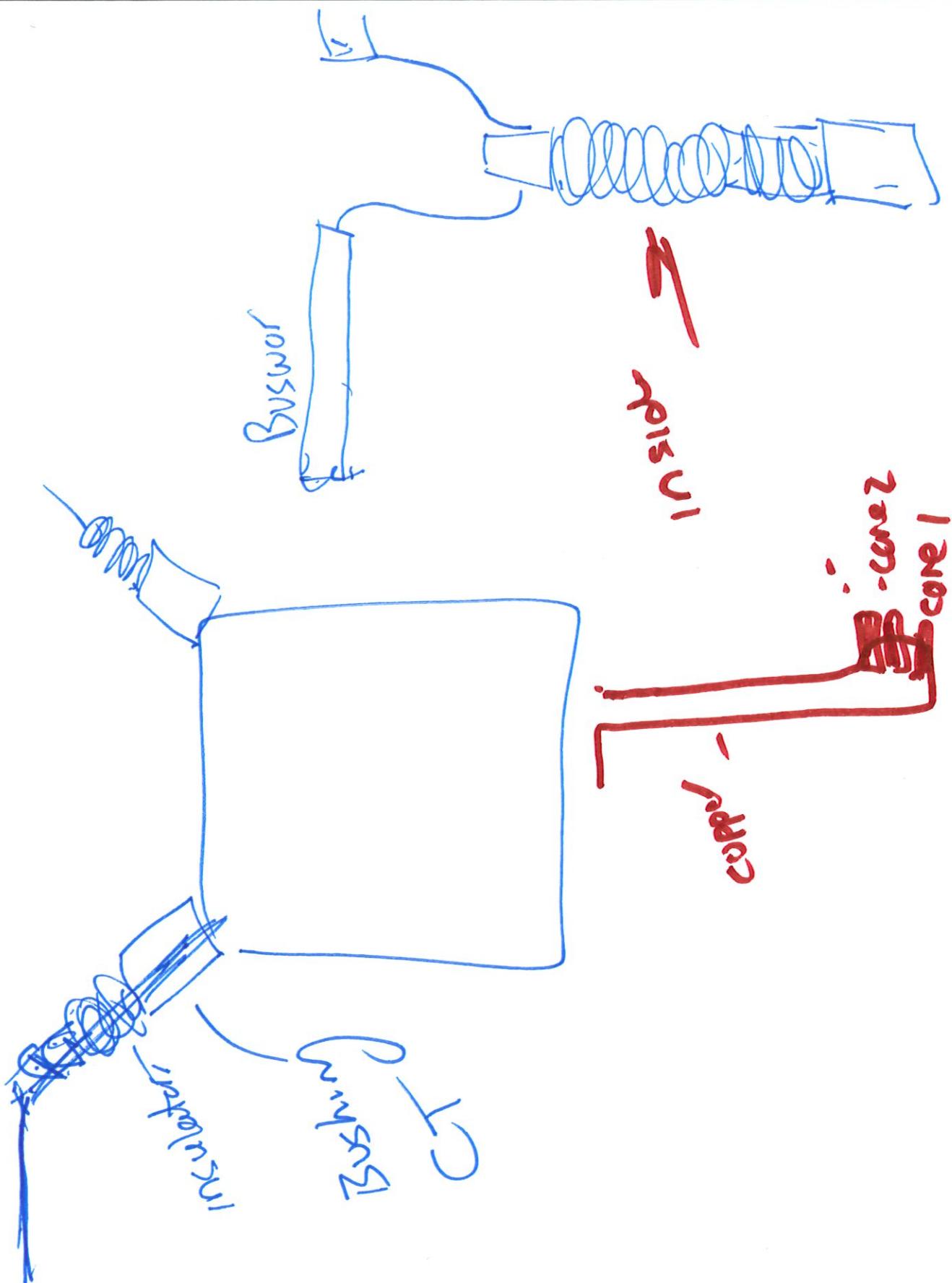
- (b) Calculate the symmetrical components of the secondary currents (I_{a0} , I_{a1} , I_{a2}).
- (c) Calculate the current measured by the fourth ammeter (I_r) and compare it to the zero sequence current calculated in part (b). How do they compare?
- (d) Using the primary current calculated in part (a), repeat part (b) if the CTs are connected in delta (relay currents should lag the primary line currents by 30 degrees).



L6 3/16

University of Idaho

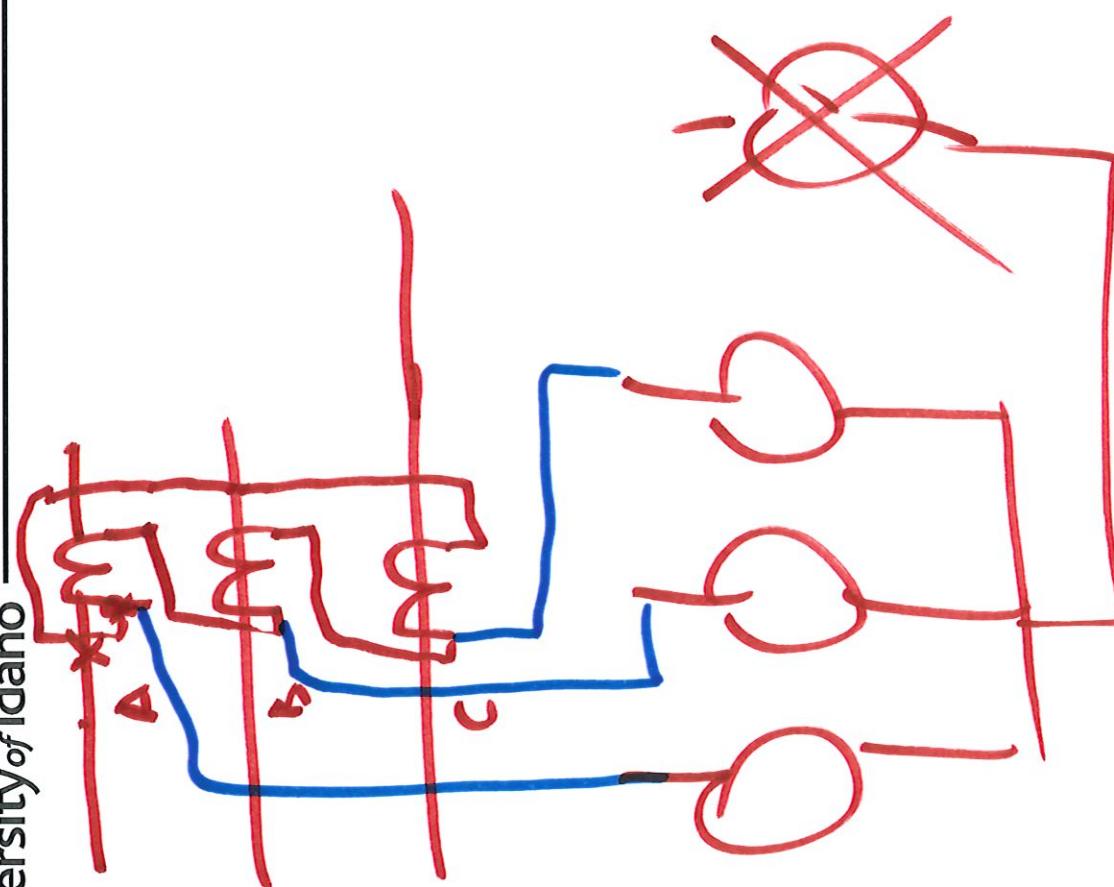

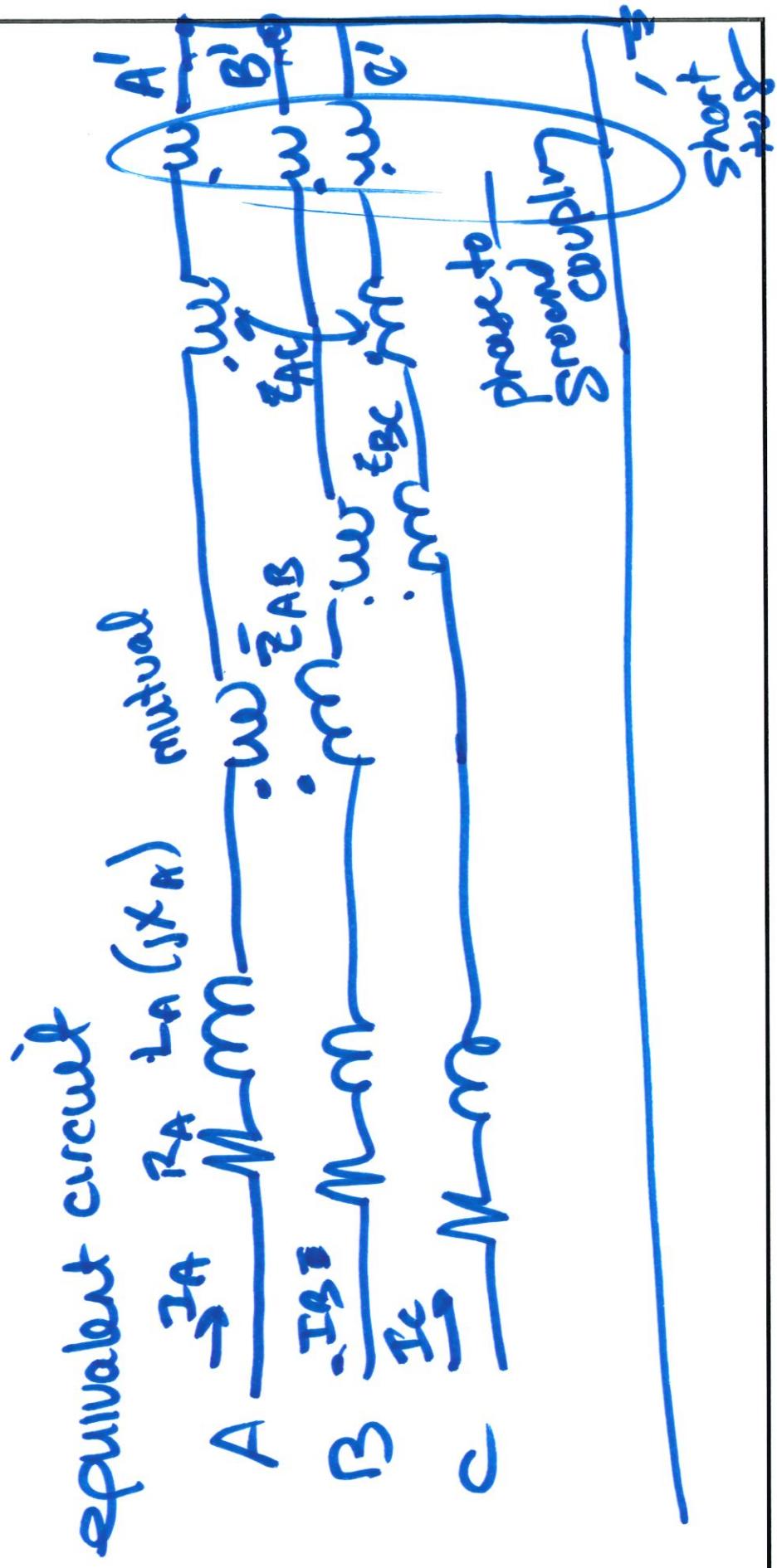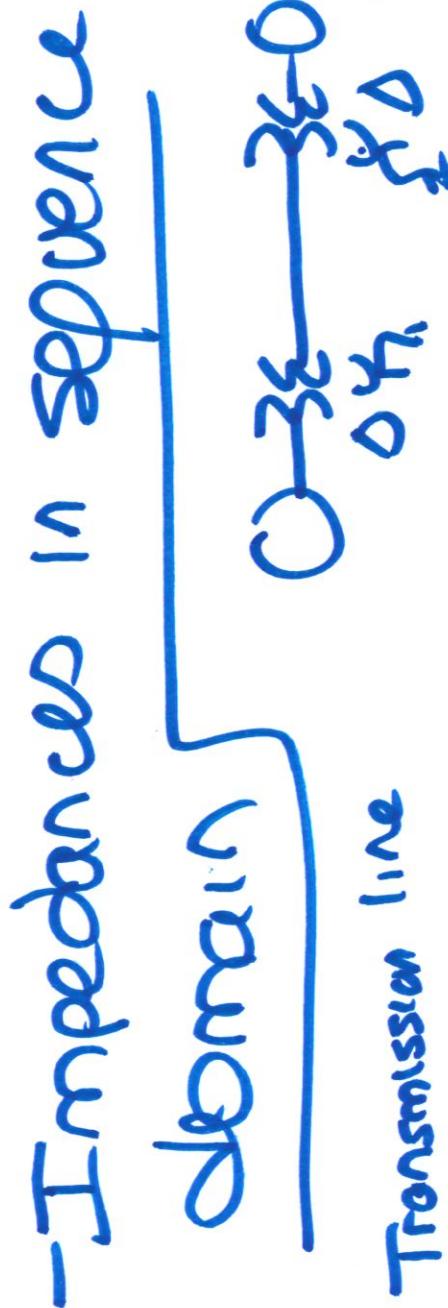

$$\begin{bmatrix} V_{A-A'} \\ V_{B-B'} \\ V_{C-C'} \end{bmatrix} = \begin{bmatrix} \bar{Z}_{AA} & \bar{Z}_{AB} & \bar{Z}_{AC} \\ \bar{Z}_{BA} & \bar{Z}_{BB} & \bar{Z}_{BC} \\ \bar{Z}_{CA} & \bar{Z}_{CB} & \bar{Z}_{CC} \end{bmatrix} \begin{bmatrix} I_A \\ -I_B \\ -I_C \end{bmatrix}$$

$$\bar{Z}_{AB} = \bar{Z}_{BA} \quad \text{etc}$$

$$V_{AG} - V_{A'G} = V_{A-A'}$$

$$\bar{Z}_{AG} = \bar{Z}_{GA}$$

$$V_{AG} - V_{A'G} = V_{A'-A} \\ \text{Now - odd } 3Q \text{ short to ground at } A', B', C' \\ V_{A'G} = V_{BG} \\ = \bar{V}_{C'G} = 0$$

$$\begin{bmatrix} \bar{V}_{AG} \\ \bar{V}_{BG} \\ \bar{V}_{CG} \end{bmatrix} = [A_{012}] \begin{bmatrix} \bar{V}_0 \\ \bar{V}_1 \\ \bar{V}_2 \end{bmatrix}$$

$$\begin{bmatrix} \bar{I}_A \\ \bar{I}_B \\ \bar{I}_C \end{bmatrix} = [A_{012}] \begin{bmatrix} \bar{I}_0 \\ \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_{AG} \\ \bar{V}_{BG} \\ \bar{V}_{CG} \end{bmatrix} = \begin{bmatrix} \bar{Z}_{ABC} \\ \vdots \\ \bar{Z}_{ABC} \end{bmatrix} \begin{bmatrix} \bar{I}_A \\ \bar{I}_B \\ \bar{I}_C \end{bmatrix}$$

↓

$$\begin{bmatrix} \bar{V}_0 \\ \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} \bar{Z}_{ABC} \\ \vdots \\ \bar{Z}_{ABC} \end{bmatrix} [A_{012}] \begin{bmatrix} \bar{I}_0 \\ \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_{AC} \\ \bar{V}_{BC} \\ V_{CG} \end{bmatrix} = \begin{bmatrix} \bar{Z}_{ABC} \\ \bar{I}_A \\ \bar{I}_B \end{bmatrix} \begin{bmatrix} \bar{I}_A \\ \bar{I}_B \\ \bar{I}_C \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_0 \\ \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} =$$

$$\begin{bmatrix} \bar{I}_0 \\ \bar{I}_1 \\ \bar{I}_2 \end{bmatrix} = \begin{bmatrix} \bar{I}_0 \\ \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

$$\begin{aligned} \bar{V}_0 &= \bar{V}_{AO} \\ \bar{V}_1 &= \bar{V}_{A1} \\ \bar{V}_2 &= \bar{V}_{A2} \end{aligned}$$

$$\begin{aligned} \bar{I}_0 &= \bar{I}_{AO} \\ \bar{I}_1 &= \bar{I}_{A1} \\ \bar{I}_2 &= \bar{I}_{A2} \end{aligned}$$

Premultiply both sides by $[A_{012}]^{-1}$

$$[A_{012}]^{-1} \begin{bmatrix} A_{012} \\ \bar{V}_0 \\ \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = [A_{012}]^{-1} \begin{bmatrix} Z_{ABC} \\ A_{012} \end{bmatrix} \begin{bmatrix} I_0 \\ \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = [I] \quad [I] \begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \bar{V}_0 \\ \bar{V}_1 \\ \bar{V}_2 \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_0 \\ \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = [A_{012}]^{-1} \begin{bmatrix} Z_{ABC} \\ A_{012} \end{bmatrix} \begin{bmatrix} I_0 \\ \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

$\{Z_{012}\}$

$$\begin{bmatrix} Z_{012} \end{bmatrix} = \begin{bmatrix} A_{012} \end{bmatrix}^{-1} \begin{bmatrix} Z_{ABC} \end{bmatrix} \begin{bmatrix} A_{012} \end{bmatrix}$$

$$\text{If } \begin{bmatrix} Z_{ABC} \end{bmatrix} = \begin{bmatrix} Z & 0 & 0 \\ 0 & Z & 0 \\ 0 & 0 & Z \end{bmatrix} = \begin{bmatrix} Z_{012} \end{bmatrix}$$

ECE 523: Lecture 5 Impedance in Sequence Domain

$$a := e^{j \cdot 120\text{deg}}$$

Phase A symmetrical components transform

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

Phase B symmetrical components transform

$$B_{012} := \begin{pmatrix} 1 & a & a^2 \\ 1 & 1 & 1 \\ 1 & a^2 & a \end{pmatrix}$$

Phase C symmetrical components transform

$$C_{012} := \begin{pmatrix} 1 & a^2 & a \\ 1 & a & a^2 \\ 1 & 1 & 1 \end{pmatrix}$$

Case 1:

$$Z_{aa} := (14.9 + j \cdot 58.4) \Omega$$

$$Z_{ab} := (4 + j \cdot 27.3) \Omega$$

$$Z_{bb} := (14.9 + j \cdot 58.4) \Omega$$

$$Z_{ac} := (4 + j \cdot 27.3) \Omega$$

$$Z_{cc} := (14.9 + j \cdot 58.4) \Omega$$

$$Z_{bc} := (4 + j \cdot 27.3) \Omega$$

$$Z_{ABC} := \begin{pmatrix} Z_{aa} & Z_{ab} & Z_{ac} \\ Z_{ab} & Z_{bb} & Z_{bc} \\ Z_{ac} & Z_{bc} & Z_{cc} \end{pmatrix}$$

$$Z_{012} := A_{012}^{-1} \cdot Z_{ABC} \cdot A_{012}$$

$$Z_{012} = \begin{pmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_1 \end{pmatrix} \Omega$$

$$Z_s := \frac{1}{3}(Z_{aa} + Z_{bb} + Z_{cc})$$


$$Z_m := \frac{1}{3} \cdot (Z_{ab} + Z_{bc} + Z_{ca})$$

$$Z_s - Z_m = (10.9 + 31.1i) \Omega$$

$$Z_s - Z_m - Z_{012}_{1,1} = 0 \Omega$$

$$Z_s + 2Z_m = (22.9 + 113i) \Omega$$

$$Z_s + 2Z_m - Z_{012}_{0,0} = 0 \Omega$$

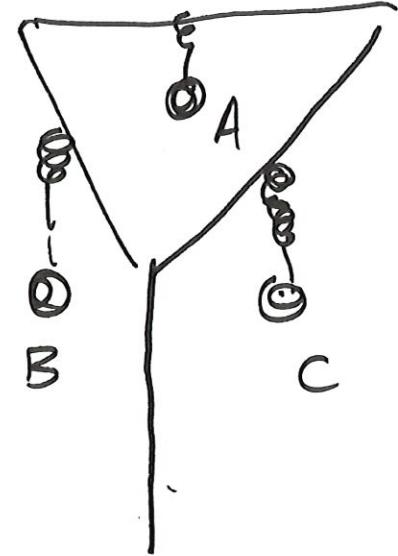

Lec 9

$Z_0 = Z_1 = Z_2$

$$Z_1 := Z_{012}_{1,1} \quad Z_1 = (10.9 + 31.1i)\Omega$$

$$Z_2 := Z_{012}_{2,2} \quad Z_2 = (10.9 + 31.1i)\Omega$$

$$Z_0 := Z_{012}_{0,0} \quad Z_0 = (22.9 + 113i)\Omega$$

$$Z_{012B} := B_{012}^{-1} \cdot Z_{ABC} \cdot B_{012} \quad Z_{012C} := C_{012}^{-1} \cdot Z_{ABC} \cdot C_{012}$$

$$Z_{012B} - Z_{012} = \begin{pmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ A & 0 & 0 \end{pmatrix} \Omega \quad Z_{012C} - Z_{012} = \begin{pmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ A & 0 & 0 \end{pmatrix} \Omega$$

Case 2: (now add imbalance to self terms--act as if it is a similar tower structure with mutual coupling to other conductors creating unbalance, although I'm being somewhat unrealistic for comparison purposes)

$$Z_{aa} := (14.9 + j \cdot 53.4)\text{ohm} \quad Z_{ab} := (4 + j \cdot 27.3)\text{ohm}$$

$$Z_{bb} := (14.9 + j \cdot 68.4)\text{ohm} \quad Z_{ac} := (4 + j \cdot 27.3)\text{ohm}$$

$$Z_{cc} := (14.9 + j \cdot 53.4)\text{ohm} \quad Z_{bc} := (4 + j \cdot 27.3)\text{ohm}$$

$$Z_{ABC} := \begin{pmatrix} Z_{aa} & Z_{ab} & Z_{ac} \\ Z_{ab} & Z_{bb} & Z_{bc} \\ Z_{ac} & Z_{bc} & Z_{cc} \end{pmatrix}$$

$$Z_{012} := A_{012}^{-1} \cdot Z_{ABC} \cdot A_{012}$$

$$Z_{012} = \begin{pmatrix} Z_0 & Z_1 & Z_2 \\ 22.9 + 113i & 4.33 - 2.5i & -4.33 - 2.5i \\ -4.33 - 2.5i & 10.9 + 31.1i & 4.33 - 2.5i \\ 4.33 - 2.5i & -4.33 - 2.5i & 10.9 + 31.1i \end{pmatrix} \Omega$$

$$Z_s := \frac{1}{3}(Z_{aa} + Z_{bb} + Z_{cc}) \quad Z_s = (14.9 + 58.4i)\Omega$$

$$Z_m := \frac{1}{3} \cdot (Z_{ab} + Z_{bc} + Z_{ca}) \quad Z_m = (4 + 27.3i)\Omega$$

Z_0, Z_1, Z_2
each an
order of
magnitude
(a lot)
than
off diagonal

$$Z_s - Z_m = (10.9 + 31.1i) \Omega \quad Z_s - Z_m - Z_{012_{1,1}} = 0 \Omega$$

$$Z_s + 2Z_m = (22.9 + 113i) \Omega \quad Z_s + 2Z_m - Z_{012_{0,0}} = 0 \Omega$$

Compare to original case:

$$Z_0 - (Z_s + 2Z_m) = 0 \Omega$$

$$Z_1 - (Z_s - Z_m) = 0 \Omega$$

$$Z_{012B} := B_{012}^{-1} \cdot Z_{ABC} \cdot B_{012}$$

$$Z_{012C} := C_{012}^{-1} \cdot Z_{ABC} \cdot C_{012}$$

$$Z_{012B} - Z_{012} = \begin{pmatrix} 0 & -4.33 + 7.5i & 4.33 + 7.5i \\ 4.33 + 7.5i & 0 & -4.33 + 7.5i \\ -4.33 + 7.5i & 4.33 + 7.5i & 0 \end{pmatrix} \Omega$$

$$Z_{012C} - Z_{012} = \begin{pmatrix} 0 & -8.66 & 8.66 \\ 8.66 & 0 & -8.66 \\ -8.66 & 8.66 & 0 \end{pmatrix} \Omega$$

Note that the diagonal terms do not change, just the coupling terms.

Case 3: (A more realistic set of unbalances)

$$Z_{aa} := (14.9 + j \cdot 57.0) \text{ ohm} \quad Z_{ab} := (4 + j \cdot 27.3) \text{ ohm}$$

$$Z_{bb} := (14.9 + j \cdot 58.2) \text{ ohm} \quad Z_{ac} := (4 + j \cdot 27.3) \text{ ohm}$$

$$Z_{cc} := (14.9 + j \cdot 60.0) \text{ ohm} \quad Z_{bc} := (4 + j \cdot 27.3) \text{ ohm}$$

$$Z_{ABC} := \begin{pmatrix} Z_{aa} & Z_{ab} & Z_{ac} \\ Z_{ab} & Z_{bb} & Z_{bc} \\ Z_{ac} & Z_{bc} & Z_{cc} \end{pmatrix}$$

$$Z_{012} := A_{012}^{-1} \cdot Z_{ABC} \cdot A_{012} \quad \text{Phase A Components}$$

$$Z_{012} = \begin{pmatrix} 22.9 + 113i & -0.52 - 0.7i & 0.52 - 0.7i \\ 0.52 - 0.7i & 10.9 + 31.1i & -0.52 - 0.7i \\ -0.52 - 0.7i & 0.52 - 0.7i & 10.9 + 31.1i \end{pmatrix} \Omega$$

Much smaller off diagonal

$$Z_s := \frac{1}{3}(Z_{aa} + Z_{bb} + Z_{cc}) \quad Z_s = (14.9 + 58.4i)\Omega$$

$$Z_m := \frac{1}{3} \cdot (Z_{ab} + Z_{bc} + Z_{ca}) \quad Z_m = (4 + 27.3i)\Omega$$

$$Z_s - Z_m = (10.9 + 31.1i)\Omega \quad Z_s - Z_m - Z_{012}_{1,1} = 0\Omega$$

$$Z_s + 2Z_m = (22.9 + 113i)\Omega \quad Z_s + 2Z_m - Z_{012}_{0,0} = 0\Omega$$

Compare to original case:

$$Z_0 - (Z_s + 2Z_m) = 0\Omega \quad Z_1 - (Z_s - Z_m) = 0\Omega$$


Phase B and Phase C components

$$Z_{012B} := B_{012}^{-1} \cdot Z_{ABC} \cdot B_{012} \quad Z_{012C} := C_{012}^{-1} \cdot Z_{ABC} \cdot C_{012}$$

$$Z_{012B} - Z_{012} = \begin{pmatrix} 0 & 1.39 + 0.6i & -1.39 + 0.6i \\ -1.39 + 0.6i & 0 & 1.39 + 0.6i \\ 1.39 + 0.6i & -1.39 + 0.6i & 0 \end{pmatrix} \Omega$$

$$Z_{012C} - Z_{012} = \begin{pmatrix} 0 & 0.17 + 1.5i & -0.17 + 1.5i \\ -0.17 + 1.5i & 0 & 0.17 + 1.5i \\ 0.17 + 1.5i & -0.17 + 1.5i & 0 \end{pmatrix} \Omega$$

Again, only the off diagonal terms change

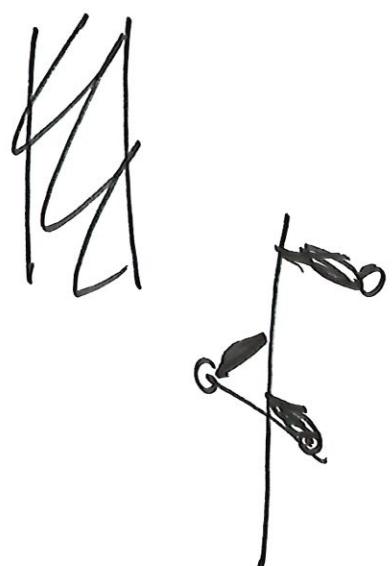

Case 4: (Now add imbalances to mutual terms only)

$$Z_{aa} := (14.9 + j \cdot 58.4)\Omega \quad Z_{ab} := (4 + j \cdot 27.4)\Omega$$

$$Z_{bb} := (14.9 + j \cdot 58.4)\Omega \quad Z_{ac} := (4 + j \cdot 28.0)\Omega$$

$$Z_{cc} := (14.9 + j \cdot 58.4)\Omega \quad Z_{bc} := (4 + j \cdot 26.5)\Omega$$

$$Z_{ABC} := \begin{pmatrix} Z_{aa} & Z_{ab} & Z_{ac} \\ Z_{ab} & Z_{bb} & Z_{bc} \\ Z_{ac} & Z_{bc} & Z_{cc} \end{pmatrix}$$

$$Z_{012} := A_{012}^{-1} \cdot Z_{ABC} \cdot A_{012}$$

$$Z_{012} = \begin{pmatrix} 22.9 + 113i & -0.17 + 0.4i & 0.17 + 0.4i \\ 0.17 + 0.4i & 10.9 + 31.1i & 0.35 - 0.8i \\ -0.17 + 0.4i & -0.35 - 0.8i & 10.9 + 31.1i \end{pmatrix} \Omega$$

$$Z_{s2} := \frac{1}{3}(Z_{aa} + Z_{bb} + Z_{cc}) \quad Z_{s2} = (14.9 + 58.4i) \Omega \quad Z_s = (14.9 + 58.4i) \Omega$$

$$Z_m := \frac{1}{3} \cdot (Z_{ab} + Z_{bc} + Z_{ac}) \quad Z_m = (4 + 27.3i) \Omega$$

$$Z_s - Z_m = (10.9 + 31.1i) \Omega \quad Z_s - Z_m - Z_{012}_{1,1} = 0 \Omega$$

$$Z_s + 2Z_m = (22.9 + 113i) \Omega \quad Z_s + 2Z_m - Z_{012}_{0,0} = 0 \Omega$$

Compare to original case:

$$Z_0 - (Z_s + 2Z_m) = 0 \Omega \quad Z_1 - (Z_s - Z_m) = 0 \Omega$$

Phase B and C based components

$$Z_{012B} := B_{012}^{-1} \cdot Z_{ABC} \cdot B_{012} \quad Z_{012C} := C_{012}^{-1} \cdot Z_{ABC} \cdot C_{012}$$

$$Z_{012B} - Z_{012} = \begin{pmatrix} 0 & -0.09 - 0.75i & 0.09 - 0.75i \\ 0.09 - 0.75i & 0 & 0.17 + 1.5i \\ -0.09 - 0.75i & -0.17 + 1.5i & 0 \end{pmatrix} \Omega$$

$$Z_{012C} - Z_{012} = \begin{pmatrix} 0 & 0.61 - 0.45i & -0.61 - 0.45i \\ -0.61 - 0.45i & 0 & -1.21 + 0.9i \\ 0.61 - 0.45i & 1.21 + 0.9i & 0 \end{pmatrix} \Omega$$

Case 5 (both self and mutual unbalanced):

$$Z_{aa} := (14.9 + j \cdot 57.0) \text{ohm} \quad Z_{ab} := (4 + j \cdot 27.4) \text{ohm}$$

$$Z_{bb} := (14.9 + j \cdot 58.2) \text{ohm} \quad Z_{ac} := (4 + j \cdot 28.0) \text{ohm}$$

$$Z_{cc} := (14.9 + j \cdot 60.0) \text{ohm} \quad Z_{bc} := (4 + j \cdot 26.5) \text{ohm}$$

complex power

$$\bar{S}_{30} = \bar{S}_{ABC} \Rightarrow S_{12}?$$

~~$$\bar{S}_{30} = \sqrt{I_A^2 + I_B^2 + I_C^2}$$~~

?

?

- balanced

$$\bar{S}_{30} = 3 \bar{V}_{GN} \bar{I}_A^*$$

$$= \bar{V}_{AG} \bar{I}_A^* + \bar{V}_{BG} \bar{I}_B^* + \bar{V}_{CG} \bar{I}_C^*$$

$$\bar{S}_{ABC} = \begin{bmatrix} \bar{V}_{AG} & \bar{V}_{BG} & \bar{V}_{CG} \end{bmatrix} \begin{bmatrix} \bar{I}_A^* \\ \bar{I}_B^* \\ \bar{I}_C^* \end{bmatrix}$$
$$= \begin{bmatrix} \bar{V}_{AG} \\ \bar{V}_{BG} \\ \bar{V}_{CG} \end{bmatrix}^\top \begin{bmatrix} \bar{I}_A^* \\ \bar{I}_B^* \\ \bar{I}_C^* \end{bmatrix}$$