

ECE 523  
Symmetrical Components  
Session 7

Complex power

$$\bar{S}_{30} = \bar{S}_{ABC} \Rightarrow \text{Solz?}$$

~~$$\bar{S}_{30} = \bar{V}_{abc} \bar{I}_{abc}$$~~

2. ~~2~~

$$\begin{aligned}\bar{S}_{30} &= 3 \bar{V}_{\text{on}} \bar{I}_P^* - \text{Balanced } \bar{S}_0 \\ &= \bar{V}_{AG} \bar{I}_A^* + \bar{V}_{BG} \bar{I}_B^* + \bar{V}_{CG} \bar{I}_C^*\end{aligned}$$

$$\bar{S}_{ABC} = \begin{bmatrix} \bar{V}_{AG} & \bar{V}_{BG} & \bar{V}_{CG} \end{bmatrix} \begin{bmatrix} \bar{I}_A^* \\ \bar{I}_B^* \\ \bar{I}_C^* \end{bmatrix}$$

$$= \begin{bmatrix} \bar{V}_{ABC} \end{bmatrix}^T \begin{bmatrix} \bar{I}_{ABC} \end{bmatrix}^*$$


$$\begin{aligned}
 & \Downarrow \\
 & = [A_{012} \cdot V_{012}]^T [A_{012}]^* I_{012}^* \\
 & = [V_{012}]^T [A_{012}]^T [A_{012}]^* I_{012}^* \\
 & = V_{012}^T [A_{012}]^* 3[A_{012}]^{-1} I_{012}^*
 \end{aligned}$$

$$\begin{bmatrix} A_{012} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ -1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} = \begin{bmatrix} A_{012} \end{bmatrix}^T$$

$$\begin{bmatrix} A_{012}^* \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} = 3 \begin{bmatrix} A_{012} \end{bmatrix}^{-1}$$


$$Q = \sqrt{\cos 120^\circ + j \sin 120^\circ} = -\frac{1}{2} + j \frac{\sqrt{3}}{2} = (\alpha^2)^*$$
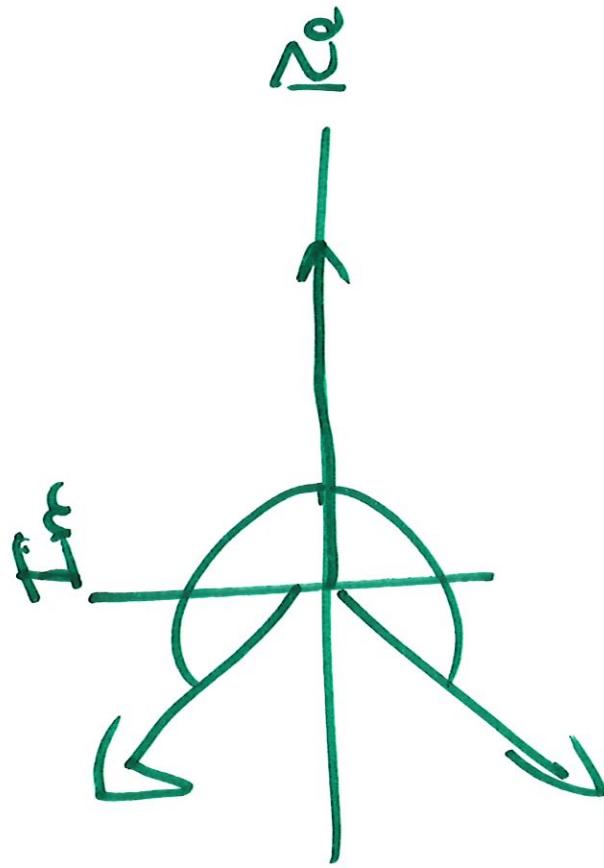
$$\alpha^2 = \cos 240^\circ + j \sin 240^\circ = -\frac{1}{2} - j \frac{\sqrt{3}}{2} = \alpha^*$$



$$\begin{aligned}\bar{S}_{ABC} &= \bar{S}_{012} = 3 \frac{\underline{V}_{012}^T \underline{I}_{012}^*}{\underline{V}_0 \underline{I}_0^* + \bar{V}_1 \bar{I}_1^* + \bar{V}_2 \bar{I}_2^*} \\ &= 3 \left[ \underline{V}_0 \underline{I}_0^* + \bar{V}_1 \bar{I}_1^* + \bar{V}_2 \bar{I}_2^* \right]\end{aligned}$$

# Flux / Flux Linkage?

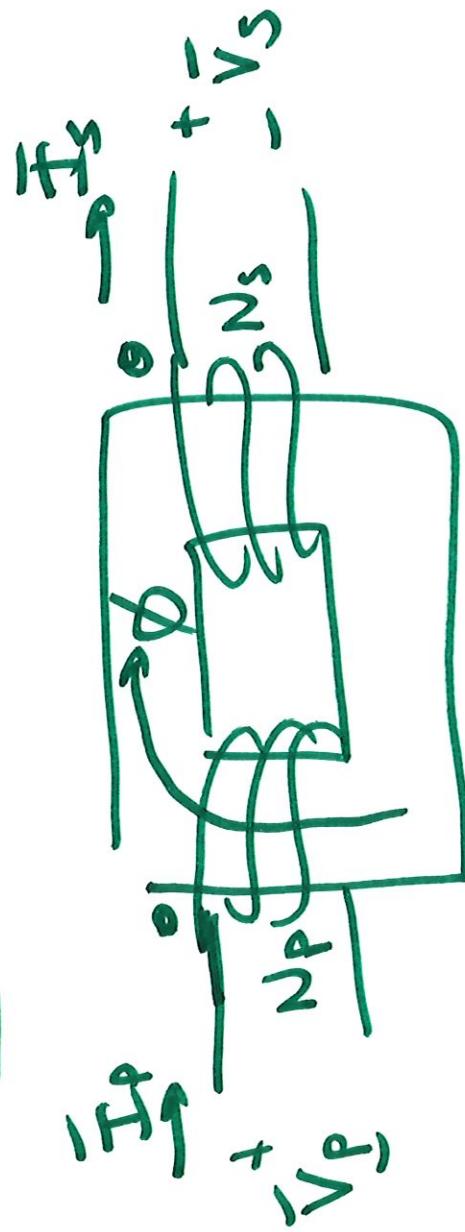

$$\mathbf{I}_p \cdot N_p + \mathbf{I}_s N_s = 0$$

$$V = N \frac{d\Phi}{dt}$$

$$V_p = \frac{\partial \Phi}{\partial t}$$

- $3\phi$  Transformers
  - will have positive, negative and zero sequence flux components.
  - same with machines

5 leg. 3 phase core



$$V_0 \rightarrow \bar{V}_{0A} = \bar{V}_{0B} = \bar{V}_{0C}$$


$$\Rightarrow \bar{\phi}_{0A} = \bar{\phi}_{0B} = \bar{\phi}_{0C}$$

$$\begin{aligned} \bar{V}_{1A} + \bar{V}_{1B} + \bar{V}_{1C} &= 0 \\ \bar{\phi}_{1A} + \bar{\phi}_{1B} + \bar{\phi}_{1C} &= 0 \end{aligned}$$


Q/B




Delta cut

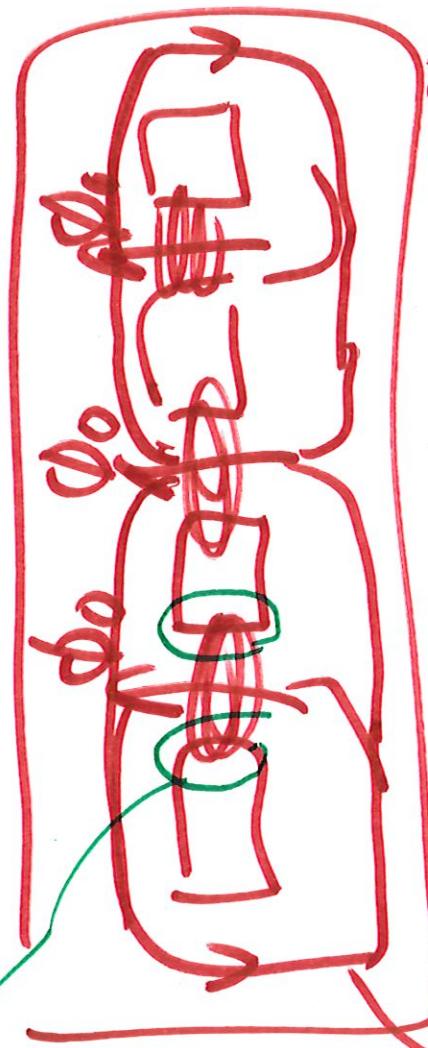

return path can zero sequence flux

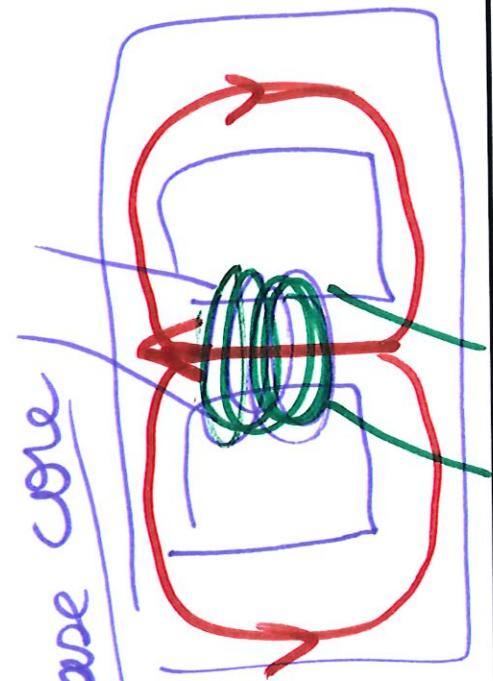


Single phase core

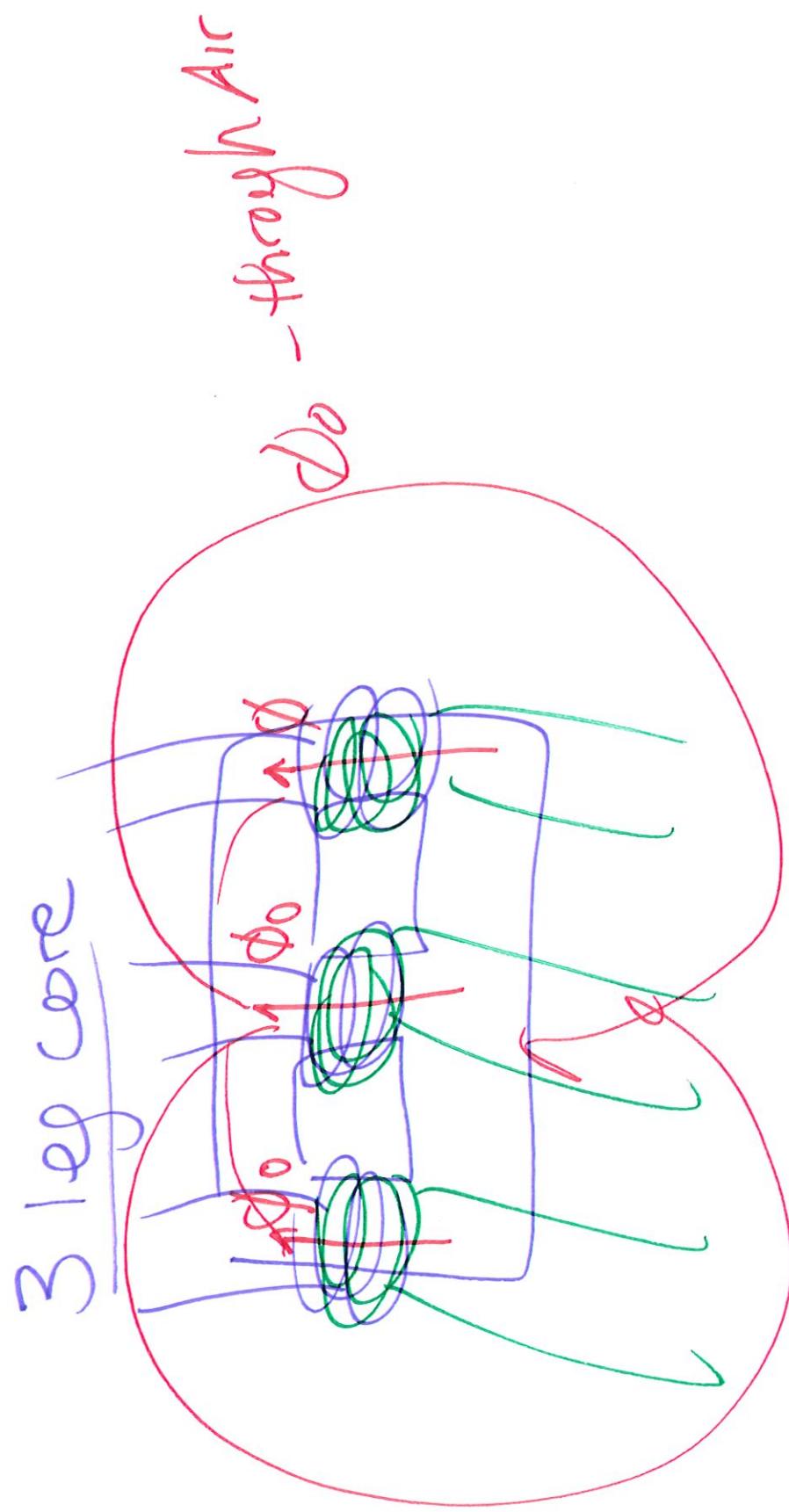


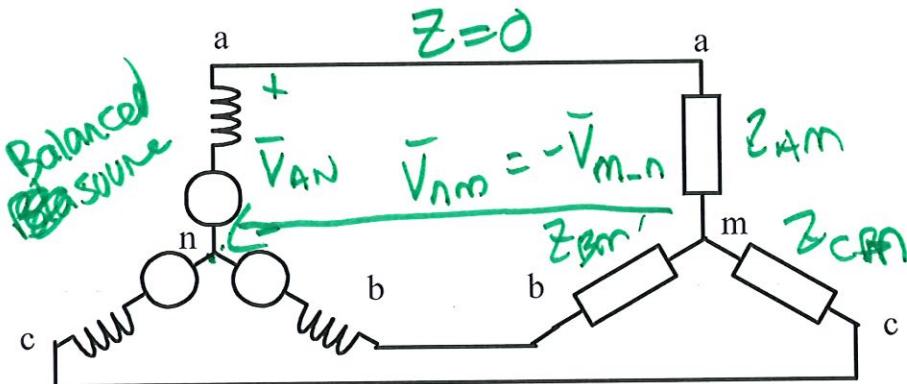
## ECE 523: Symmetrical Components Examples

If a load is unbalanced, its neutral, m, will not be at the same potential as the source neutral, n. Derive the relationship between the neutral shift  $V_{mn}$  and the zero sequence voltage  $V_{am0}$  for the system shown below. Similar to Problem 2.11. Hint, consider the line to ground voltages, line to neutral voltages and neutral to ground voltages.



$$V_{m\_n} = V_{m\_ground} - V_{n\_ground}$$

$$V_{an} = V_{a\_ground} - V_{n\_ground}$$

$$\text{and } V_{am} = V_{a\_ground} - V_{m\_ground}$$

so, substituting

$$V_{m\_n} = V_{m\_ground} - V_{n\_ground} = (V_{a\_ground} - V_{am}) - ((V_{a\_ground} - V_{an}) - V_{an})$$


Then rearranging terms:

$$V_{m\_n} = V_{an} - V_{am}$$


$$\text{similarly } V_{m\_n} = V_{bn} - V_{bm}$$

$$V_{m\_n} = V_{cn} - V_{cm}$$

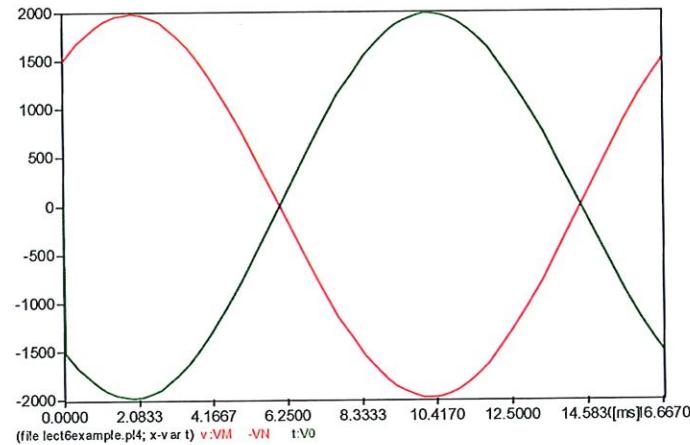- Next plot instantaneous values of  $V_{mn}$  and  $V_0$  (note that  $V_0$  is simply  $\frac{1}{3} \cdot (V_{am} + V_{bm} + V_{cm})$ ). No degree phase difference.



ATPDraw Schematic

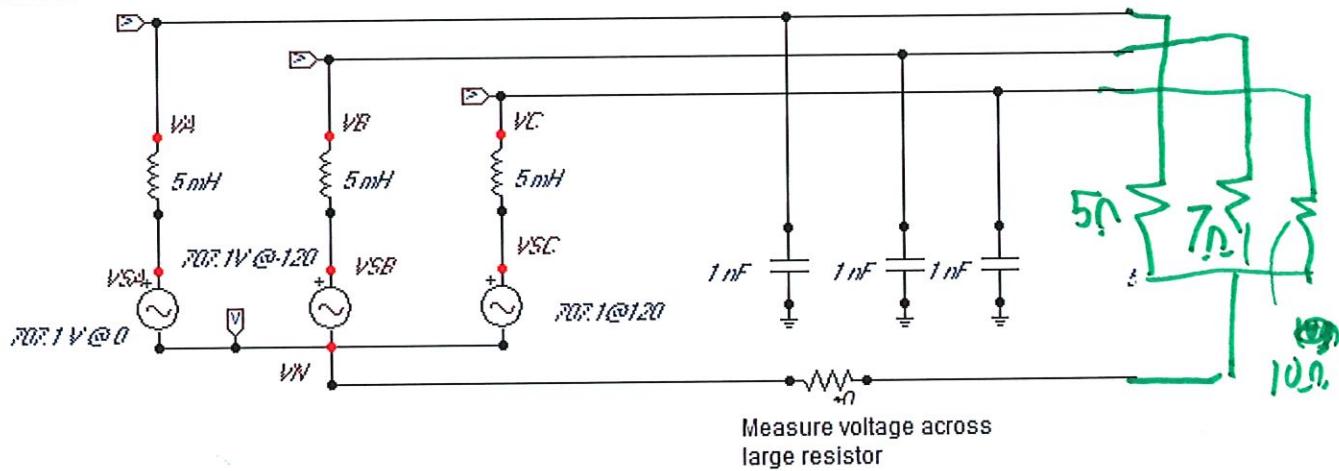

- The capacitors were added to provide a ground reference. The capacitive reactances are quite large and results otherwise.
- Control modelling language TACS used to calculate  $V_0$

- Adding these three expressions, results in:  $3V_{m\_n} = (V_{an} + V_{bn} + V_{cn}) - (V_{am} + V_{bm} + V_{cm})$
  - Applying the Symmetrical Components transformation:
- $$3V_{an0} = (V_{an} + V_{bn} + V_{cn}) = 0 \quad \text{Since the source is still balanced}$$

Similarly


$$3V_{am0} = (V_{am} + V_{bm} + V_{cm}) \quad \text{This does not sum to 0, since the load is unbalanced}$$

Therefore


$$3V_{m\_n} = 3V_{an0} - 3V_{am0} = -3V_{am0} \quad V_{m\_n} = -V_{am0}$$


As a check, the circuit was simulated with ATPDraw, which was also used to determine the symmetrical instantaneous quantities.

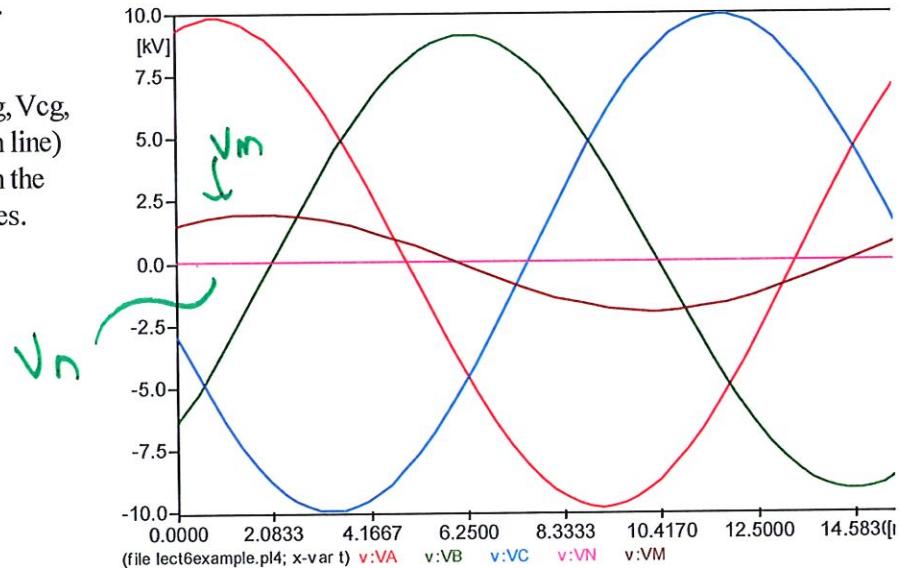
- First we see  $V_{ag}$ ,  $V_{bg}$ ,  $V_{cg}$ ,  $V_{ng}$  and  $V_{mg}$  (brown line)
- Note the unbalance in the line-to-ground voltages.



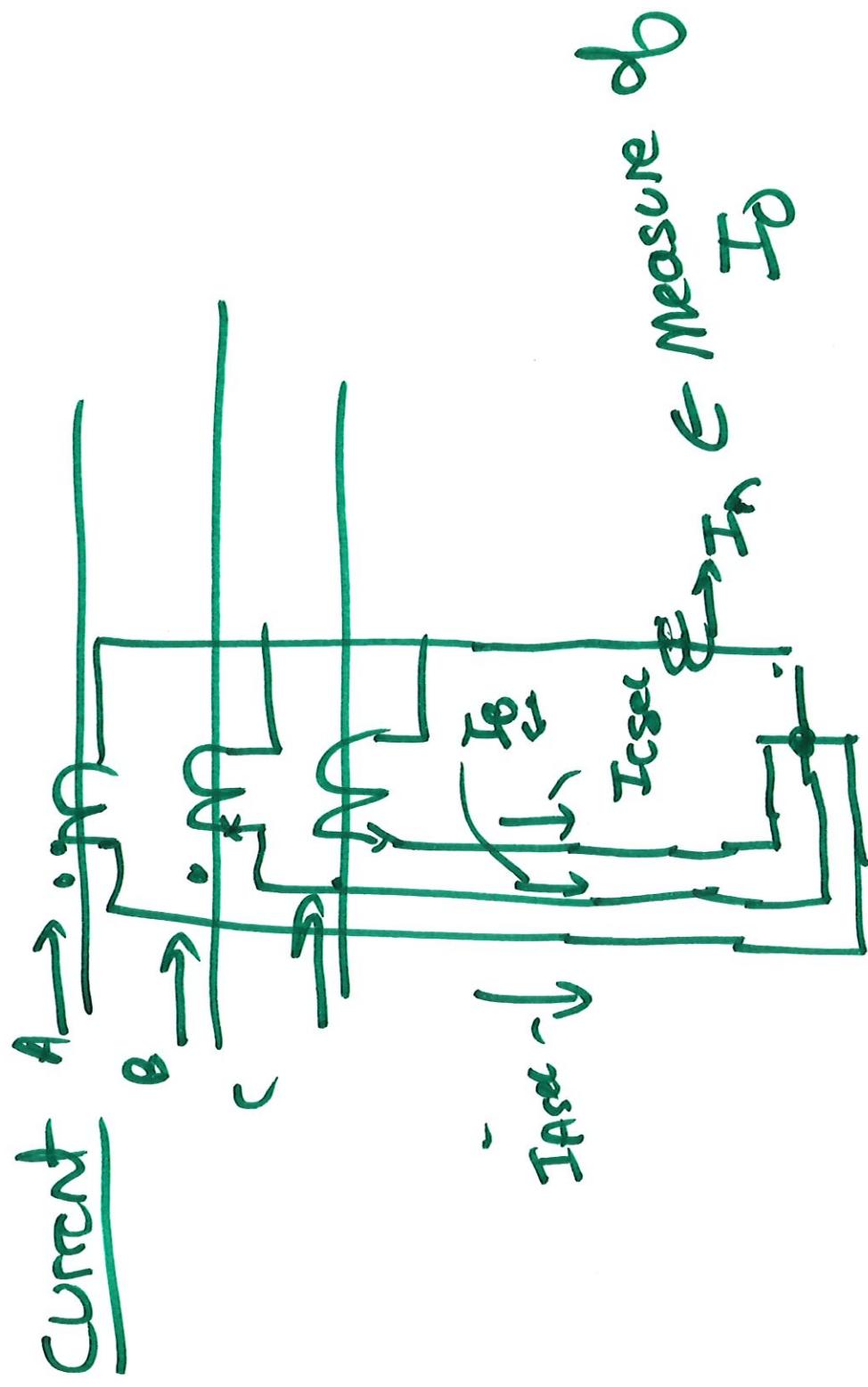- Measurement of sequence voltages and currents?



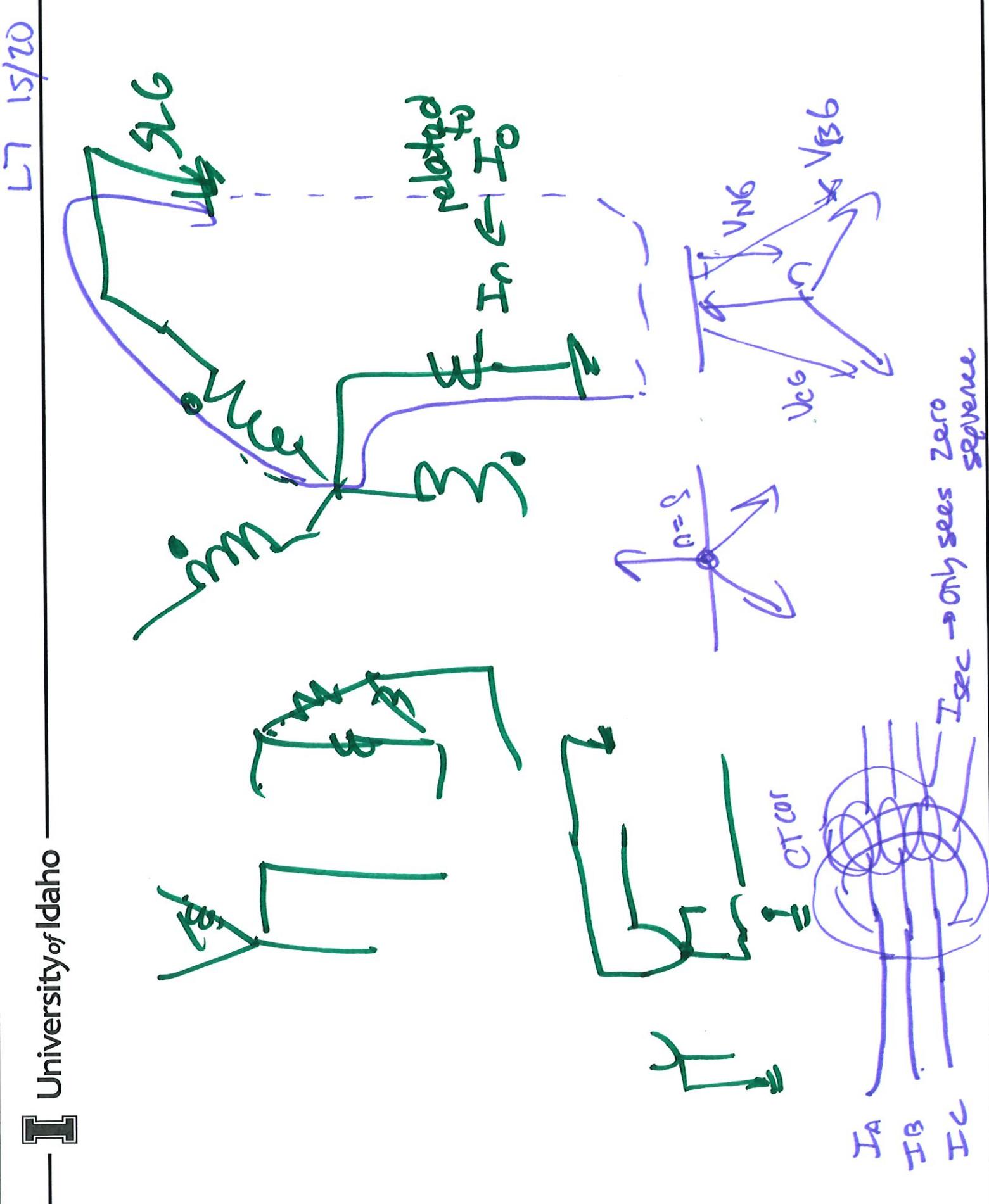

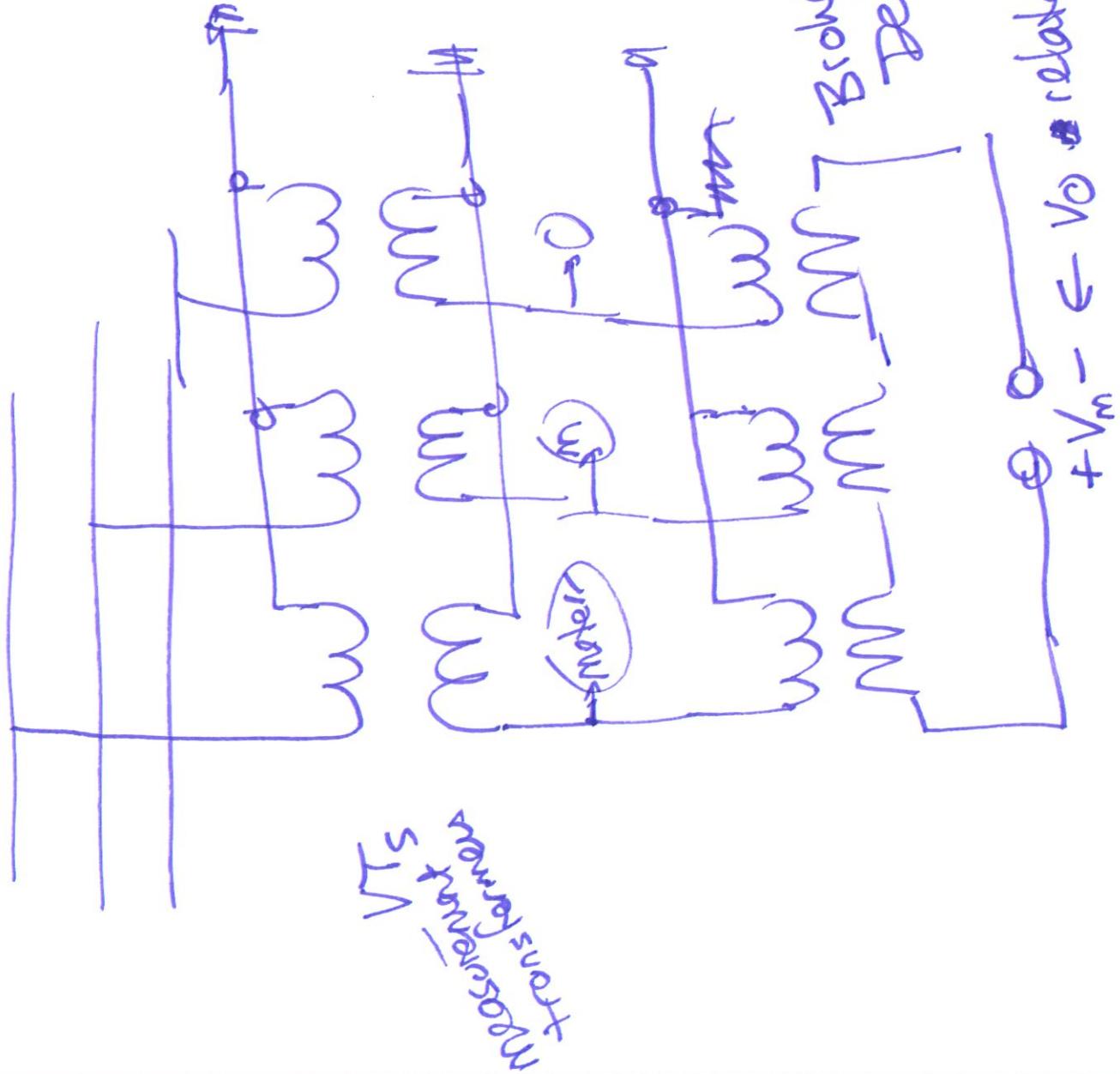

## Symmetrical Components Example

$$\text{MVA} := \text{MW} \quad a := 1 \cdot e^{j \cdot 120\text{deg}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix} \quad \text{Inv\_} A_{012} = \frac{1}{3} \begin{pmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{pmatrix}$$

$$S_B := 100\text{MVA} \quad V_{BLL} := 230\text{kV} \quad I_B := \frac{S_B}{\sqrt{3} \cdot V_{BLL}} \quad I_B = 251.022\text{A}$$

- Voltages and currents from a single line to ground fault with load flow on weak 230 kV system

*Upder*  $Z_1 := 2(0.852 + j \cdot 9.739)\Omega$

$$Z_1 = (1.704 + 19.478i)\Omega$$



$$Z_0 := 3 \cdot Z_1 \quad Z_0 = (5.112 + 58.434i)\Omega$$

$$V_S := \frac{230\text{kV}}{\sqrt{3}} \cdot e^{j \cdot 0\text{deg}}$$

$$V_R := \frac{230\text{kV}}{\sqrt{3}} \cdot e^{-j \cdot 16\text{deg}}$$

*Total 2*  $I_{A\_prefault} := \frac{(V_S - V_R)}{2Z_1} \quad |I_{A\_prefault}| = 945.198\text{A} \quad \arg(I_{A\_prefault}) = -3\text{-deg}$

Fault currents and voltages from EMT simulation

*SLG*  $I_{ABC} := \begin{pmatrix} 4144\text{A} \cdot e^{-j \cdot 79.74\text{deg}} \\ 945.1\text{A} \cdot e^{-j \cdot 122.9\text{deg}} \\ 945.1\text{A} \cdot e^{j \cdot 117.1\text{deg}} \end{pmatrix}$

$$V_{ABC} := \begin{pmatrix} 10^{-5}\text{V} \cdot e^{j \cdot 0\text{deg}} \\ 164.3\text{kV} \cdot e^{-j \cdot 144.0\text{deg}} \\ 164.2\text{kV} \cdot e^{j \cdot 128.2\text{deg}} \end{pmatrix}$$

*load current of B+C*  $I_{012} := A_{012}^{-1} \cdot I_{ABC}$

$$\overrightarrow{|I_{012}|} = \begin{pmatrix} 1345.057 \\ 1643.583 \\ 1345.057 \end{pmatrix} \cdot \text{A} \quad \overrightarrow{\arg(I_{012})} = \begin{pmatrix} -92.923 \\ -57.822 \\ -92.923 \end{pmatrix} \cdot \text{deg}$$

*total*  $V_{012} := A_{012}^{-1} \cdot V_{ABC}$

$$\overrightarrow{|V_{012}|} = \begin{pmatrix} 78.9 \\ 105.205 \\ 26.305 \end{pmatrix} \cdot \text{kV} \quad \overrightarrow{\arg(V_{012})} = \begin{pmatrix} 172.117 \\ -7.905 \\ 172.03 \end{pmatrix} \cdot \text{deg}$$

*I<sub>0</sub> = I<sub>2</sub>*  
*I<sub>1</sub> ≠ superposition of I<sub>f</sub> + I<sub>2</sub>*

- Comparing our model to the simulation results

$$V_{0f} := 0 - I_{012_0} \cdot (Z_0) \quad |V_{0f}| = 78.897 \text{ kV} \quad \arg(V_{0f}) = 172.077 \text{ deg}$$

$$V_{1f} := \frac{230 \text{ kV}}{\sqrt{3}} - I_{012_1} \cdot (Z_1) \quad |V_{1f}| = 105.232 \text{ kV} \quad \arg(V_{1f}) = -8.018 \text{ deg}$$

$$V_{2f} := 0 - I_{012_2} \cdot (Z_2) \quad |V_{2f}| = 26.299 \text{ kV} \quad \arg(V_{2f}) = 172.077 \text{ deg}$$

$$V_{ABCf} := A_{012} \begin{pmatrix} V_{0f} \\ V_{1f} \\ V_{2f} \end{pmatrix} \quad \overrightarrow{|V_{ABCf}|} = \begin{pmatrix} 0.179 \\ 164.32 \\ 164.223 \end{pmatrix} \text{ kV} \quad \overrightarrow{\arg(V_{ABCf})} = \begin{pmatrix} -86.602 \\ -144.08 \\ 128.117 \end{pmatrix} \text{ deg}$$

**Now look at behavior in the time domain.**


Set up an array 3 cycle long, with 16 samples per cycle

$$t := 0 \text{ sec}, \frac{1}{16 \cdot 60 \text{ Hz}}, \dots, \frac{2}{60 \text{ Hz}} \quad \omega := 2 \cdot \pi \cdot 60 \text{ Hz}$$

$$i_a(t) := \sqrt{2} \cdot |I_{ABC_0}| \cdot \cos(\omega \cdot t + \arg(I_{ABC_0}))$$

$$i_b(t) := \sqrt{2} \cdot |I_{ABC_1}| \cdot \cos(\omega \cdot t + \arg(I_{ABC_1}))$$


$$i_c(t) := \sqrt{2} \cdot |I_{ABC_2}| \cdot \cos(\omega \cdot t + \arg(I_{ABC_2}))$$

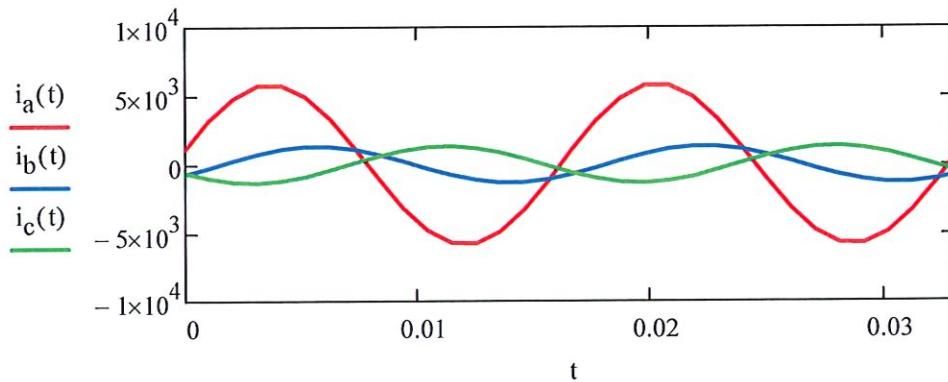

$$v_a(t) := \sqrt{2} \cdot |V_{ABC_0}| \cdot \cos(\omega \cdot t + \arg(V_{ABC_0}))$$

$$v_b(t) := \sqrt{2} \cdot |V_{ABC_1}| \cdot \cos(\omega \cdot t + \arg(V_{ABC_1}))$$

$$v_c(t) := \sqrt{2} \cdot |V_{ABC_2}| \cdot \cos(\omega \cdot t + \arg(V_{ABC_2}))$$

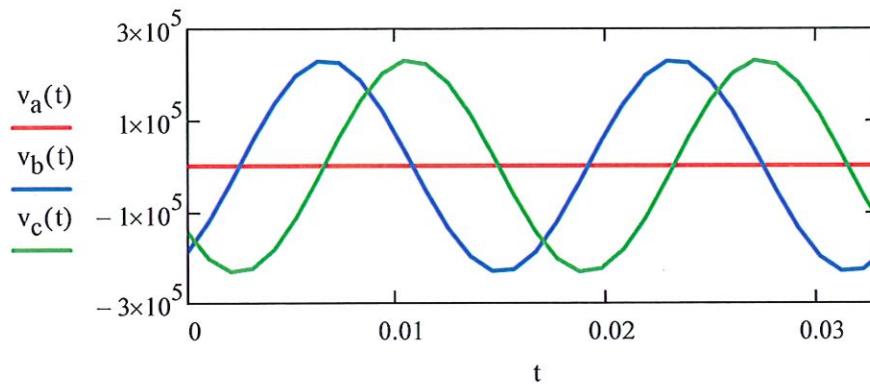

- Convert  $a$  and  $a^2$  to units of time

$$T_a := \frac{\arg(a)}{360\text{deg} \cdot 60\text{Hz}} \quad T_a = 5.556 \cdot \text{ms}$$

$$T_{a\_sq} := \frac{\arg(a^2) + 360\text{deg}}{360\text{deg} \cdot 60\text{Hz}} \quad T_{a\_sq} = 11.111 \cdot \text{ms}$$

Note that:  $I_1 = I_A + a \cdot I_B + a^2 \cdot I_C$

- This equation involves rotating  $I_B$  and  $I_C$  by positive angles, which would mean advancing in time.
- We can only delay measurements, not advance them
- Recall that:

$$a = a^{-2} \quad a - a^{-2} = 0$$

$$a^2 = a^{-1} \quad a^2 - a^{-1} = 0$$

- Instead we will use the following equations for  $I_1$  and  $I_2$  with time delays.

$$I_{1\_alt} := \frac{(I_{ABC_0} + a^{-2} \cdot I_{ABC_1} + a^{-1} \cdot I_{ABC_2})}{3}$$

↑  
delay      delay

$$I_2 \text{ alt} := \frac{I_{ABC_0} + a^{-1} \cdot I_{ABC_1} + a^{-2} \cdot I_{ABC_2}}{3}$$

*$I_A - a^2 I_B + a I_C$*

As a check

 *$\Sigma$* 

$$I_1 \text{ alt} - I_{012_1} = (-4.547 \times 10^{-13} - 2.274i \times 10^{-13}) A$$

$$I_1 \text{ alt} - I_{012_1} = (-4.547 \times 10^{-13} - 2.274i \times 10^{-13}) A$$


 *$\Sigma'$* 

- Find sequence current breaking angle rotations as time delays

$$i_0(t) := \frac{(i_a(t) + i_b(t) + i_c(t))}{3}$$

$$i_1(t) := \frac{(i_a(t) + i_b(t - T_{a\_sq}) + i_c(t - T_a))}{3}$$
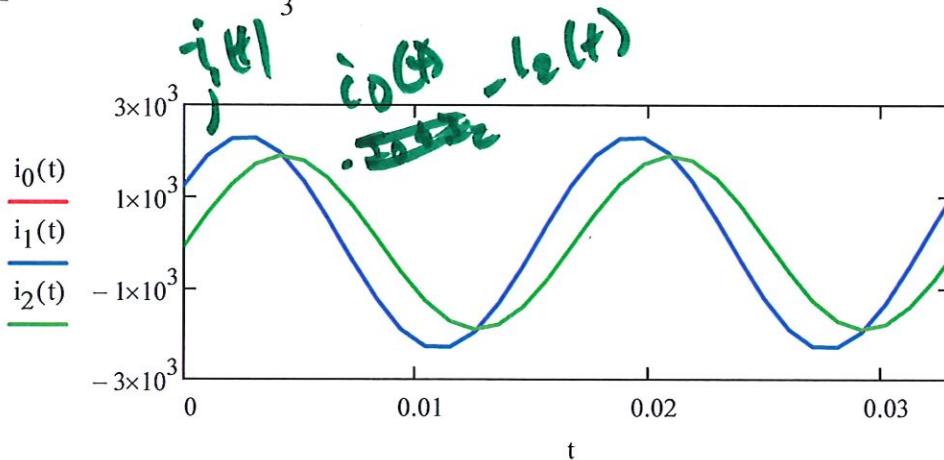
$$i_2(t) := \frac{(i_a(t) + i_b(t + T_a) + i_c(t + T_a))}{3}$$



$$i_0 \text{ check}(t) := i_0(t) - \sqrt{2} \cdot |I_{012_0}| \cdot \cos(\omega \cdot t + \arg(I_{012_0}))$$

$$i_1 \text{ check}(t) := i_1(t) - \sqrt{2} \cdot |I_{012_1}| \cdot \cos(\omega \cdot t + \arg(I_{012_1}))$$

$$i_2 \text{ check}(t) := i_2(t) - \sqrt{2} \cdot |I_{012_2}| \cdot \cos(\omega \cdot t + \arg(I_{012_2}))$$