


ECE 523
Symmetrical Components

Session 8

$$v_a(t) := \sqrt{2} \cdot |V_{ABC_0}| \cdot \cos(\omega \cdot t + \arg(V_{ABC_0}))$$

$$v_b(t) := \sqrt{2} \cdot |V_{ABC_1}| \cdot \cos(\omega \cdot t + \arg(V_{ABC_1}))$$

$$v_c(t) := \sqrt{2} \cdot |V_{ABC_2}| \cdot \cos(\omega \cdot t + \arg(V_{ABC_2}))$$

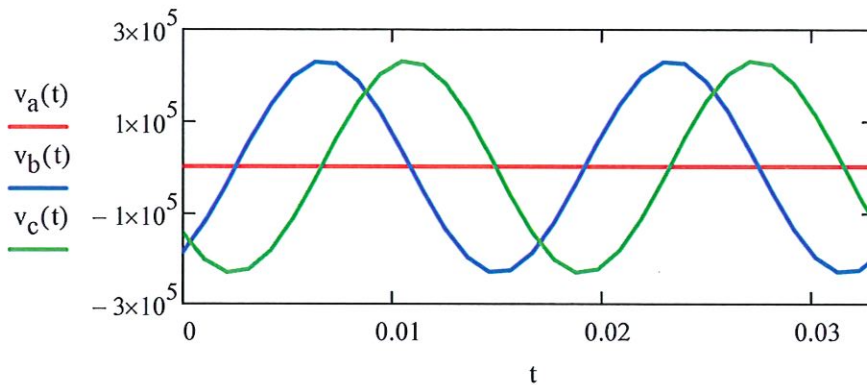

- Convert a and a^2 to units of time

$$T_a := \frac{\arg(a)}{360\text{deg} \cdot 60\text{Hz}} \quad T_a = 5.556 \cdot \text{ms}$$

$$T_{a_sq} := \frac{\arg(a^2) + 360\text{deg}}{360\text{deg} \cdot 60\text{Hz}} \quad T_{a_sq} = 11.111 \cdot \text{ms}$$

-1200
-2400

Note that: $I_1 = (I_A + a \cdot I_B + a^2 \cdot I_C) / 3$

- This equation involves rotating I_B and I_C by positive angles, which would mean advancing in time.
- We can only delay measurements, not advance them
- Recall that:

$$a = a^{-2} \quad a - a^{-2} = 0$$

$$a^2 = a^{-1} \quad a^2 - a^{-1} = 0$$

- Instead we will use the following equations for I_1 and I_2 with time delays.

$$I_{1_alt} := \frac{I_A + a^2 I_B + a I_C}{3}$$

(I_{ABC_0} + a^{-2} \cdot I_{ABC_1} + a^{-1} \cdot I_{ABC_2})

delay *delay*

02/19/27
61/19
87

$$I_{2_alt} := \frac{I_{ABC_0} + a^{-1} \cdot I_{ABC_1} + a^{-2} \cdot I_{ABC_2}}{3}$$

As a check

$$I_{1_alt} - I_{012_1} = (-4.547 \times 10^{-13} - 2.274i \times 10^{-13}) A$$


$$I_{2_alt} - I_{012_2} = (-4.547 \times 10^{-13} - 2.274i \times 10^{-13}) A$$

- Find sequence current tracking angle rotations as time delays

$$i_0(t) := \frac{i_a(t) + i_b(t) + i_c(t)}{3}$$

$$i_1(t) := \frac{i_a(t) + i_b(t - T_{a_sq}) + i_c(t - T_a)}{3}$$
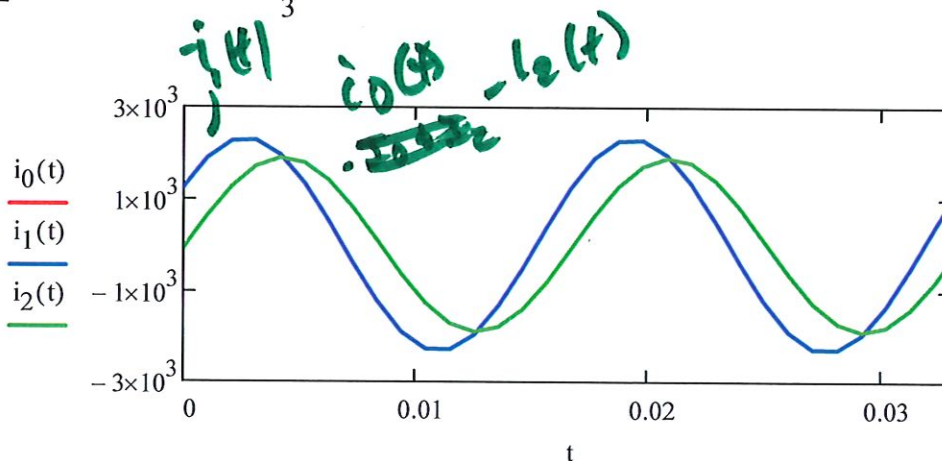
$$i_2(t) := \frac{i_a(t) + i_b(t + T_a) + i_c(t + T_a)}{3}$$




$$i_{0_check}(t) := i_0(t) - \sqrt{2} \cdot |I_{012_0}| \cdot \cos(\omega \cdot t + \arg(I_{012_0}))$$

$$i_{1_check}(t) := i_1(t) - \sqrt{2} \cdot |I_{012_1}| \cdot \cos(\omega \cdot t + \arg(I_{012_1}))$$


$$i_{2_check}(t) := i_2(t) - \sqrt{2} \cdot |I_{012_2}| \cdot \cos(\omega \cdot t + \arg(I_{012_2}))$$

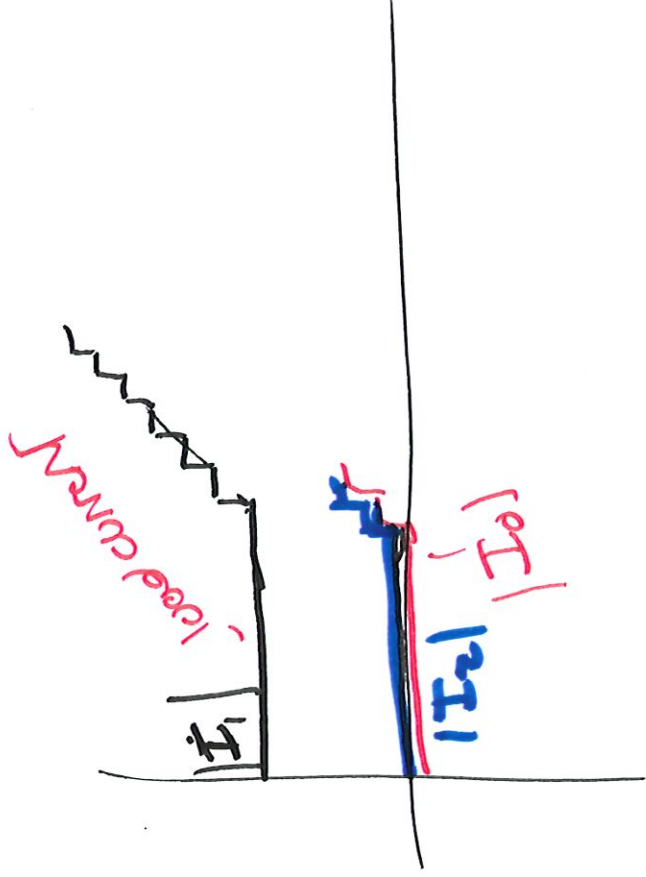Processing measurement with
digital filter



Analyzing Shunt & Series Unbalanced Conditions \Rightarrow FAULTS

(1) Shunt faults
(1) 3 phase fault

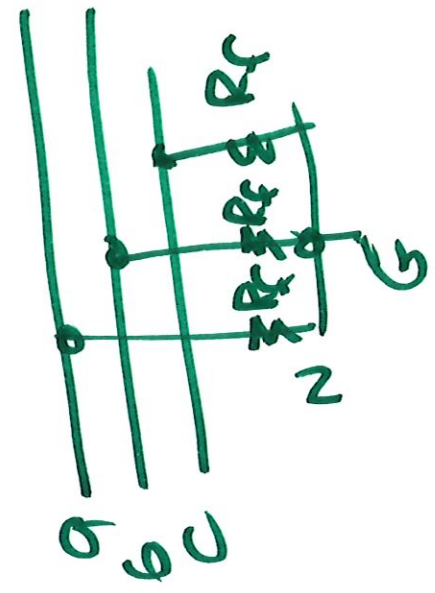

- Generally analyzed as balanced
- If balanced just positive sequence
- worst case - $R_f = 0 \Rightarrow$ Bolted Fault

(2) Single line to ground (single phase to ground faults) → (80-85% of fault overhead lines) (ground faults)

(3) Line to line (phase to phase)

(4) Double line to ground - often evolve from single line to ground

(5) Simultaneous shunt faults at different locations: BG
AG

Series unbalance (series faults)

usually has conductor
fail to ground

(1) single phase open

→ Failure cases: (1) Broken conductor

(2) Breaker pole fails to close

→ controlled cases . . .


→ Single pole tripping
- trip both ends

(2) Two phase open → one breaker pole fails to open




③ Transient series imbalance

→ series capacitors

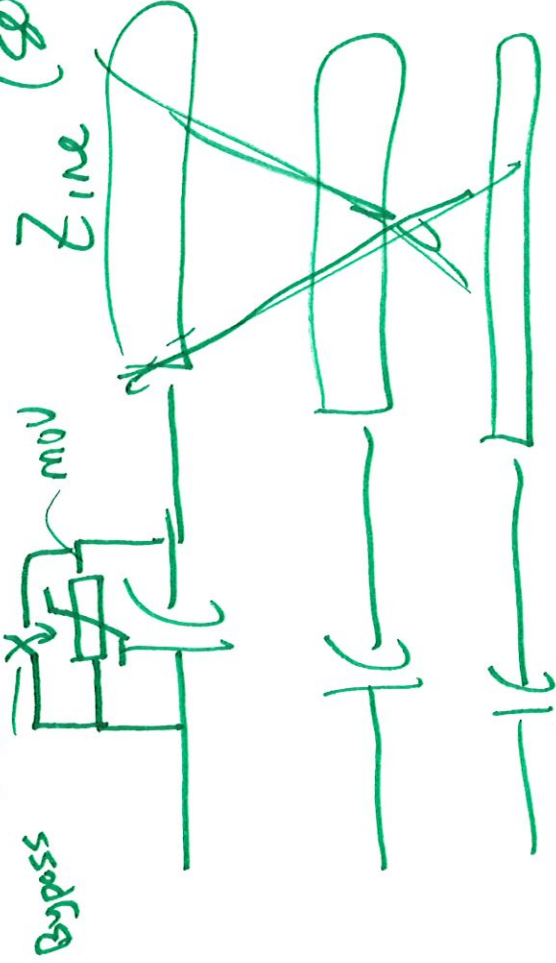


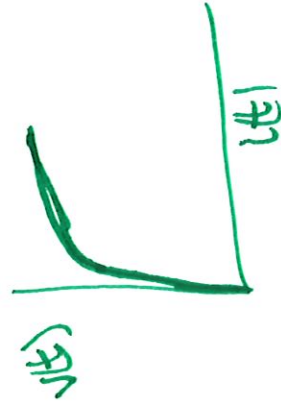(self & mutual) $f_2 \Rightarrow f_0, f_1$



3 phase fault

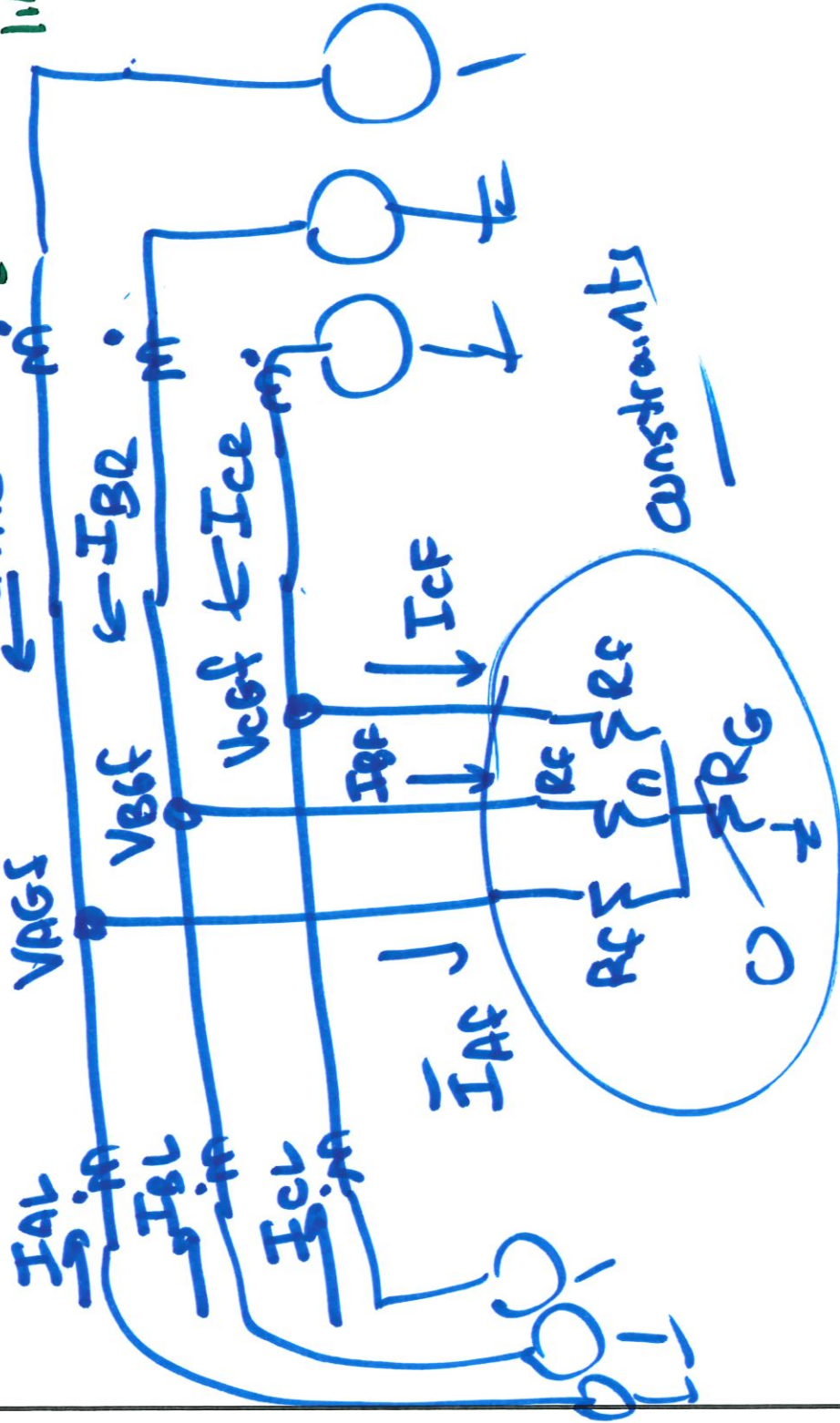- constraints at fault point
- Positive polarity into line.



Constraints at fault point

$$\bar{V}_{AGf} = R_f \cdot \bar{I}_{Af}$$

$$\bar{V}_{BGf} = R_f \cdot \bar{I}_{Bf}$$

$$\bar{V}_{CGf} = R_f \cdot \bar{I}_{Cf}$$


Balanced if system / sources / impedances / balanced

manipulate

$$\bar{V}_{AG} + \bar{V}_{BG} + \bar{V}_{CG} = R_f (\bar{I}_{Af} + \bar{I}_{Bf} + \bar{I}_{Cf}) = 0$$

$$3I_0 = 0$$

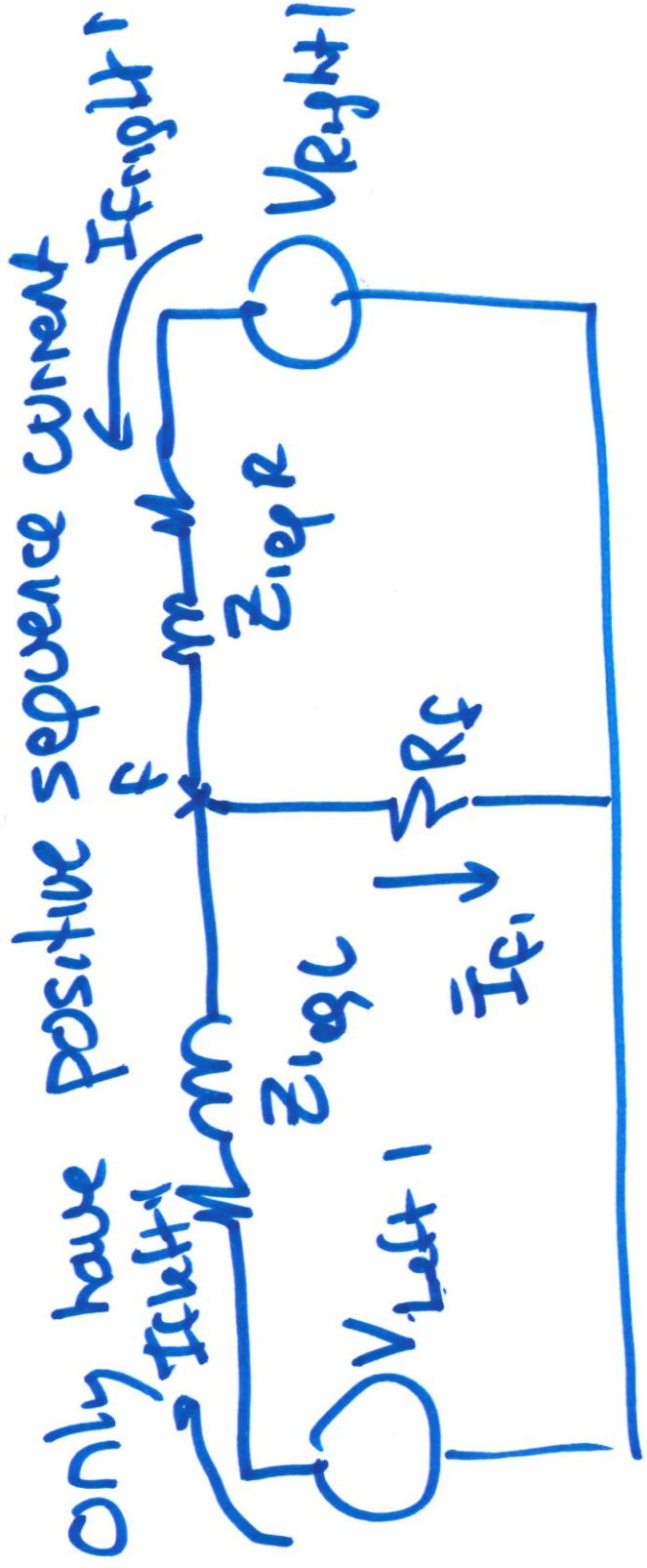
Since ~~some~~ balanced $\bar{V}_2 \neq \bar{I}_2$ are zero



Solution approach - General (not just 30)

1) Build per unit equivalent circuits in pos, neg & zero sequence for the system.

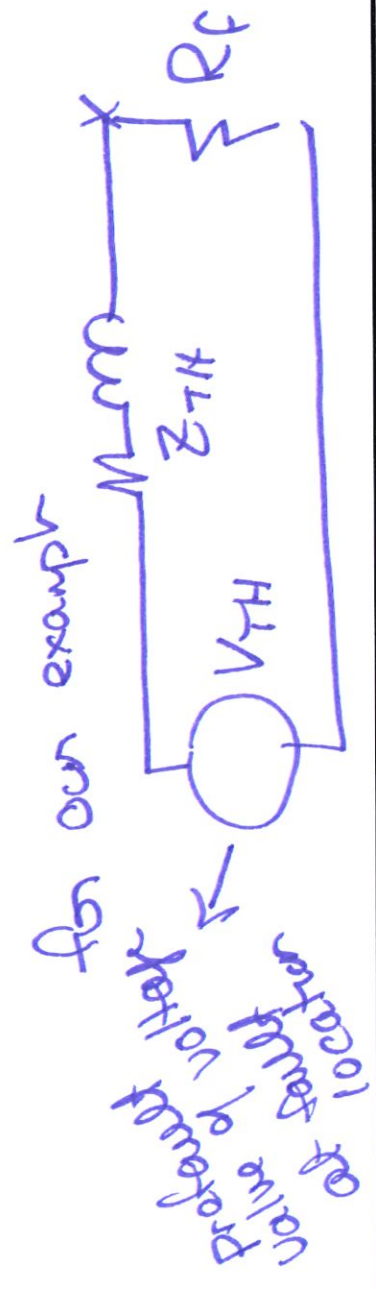2) Thevenin' equivalent impedances looking from fault location $Z_{TH0}, Z_{TH1}, Z_{TH2}$



(3) find I_{if} , I_{zf} , I_{of}

(4) use current divider (or other) to

find sequence current from

left + right = convert sequence currents to ABC if needed

(5) Find sequence voltages


at buses of interest - convert to ABC

LE 13/19

Fault Analysis Techniques to Find Voltages and Currents at Other Buses With Transformer Phase Shifts

Define units: MVA := MW
MVAR := MVA

System Description:

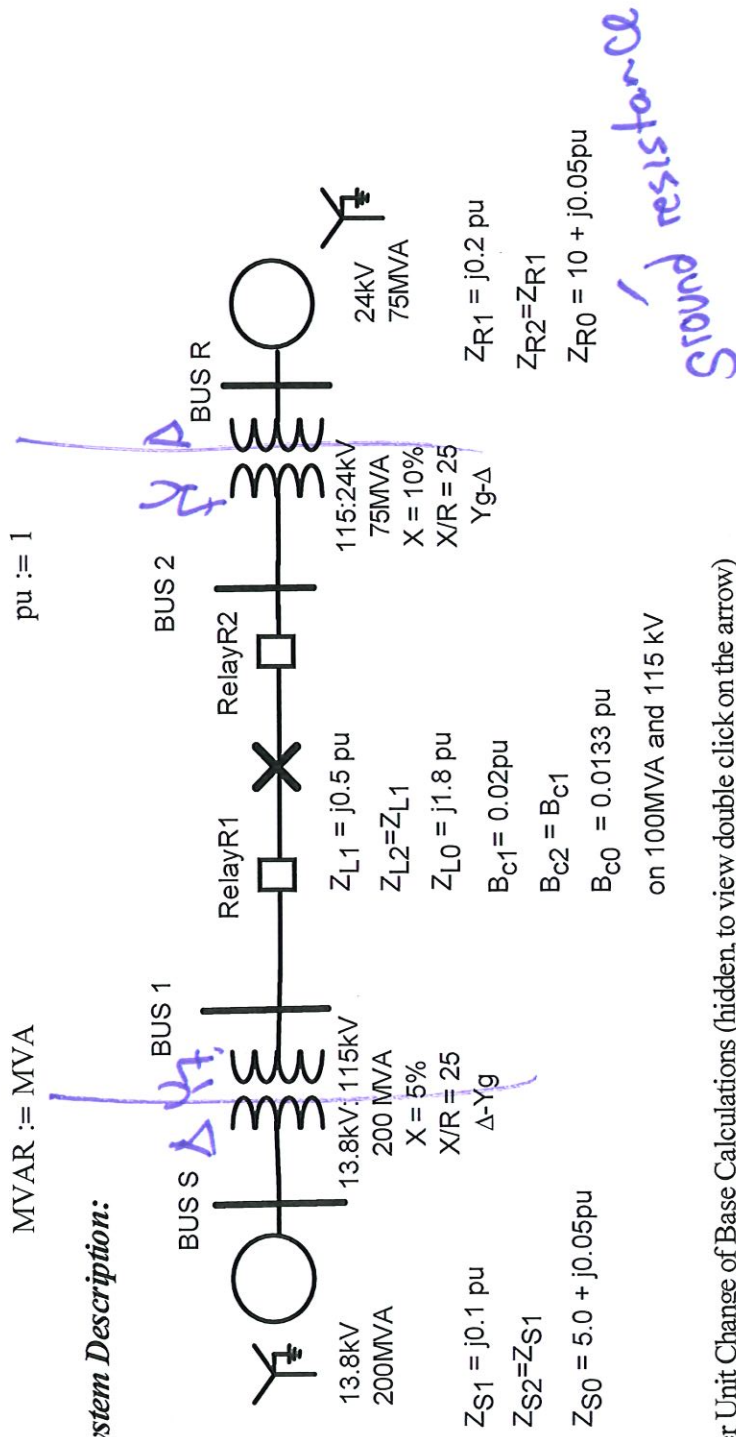

Per Unit Change of Base Calculations (hidden, to view double click on the arrow)

Set bases (Use the line voltage of 115kV as the reference):

$$S_b := 100\text{MVA} \quad V_{b2} := 115\text{kV} \quad V_{b3} = 24\text{kV}$$

$$V_{b1} := V_{b2} \cdot \frac{13.8\text{kV}}{115\text{kV}} \quad V_{b3} := V_{b2} \cdot \frac{24\text{kV}}{115\text{kV}}$$

$$V_{b1} = 13.8\text{kV} \quad V_{b3} = 24\text{kV}$$

18 14/19

Change of Base Calculations:

Generator 1: $S_{g1} := 200\text{MVA}$ $X_{G1\text{old}} := 0.1\text{pu}$ $Z_{G1\text{old}} := 5.0 + j \cdot 0.05\text{pu}$

$V_{g1} := 13.8\text{kV}$

$X_{G11} := X_{G1\text{old}} \cdot \left(\frac{V_{g1}}{V_{b1}}\right)^2 \cdot \left(\frac{S_b}{S_{g1}}\right)$ $X_{G11} = 0.05\text{pu}$ $X_{G12} := X_{G11}$

$Z_{G10} := Z_{G1\text{old}} \cdot \left(\frac{V_{g1}}{V_{b1}}\right)^2 \cdot \left(\frac{S_b}{S_{g1}}\right)$ $Z_{G10} = (2.5 + 0.025j)\text{pu}$

Transformer 1: $X_{T1\text{old}} := 0.05\text{pu}$ $R_{T1\text{old}} := \frac{X_{T1\text{old}}}{25}$ $R_{T1\text{old}} = 0.002\text{pu}$ • Small enough to neglect

$X/R = 25$

$V_{T1\text{old}} := 13.8\text{kV}$ $S_{T1} := 200\text{MVA}$

$X_{T11} := X_{T1\text{old}} \cdot \left(\frac{V_{T1\text{old}}}{V_{b1}}\right)^2 \cdot \left(\frac{S_b}{S_{T1}}\right)$ $X_{T11} = 0.025\text{pu}$

$Z_{T11} := j \cdot X_{T11}$ $|Z_{T11}| = 0.025\text{pu}$ $\arg(Z_{T11}) = 90\text{deg}$

$Z_{T12} := Z_{T11}$ $Z_{T10} := Z_{T11}$

Transmission Line (no change of base needed):

$Z_{L11} := 0.5\text{pu} \cdot e^{j \cdot 90\text{deg}}$ $Z_{L11} = 0.5j\text{pu}$

L8 15/19

concentrated
or series impedances

$$Z_{L12} := Z_{L11}$$

$$Z_{L10} := 1.8 \text{ pu} \cdot e^{j \cdot 90 \text{ deg}} \quad Z_{L10} = 1.8i \cdot \text{pu}$$

Transformer 2: $X_{T2old} := 0.10 \text{ pu}$ $R_{T2old} := \frac{X_{T2old}}{25}$ $R_{T2old} = 0.004 \cdot \text{pu}$ • Again, neglect

$$V_{T2old} := 115 \text{ kV} \quad S_{T2} := 75 \text{ MVA}$$

$$X_{T21} := X_{T2old} \cdot \left(\frac{V_{T2old}}{V_{b2}} \right)^2 \cdot \left(\frac{S_b}{S_{T2}} \right) \quad X_{T21} = 0.1333 \cdot \text{pu}$$

$$Z_{T21} := j \cdot X_{T21} \quad |Z_{T21}| = 0.1333 \cdot \text{pu} \quad \arg(Z_{T21}) = 90 \cdot \text{deg}$$

$$Z_{T22} := Z_{T21} \quad Z_{T20} := Z_{T21}$$

Generator 2: $S_{g2} := 75 \text{ MVA}$ $X_{G21old} := 0.2 \text{ pu}$ $Z_{G20old} := 10.0 + j \cdot 0.05 \text{ pu}$



$$V_{g2} := 24 \text{ kV}$$

$$X_{G21} := X_{G21old} \cdot \left(\frac{V_{g2}}{V_{b3}} \right)^2 \cdot \left(\frac{S_b}{S_{g2}} \right) \quad X_{G21} = 0.2667 \cdot \text{pu} \quad X_{G22} := X_{G21}$$

$$Z_{G20} := Z_{G20old} \cdot \left(\frac{V_{g2}}{V_{b3}} \right)^2 \cdot \left(\frac{S_b}{S_{g2}} \right) \quad Z_{G20} = (13.3333 + 0.0667j) \cdot \text{pu}$$



L8 16/19

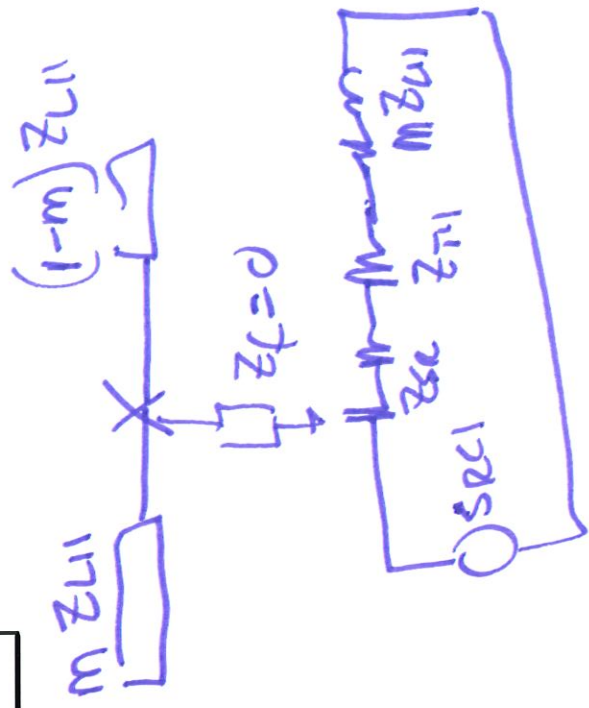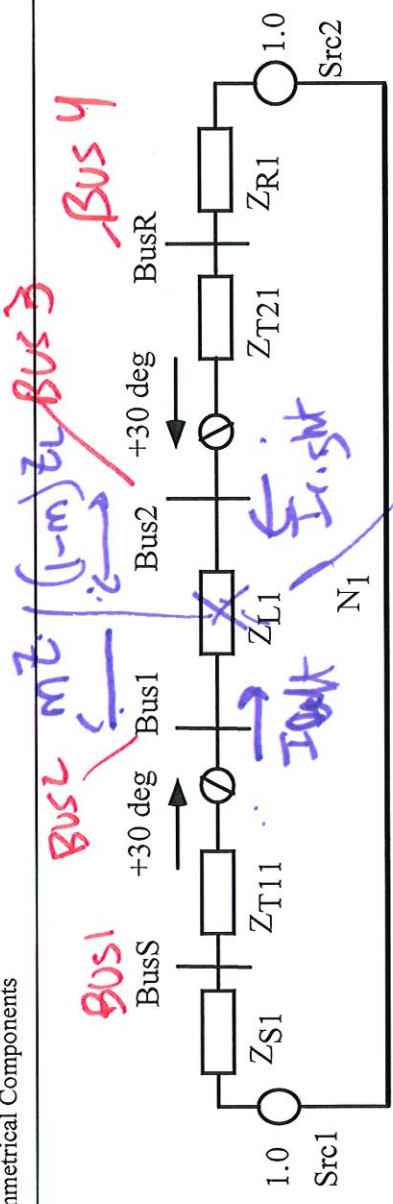

- Regular circuit analysis approach:
- Calculate reduced equivalent for several fault locations
- Use a generic location, M , and define a Mathcad function:

$$Z_{left}(M) := j \cdot X_{G11} + Z_{T11} + Z_{L11} \cdot M$$

$$Z_{right}(M) := Z_{L11} \cdot (1 - M) + Z_{T21} + j \cdot X_{G21}$$

$$Z_{1equiv}(M) := \left[\frac{1}{j \cdot X_{G11} + Z_{T11} + Z_{L11} \cdot M} + \frac{1}{Z_{L11} \cdot (1 - M) + Z_{T21} + j \cdot X_{G21}} \right]^{-1}$$

- More compactly: $Z_{1thev}(M) := \left(\frac{1}{Z_{left}(M)} + \frac{1}{Z_{right}(M)} \right)^{-1}$

$V_f := 1.0pu \rightarrow$ Both sources at 1.0 - referred to side of transformer high side of transformer

$$I_{3ph}(M) := \frac{V_f}{Z_{1equiv}(M)}$$

$$I_{3ph}(0.5) = -4.6154i$$

Total fault current on phase A

$M = 0.5$

L8 17/19

- Now use current divider to find current from left and right (through the relays)

$$I_{\text{left}}(M) := I_{3\text{ph}}(M) \cdot \frac{Z_{\text{right}}(M)}{Z_{\text{left}}(M) + Z_{\text{right}}(M)}$$

$$I_{\text{left}}(0.5) = -3.0769i$$

$$I_{\text{right}}(M) := I_{3\text{ph}}(M) \cdot \frac{Z_{\text{left}}(M)}{Z_{\text{left}}(M) + Z_{\text{right}}(M)}$$

$$I_{\text{right}}(0.5) = -1.5385i$$

- Now find voltages at bus 1 and bus 2 (start from sequence neutral plane, not fault location):

$$V_S := 1.0 \quad V_R := 1.0 \quad \text{- referred to HV side}$$

$$V_{\text{bus2}}(M) := V_S - I_{\text{left}}(M) \cdot (j \cdot X_{G11} + Z_{T11})$$

$$V_{\text{bus2}}(0.5) = 0.7692$$

$$V_{\text{bus3}}(M) := V_R - I_{\text{right}}(M) \cdot (j \cdot X_{G21} + Z_{T21})$$

$$V_{\text{bus3}}(0.5) = 0.3846$$

- Now find voltage and current on the generator side of the transformer (including transformer phase shift)

$$I_{\text{SrcS}}(M) := I_{\text{left}}(M) \cdot e^{-j \cdot 30\text{deg}}$$

$$|I_{\text{SrcS}}(0.5)| = 3.0769$$

$$\arg(I_{\text{SrcS}}(0.5)) = -120\text{deg}$$

$$I_{\text{SrcR}}(M) := I_{\text{right}}(M) \cdot e^{-j \cdot 30\text{deg}}$$

$$|I_{\text{SrcR}}(0.5)| = 1.5385$$

$$\arg(I_{\text{SrcR}}(0.5)) = -120\text{deg}$$

$$V_{\text{bus1}}(M) := V_S \cdot e^{-j \cdot 30\text{deg}} - I_{\text{SrcS}}(M) \cdot (j \cdot X_{G11})$$

$$|V_{\text{bus1}}(0.5)| = 0.8462$$

$$\arg(V_{\text{bus1}}(0.5)) = -30\text{deg}$$

$$V_{\text{bus4}}(M) := V_R \cdot e^{-j \cdot 30\text{deg}} - I_{\text{SrcR}}(M) \cdot (j \cdot X_{G21})$$


$$|V_{\text{bus4}}(0.5)| = 0.5897$$

$$\arg(V_{\text{bus4}}(0.5)) = -30\text{deg}$$

Handwritten notes:
 $I_{\text{left}}(M) \cdot M Z_{\text{fault}}(M)$
 $I_{\text{right}}(M) \cdot (1-M) Z_{\text{fault}}(M)$
 - same as

Handwritten notes:
 for fault
 $\angle -30^\circ$

Pos sequence voltage profile

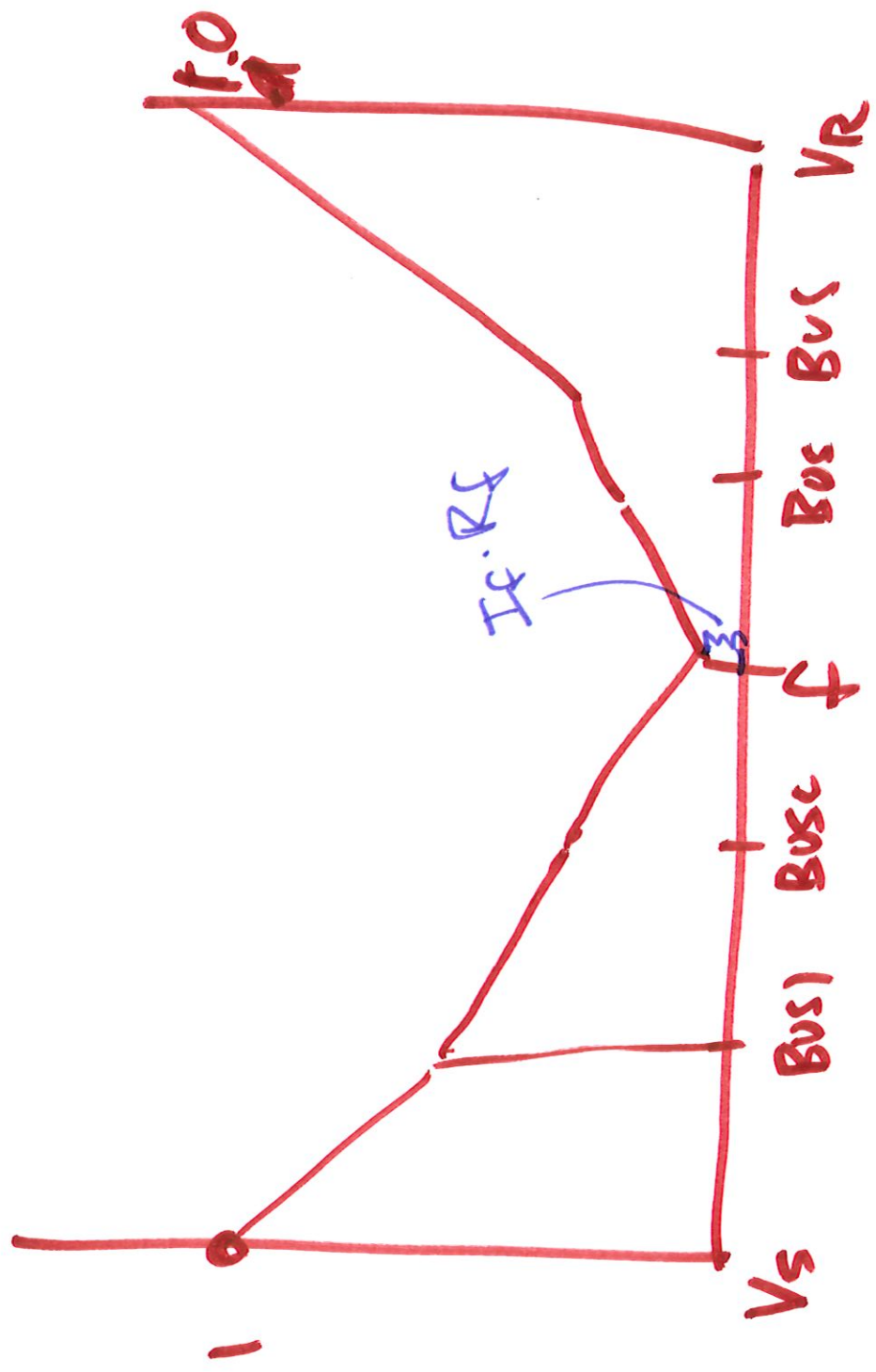

- modified 4 BUS

1. neglect shunt caps of lines.
2. Include internal impedances of generators & large motors



3 Z Bus Matrix Approach

Easiest Approach is to Create Ybus Matrix. Modified for Fault Calculations:

Transformer Phase Shift:

$$Y_1(M) := \begin{bmatrix} \frac{1}{jX_{G11}} + \frac{1}{Z_{T11}} & \frac{-1 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T11}} & 0 & 0 & 0 \\ \frac{-1 \cdot e^{j \cdot 30 \text{deg}}}{Z_{T11}} & \frac{1}{Z_{T11}} + \frac{1}{M \cdot Z_{L11}} & 0 & 0 & \frac{-1}{M \cdot Z_{L11}} \\ 0 & 0 & \frac{1}{Z_{T21}} + \frac{1}{(1-M) \cdot Z_{L11}} & \frac{-1 \cdot e^{j \cdot 30 \text{deg}}}{Z_{T21}} & \frac{-1}{(1-M) \cdot Z_{L11}} \\ 0 & 0 & \frac{-1 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T21}} & \frac{1}{Z_{T21}} + \frac{1}{jX_{G21}} & 0 \\ 0 & \frac{-1}{M \cdot Z_{L11}} & \frac{-1}{(1-M) \cdot Z_{L11}} & 0 & \frac{1}{M \cdot Z_{L11}} + \frac{1}{(1-M) \cdot Z_{L11}} \end{bmatrix}$$

$$Z_1(M) := Y_1(M)^{-1}$$

$$Z_1(0.5) = \begin{pmatrix} 0.0474i & 0.0231 + 0.04i & 0.0103 + 0.0178i & 0.0137i & 0.0167 + 0.0289i \\ -0.0231 + 0.04i & 0.0692i & 0.0308i & -0.0103 + 0.0178i & 0.05i \\ -0.0103 + 0.0178i & 0.0308i & 0.2359i & -0.0786 + 0.1362i & 0.1333i \\ 0.0137i & 0.0103 + 0.0178i & 0.0786 + 0.1362i & 0.1937i & 0.0444 + 0.077i \\ -0.0167 + 0.0289i & 0.05i & 0.1333i & -0.0444 + 0.077i & 0.2167i \end{pmatrix}$$