


ECE 525


POWER SYSTEM PROTECTION
AND RELAYING

SESSION no. 10

HW 2

Problem 4

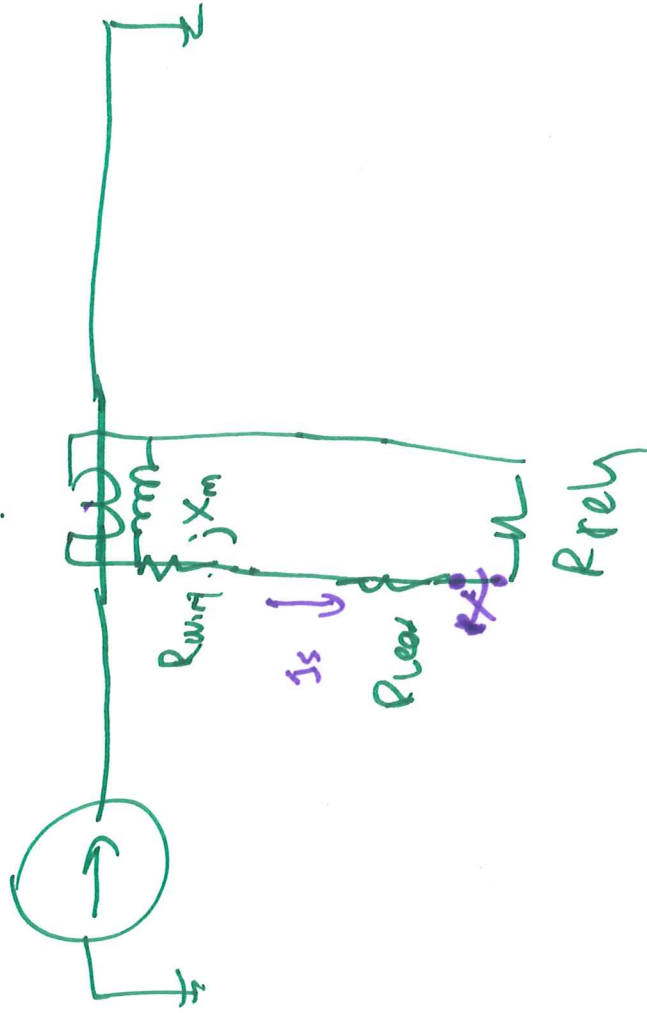

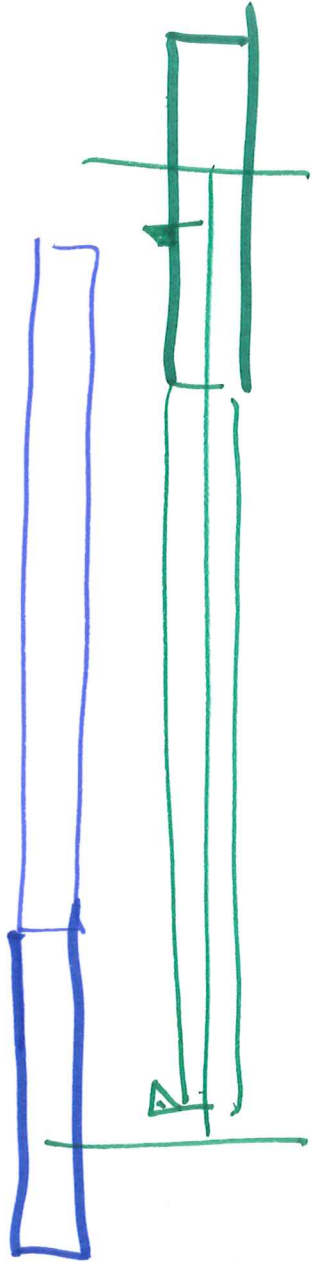

POTI, - other comm aided distance

M/K
L10
017


Then:
$$\frac{1}{\omega \cdot C_1} = \left(\frac{1}{\omega \cdot C_2} \right) \cdot \left[\left(\frac{V_{LL}}{\sqrt{3} \cdot V_{C2}} \right) - 1 \right]$$

$$C_1 := \left[\left(\frac{\omega}{\omega \cdot C_2} \right) \cdot \left[\left(\frac{V_{LL}}{\sqrt{3} \cdot V_{C2}} \right) - 1 \right] \right]^{-1}$$

$C_1 = 7.89 \cdot \text{nF}$

As a check:
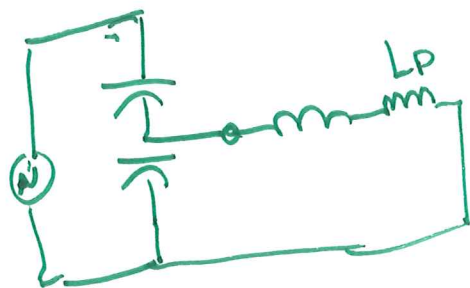
$$\left(\frac{V_{LL}}{\sqrt{3}} \cdot \frac{\frac{1}{\omega \cdot C_2}}{\frac{1}{\omega \cdot C_1} + \frac{1}{\omega \cdot C_2}} \right) = 11 \cdot \text{kV}$$



b) Determine the tuning inductance, L_T

$$C_{\text{equiv}} := C_1 + C_2$$

$$L_T := \left[\frac{1}{(2 \cdot \pi \cdot f_{\text{nominal}})^2 \cdot C_{\text{equiv}}} - L_p \right]$$

$L_T = 43.64 \cdot \text{H}$

60Hz
LC resonance

c) Given the following burden and ferro-resonance filter information calculate the magnitude and phase error in the voltage across the burden under steady-state nominal conditions.



Burden

$R_b := 400.9 \cdot \Omega$

$L_b := 1.84 \cdot \text{H}$

$R_{bp} := 785 \cdot \Omega$

Ferroresonance Filter

$R_{F1} := 1.06 \cdot \Omega$

$R_{F2} := 4.24 \cdot \Omega$

$C_F := 13.8 \cdot 10^{-6} \cdot \text{F}$

$L_{F1} := 0.1 \cdot \text{H}$

$L_{F2} := 0.394 \cdot \text{H}$

$R_F := 40 \cdot \Omega$


- The impedance of the ferroresonance filter is ~~much higher than that of the burden~~, so it can be neglected. But if it is included, it has a 60Hz impedance of:

$f := 0,001\text{Hz}..200\text{Hz} \quad \omega(f) := 2 \cdot \pi \cdot f$

$$Z_{\text{ferro}}(\omega) := R_F + \left(\frac{1}{R_{F1} + j \cdot \omega \cdot L_{F1}} + \frac{1}{\frac{1}{j \cdot \omega \cdot C_F} + R_{F2} + j \cdot \omega \cdot L_{F2}} \right)^{-1}$$

$$|Z_{\text{ferro}}(2 \cdot \pi \cdot 60\text{Hz})| = 233.65 \Omega$$
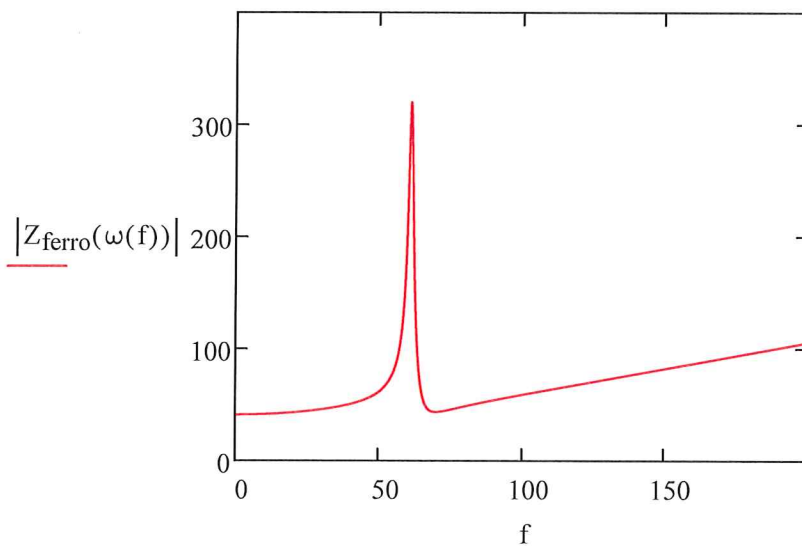
$$\arg(Z_{\text{ferro}}(2 \cdot \pi \cdot 60\text{Hz})) = 44.6 \cdot \text{deg}$$



Reset ω

$$\omega := 2 \cdot \pi \cdot 60\text{Hz}$$

- Equivalent burden impedance:

$$Z_{\text{Burden}} := \left(\frac{1}{R_{bp}} + \frac{1}{R_b + j \cdot \omega \cdot L_b} \right)^{-1}$$

$$|Z_{\text{Burden}}| = 457.78 \Omega$$

$$\arg(Z_{\text{Burden}}) = 29.65 \cdot \text{deg}$$

- Parallel Burden with Filter:

$$Z_{\text{para}} := \left(\frac{1}{Z_{\text{ferro}}(\omega)} + \frac{1}{Z_{\text{Burden}}} \right)^{-1}$$

$$|Z_{\text{para}}| = 155.88 \Omega$$

$$\arg(Z_{\text{para}}) = 39.56 \cdot \text{deg}$$

- Secondary winding:

$$Z_{\text{sec_winding}} := R_s + j \cdot \omega \cdot L_s \quad Z_{\text{sec_winding}} = (0.03 + 0.01i) \Omega$$

- Primary impedances:

$$Z_{c1} := \frac{1}{j \cdot \omega \cdot C_1} \quad Z_{c2} := \frac{1}{j \cdot \omega \cdot C_2} \quad Z_T := j \cdot \omega \cdot L_T$$

$$Z_{\text{prim_winding}} := R_p + j \cdot \omega \cdot L_p$$

- Refer primary impedances to secondary: $a := \frac{11\text{kV}}{67\text{V}}$

$$Z'_{c1} := \frac{Z_{c1}}{a^2} \quad Z'_{c1} = -12.47i \Omega \quad Z'_{c2} := \frac{Z_{c2}}{a^2} \quad Z'_{c2} = -0.73i \Omega$$

$$Z'_T := \frac{Z_T}{a^2} \quad Z'_T = 0.61i \Omega \quad Z'_{\text{prim_winding}} := \frac{Z_{\text{prim_winding}}}{a^2}$$

$$Z'_{\text{prim_winding}} = (0.01 + 0.08i) \Omega$$

- Equivalent impedance seen from source, referred to secondary:


$$Z_{\text{equiv_CCVT}} := Z'_{c1} + \left[\frac{1}{Z'_{c2}} + \frac{1}{(Z'_T + Z'_{\text{prim_winding}} + Z_{\text{sec_winding}} + Z_{\text{para}})} \right]^{-1}$$

$$Z_{\text{equiv_CCVT}} = (0 - 13.2i) \Omega$$

- Total current drawn by CCVT from source (secondary amps)-includes both capacitors referred to secondary, so use system voltage not V_{c2}

$$V_{\text{Line_sec}} := \frac{V_{LL}}{a \cdot \sqrt{3}} \quad V_{\text{Line_sec}} = 1213.22 \text{ V}$$
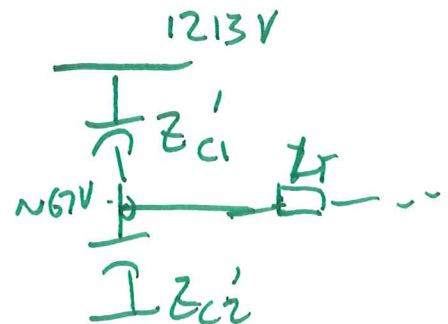
$$I_{\text{total}} := \frac{V_{\text{Line_sec}}}{Z_{\text{equiv_CCVT}}} \quad I_{\text{total}} = (0.02 + 91.9i) \text{ A}$$



M/E 017

- Current Divider between C2 and VT:

$$I_{VT} := I_{total} \cdot \left[\frac{Z'_{c2}}{Z'_{c2} + (Z'_T + Z'_{prim_winding} + Z'_{sec_winding} + Z_{para})} \right]$$

$$|I_{VT}| = 0.43 \text{ A}$$

- Voltage across burden

$$V_{burden} := I_{VT} \cdot Z_{para} \quad |V_{burden}| = 66.98 \text{ V} \quad \arg(V_{burden}) = 0.01 \cdot \text{deg}$$

- Error Calculations

$$V_{rated_sec} := \left(\frac{V_{LL}}{\sqrt{3}} \cdot \frac{\frac{1}{\omega \cdot C_2}}{\frac{1}{\omega \cdot C_1} + \frac{1}{\omega \cdot C_2}} \right) \cdot \frac{1}{a} \quad V_{rated_sec} = 67 \text{ V}$$

Magnitude Error:

$$V_{rated_sec} - |V_{burden}| = 0.02 \text{ V}$$

Percent Magnitude Error:

$$\frac{V_{rated_sec} - |V_{burden}|}{V_{rated_sec}} = 0.03 \cdot \%$$

- Since reference voltage is at 0 degrees

$$\text{Angle_error} := \arg(V_{burden}) \quad \text{Angle_error} = 0.01 \cdot \text{deg}$$

Define units for angle smaller than degree


$$\text{arcmin} := \frac{\text{deg}}{60} \quad \text{Angle_error} = 0.47 \cdot \text{arcmin} \quad \text{in minutes of arc}$$

$$\text{arcsec} := \frac{\text{arcmin}}{60} \quad \text{Angle_error} = 28.3 \cdot \text{arcsec} \quad \text{in seconds of arc}$$

"Emerging" Technologies

- CTs without iron cores
- Linear couplers
- Rogowski coils
- Optical CTs
- optical VTs

Most Applications

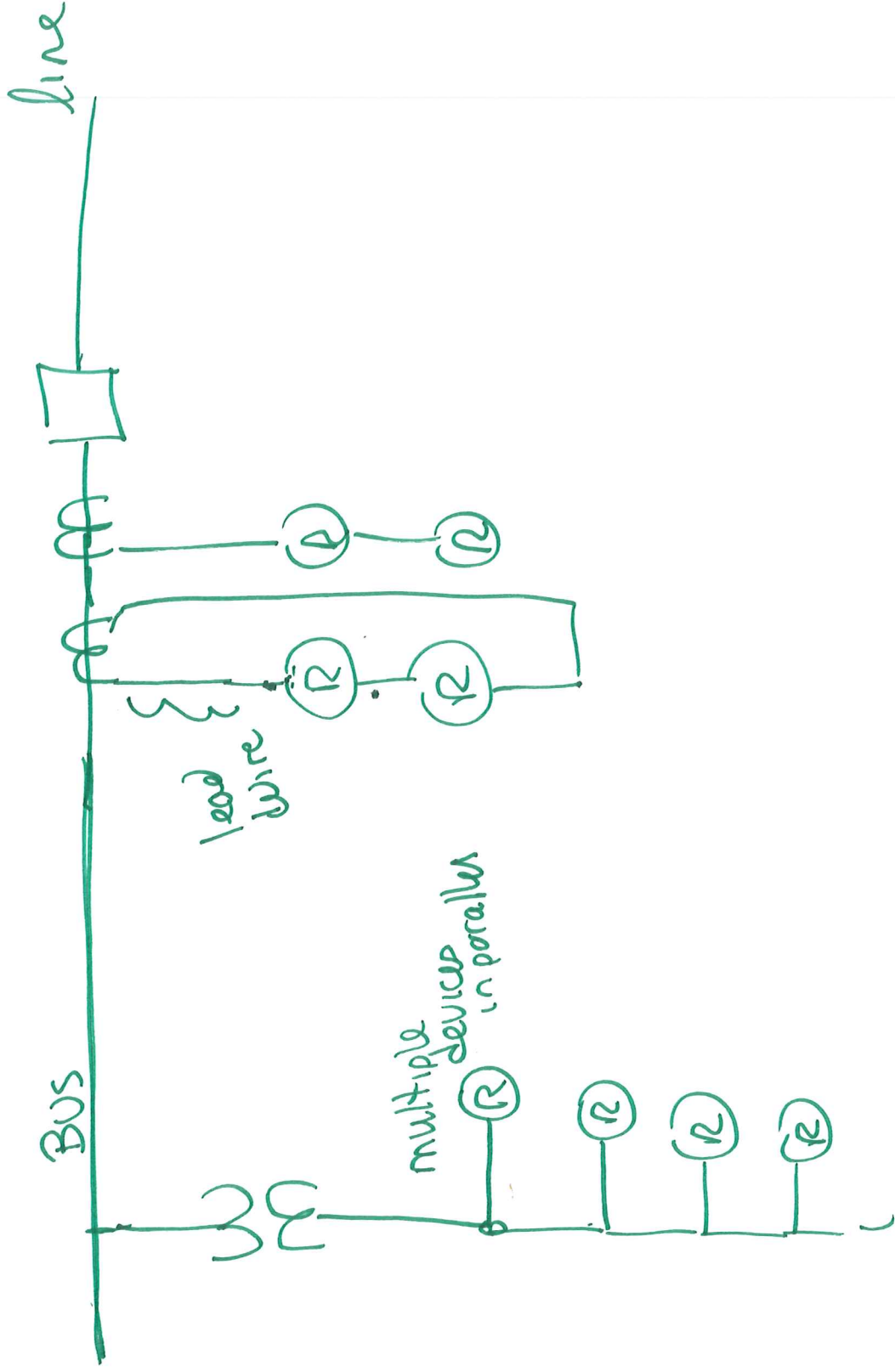

- ~~can~~ "Relays" or Metering devices
subscribe to measurements
off that network
- provides opportunity
to combine measurements

IEC 61850

→ Communication inside a substation

- initial driver - interoperability
between vendors

→ Process Bus/Sampled Values

→ measurement devices

(CT, PT/VT etc)


→ physical connection to

device that calculates/processes
measurement


→ Broadcast them on a substation
network

Distribution System Protection

→ Now vs Future

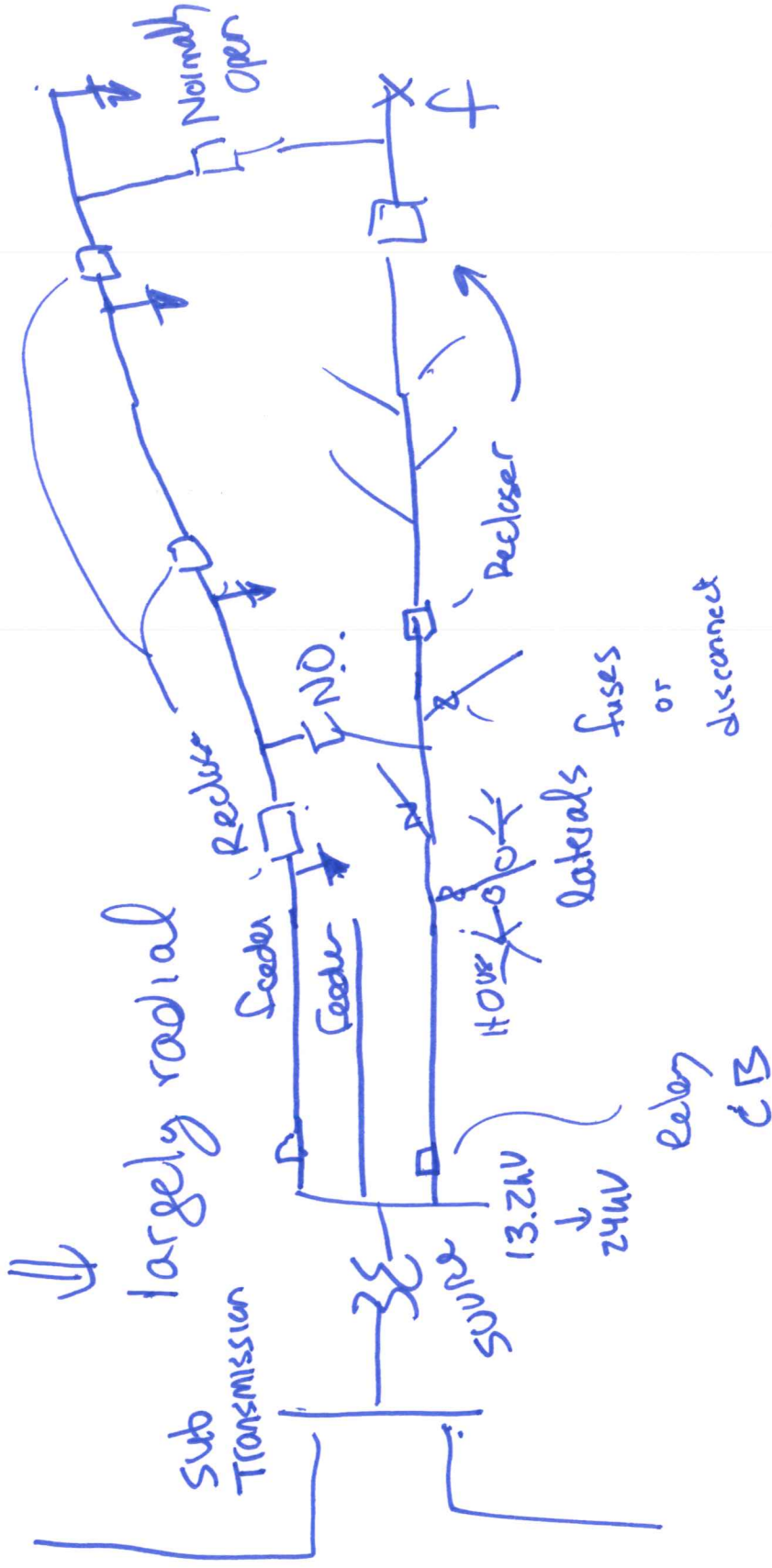

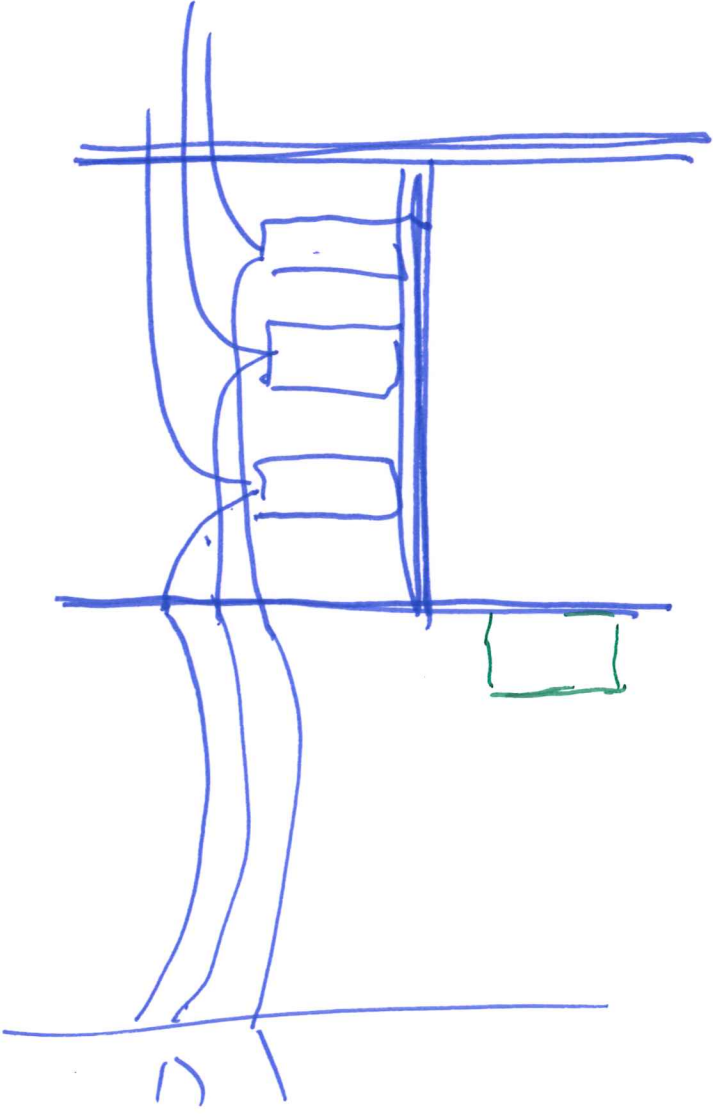→ Primary protected with overcurrent relays



Complications

- Increased reconfigurability
 - Distributed generation
 - ↳ Household or building generation
- PV
- Complicate protection
 - Coordination