

Symmetrical Components

ECE525
Lecture 15

- Review of basics
- Sequence Equivalents
- Fault Analysis

Symmetrical Components

Fall 2018

References

ECE525
Lecture 15

- Your power systems analysis class text book
- NPAG: Chapter 4 (analysis) Chapter 5 (equipment models)
- J.L. Blackburn, *Protective Relaying: Principles and Applications*, Any Edition: Chapter 4
- P.M. Anderson, *Analysis of Faulted Power Systems*, IEEE Press 1995
- J.L. Blackburn, *Symmetrical Components for Power Systems Engineering*, Marcel-Dekker, 1993.
- Nasser Tleis, *Power Systems Modelling and Fault Analysis: Theory and Practice*. Newnes Power Engineering Series. 2008

Symmetrical Components

Fall 2018

History

- Fortescue, 1918
 - » Unbalanced n-phase system can be broken down into sets of balanced n-phase systems
 - » Add using superposition

What is it?

- Method for analysis of multiphase systems under unbalanced conditions
 - » Steady-state conditions
 - » Phasor Analysis
 - » Visualization
- Allows a fast, efficient way to analyze unbalanced condition in real time
- Relays set to look at specific components

Basic Equations

- De-couple voltage or current into 3 balanced 3 phase sets
 - » Positive phase sequence (ABCABC...): V_1
 - » Negative phase sequence (ACBACB...): V_2
 - » Zero phase sequence (A=B=C), V_0
 - » All RMS phasors
 - » Per phase analysis

Per Phase Symmetrical Component Equations

$$\mathbf{a} = 1 @ 120^\circ$$

$$\mathbf{V}_A = \mathbf{V}_{A0} + \mathbf{V}_{A1} + \mathbf{V}_{A2}$$

$$\begin{aligned}\mathbf{V}_B &= \mathbf{V}_{B0} + \mathbf{V}_{B1} + \mathbf{V}_{B2} \\ &= \mathbf{V}_{A0} + \mathbf{a}^2\mathbf{V}_{A1} + \mathbf{a}\mathbf{V}_{A2}\end{aligned}$$

$$\begin{aligned}\mathbf{V}_C &= \mathbf{V}_{C0} + \mathbf{V}_{C1} + \mathbf{V}_{C2} \\ &= \mathbf{V}_{A0} + \mathbf{a}\mathbf{V}_{A1} + \mathbf{a}^2\mathbf{V}_{A2}\end{aligned}$$

Analysis Equations

$$\mathbf{V}_{A0} = \mathbf{V}_0 = (\mathbf{V}_A + \mathbf{V}_B + \mathbf{V}_C)/3$$

$$\mathbf{V}_{A1} = \mathbf{V}_1 = (\mathbf{V}_A + \mathbf{a}\mathbf{V}_B + \mathbf{a}^2\mathbf{V}_C)/3$$

$$\mathbf{V}_{A2} = \mathbf{V}_2 = (\mathbf{V}_A + \mathbf{a}^2\mathbf{V}_B + \mathbf{a}\mathbf{V}_C)/3$$

- Same expressions for current
- Can express in Matrix form too

Analysis Equations


$$\begin{pmatrix} \mathbf{V}_{a0} \\ \mathbf{V}_{a1} \\ \mathbf{V}_{a2} \end{pmatrix} = \frac{1}{3} \begin{pmatrix} 1 & 1 & 1 \\ 1 & \mathbf{a} & \mathbf{a}^2 \\ 1 & \mathbf{a}^2 & \mathbf{a} \end{pmatrix} \cdot \begin{pmatrix} \mathbf{V}_a \\ \mathbf{V}_b \\ \mathbf{V}_c \end{pmatrix}$$

$$\begin{pmatrix} \mathbf{V}_a \\ \mathbf{V}_b \\ \mathbf{V}_c \end{pmatrix} = \begin{pmatrix} 1 & 1 & 1 \\ 1 & \mathbf{a}^{3-1} & \mathbf{a}^{3-2} \\ 1 & \mathbf{a}^{3-2} & \mathbf{a}^{3-1} \end{pmatrix} \cdot \begin{pmatrix} \mathbf{V}_{a0} \\ \mathbf{V}_{a1} \\ \mathbf{V}_{a2} \end{pmatrix} = \begin{pmatrix} 1 & 1 & 1 \\ 1 & \mathbf{a}^2 & \mathbf{a} \\ 1 & \mathbf{a} & \mathbf{a}^2 \end{pmatrix} \cdot \begin{pmatrix} \mathbf{V}_{a0} \\ \mathbf{V}_{a1} \\ \mathbf{V}_{a2} \end{pmatrix}$$

Circuit Analysis

- Represent power system in per phase sequence networks
- Each network contains voltage and impedance elements for the sequence
- Reduce network to Thevenin Equivalent in each phase sequence
- All sources generally positive sequence

Basic Sequence Networks

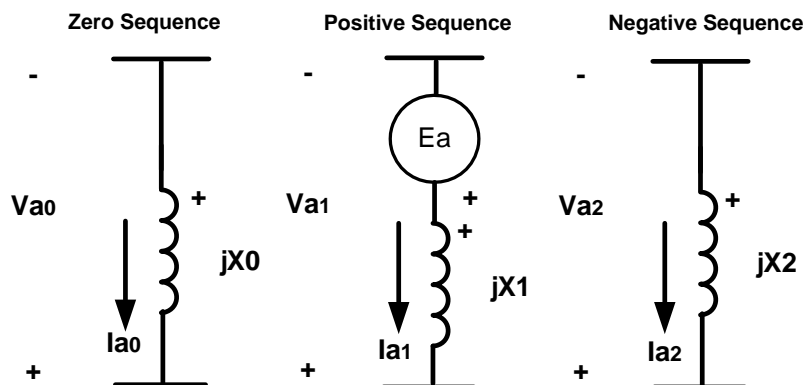

Basic Sequence Networks

ECE525
Lecture 15

- Impedance will differ between sequences
- Zero sequence will also include ground impedance
- Connect them as appropriate for different fault types

Symmetrical Components

Fall 2018

Fault Analysis

ECE525
Lecture 15

- Fault Types:
 - » Single line to ground
 - » Line to line
 - » Double line to ground
 - » Three phase (positive sequence unless unbalanced fault impedances)
 - » Phase open
 - » Phase open and line to ground
 - » Simultaneous faults

Symmetrical Components

Fall 2018

Fault Detection For Protection Purposes

ECE525
Lecture 15

- Basic fault analysis techniques calculate currents/voltages at fault location
 - » ABC or symmetrical components
- Need fault signature as seen at the relay location
 - » Rough location of fault for correct response

Symmetrical Components

Fall 2018

Single Line to Ground Connections

ECE525
Lecture 15


- Constraints at fault location (phase A):
 - » $V_A = 0$
 - » $I_B = I_C \cong 0$
- Therefore:
 - » $V_A = V_0 + V_1 + V_2 = 0$
 - » $I_0 = (I_A + 0 + 0)/3$ and
 - » $I_1 = I_2 = (I_A + 0 + 0)/3$ so
 - » $I_0 = I_1 = I_2 = (I_A)/3$

Symmetrical Components

Fall 2018

SLG Connections

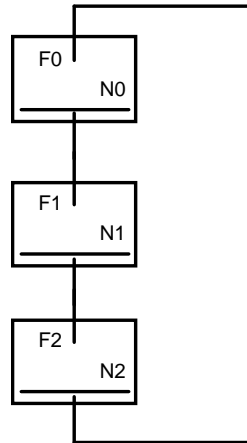- To Satisfy these constraints we connect the three networks in series
- Connect reference point of one network to fault location of next one



SLG Faults


- Solve for I_0 , can calculate I_A
- Next solve for V_1 , V_2 , and V_0 and calculate phase voltage
- Note that in general jX_0 will be replaced with $Z_0 = jX_0 + 3Z_{gr} + 3Z_f$
 - » The factor of 3 results since 0 sequence is the same to all 3 phases

Phase to Phase Faults

- Two phases (often B and C for analysis) shorted together
 - » Not shorted to ground
 - » $V_B = V_C$
 - » $I_B = -I_C$
- From symmetrical component equations:
 - » $I_0 = 0$
 - » $I_1 = -I_2$ and $V_1 = V_2$


Phase to Phase Faults

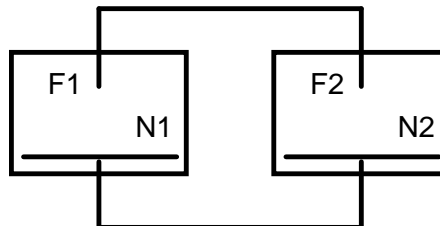- Fault impedance (if any) appears between the networks
- No Zero Sequence Network
- $V_B = I_B * Z_f + V_C$



Double Line to Ground

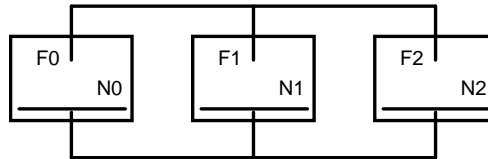- Two phases shorted together and to ground
- Could have several impedances
 - » $I_A \cong 0$
 - » $V_B = (Z_f + Z_{gr}) * I_B + Z_f * I_f$
 - » $V_C = (Z_f + Z_{gr}) * I_C + Z_f * I_f$




Fault Detection For Protection Purposes

- Basic fault analysis techniques calculate currents/voltages at fault location
 - » ABC or symmetrical components
- Need fault signature as seen at the relay location
 - » Rough location of fault for correct response

What Type of Fault?

ECE525


Lecture 15

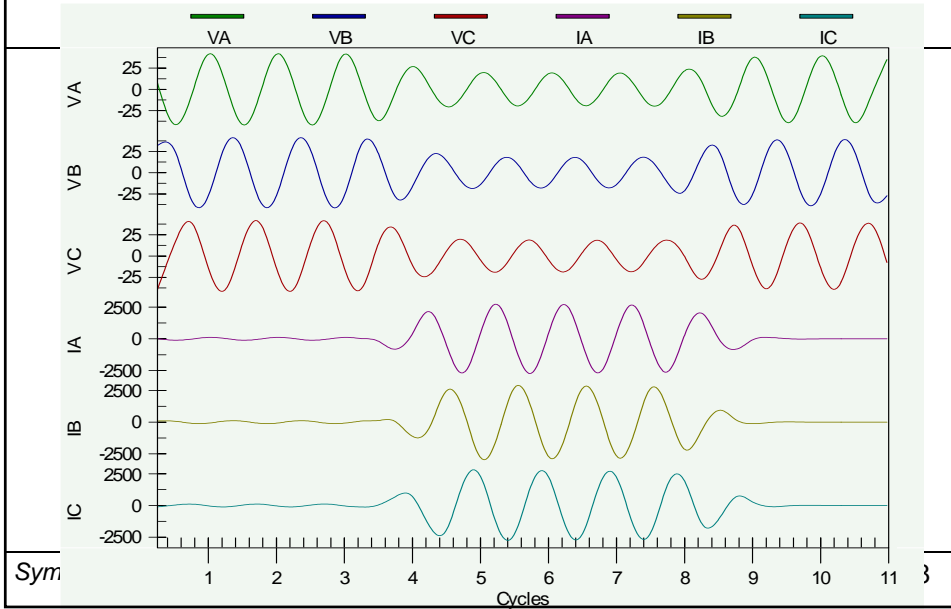

What Type of Fault?

ECE525


Lecture 15

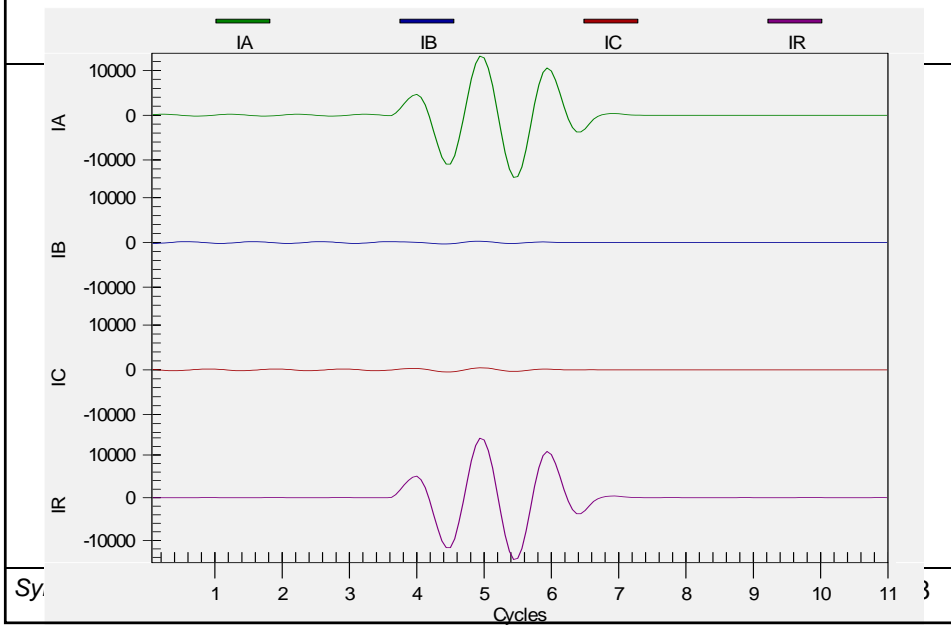

What Type of Fault?

ECE525


Lecture 15

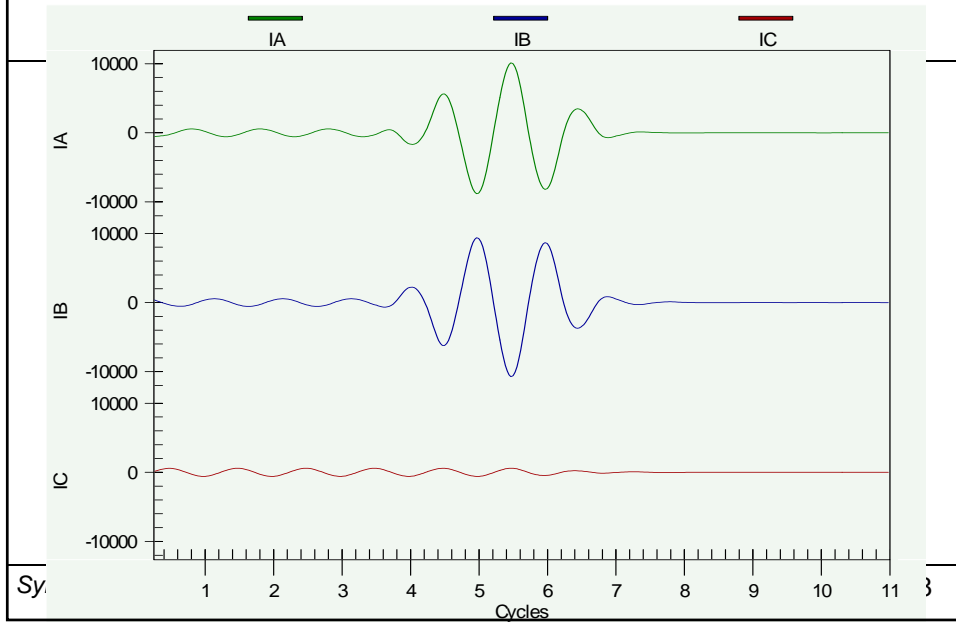

What Type of Fault?

ECE525


Lecture 15

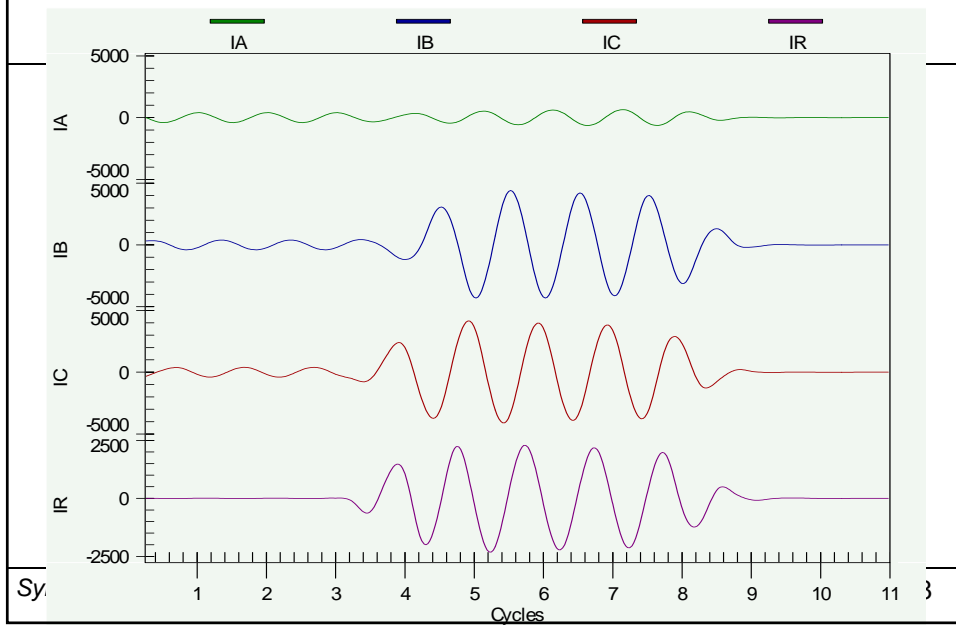

What Type of Fault?

ECE525


Lecture 15

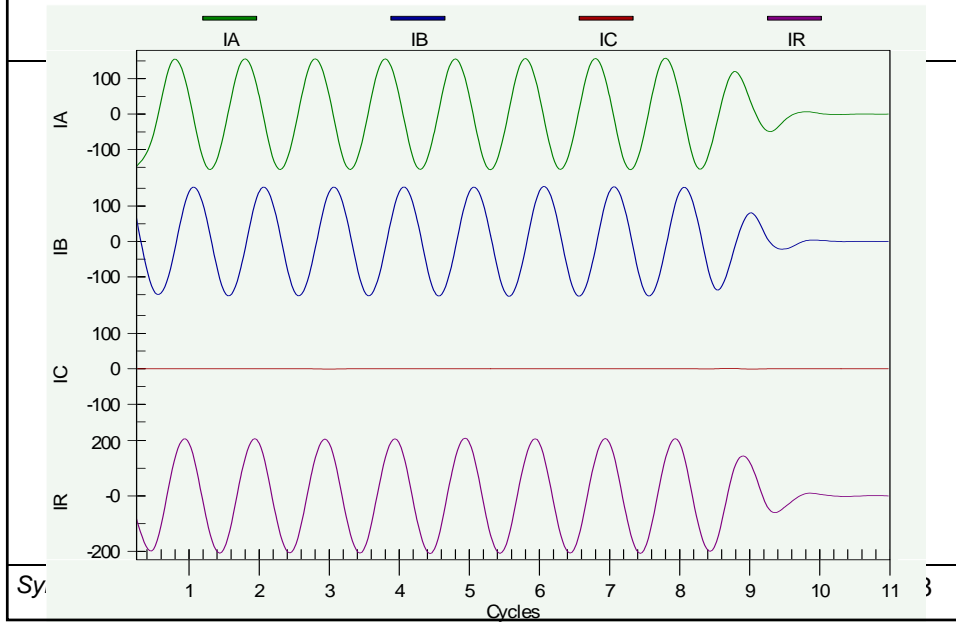

What Type of Fault?

ECE525


Lecture 15

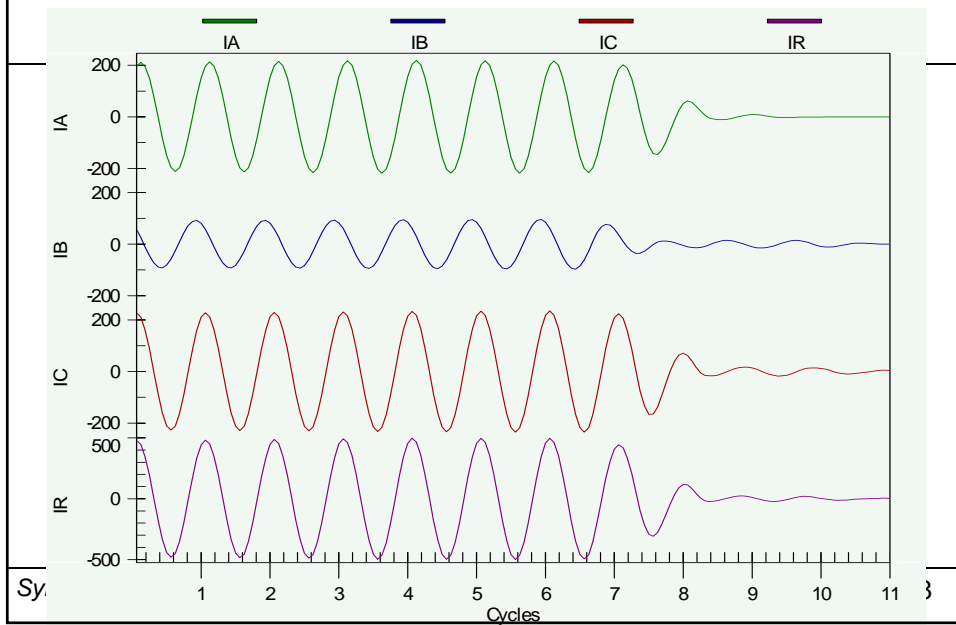

What Type of Fault?

ECE525


Lecture 15

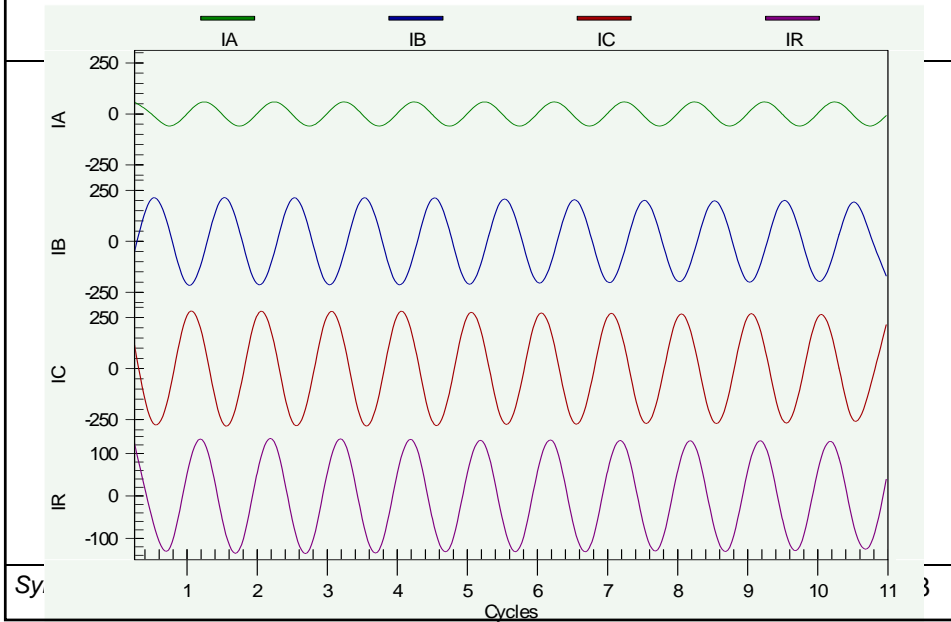

Three Phase Fault, Right?

ECE525


Lecture 15

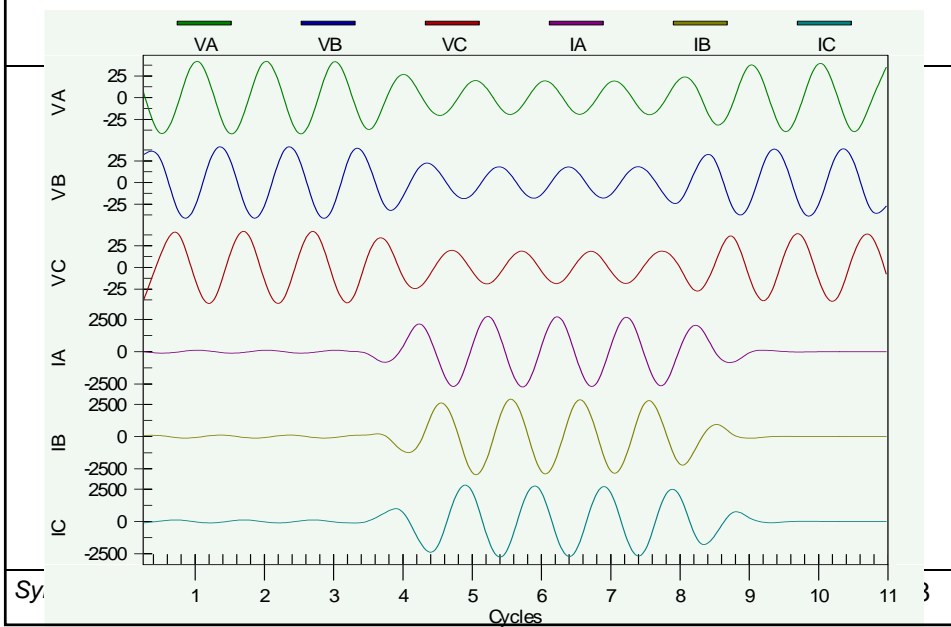

A Symmetrical Component View of an Three-Phase Fault

ECE525
Lecture 15

A-Ground Fault		
Component	Magnitude	Angle
Ia0	7.6	175
Ia1	2790	-64
Ia2	110	75.8
Va0	0	0
Va1	18.8	0

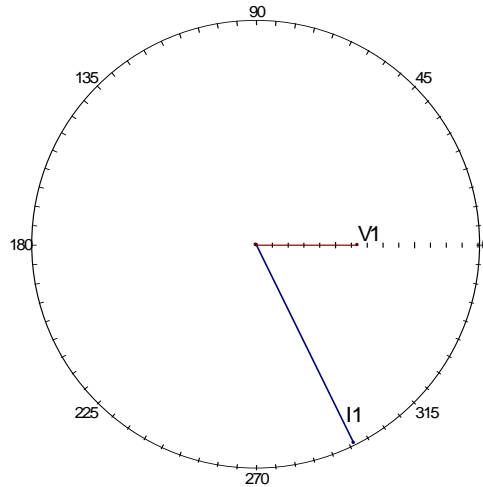


Symmetrical Components

Fall 2018

A to Ground Fault, Okay?

ECE525
Lecture 15

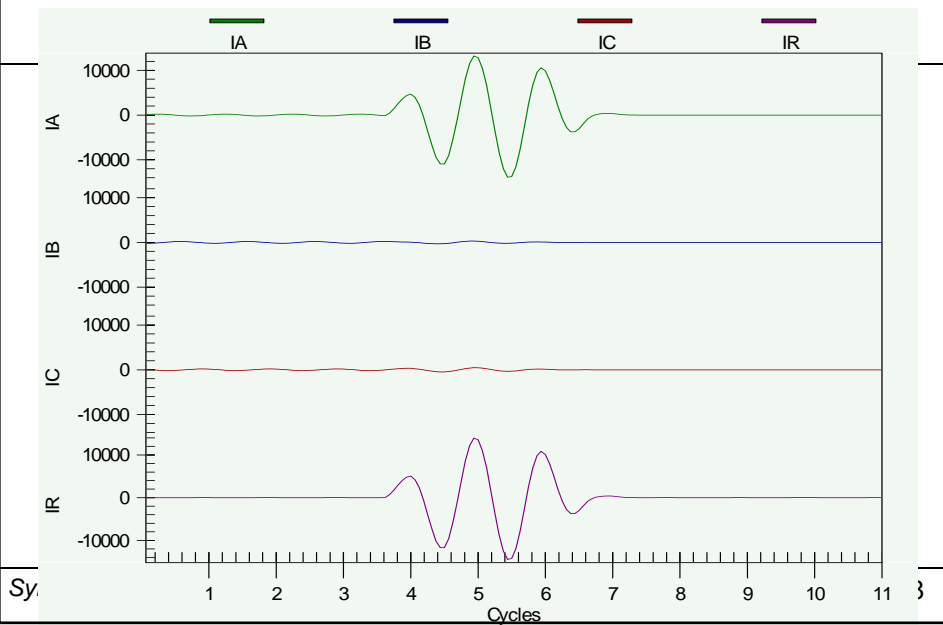


A Symmetrical Component View of an A-Phase to Ground Fault

ECE525

Lecture 15

A-Ground Fault		
Component	Magnitude	Angle
I_{a0}	7340	-79
I_{a1}	6447	-79
I_{a2}	6539	-79
V_{a0}	46	204
V_{a1}	123	0

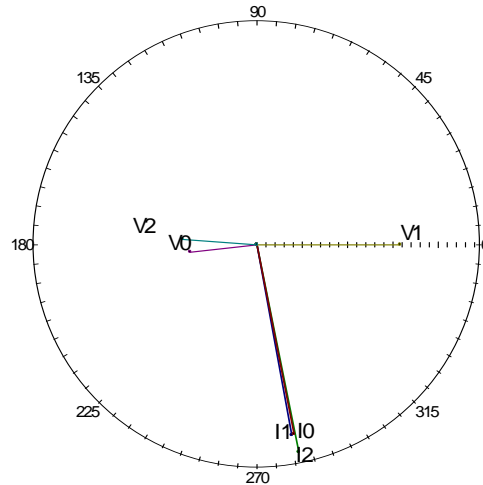

Symmetrical Components

Fall 2018

Single Line to Ground Fault

ECE525

Lecture 15


- Voltage
 - » Negative and zero sequence 180° out of phase with positive sequence
- Current
 - » All sequence are in phase

Symmetrical Components

Fall 2018

A to B Fault, Easy?


ECE525
Lecture 15

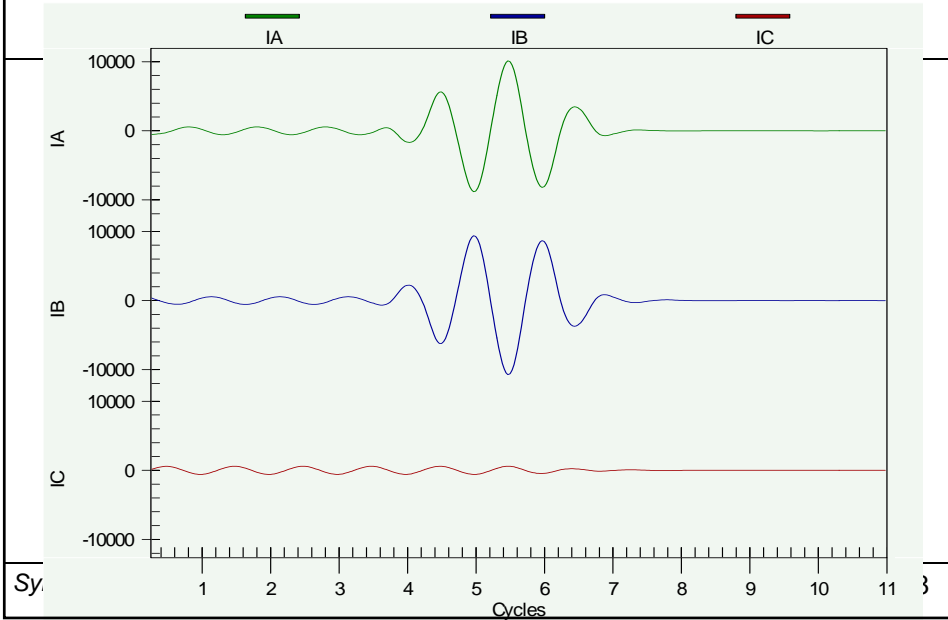

A Phase Symmetrical Component View of an A to B Phase Fault

ECE525
Lecture 15

A-B Fault		
Component	Magnitude	Angle
I_{a0}	3	-102
I_{a1}	5993	-81
I_{a2}	5961	-16
V_{a0}	1	45
V_{a1}	99	0

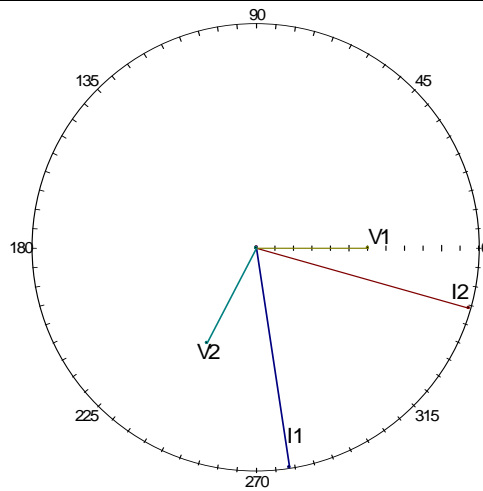

Symmetrical Components


Fall 2018

C Phase Symmetrical Component View of an A to B Phase Fault

ECE525

Lecture 15

Component	Magnitude	Angle
Ic0	3	138
Ic1	5993	279
Ic2	5961	104
Vc0	1	-75
Vc1	99	0
Vc2	95	2.5

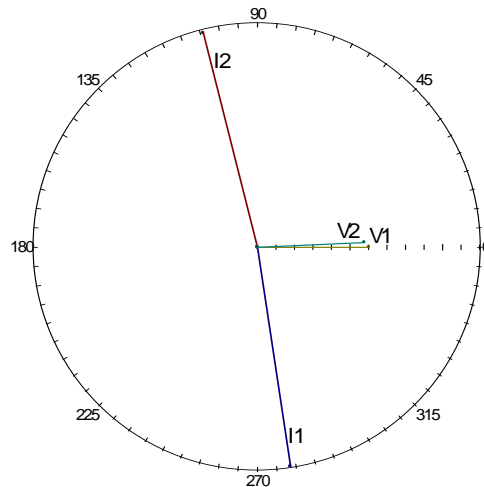

Symmetrical Components

Fall 2018

Line to Line Fault

ECE525

Lecture 15

- Voltage
 - » Negative in phase with positive sequence
- Current
 - » Negative sequence 180° out of phase with positive sequence


Symmetrical Components

Fall 2018

B to C to Ground

ECE525

Lecture 15

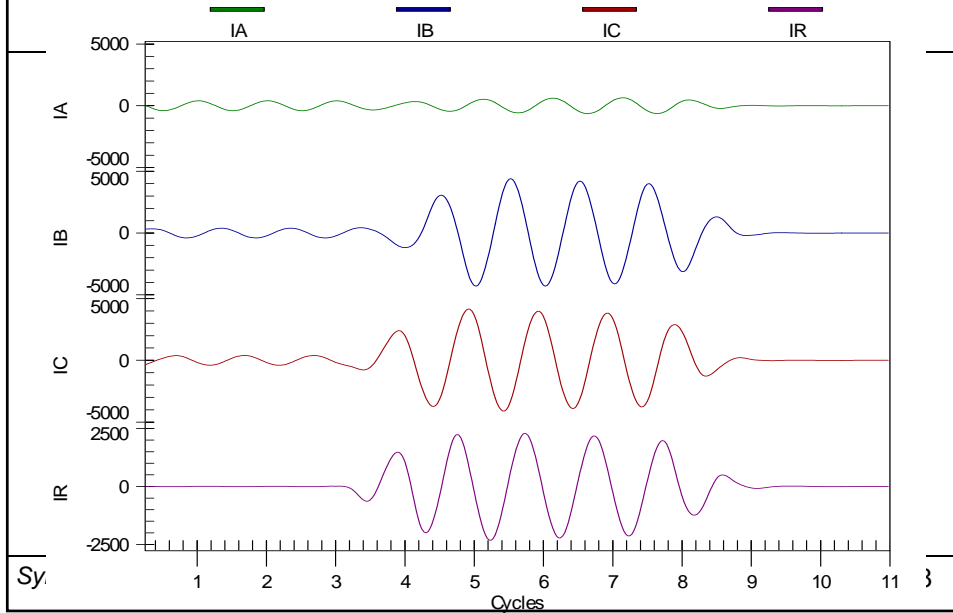


A Symmetrical Component View of a B to C to Ground Fault

ECE525

Lecture 15

Component	Magnitude	Angle
I_{a0}	748	97
I_{a1}	2925	-75
I_{a2}	1754	101
V_{a0}	8	351
V_{a1}	101	0
V_{a2}	18	348

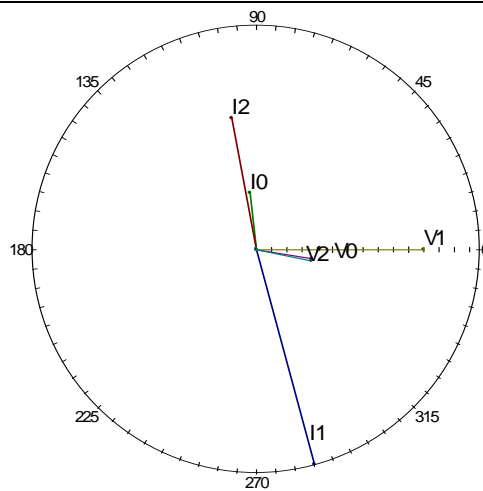

Symmetrical Components

Fall 2018

Line to Line to Ground Fault

ECE525
Lecture 15


- Voltage
 - » Negative and zero in phase with positive sequence
- Current
 - » Negative and zero sequence 180° out of phase with positive sequence

Symmetrical Components

Fall 2018

Again, What Type of Fault?


ECE525
Lecture 15

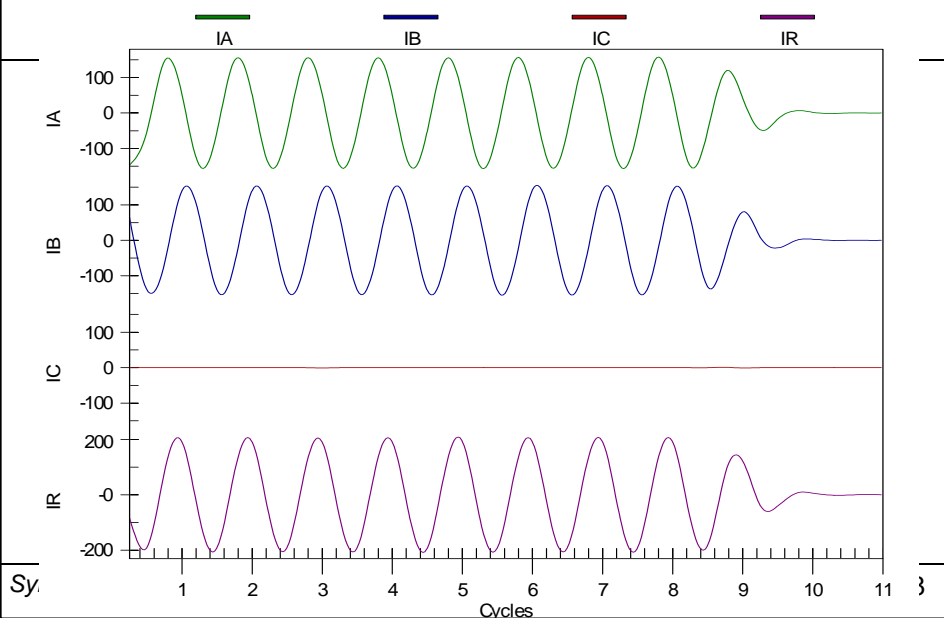

C Symmetrical Component View of a C-Phase Open Fault

ECE525
Lecture 15

Component	Magnitude	Angle
Ic0	69	184
Ic1	101	4
Ic2	32	183
Vc0	0	162
Vc1	79	0
Vc2	5	90

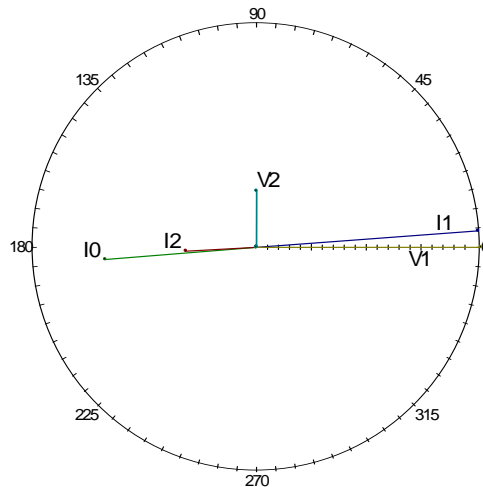

Symmetrical Components

Fall 2018

One Phase Open (Series) Faults

ECE525
Lecture 15


- Voltage
 - » No zero sequence voltage
 - » Negative 90° out of phase with positive sequence
- Current
 - » Negative and zero sequence 180° out of phase with positive sequence

Symmetrical Components

Fall 2018

What About This One?


ECE525
Lecture 15

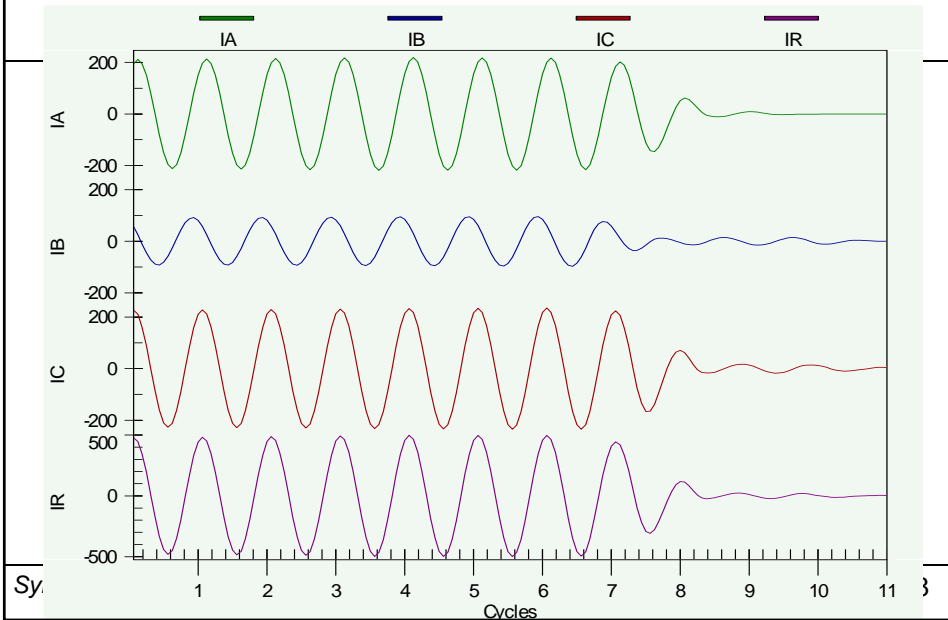

Ground Fault with Reverse Load

ECE525
Lecture 15

I_{c0}	164	-22
I_{c1}	89	-113
I_{c2}	41	-6
V_{c0}	4	-123
V_{c1}	38	0
V_{c2}	6	-130

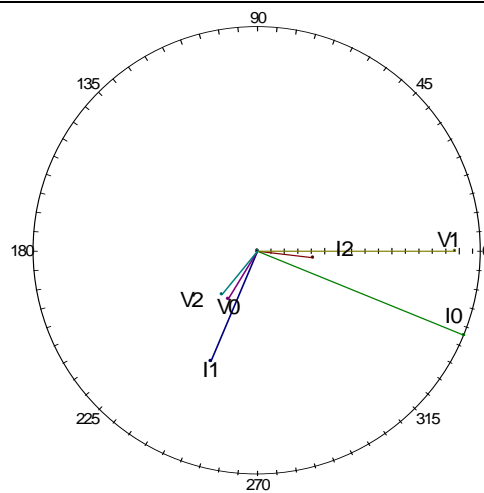


Symmetrical Components

Fall 2018

Finally, The Last One!

ECE525

Lecture 15

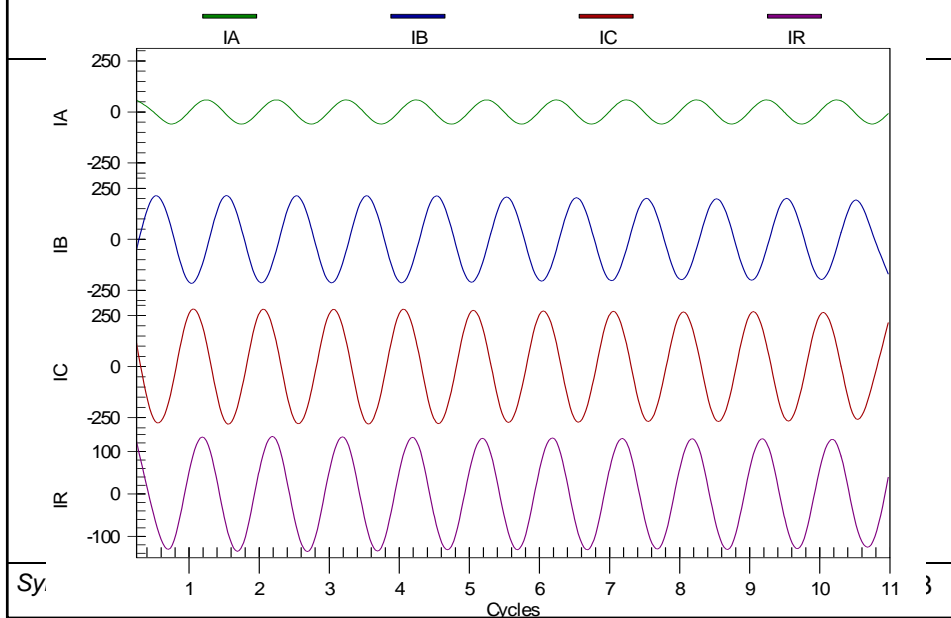


Fault on Distribution System with Delta - Wye Transformer

ECE525

Lecture 15

Component	Magnitude	Angle
Ic0	45	40
Ic1	153	-4
Ic2	132	180
Vc0	0.5	331
Vc1	40	0
Vc2	0.5	93

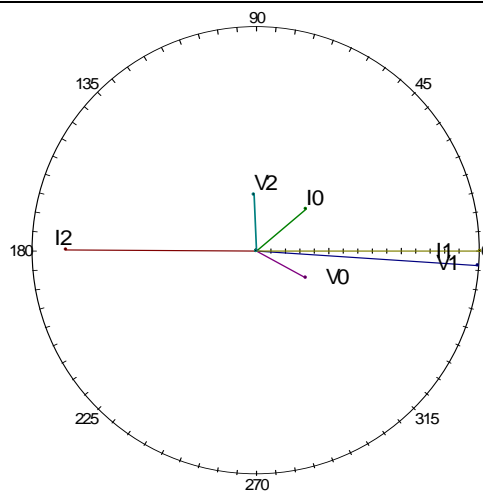

Symmetrical Components

Fall 2018