



ECE 525

POWER SYSTEM PROTECTION
AND RELAYING

SESSION no. 16

University of Idaho

L16 4/19

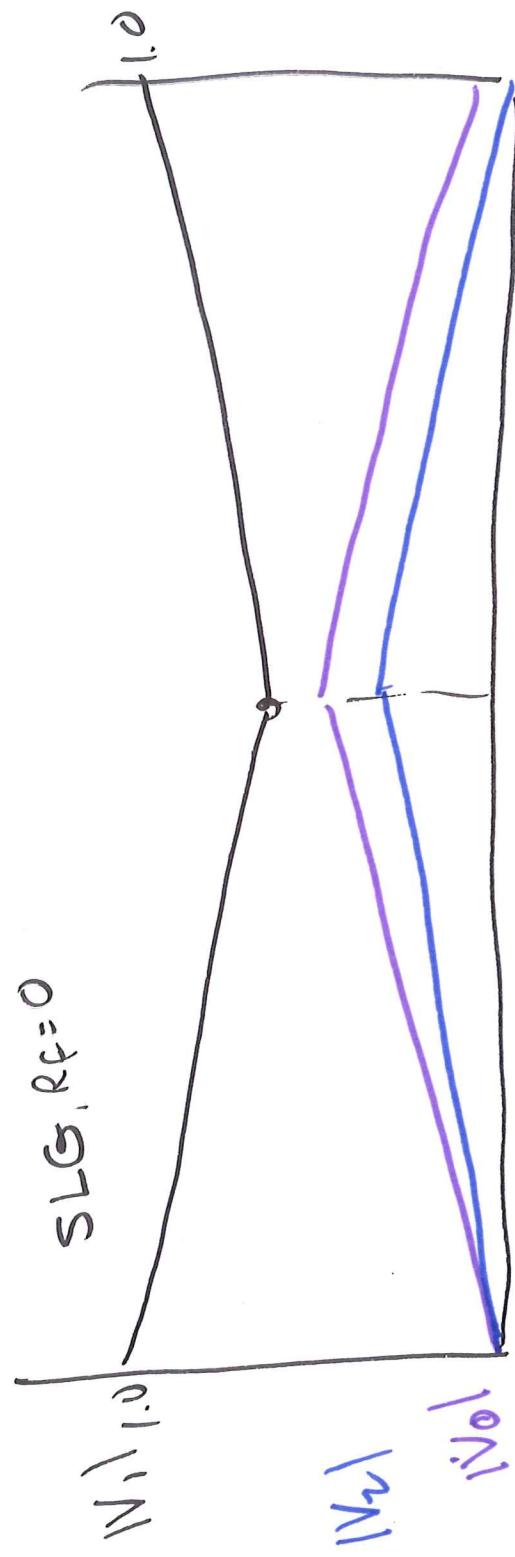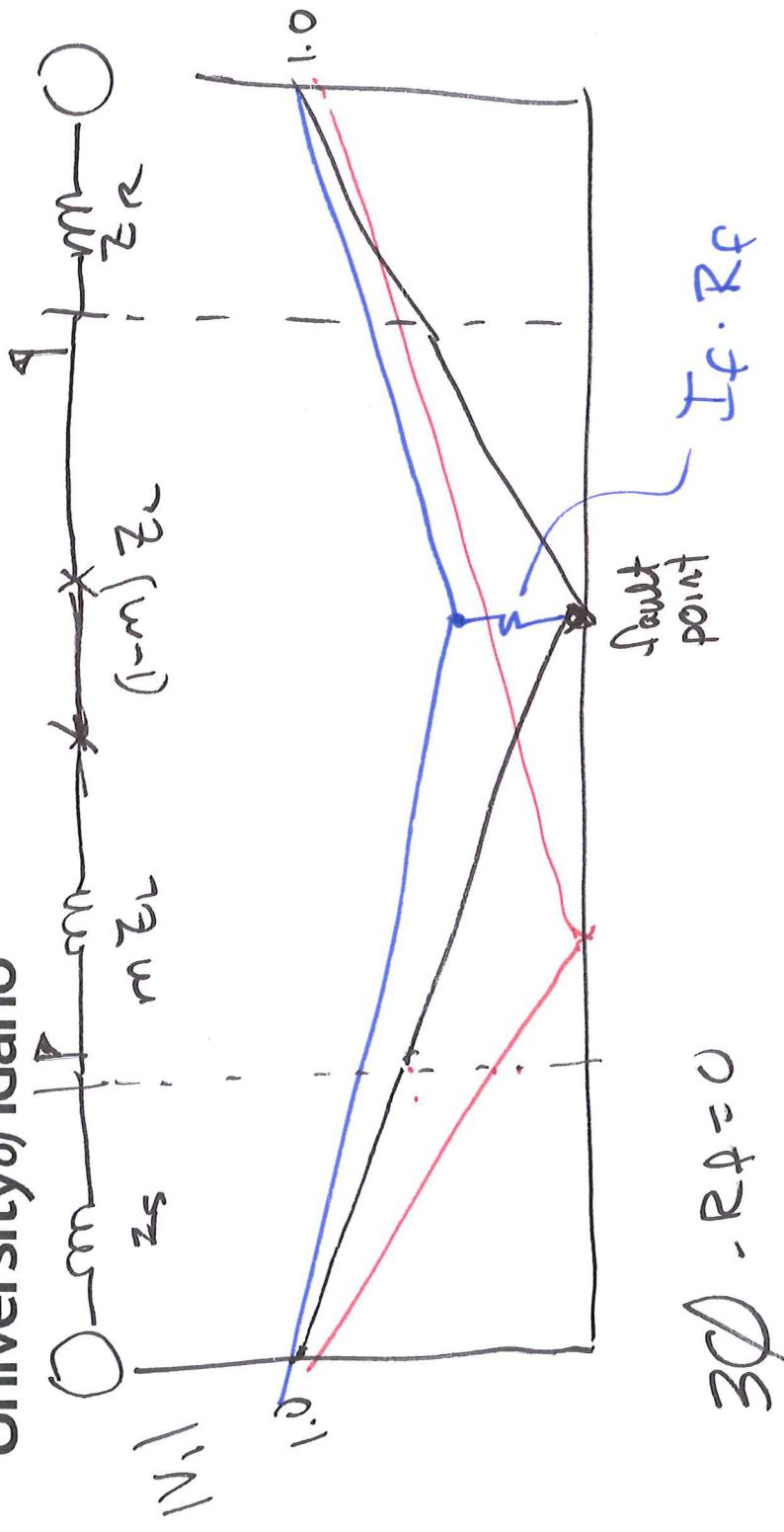


University of Idaho

L16 2/19




SLP

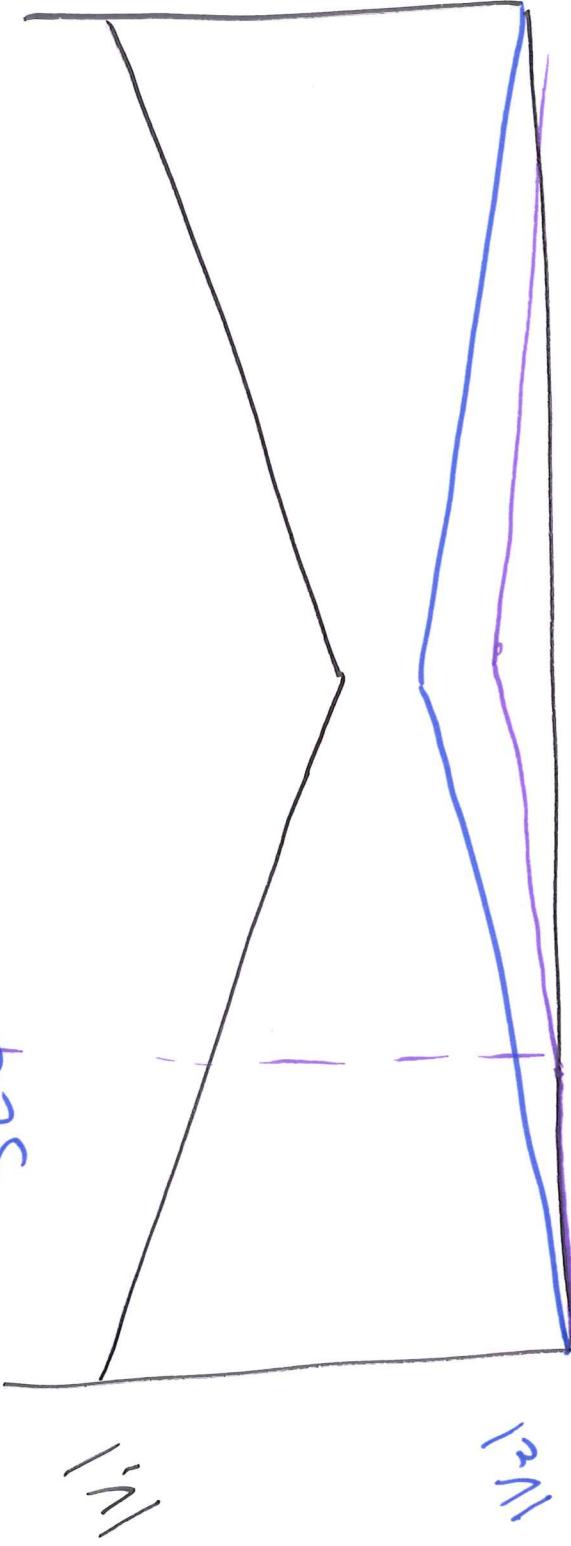

University of Idaho

$$DLG - R_f = 0$$

116 3) 19

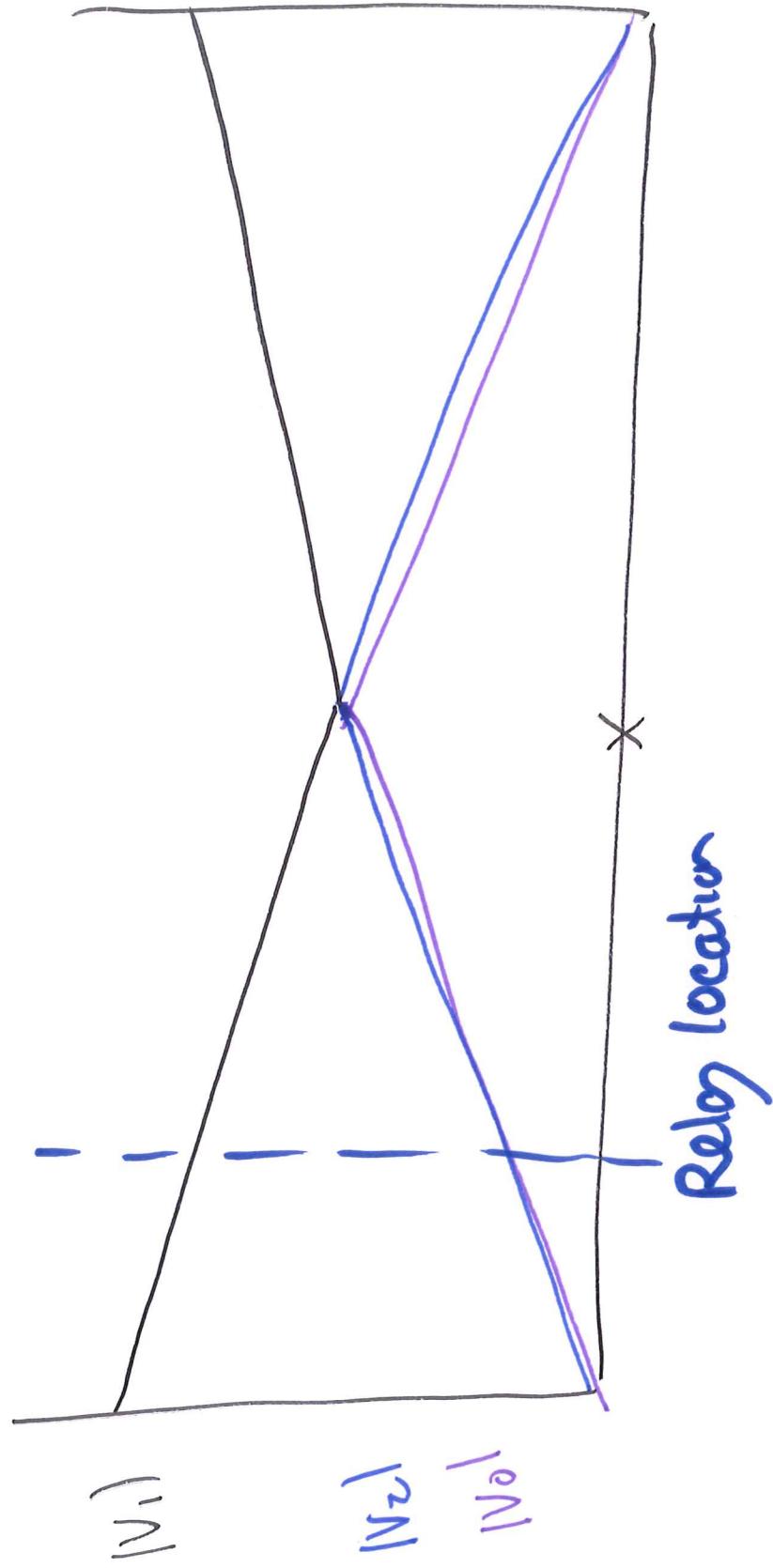

C Symmetrical Component View of a C-Phase Open Fault

ECE525
Lecture 15

| Component | Magnitude | Angle |
|-----------------|-----------|-------|
| I _{c0} | 69 | 184 |
| I _{c1} | 101 | 4 |
| I _{c2} | 32 | 183 |
| V _{c0} | 0 | 162 |
| V _{c1} | 79 | 0 |
| V _{c2} | 5 | 90 |

Symmetrical Components

Fall 2018

One Phase Open (Series) Faults

ECE525
Lecture 15

- Voltage
 - » No zero sequence voltage
 - » Negative 90° out of phase with positive sequence
- Current
 - » Negative and zero sequence 180° out of phase with positive sequence


Symmetrical Components

Fall 2018



University of Idaho

Phase open (series imbalance)

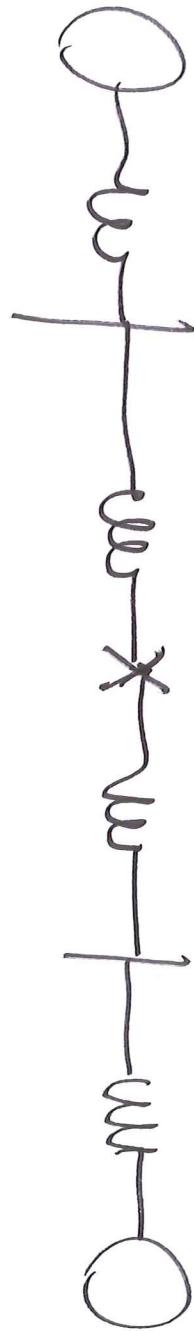
- Requires 2 port Thevenin equivalent circuits




Single port equiv

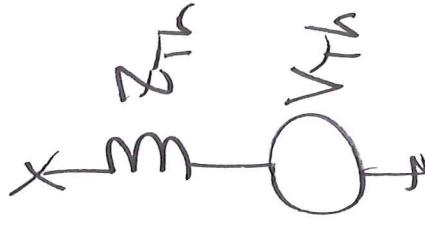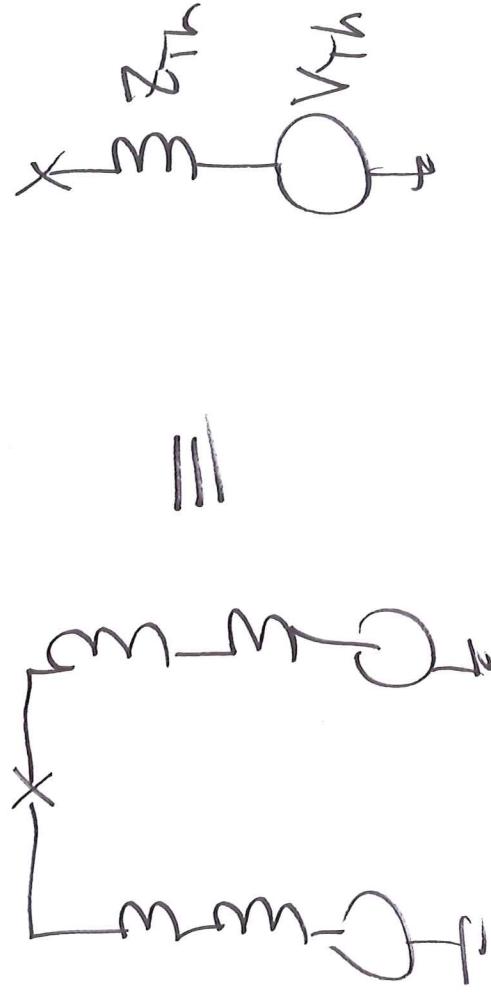


\equiv

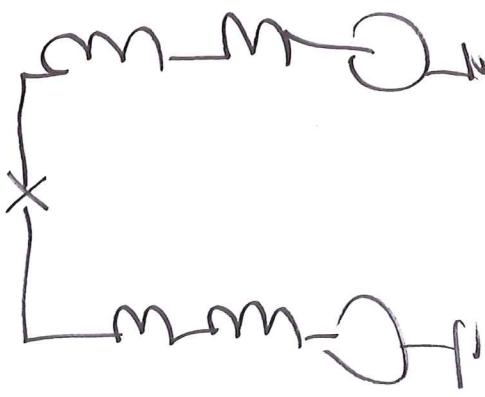

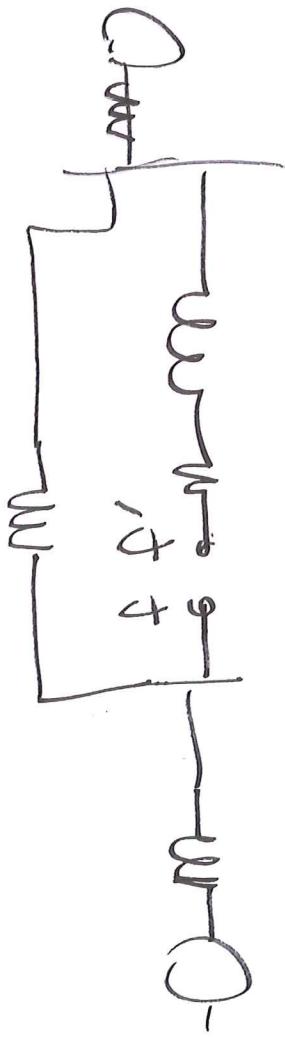

① $\omega \gg \omega_0$ parallel line

Pos Sep Equiv

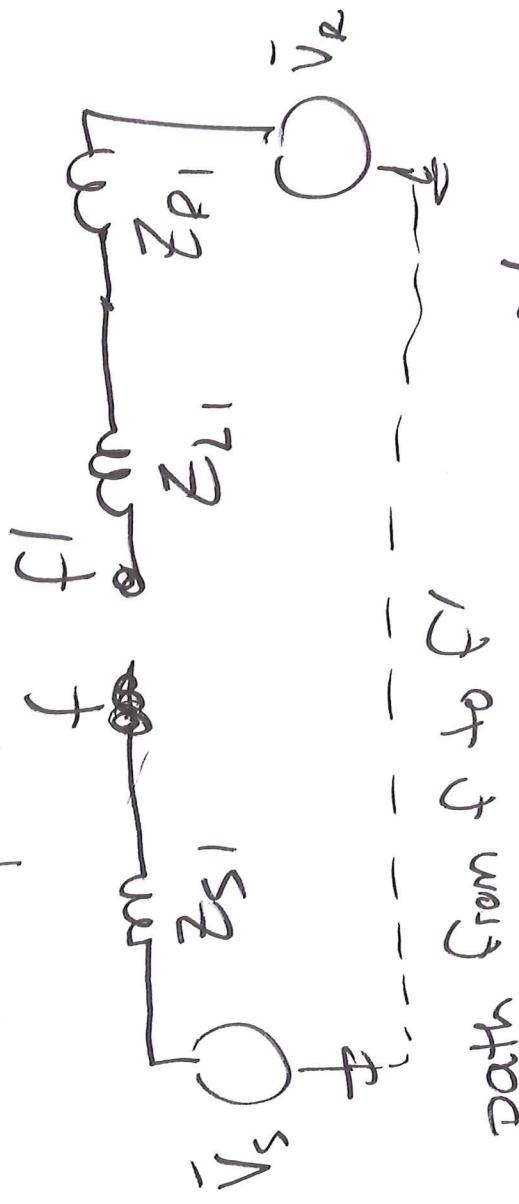

$\bar{V}_s - \bar{V}_{L1}$



$\bar{V}_{L1} - \bar{V}_{L2}$

path from f to f'



$\bar{V}_s \neq \bar{V}_2$

Assuming $\bar{V}_s \neq \bar{V}_2$ (load flow)


(2) Add parallel line

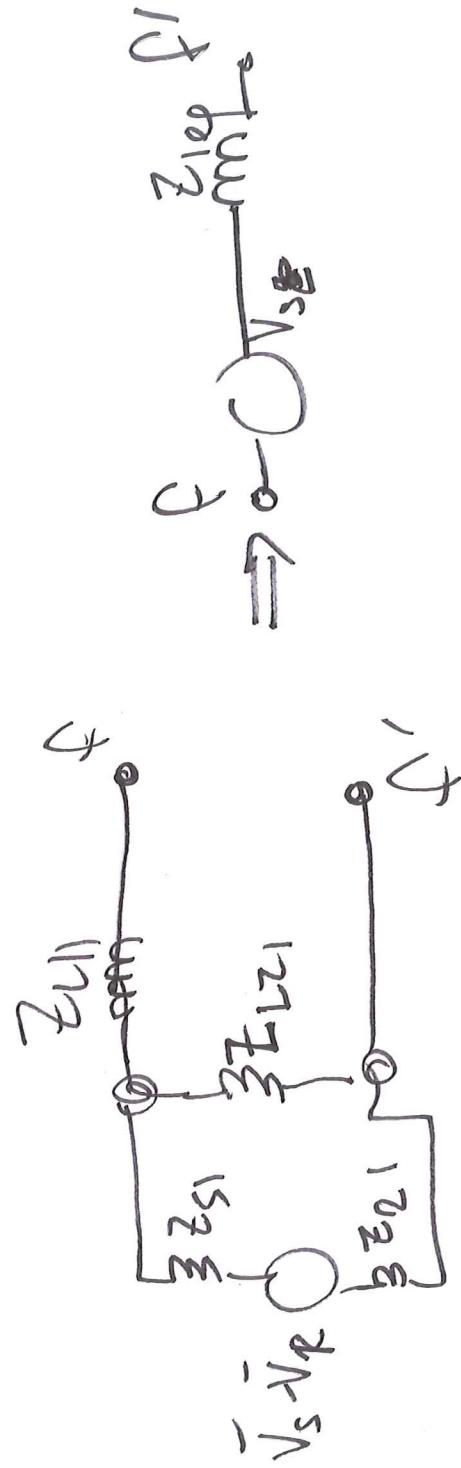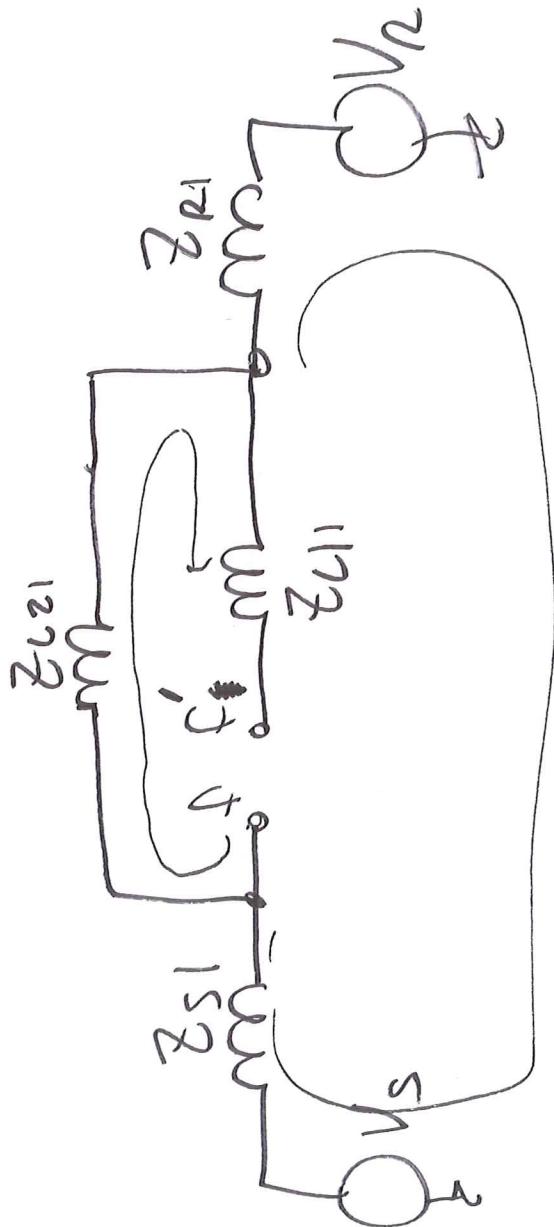


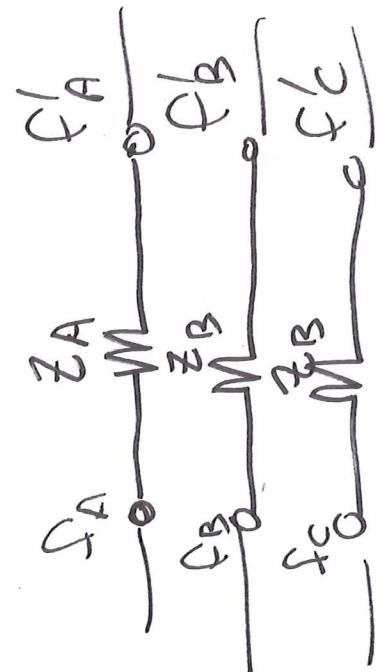
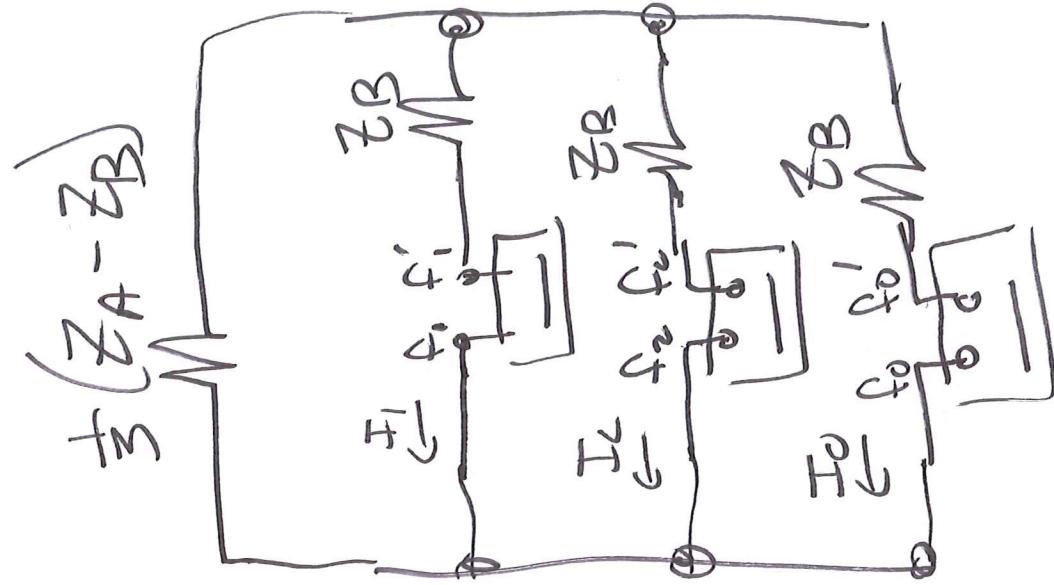
General sequence connection
for series fault



Special case of 1 phase closed, 2 open


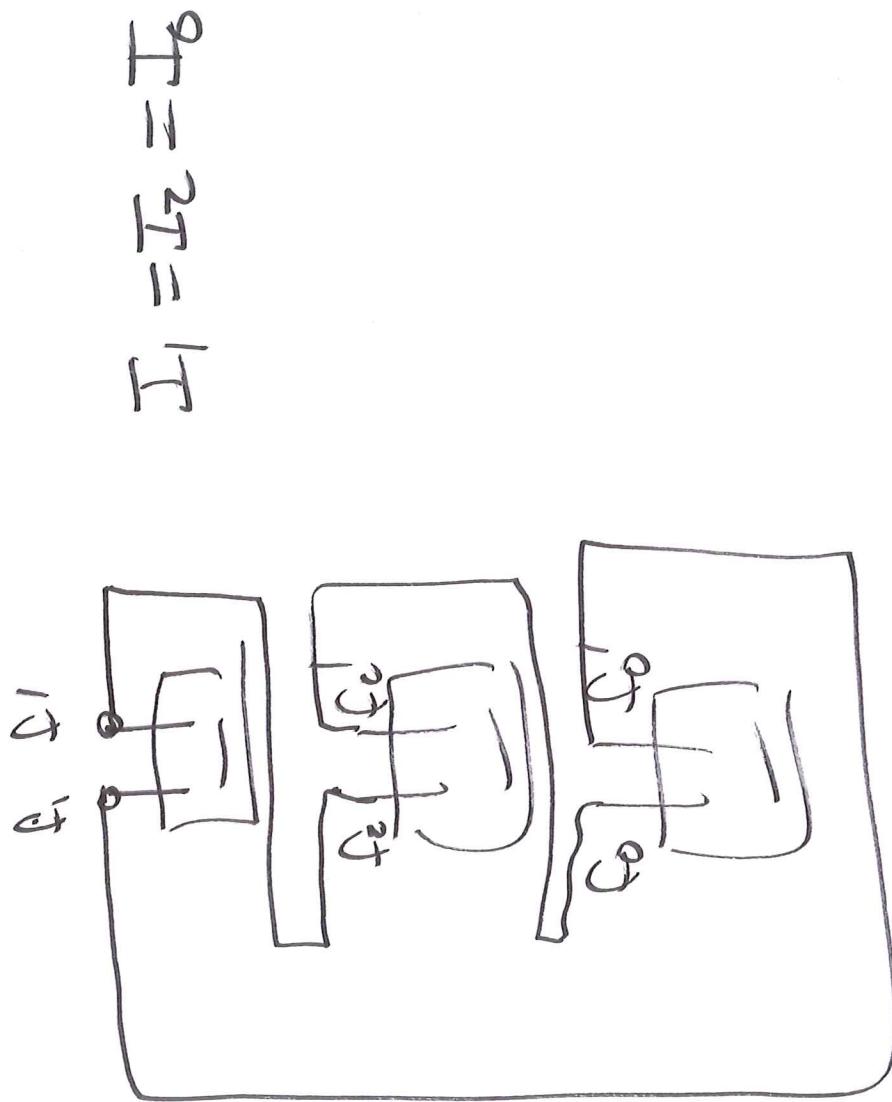


L16 10/5

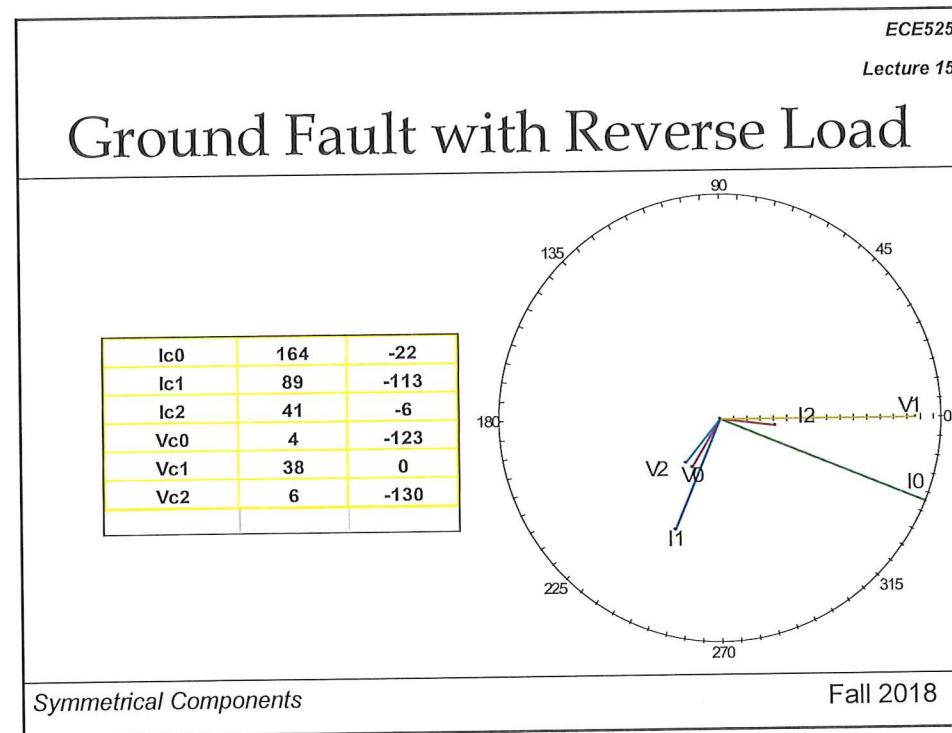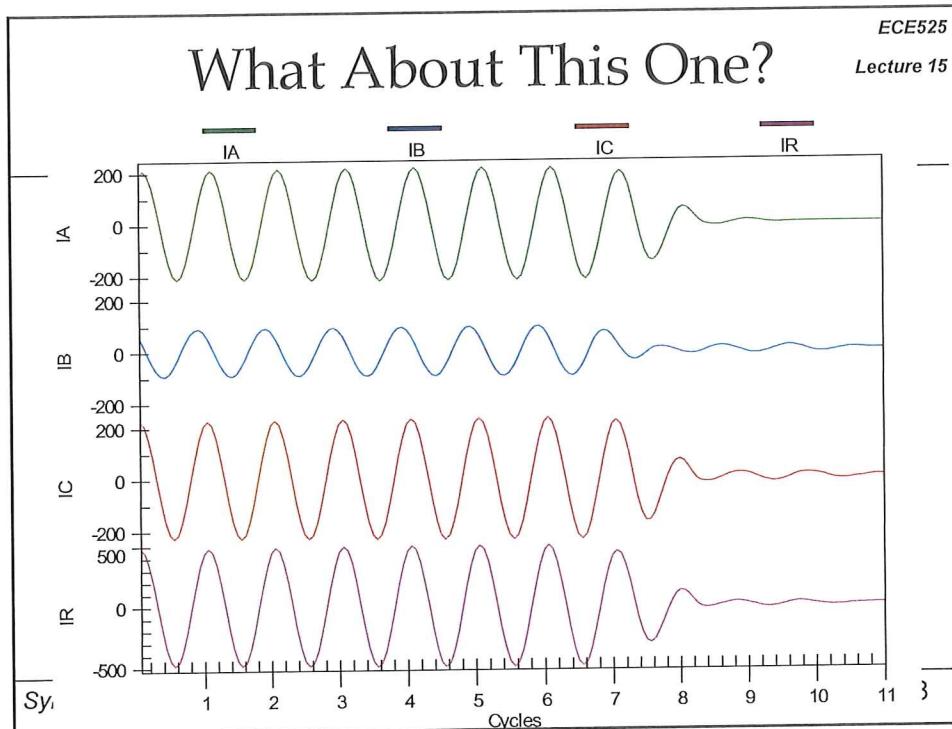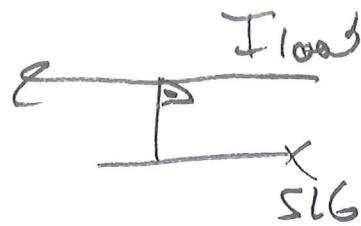

L16 II/9

350

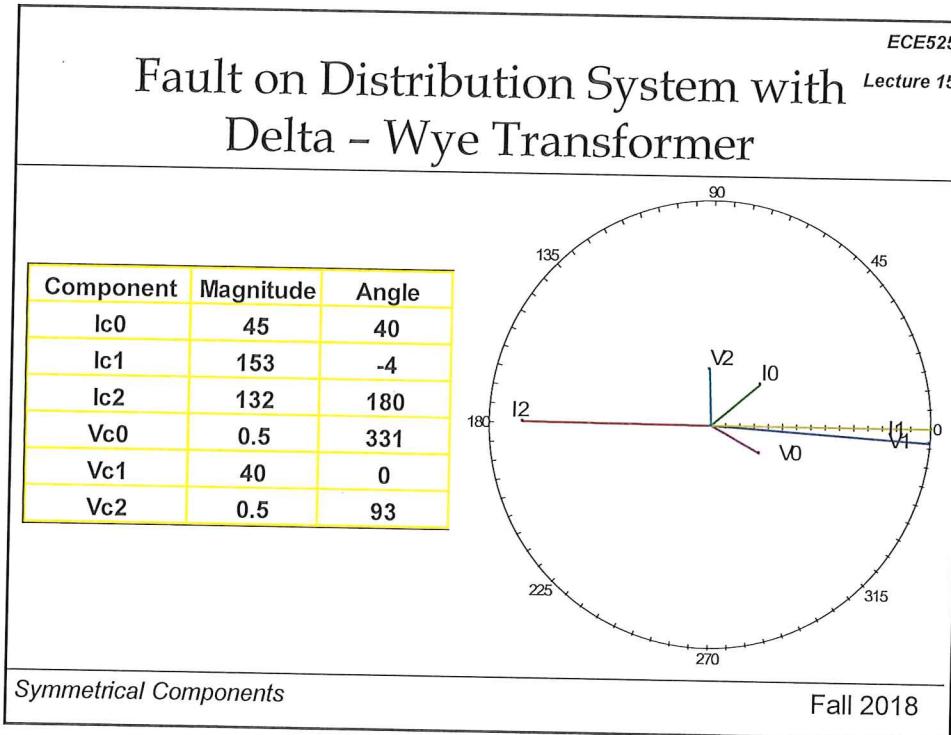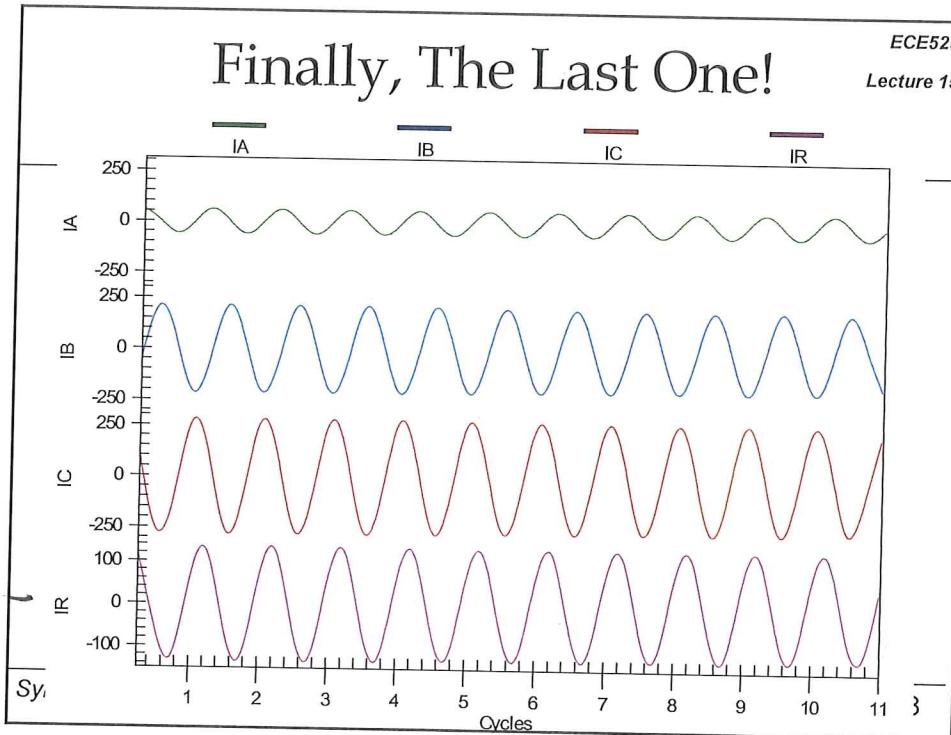

9/21
L11

U_I

Apparatus Models: Transformers

ECE525

Lecture 16

- Normally model as series impedance from winding resistance and leakage reactance
- Positive and negative impedances equal
- In a Y- Δ transformer that phase shift is in the opposite direction for negative sequence

Z_0
- Del (Bob)

Sequence Models of Apparatus

Fall 2018

U_I

Transformers (continued)

ECE525

Lecture 16


- Zero sequence impedance of the transformer depends on core construction
- $X_0 = X_1$ for single phase cores
- $X_0 = X_1$ for 5 leg or shell type core
 - Both have similar path for zero sequence current

Sequence Models of Apparatus


Fall 2018

Single phase core


HV


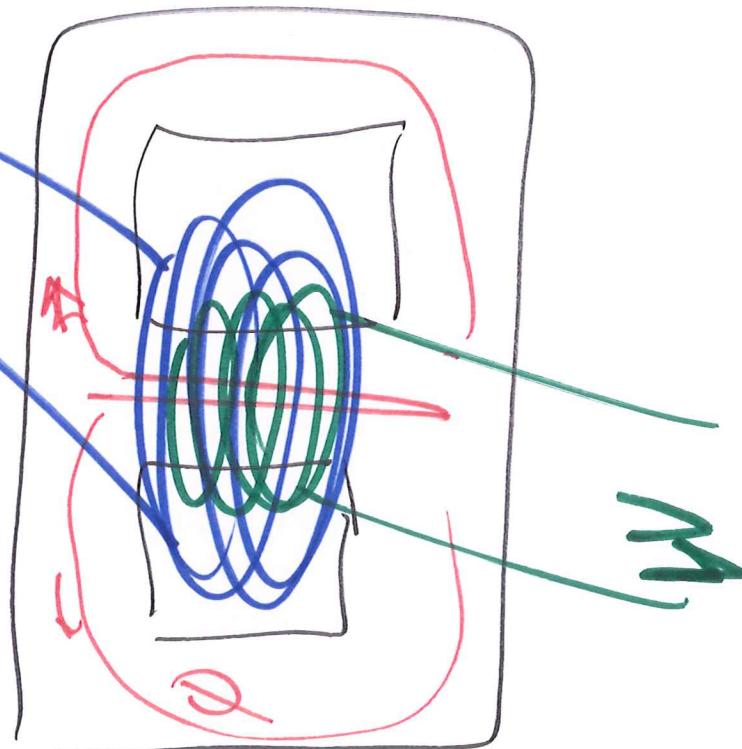


$\phi_a(t)$ $\phi_b(t)$ $\phi_c(t)$

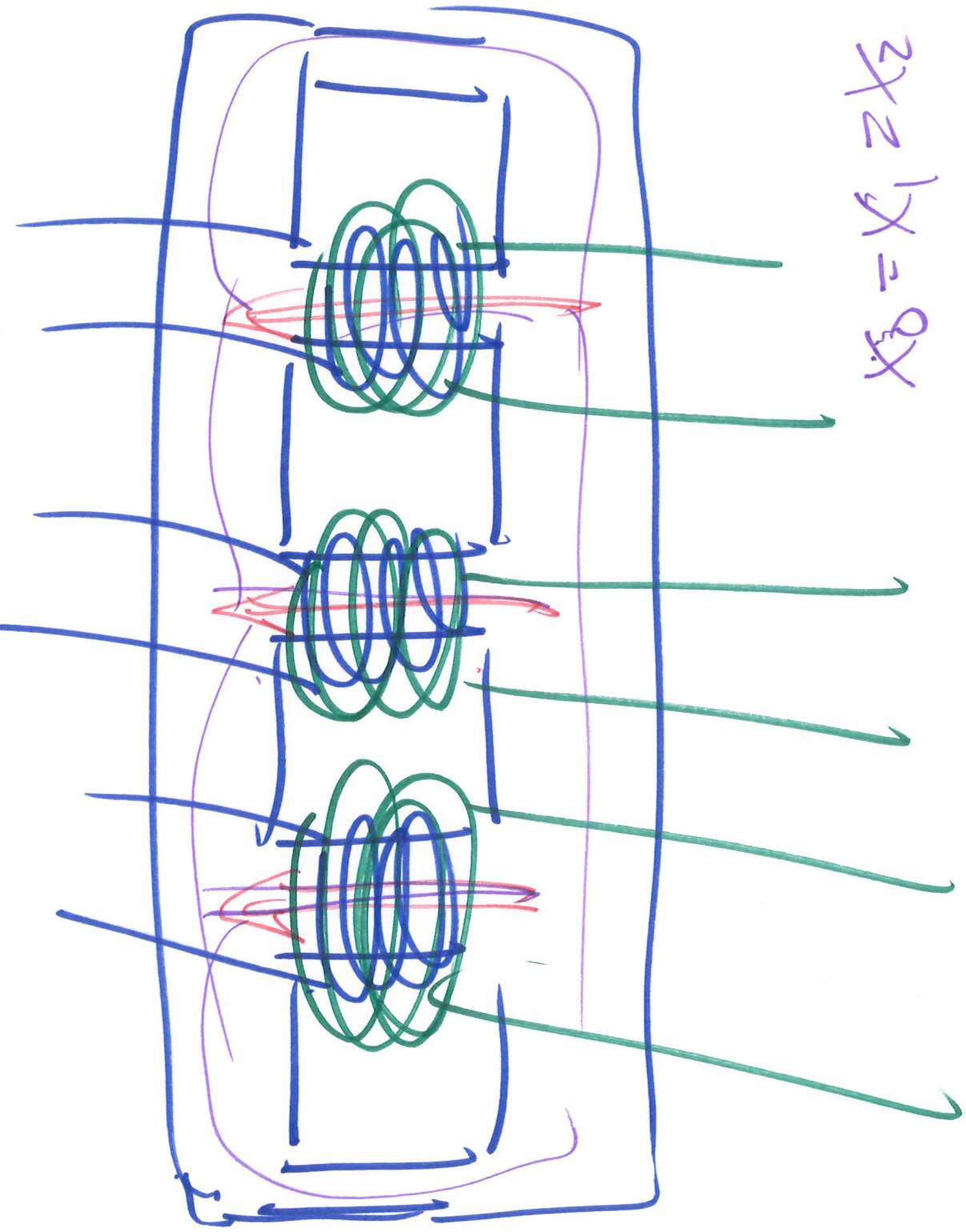


$\chi_1 = \chi_2$

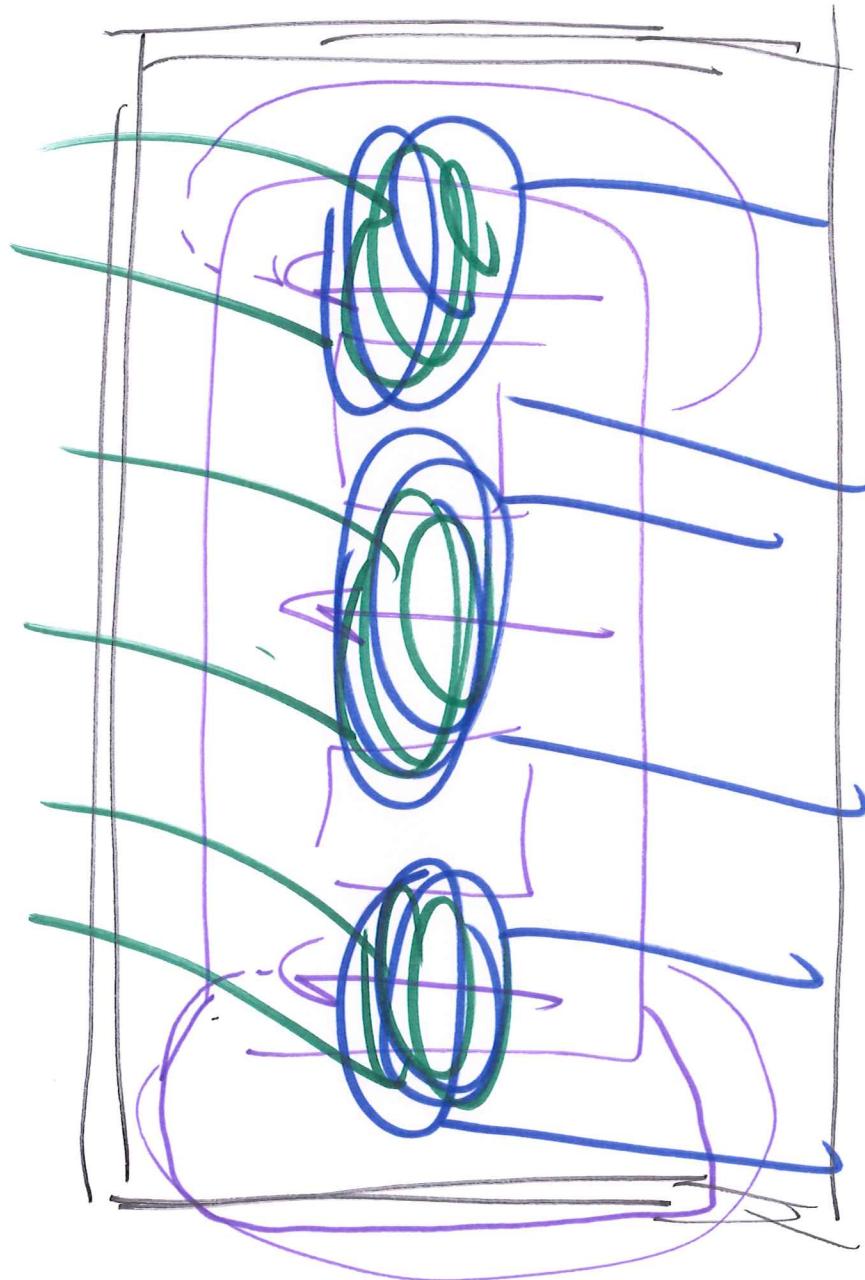

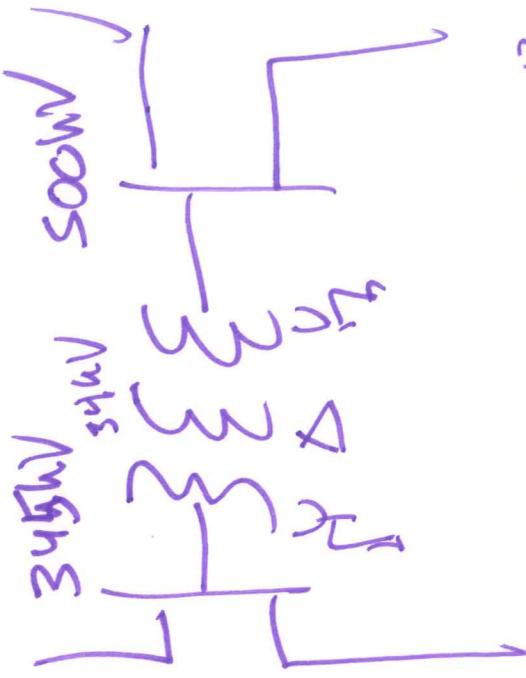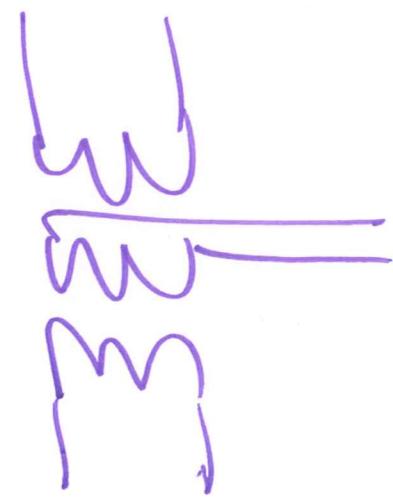

1, 5, 7, 11, 13

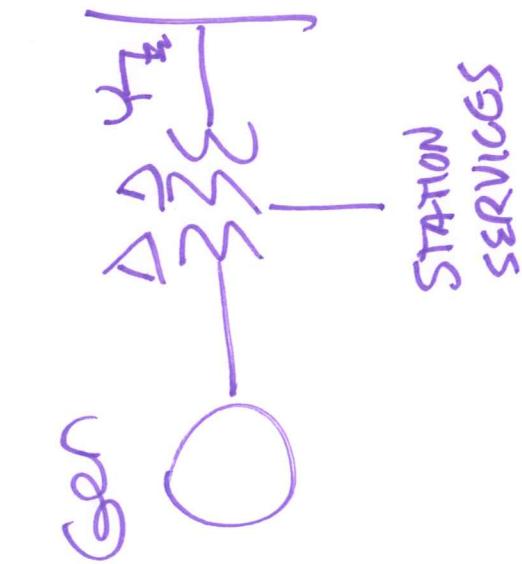

STATION
SERVICES


bV17917

 U_I

Transformer Connections

ECE525

Lecture 16

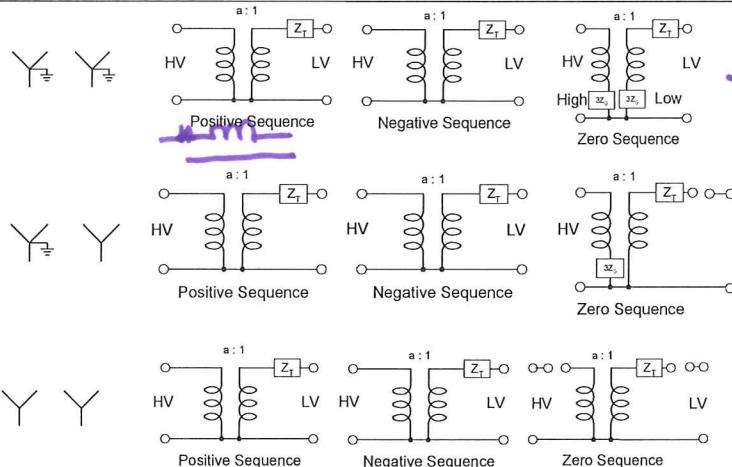

$R > X$
 $3Z_1$

Sequence Models of Apparatus


Fall 2018

 U_I

More Transformer Connections

ECE525

Lecture 16

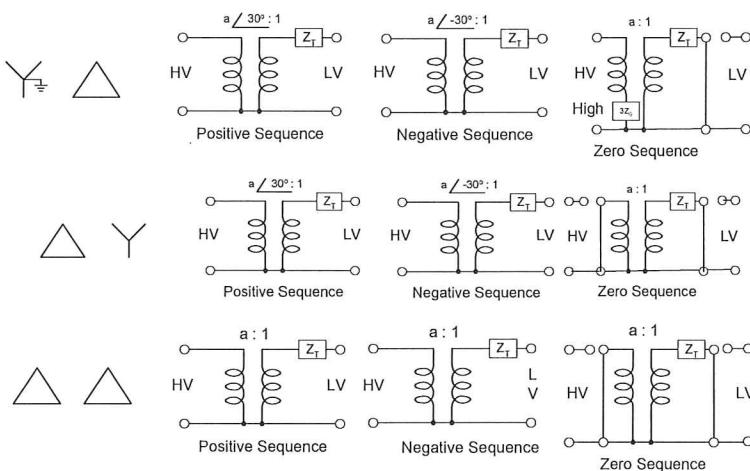

$R > X$
 $3Z_1$

Sequence Models of Apparatus

Fall 2018

U_I


Transformers with Tertiaries

ECE525

Lecture 16

in Blackboard

- See Fig A4.2.3 for more configurations

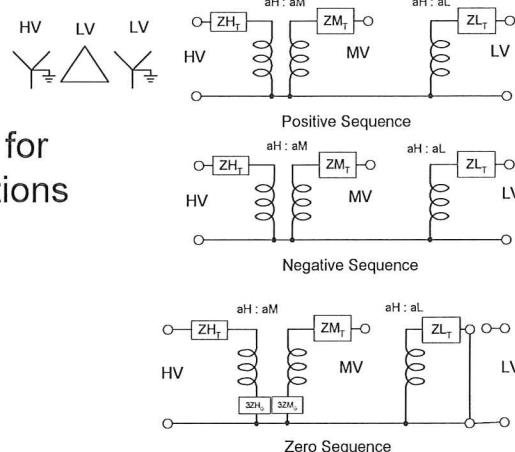

Sequence Models of Apparatus


Fall 2018

 U_I

Per Unit Equivalents (solid grounding)

ECE525

Lecture 16

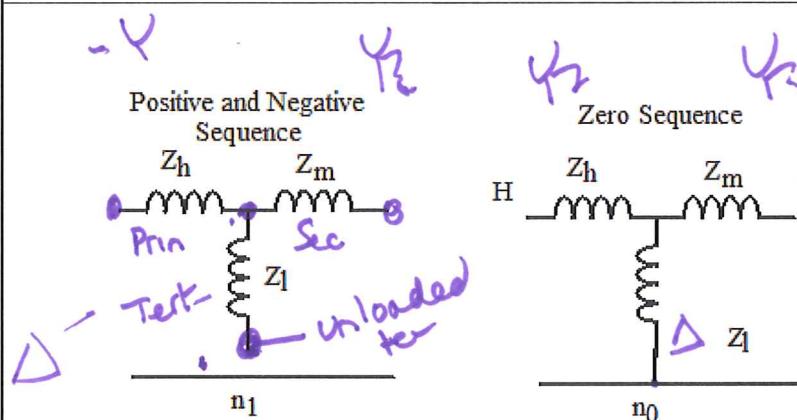

Sequence Models of Apparatus

Fall 2018

U_I Calculating Z_h , Z_m and Z_l

ECE525

Lecture 16

- Often given short circuit test data as Z_{hm} , Z_{hl} and Z_{ml}
- Not all on same per unit base, so first do change of base

$$X_h := \left(\frac{1}{2}\right) \cdot (X_{hl} + X_{hm} - X_{ml})$$

$$X_m := \left(\frac{1}{2}\right) \cdot (X_{hm} + X_{ml} - X_{hl})$$

$$X_l := \left(\frac{1}{2}\right) \cdot (X_{ml} + X_{hl} - X_{hm})$$

same on h, short L with m open

 U_I Component Modeling:
Lines

ECE525

Lecture 16

- $Z_1 = Z_2$ -phase rotation doesn't impact
- Often approximated with per phase equivalent self impedance
- Zero sequence current flows through earth and Z_0 often 2-6 times Z_1
- Usually neglect capacitances unless transient case
 - » Transient response matters for fast detection