

University of Idaho

ECE 525

POWER SYSTEM PROTECTION
AND RELAYING

SESSION no. 17

~~L16 19~~ 19
 917
 L17 13 217

U
I Calculating Z_h , Z_m and Z_l ECE525
Lecture 16

- Often given short circuit test data as Z_{hm} , Z_{hl} and Z_{ml}
- Not all on same per unit base, so first do change of base

$$X_h := \left(\frac{1}{2}\right) \cdot (X_{hl} + X_{hm} - X_{ml})$$

$$X_m := \left(\frac{1}{2}\right) \cdot (X_{hm} + X_{ml} - X_{hl})$$

$$X_l := \left(\frac{1}{2}\right) \cdot (X_{ml} + X_{hl} - X_{hm})$$

same on h, short L with m open

Z_{hm} at 100mV
 Z_{hl} at 20mVA
 Z_{ml} at 20mVA


U
I Component Modeling:
 Lines ECE525
Lecture 16

- $Z_1 = Z_2$ -phase rotation doesn't impact
- Often approximated with per phase equivalent self impedance
- Zero sequence current flows through earth and Z_0 often 2-6 times Z_1
- Usually neglect capacitances unless transient case
 - » Transient response matters for fast detection



$$Z_{012} = \begin{pmatrix} z_{00} & z_{01} & z_{02} \\ z_{10} & z_{11} & z_{12} \\ z_{20} & z_{21} & z_{22} \end{pmatrix}$$


- off diagonal small
- approximation to neglect them

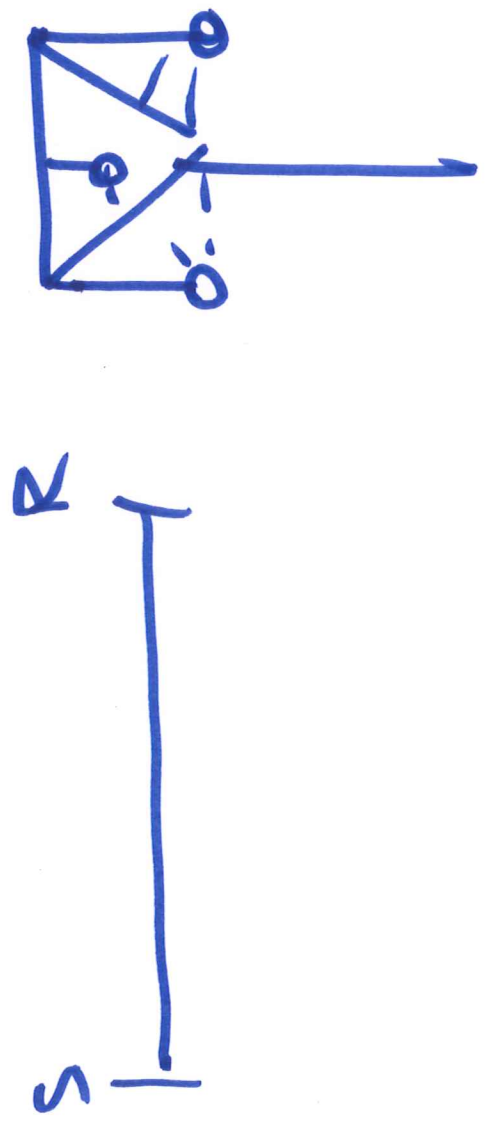If line untransposed (and not an equilateral triangle space)




Transposed line?

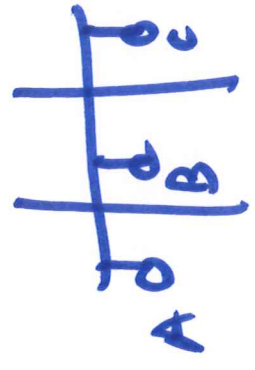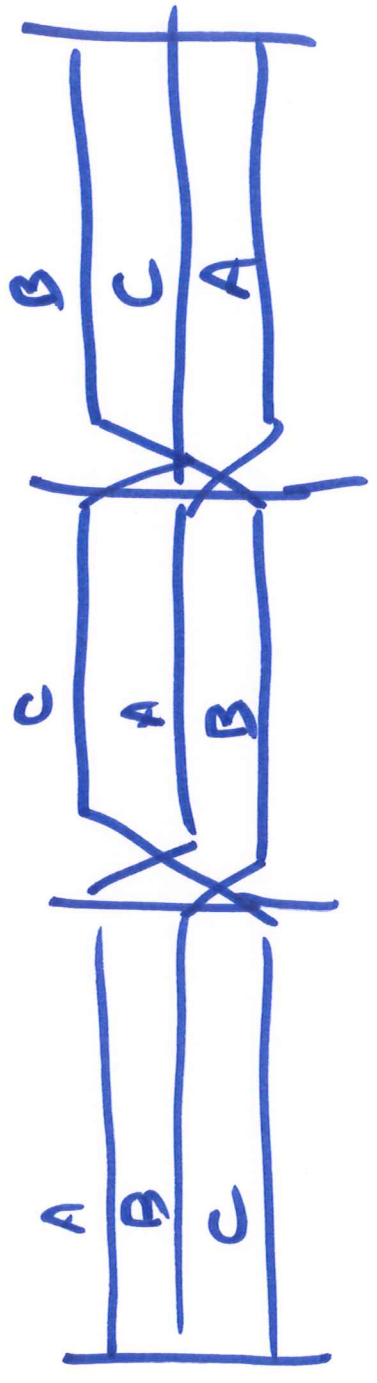

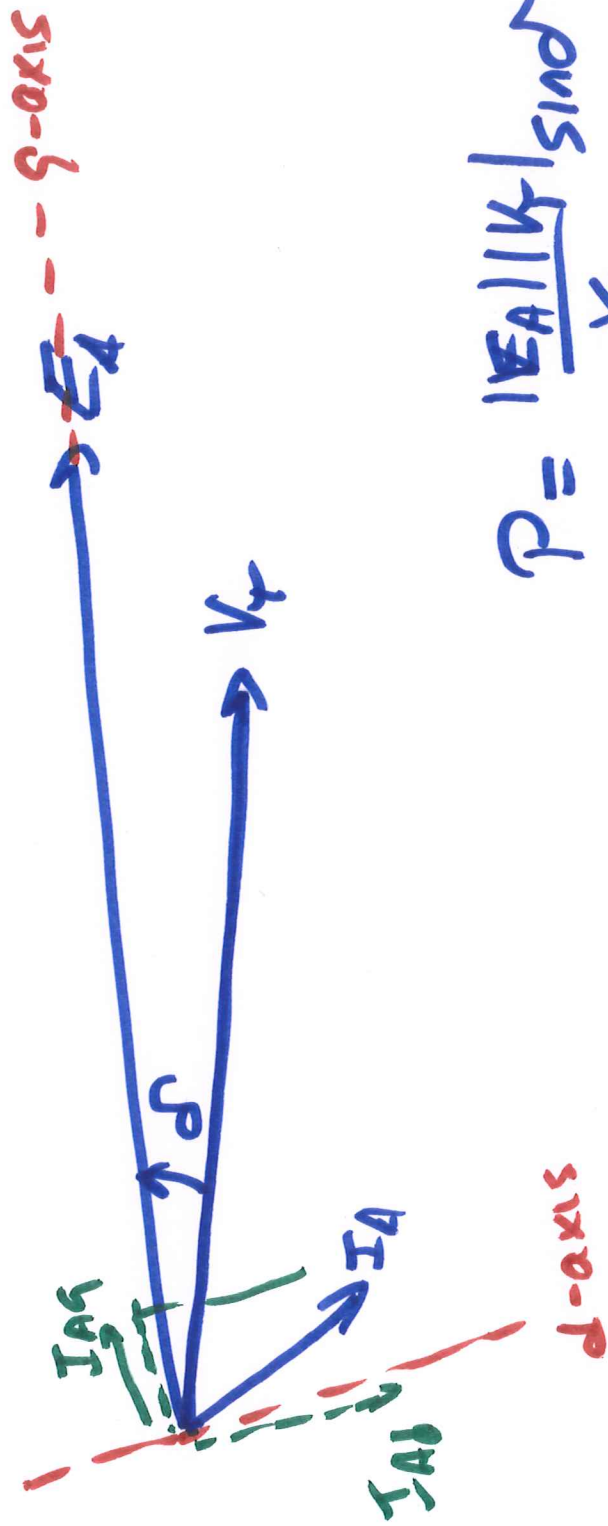

$$P = \frac{|E_A| |V_x| \sin \delta}{|V_x|}$$

$$P = 0$$

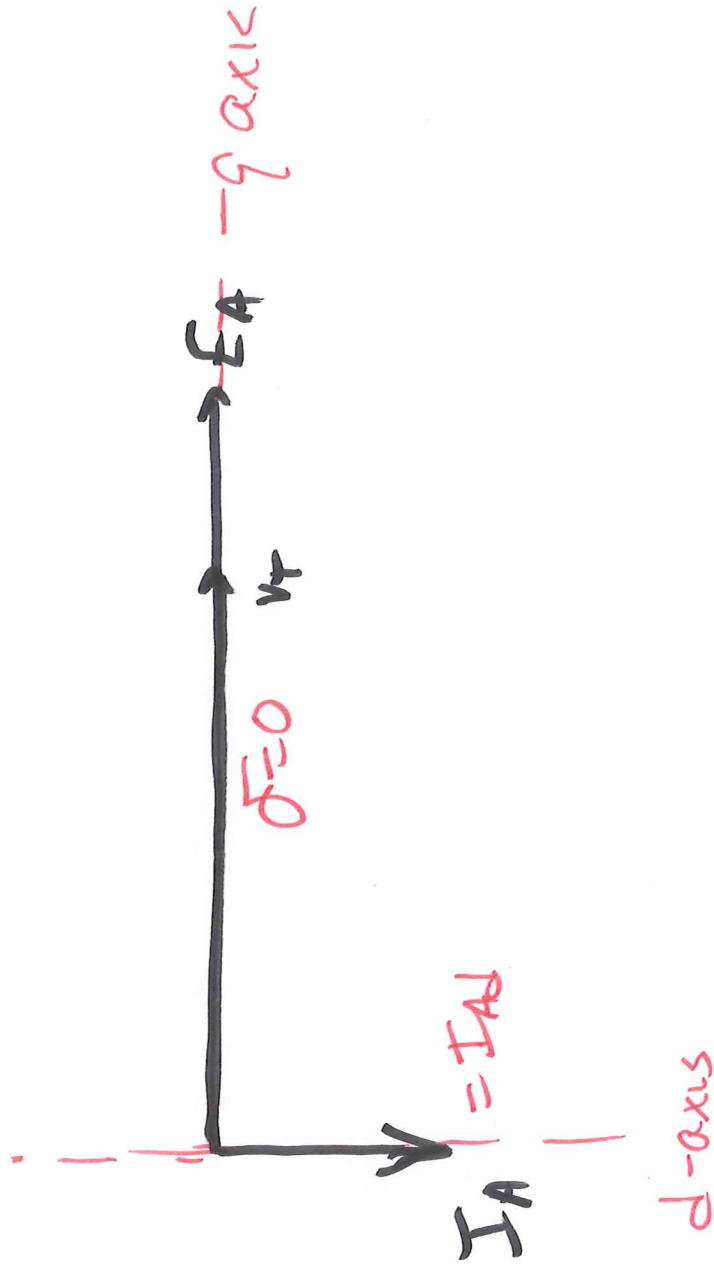

L17 6/15

U
I

Component Modeling: Lines

ECE525


Lecture 16

- Need to do detailed line constants calculation to get impedances accurately
- Form impedance matrix and then transform with Symmetrical Components Transformation matrix $Z_s = (A^{-1} * Z * A)$

$$Z_{ABC} = \begin{bmatrix} Z_{AA} & Z_{AB} & Z_{AC} \\ Z_{BA} & Z_{BB} & Z_{BC} \\ Z_{CA} & Z_{CB} & Z_{CC} \end{bmatrix}$$

Sequence Models of Apparatus

Fall 2018

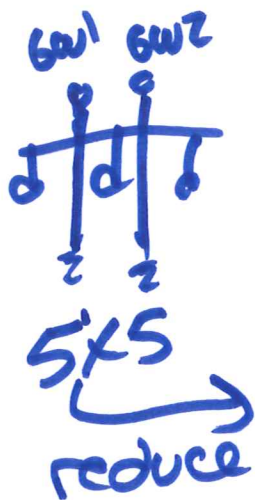


U
I

Generators

ECE525

Lecture 16

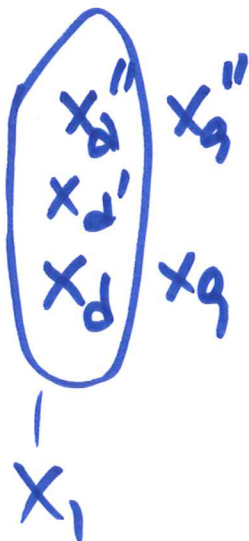- Positive sequence reactance broken into
 - subtransient, transient and steady-state
- Direct vs Quadrature axis
 - » Fault currents typically near zero power factor
 - » D-axis only
- Subtransient or transient reactance based on time scale of interest





Sequence Models of Apparatus

Fall 2018

L17 7/16

U I	Generators: Negative Sequence	ECE525 Lecture 16
	<ul style="list-style-type: none"> • MMF rotates backwards at twice the machines synchronous speed • Double frequency currents in the rotor field and amortisseur windings • Flux peak occurs along the d and q - axes • $X_2 \approx 0.5 \cdot (X_d'' + X_q'')$ 	
Sequence Models of Apparatus		Fall 2018

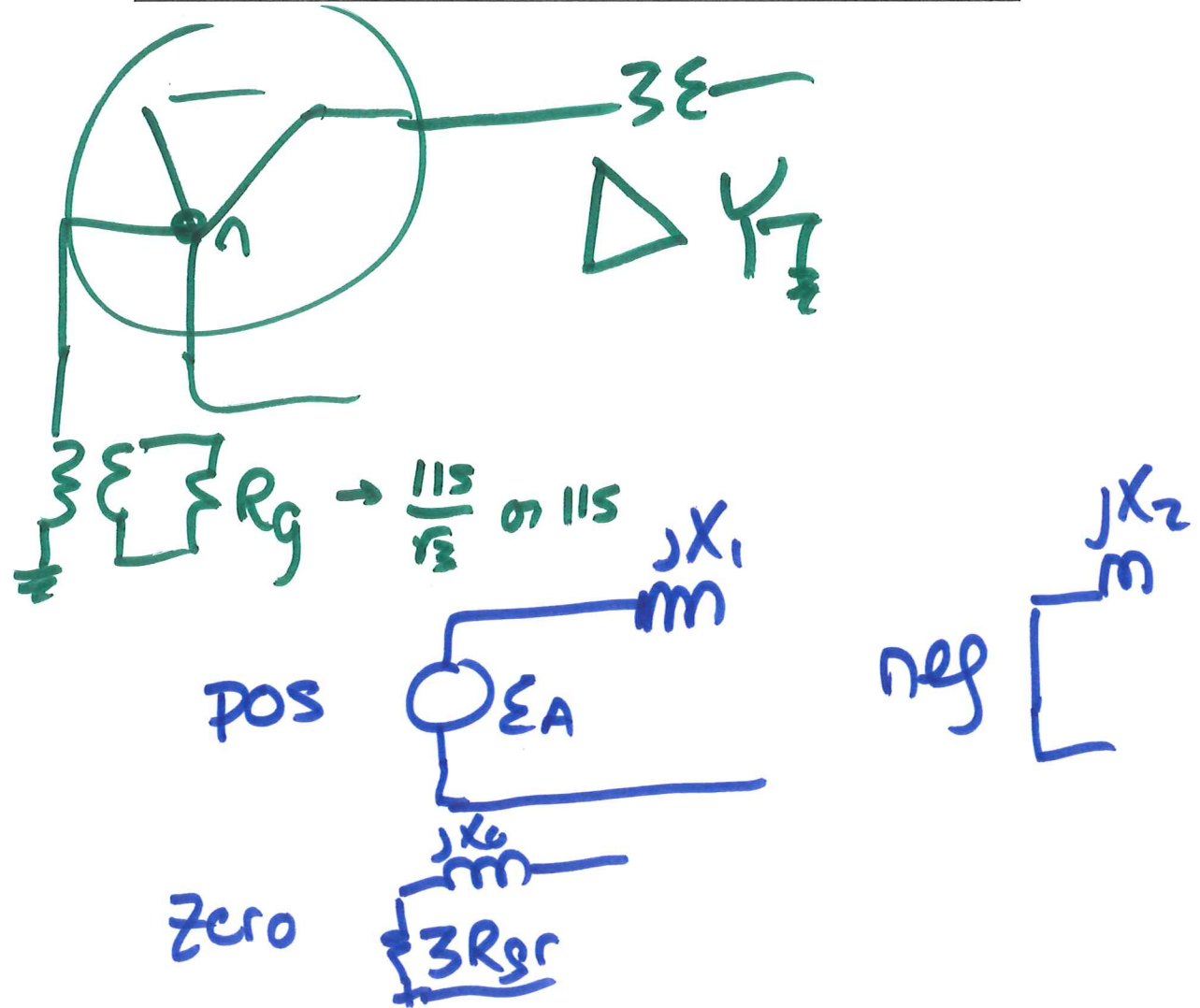

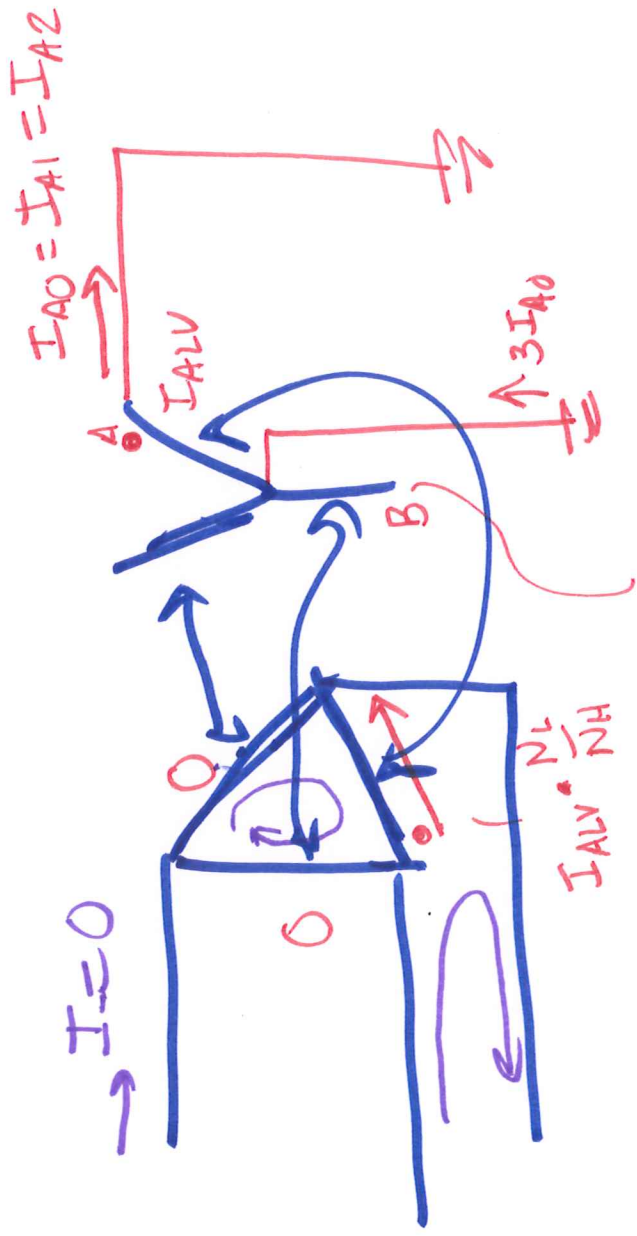

$$I_{B0} + I_{B1} + I_{B2}$$

$$I_{A0} + \alpha^2 I_{A1} + \alpha I_{A2} = I_{A0} (1 + \alpha^2 + \alpha) = 0$$

Now move the currents from the low side to the high side (note, you must transform the sequence currents):

$$I_{1_LLH} := I_{1_LLf} \cdot e^{j \cdot 30 \text{deg}} \quad I_{0_LLH} := 0 \text{pu}$$

$$I_{2_LLH} := I_{2_LLf} \cdot e^{-j \cdot 30 \text{deg}}$$

$$I_{abc_LLh} := A_{012} \cdot \begin{pmatrix} I_{0_LLH} \\ I_{1_LLH} \\ I_{2_LLH} \end{pmatrix}$$

$$\overrightarrow{|I_{abc_LLh}|} = \begin{pmatrix} 2.027 \\ 4.0541 \\ 2.027 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(I_{abc_LLh})} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

- negative sequence
overcurrent event
have this problem

Phase B per unit current is larger on the high side of the transformer than on the low side, use caution with coordination

Voltage at the fault point:

$$V_{1_LL} := V_{src} - j \cdot X_1 \cdot I_{1_LLf} \quad |V_{1_LL}| = 0.5 \cdot \text{pu} \quad \arg(V_{1_LL}) = 0 \cdot \text{deg}$$

$$V_{2_LL} := 0 - j \cdot X_2 \cdot I_{2_LLf} \quad |V_{2_LL}| = 0.5 \cdot \text{pu} \quad \arg(V_{2_LL}) = 0 \cdot \text{deg}$$


$$V_{0_LL} := 0 - j \cdot X_0 \cdot I_{0_LLf} \quad |V_{0_LL}| = 0 \cdot \text{pu}$$

$$V_{abc_LL} := A_{012} \cdot \begin{pmatrix} V_{0_LL} \\ V_{1_LL} \\ V_{2_LL} \end{pmatrix}$$

$$\overrightarrow{|V_{abc_LL}|} = \begin{pmatrix} 1 \\ 0.5 \\ 0.5 \end{pmatrix} \cdot \text{pu}$$

www.powerword.com/glover-sarma-overbye


Directional Determination

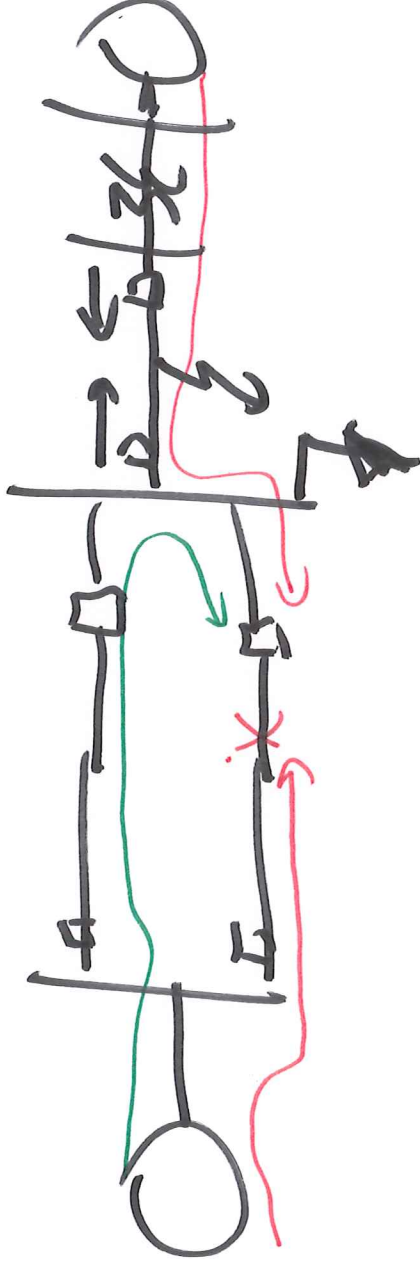



- Directional supervision protection elements to minimize amount of system tripped
- improve selectivity

- Need a stable angle reference
- something that doesn't move as much as angle of current
- voltage angles don't change as much

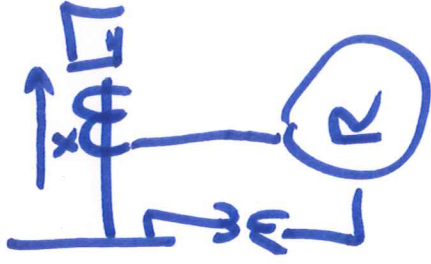→ direction based on angle of current compared to voltage



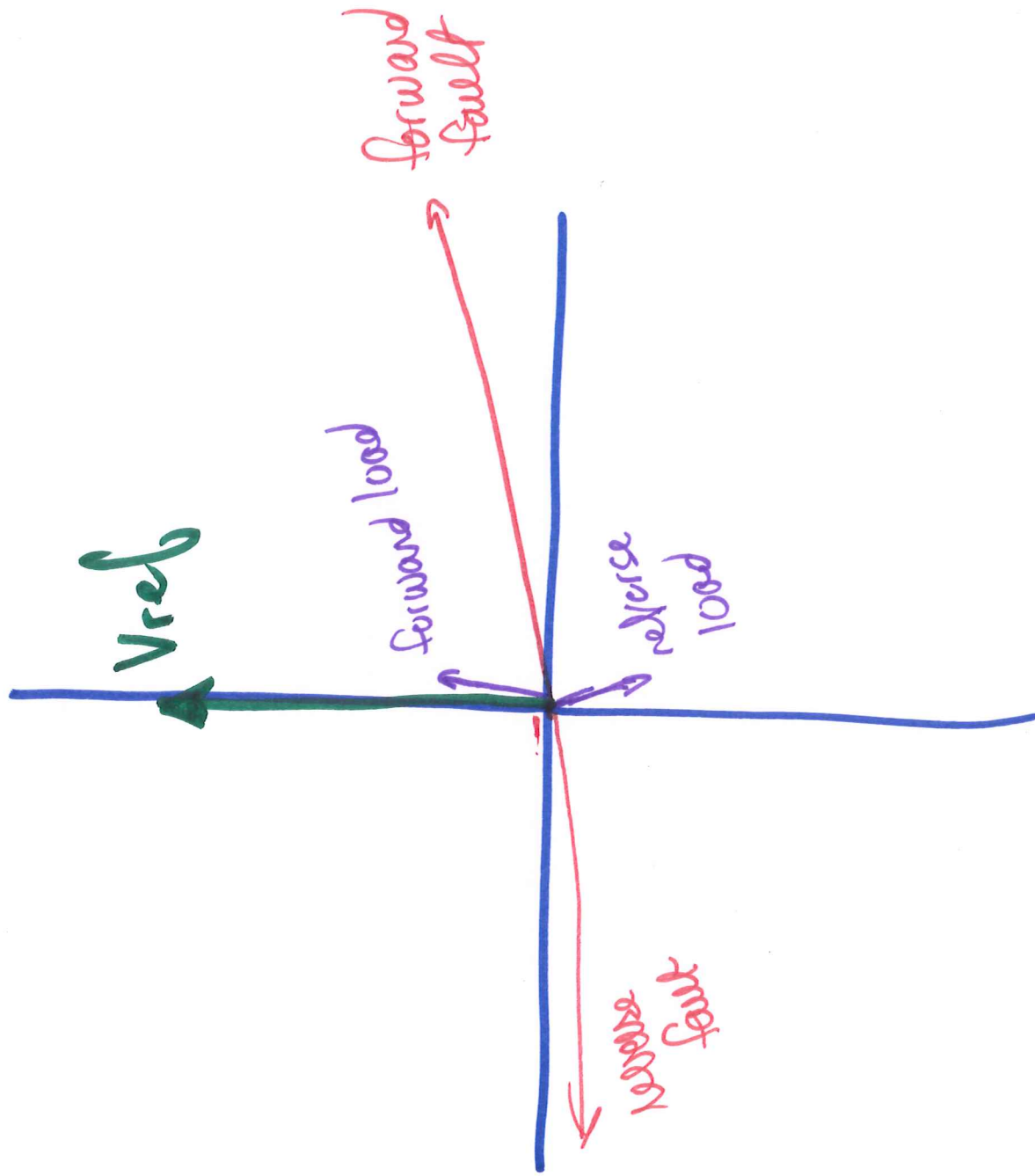

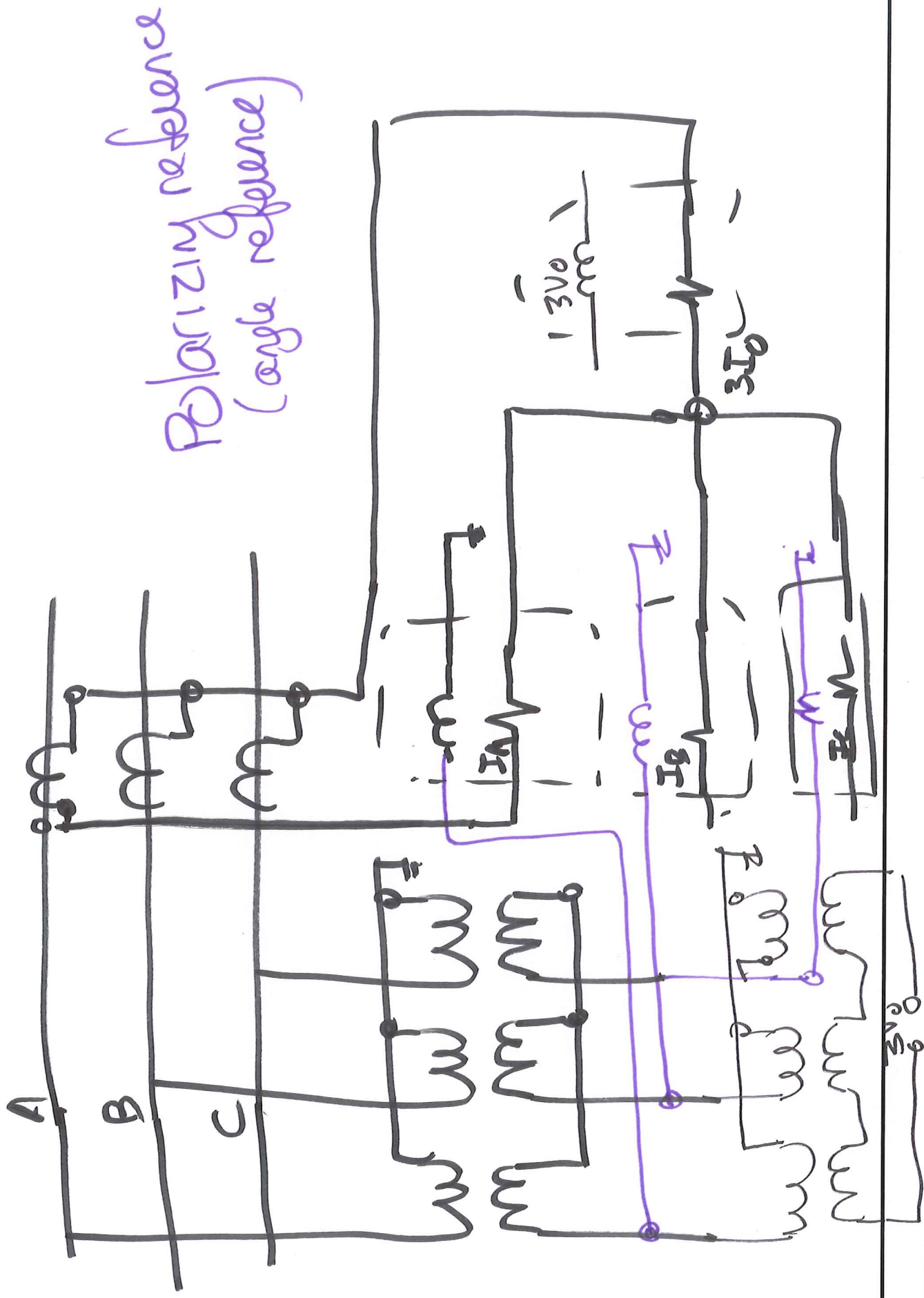

Self polarized directional

Hybrid
angle of line
impedance

$$T_{ST} = \underbrace{V_{ref}}_{VAS} |I_A| \cos(\theta_V - (\theta_I + mTA))$$

Torp

max
torque
angle

