

Introduction to Bus Protection



Purpose & Learning Objectives



By Matt Horvath, P.E.
November 6, 2018



Presentation Outline


1. Physical Bus Types
 2. Typical Bus Configurations
 3. Bus Protection Methods & Schemes
 4. High Z Bus Differential Protection
- After this presentation you will be able to:
- Identify common bus arrangements
 - Identify and understand the operation of common bus protection schemes
 - Understand high impedance bus differential operating principles (SEL-58Z)

Open Air Rigid Bus




- Main Components
 - Copper or aluminum conductor
 - Supporting structures
 - Post Insulators
 - Solid and/or flexible connectors
- Advantages
 - Relatively Economical
 - Simple
 - Easy to trouble shoot
 - Short repair time
 - Longer Free Spans
- Disadvantages
 - Exposure
 - Larger footprint required

Electrical Buses

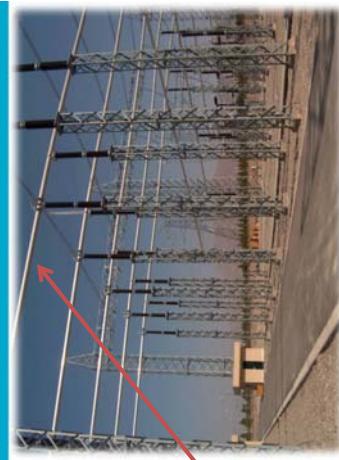

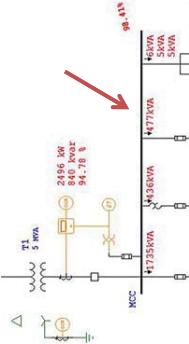Physical and Electrical Junction
“A bus is a critical element of a power system, as it is the point of convergence of many circuits.”
From IEEE Std. C37.97 A Guide for Protective Relay Applications to Power System Buses



Strain Bus




- Main Components
 - Flexible Conductors
 - Supporting Structures
 - Strain insulators
- Advantages
 - Small footprint
 - Simplicity
 - Very Economical
 - Short repair time
- Disadvantages
 - Lower reliability
 - Exposure
 - Conductor spacing and capacity



Gas Insulated Bus



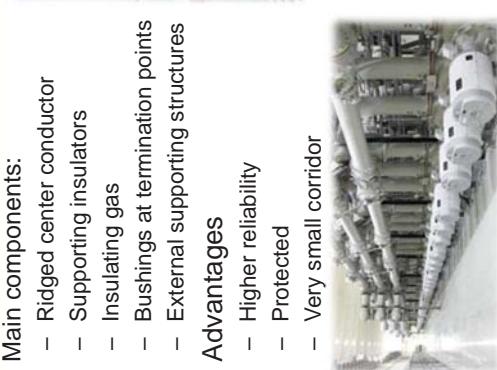- Main components:
 - Ridged center conductor
 - Supporting insulators
 - Insulating gas
 - Bushings at termination points
 - External supporting structures
- Advantages
 - Higher reliability
 - Protected
 - Very small corridor
- Disadvantages
 - High cost
 - Difficult troubleshooting
 - Long repair time



Indoor Switchgear Bus



- Main components:
 - Ridged center conductor
 - Supporting insulators
 - Air dielectric
 - Bushings at termination points
 - External supporting structures
- Advantages
 - Higher reliability
 - Protected
 - Smaller conductor spacing
 - Forced air cooling possible
- Disadvantages
 - High cost
 - Long repair time
 - Expensive



Isolated-Phase Bus



- Main components:
 - Ridged center conductor
 - Supporting insulators
 - Air dielectric
 - Bushings at termination points
 - External supporting structures
- Advantages
 - Higher reliability
 - Protected
 - Smaller conductor spacing
 - Forced air cooling possible
- Disadvantages
 - High cost
 - Long repair time
 - Expensive

Importance of Bus Protection



Bus Fault Characteristics


- Not very common

When they do occur:

- Usually bolted faults
- Higher fault magnitudes

Bus Fault Impact:

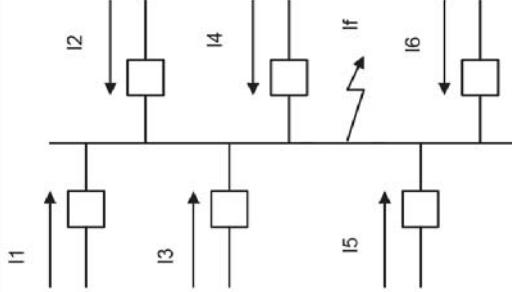
- All bus circuits must be interrupted
- Can result in severe system disturbances



Bus Protection Philosophy



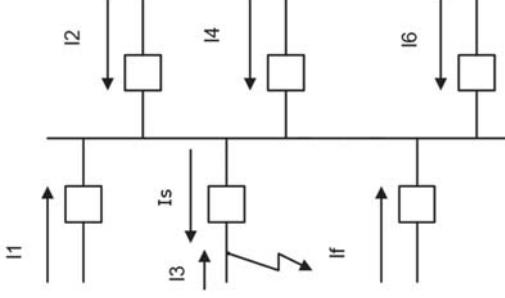- Dedicated protection
- High speed operation for internal faults
- Two-out-of-two trip criteria
- Optional redundant protection scheme
- Remote backup protection
- Time overcurrent protection
- Security for out-of-zone faults
- Sensitivity for minimum internal faults




Bus Lockout Relays




Principle and Operation

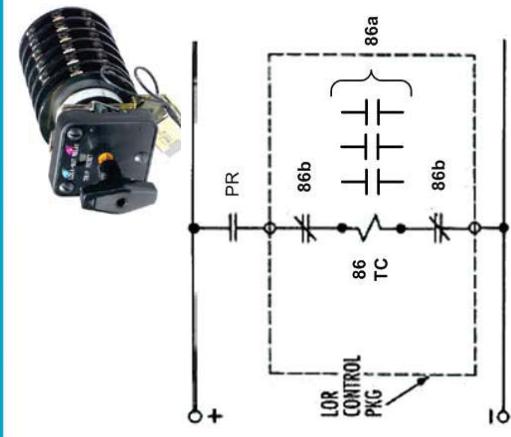- Trips and lockouts the bus breakers
- Many output contacts
- Operation isolates its trip coil
- Very fast operation
- Hardwired to breaker trip circuits
- Can be used to protect relay contacts



Bus Sectionalizing

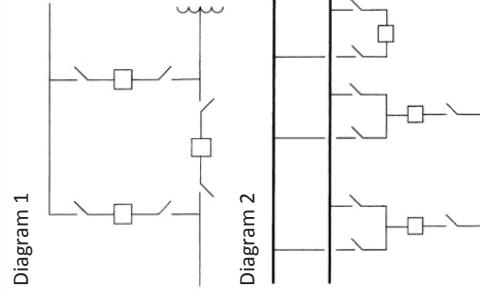- Improves system reliability
- Minimizes Impact of Outages
- Utilizes Various Arrangements
 - Combined Arrangements
 - Operating Flexibility
 - Selectivity
 - Bus protection must adapt



Single Bus – Single Breaker




One of the most basic and economical designs

No operating flexibility

Zone of Protection


- Encompasses the whole bus

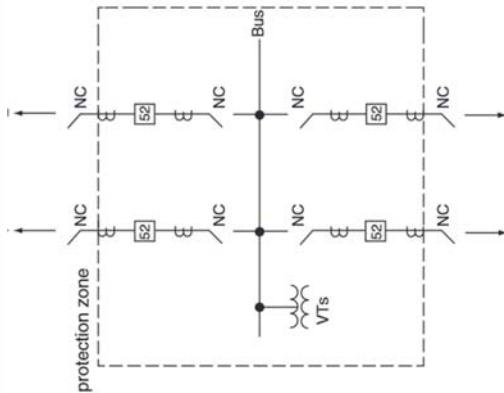Bus fault will interrupt all associated services



Bus & Transformer Single Breaker

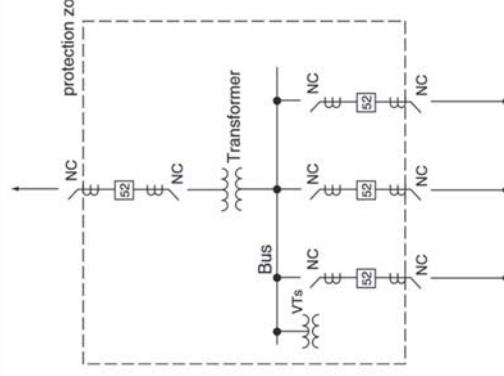
- Zone of Protection:
 - Bus and Transformer protection is combined
- Usually used in distribution substations
- No selectivity
- No flexibility
- Fault location difficulty
- Very economical



Double Bus w/Bus Tie – Single Breaker



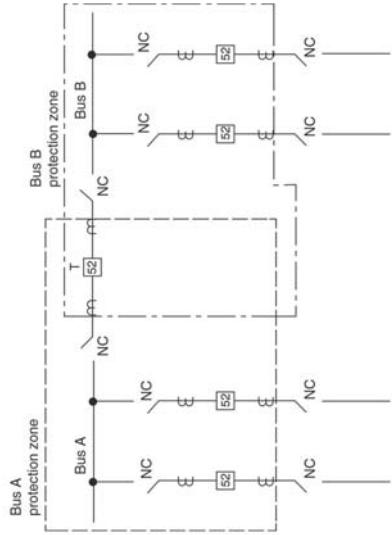- Zone of Protection:
 - Bus A and Bus B have independent and dedicated protection
 - Little Flexibility
 - Some Selectivity



Main & Transfer Bus – Single Breaker




Breaker substitution

Zone of Protection
Encompasses main bus only

Transfer bus protection
provided by transfer breaker

No selectivity

Flexibility increases
Often Combined

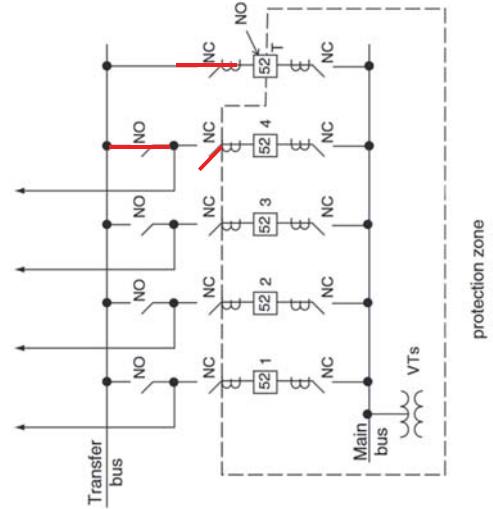


Double Bus – Single Breaker



Double Bus – Double Breaker

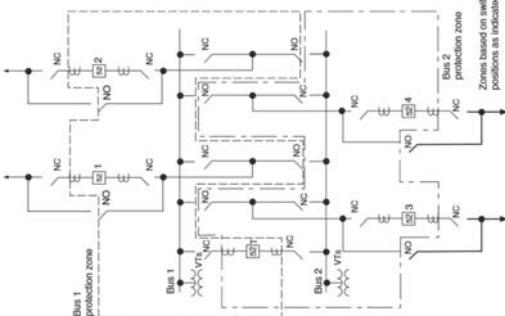- Zone of Protection:
 - Bus 1 and Bus 2 have independent protection assigned based on switching condition
- Lots of operating flexibility
- Some selectivity
- Complex switching
- CT winding assignments change
- Not commonly used in the U.S.




2 zones based on switch positions as indicated

Ring Bus




Breaker-And-A-Half Bus

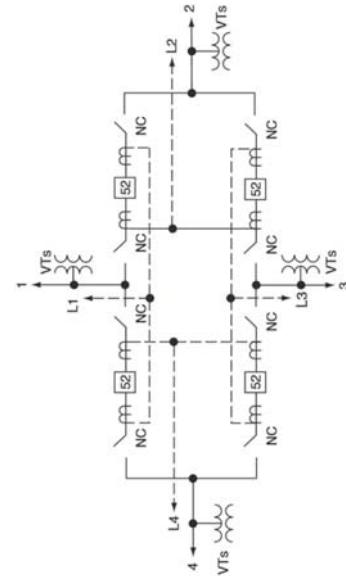- No dedicated bus protection
- Full operating flexibility
- Good selectivity
- Shared breakers
- Economical



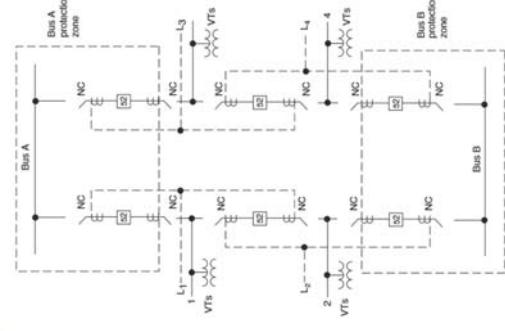
- Zone of Protection:
 - Bus A and Bus B have independent and dedicated protection zones.
- Line position protection provided by branch circuits
- Economical



Differential Overcurrent



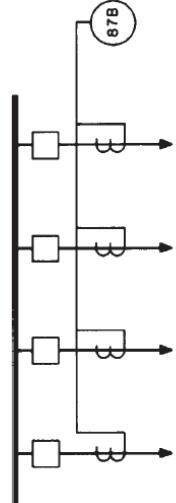- CT secondary leads summed outside the relay
- Identical Tap ratios
- CT matching
- Difference Current using 51/50 elements
- Time delayed
 - Avoid misoperation due to transient saturation



Differential Overcurrent




Advantages

- Economical

Disadvantages

- Security
- Strong sources
- Time-delayed clearing
- Difficult to set properly
- Not suitable in areas of system with high X/R ratio

Differential Overcurrent (continued)

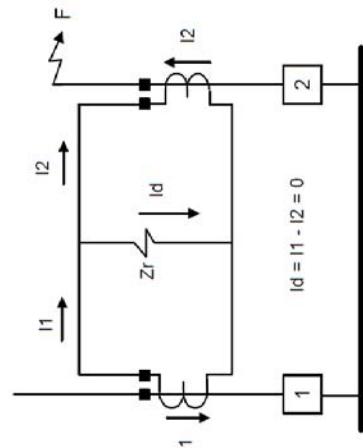


Partial Bus Differential



Operating Principles:

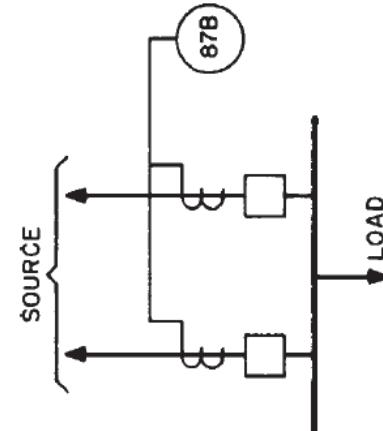- Source CT leads summed outside relay
- Tie breaker CTs included
- Overcurrent element
- Pickup set above load
- Selectivity required
- Optional: Distance elements



Partial Bus Differential (Continued)




Partial Bus Differential (Continued)

Advantages:

- Very economical

Disadvantages:

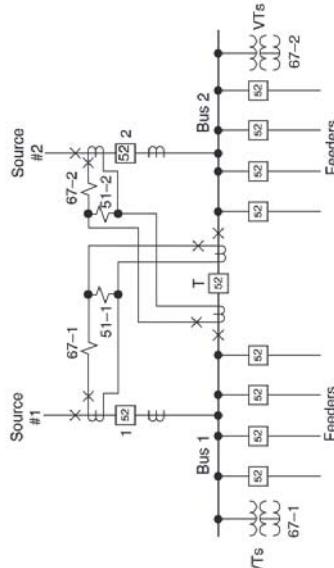- Fault Current/FLA
- Required selectivity
- Reduced sensitivity
- Used with radial circuits




Zone Interlock Scheme (Fast Bus Tripping)



Zone Interlock Scheme (Continued)

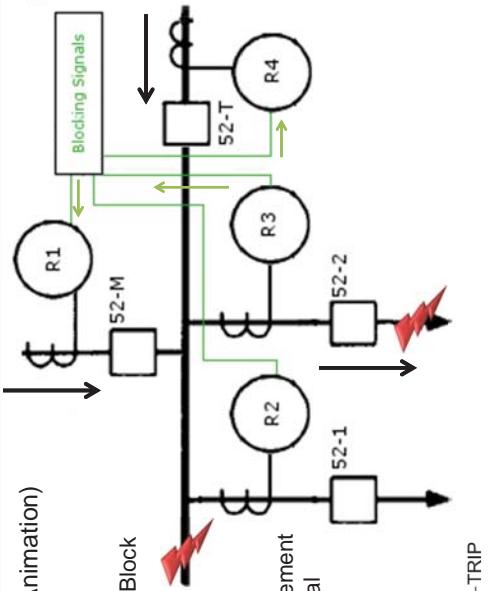- Operating Principle: (Animation)**
- Source circuit(s)
 - Time delayed
 - Receives/Sends Block Signal
 - Directionality
 - Radial circuit(s)
 - Instantaneous element sends block signal
 - Communication




50_{SRC} — D — 50_{FDR} — PU — 0 — TRIP

Directional Comparison



- Operating Principle:**
- Distance Elements
- Advantages**
- Relatively Economical
 - Few CT constraints


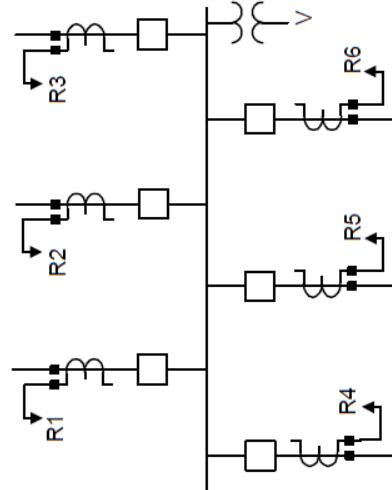
- Disadvantages**
- Voltage Reference
 - Multiple Failure Points



High Current Interruption & Limiting



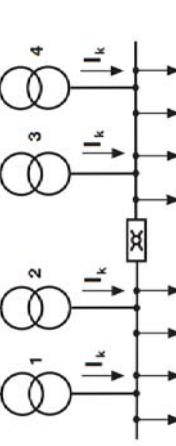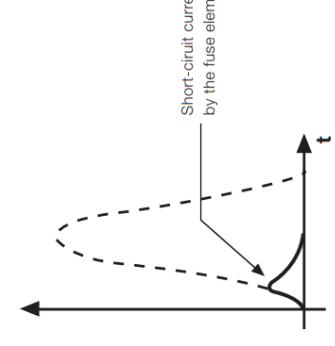- Fuses & Short Circuit Limiters**
- High Interrupt rating
 - IS limiter operates in less than 1ms



- Advantages**
- Extremely High Speed
- Disadvantages**
- Replacements needed with fusible interrupters

Arc Flash Protection



Optical Sensors

- Fiber optic sensors or loops
- Indoor Switchgear



Advantages

- Relatively Economical
- Extremely High Speed




Dissadvantages

- Supervision with optical

Operating Principle: (Animation)

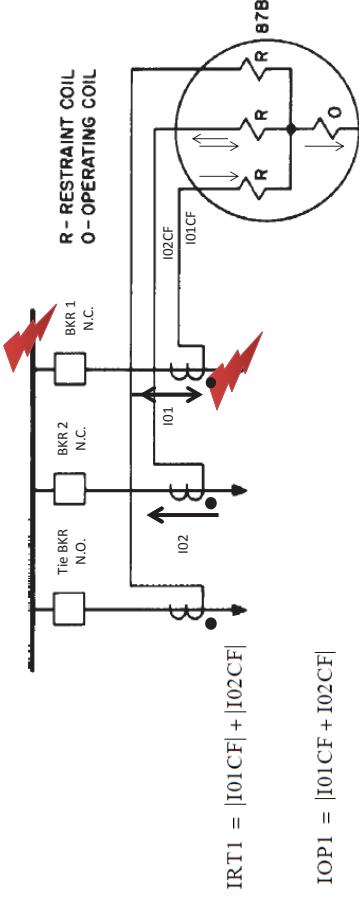- Relay measures difference and restraint quantities
- Trip if difference current exceeds a set percentage of the restraining quantity



Percentage Restrained Differential




Operating Principle: (Animation)

- Relay measures difference and restraint quantities
- Trip if difference current exceeds a set percentage of the restraining quantity


Percentage Restrained Differential (Continued)



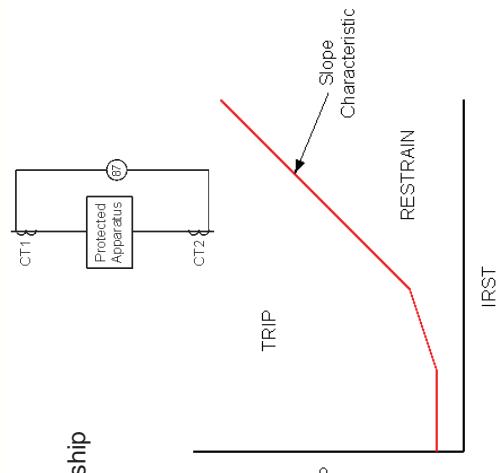- Operate vs. Restraint Relationship
- Slope Setting
- Controlling Factors
 - CT Performance
 - X/R Ratio
 - Fault Magnitude
- Dual Slope Characteristic



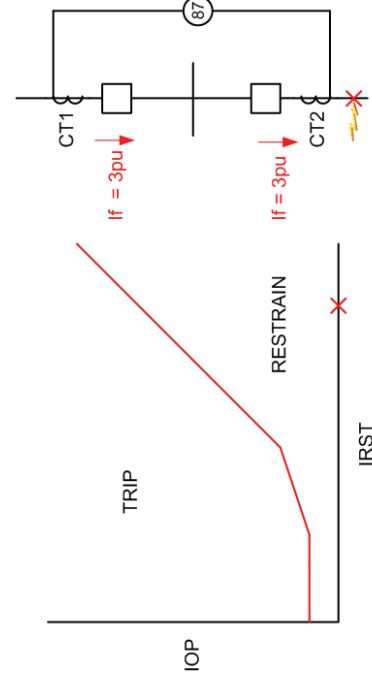Percentage Restrained Differential (Continued)




$$\begin{aligned} \text{IRST} &= |3| + |3| = 6 \\ \text{IOP} &= |3 + (-3)| = 0 \end{aligned}$$

Percentage Restrained Differential (Continued)



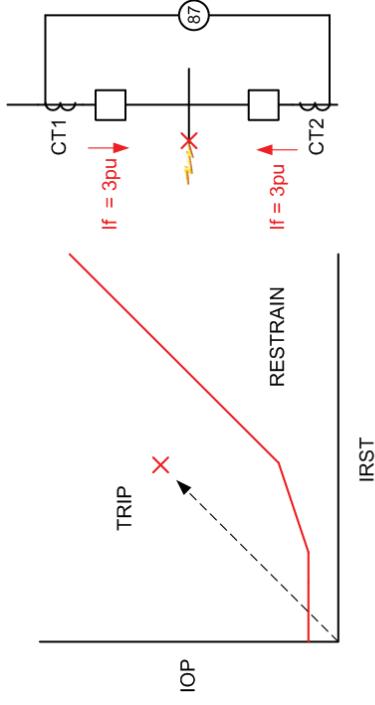Percentage Restrained Differential (Continued)



$$|I_{RST}| = |3| + |3| = 6$$


$$|I_{OP}| = |3 + 3| = 6$$

Percentage Restrained Differential (Continued)




Percentage Restrained Differential (Continued)

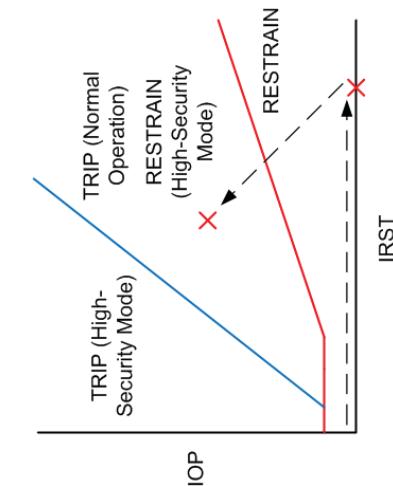- Relay constantly monitors changes in operate and restraint currents
- Increase in restraint without an increase in operate current indicates external fault
 - Relay enters high-security mode
- Only requires short period (~2-4ms) of unsaturated operation




Settings Considerations

- Minimum pickup must be greater than error difference current, but less than minimum available fault current
 - Typically set to 1pu of bus continuous rating on solid-grounded systems
 - Lower pickups used on impedance-grounded systems
- Slope settings
 - Withstand measurement errors at low currents
 - Withstand saturation-induced errors at high currents
- Modern relays with adaptive slope characteristics provide enhanced security and sensitivity

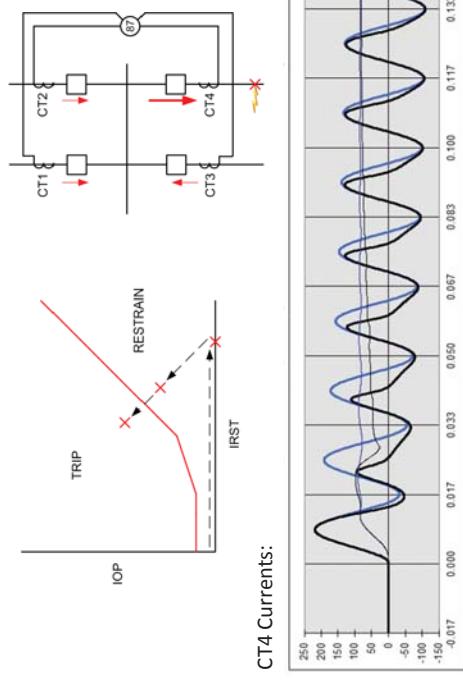

CT4 Currents:

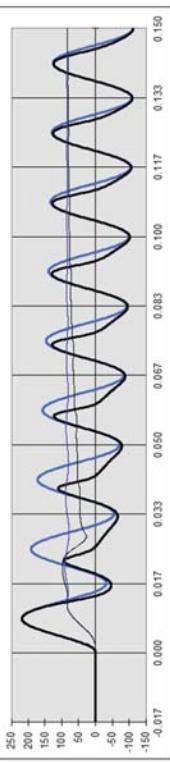

Percentage Restrained Differential (Continued)




- Advantages:
- Fast Operation
- Good security

Disadvantages:

- CT criteria and performance critical
- May require many relay current inputs
- Sensitivity—High Z Grounded Systems

$$IOP = |I_1 + I_2|$$

$$IRST = |I_1| + |I_2|$$

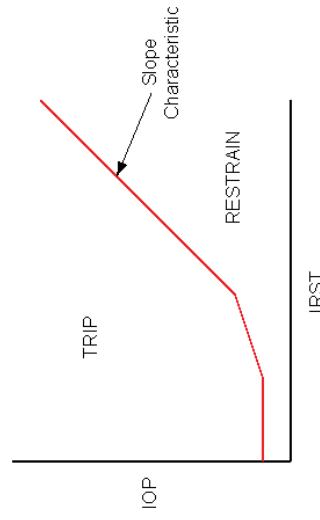


High Impedance Bus (Voltage) Differential



Introduction and Basic Concept (Animation)

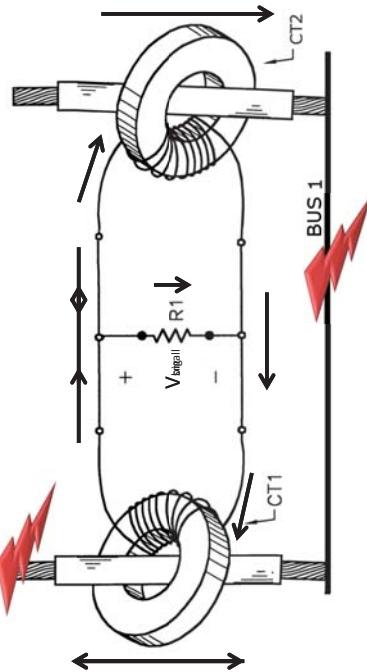- Popular Bus Protection Scheme
- Arc Flash Mitigation




High Impedance Bus Differential (Continued)




Characteristics and Typical Application Layout

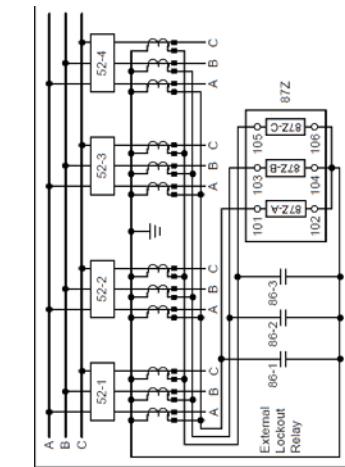- CTs connected in parallel with high-impedance relay input
- Relay operates on voltage across high-impedance inputs
- Can accommodate a large number of terminals
- Excellent sensitivity and speed
- Simple element to configure



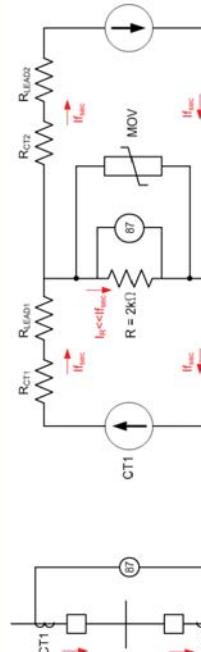High Impedance Bus Differential (Continued)



External Fault (or typical loading) Case:


- Current circulates between CTs
- Negligible current flow through high-impedance relay input (high resistance/burden path)




High Impedance Bus Differential (Continued)



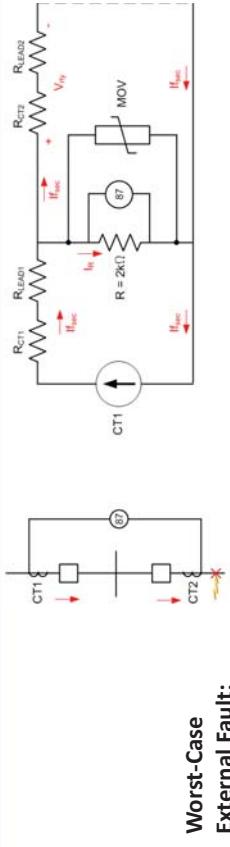High Impedance Bus Differential (Continued)




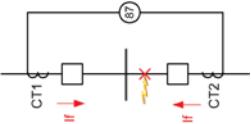- CT2 completely saturates (does not supply any representative secondary current waveform)
- High impedance input sees voltage developed by secondary current flowing through CT winding resistance and lead resistance
- Element pickup must be set greater than this voltage (typically by a factor of 1.5 to 2) for security



Internal Fault Case:

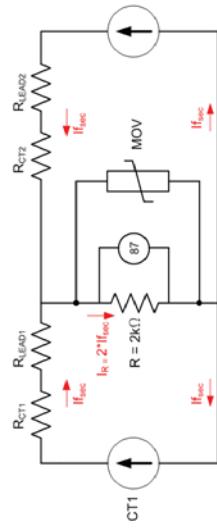
- Current flows through stabilizing resistor and produces high secondary voltages
- Voltage magnitude limited by MOV
 - LOR 'a' contacts required across high-impedance input
- CTs produce current and secondary voltage until they saturate




High Impedance Bus Differential (Continued)



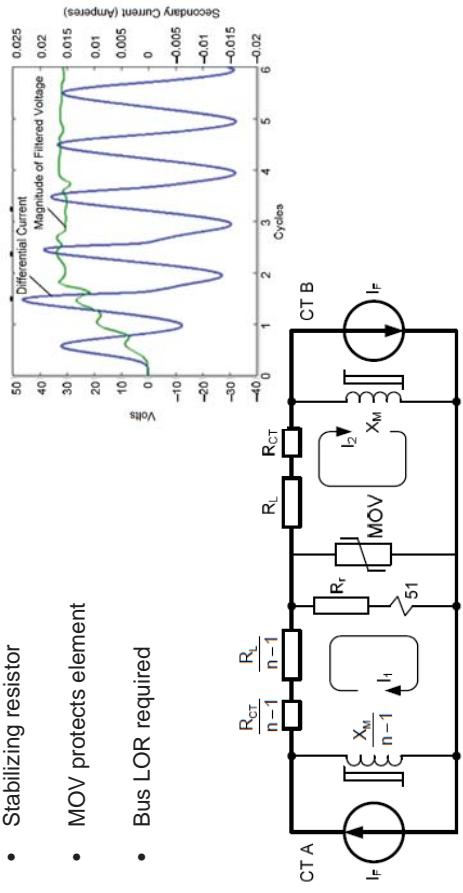High Impedance Bus Differential (Continued)



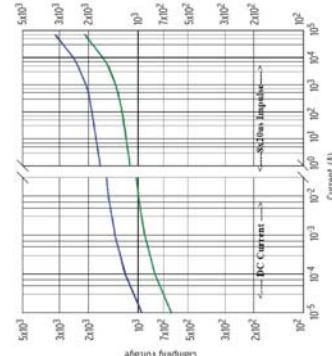- Stabilizing resistor
- MOV protects element
- Bus LOR required



Cutaway view showing stabilizing resistors and MOVs.

High Impedance Bus Differential (Continued)




POWER
UNIVERSITY


High Impedance Bus Differential (Continued)

Manufacturer Internal Fault Testing

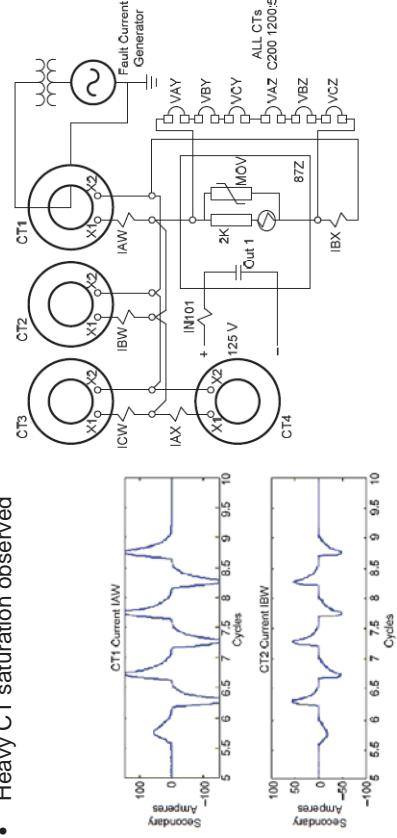- Test currents of 20 kA, 40 kA and 60 kA applied.
 - Heavy CT saturation observed



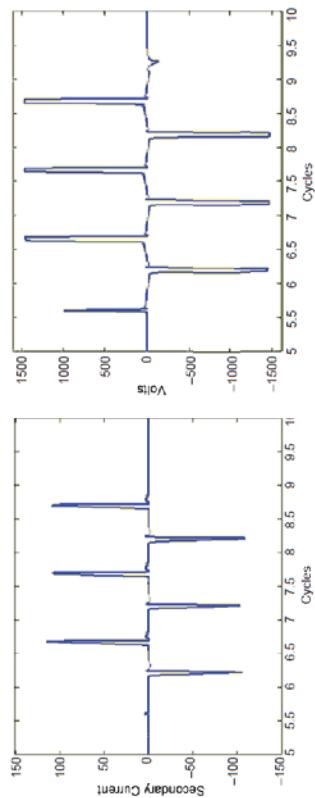- Differential current and voltage waveforms
 - Note the voltage is limited to 1500V by the internal MOV
 - C200 1200:5 CTs, 60 kA internal fault




High Impedance Bus Differential (Continued)



High Impedance Bus Differential (Continued)

60 kA Internal Fault Test

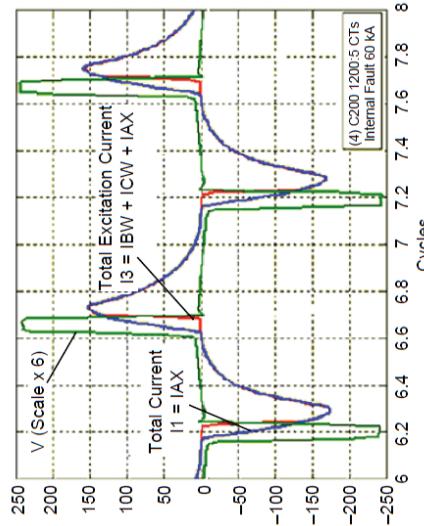- The volt-time area
Resistor vs. Magnetizing Current




High Impedance Bus Differential (Continued)



High Impedance Bus Differential (Continued)

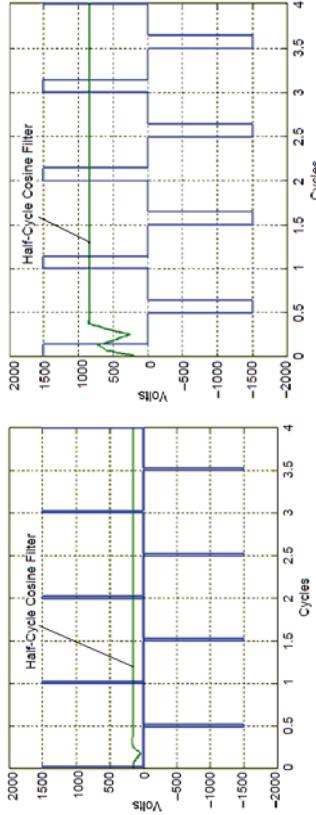Volt-time area proportional to C-rating
Dictated by lowest-rated CT in differential circuit




High Impedance Bus Differential (Continued)



Volt-time area is similar for CTs with equivalent C-rating,
even if ratios are different

Maximum voltage limited by MOV

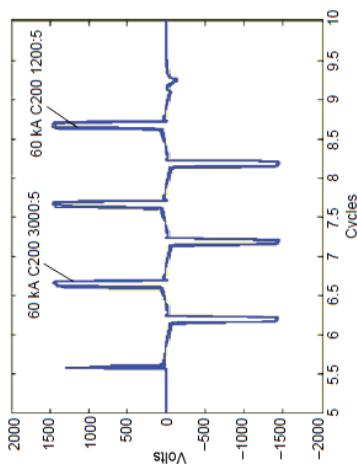


High Impedance Bus Differential (Continued)



Manufacturer External Fault Testing Results

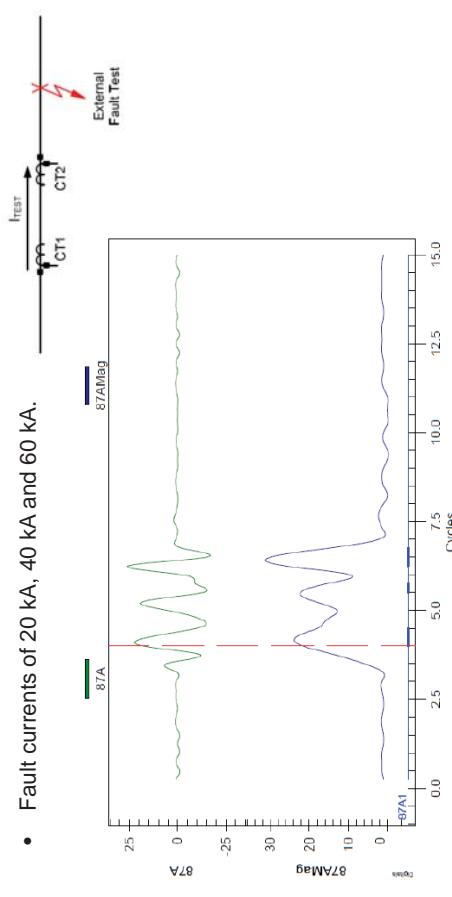- Fault currents of 20 kA, 40 kA and 60 kA.




High Impedance Bus Differential (Continued)



MOV Sizing for SEL-587Z

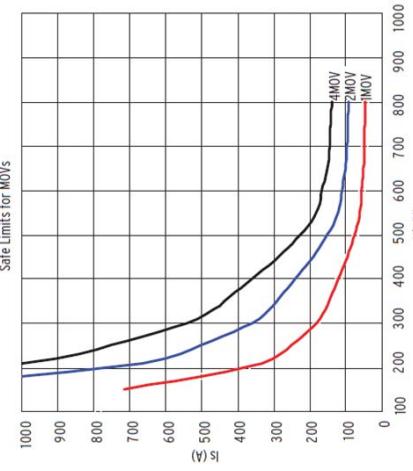- MOV requirements based on energy dissipation limits for 4-cycle duration
- Requires 86 "a" contacts wired across relay inputs!
- Energy rating is a function of knee-point voltage and maximum secondary current



High Impedance Bus Differential (Continued)




Manufacturer Testing Results for SEL-587Z

Recommended High-Value Setting:

- 200V with no time delay
- Sensitive and Secure

Optional Recommendations For Low-Value Setting:

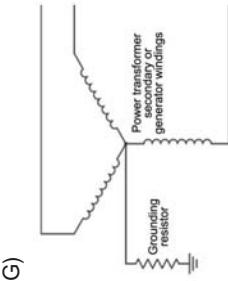- Only needed in some applications (e.g. HRG/LRG)
 - Minimum sensitivity calculations
 - Implement a time delay (min 1 cycle).





High Impedance Bus Differential (Conclusion)

Secure Voltage Setting Calculation

- Sensitivity impacted by wiring design
- Worst-case out-of-zone fault condition
- Relay pickup set to a multiple of V_r

$$V_r = (R_{CT} + P \cdot R_{LEAD}) \cdot \frac{I_F}{N}$$

V_r = voltage across the high-impedance element
 I_F = maximum external fault current
 N = CT ratio

R_{CT} = the CT secondary winding and lead resistance up to the CT terminals

R_{LEAD} = the one-way resistance of lead from junction points to the most distant CT

P = 1 for three-phase faults and 2 for single-phase-to-ground faults

High Impedance Bus Differential (Continued)

Minimum Sensitivity Calculation

- Verify for Internal Fault
- Ignore MOV leakage current
- Use CT Excitation Characteristic
- When $V_s <$ knee point voltage:

$$I_{min} = (n \cdot I_e + I_r + I_m) \cdot N$$

- When $V_s >$ knee point voltage:

$$I_{MIN} = \left[n \cdot \left(I_e @ V_s / 2 \right) \cdot 2 + I_r @ V_s \right] \cdot CTR$$

I_{min} = minimum current
 n = number of current transformers in parallel with the relay, per single phase
 I_e = current transformer exciting current at relay setting voltage = V_s
 I_r = current through the relay at relay setting voltage = V_s
 I_m = current through the MOV at relay setting voltage = V_s

High Impedance Bus Differential (Conclusion)



Advantages:

- Very fast operation
- High security
- Incorporates large number of terminals

Disadvantages:

- Sensitivity decreases as number of CTs and/or lead lengths increases
- Must use CTs with C200 rating or greater
- Complexities associated with mixed-ratio CTs



Summary



- Bus protection is critical
- Bus Sectionalizing
 - Operating flexibility
 - Selectivity
- Bus Protection Schemes
 - Wide variety of schemes
 - Criticality
 - Available fault current & X/R ratio
 - Sensitivity/Speed Requirements
 - CT availability

References

- IEEE Std. C37.97, *Guide for Protective Relay Applications to Power Buses*
- Blackburn, J. Lewis, *Protective Relaying, Principles and Applications, Third Edition*, New York: Marcel Dekker, 1998
- Basler Electric Company, *Bus Protective Relaying, Methods and Application*, Revision Date: 6-8-2005
- General Electric Company, *Bus Differential Protection, WPRC 1995*, GER-3961
- Zocholl, E. Stanley and Costello, David, *Schweitzer Engineering Laboratories, Inc., Application Guidelines for Microprocessor-Based, High-Impedance Bus Differential Relays*
- Costello, David and Mooney, Joe, *Applying the SEL-587Z in Switchgear*, SEL Application Note AN2008-01

Thank you for your time!

This concludes the educational content of this activity.

QUESTIONS?



Matt Horvath, P.E.
Electrical Engineer
(509) 780-0042
matt.Horvath@powering.com