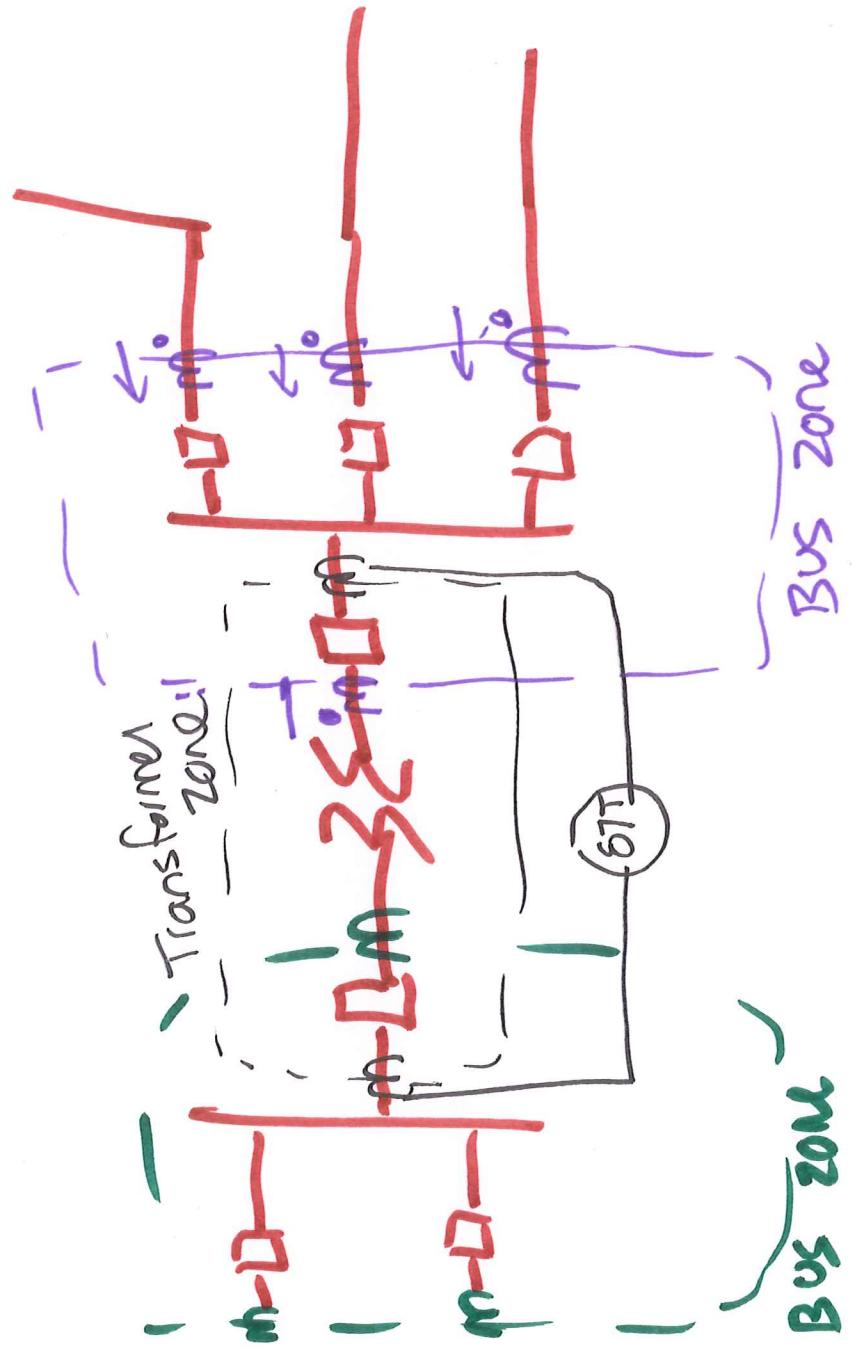



ECE 525

POWER SYSTEM PROTECTION  
AND RELAYING

SESSION no. 24



- Simplest scheme - Bus Differential 87B

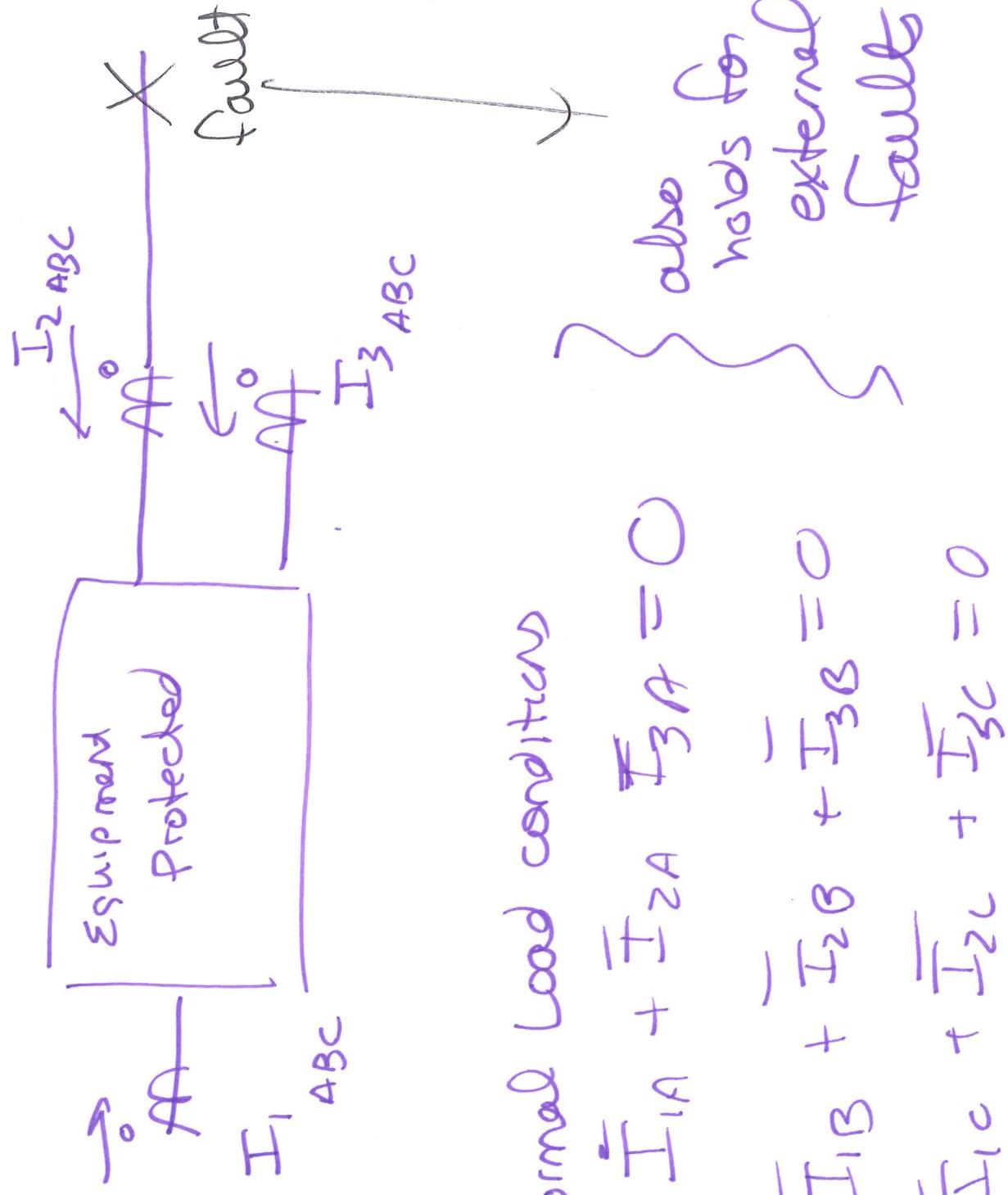

## Internal Fault


- Between the CTS

$$\bar{I}_{1A} + \bar{I}_{2A} + \bar{I}_{3A} = \bar{I}_{AF}$$


- Setting a threshold to differentiate a fault from external fault or load
  - (internal)

→ Rely operators on secondary current

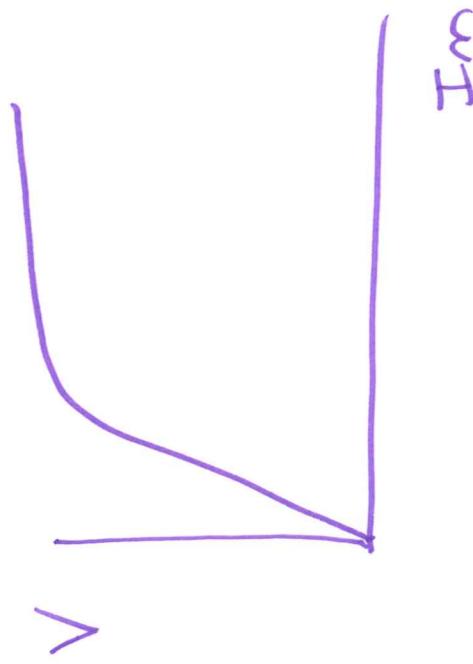- For bus scheme
- matched CTs
- ~~also~~ same C-class



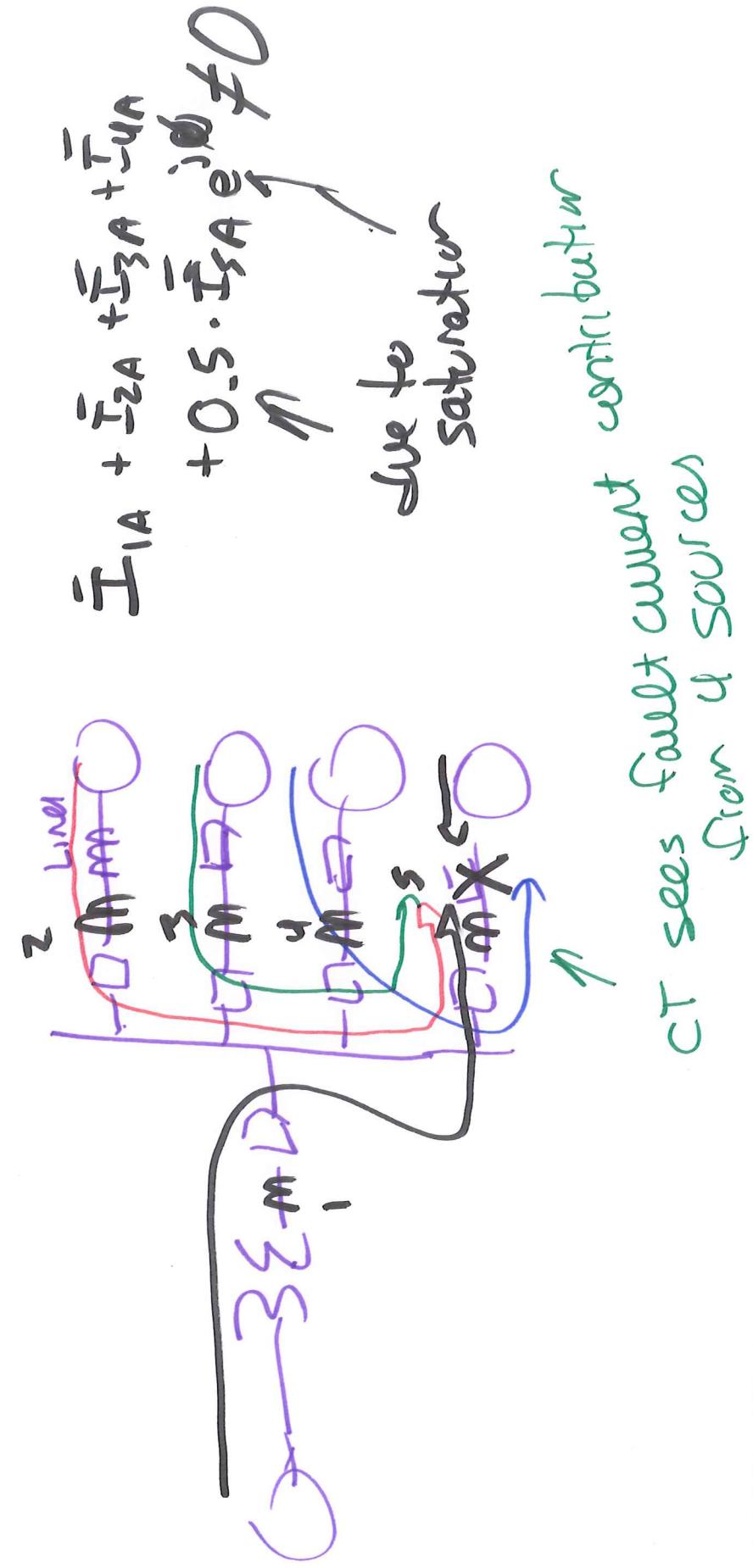- CT saturation concerns
  - Big concern is external faults



## Possible Fixes

### ① Linear CTs (no iron core)

- Linear couplers
- Optical CTs

### ② Restrained Differential Element

element restraint coil  


→ will discuss microprocessor  
implementation next

  
long range of  
measured differential  
element

(3) High impedance differential

→ you know @ the CT on  
external (winding) circuit

- once it ~~to~~ saturate  
will saturate  
- once it ~~to~~ saturate  
will saturate  
in protection scheme  
depends on what

## Low Impedance Bus Differential

$$I_{\text{topA}} = \left| \bar{I}_{1A} + \bar{I}_{2A} + \bar{I}_{3A} + \dots + \bar{I}_{nA} \right|$$


$$I_{\text{RTA}} = |I_{1A}| + |I_{2A}| + |I_{3A}| + \dots + |I_{nA}|$$

$\rightarrow$  for load or external fault (not saturation)

$I_{\text{topA}} \rightarrow \text{small}$

$I_{\text{RTA}} \rightarrow \text{large}$


Internal Fault	$I_{\text{topA}}$	long
External Fault	$I_{\text{RTA}}$	long

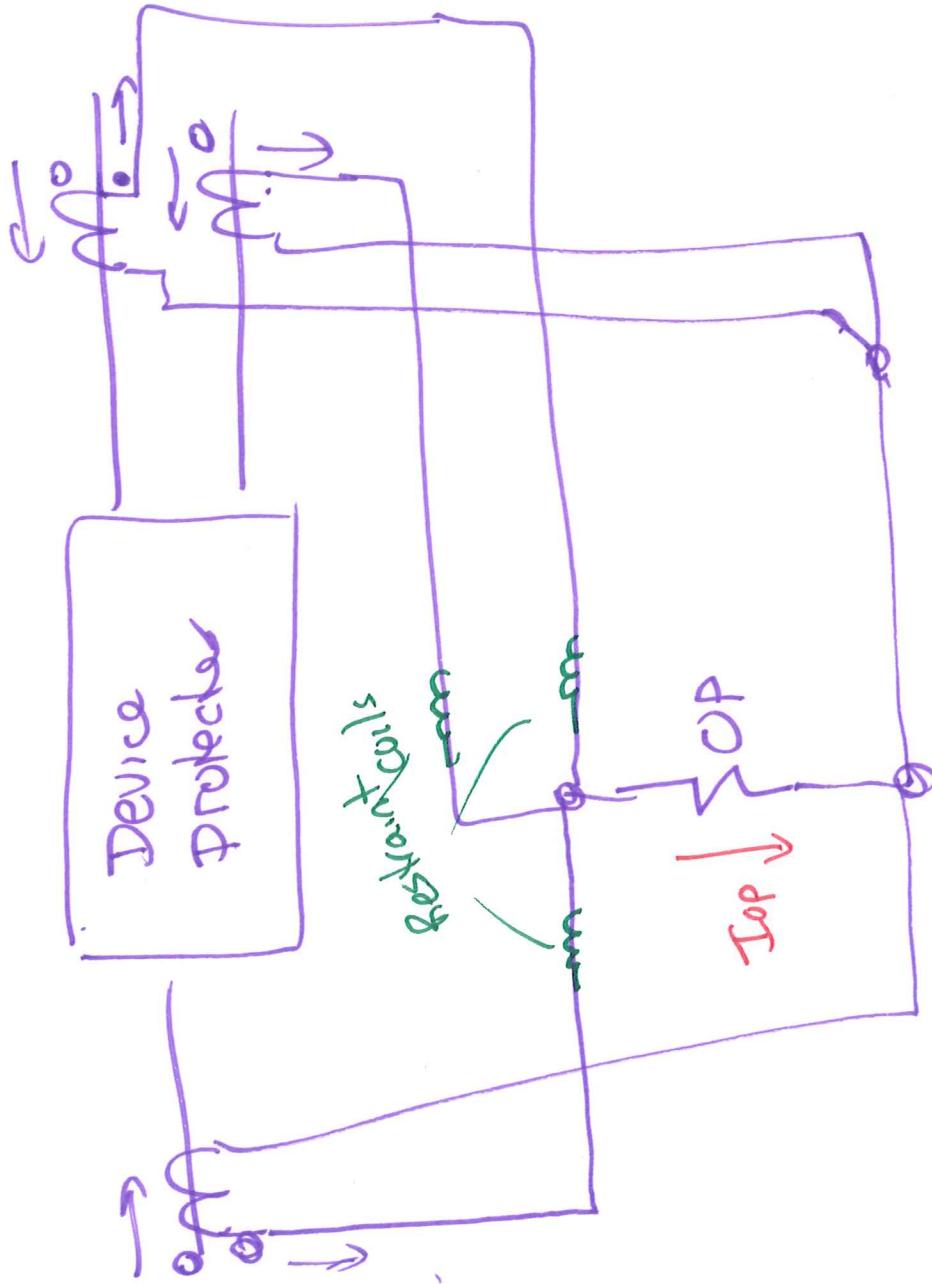

TRIP if  $\text{Top} > k \cdot T_{PT}$


$$k \cdot |I_{1A}| + k \cdot |I_{2A}| + k \cdot |I_{3A}|$$

• Internal fault

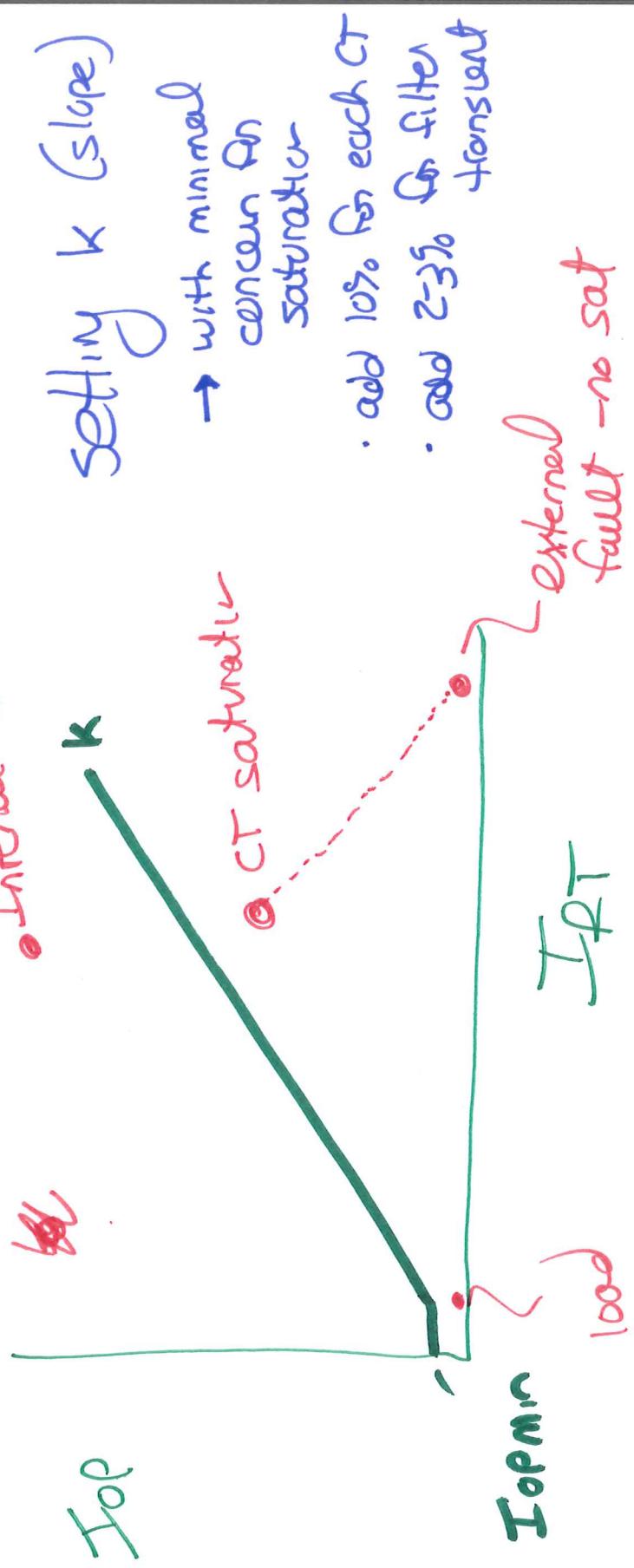

How do you handle CT saturation?


① Dual slope characteristic

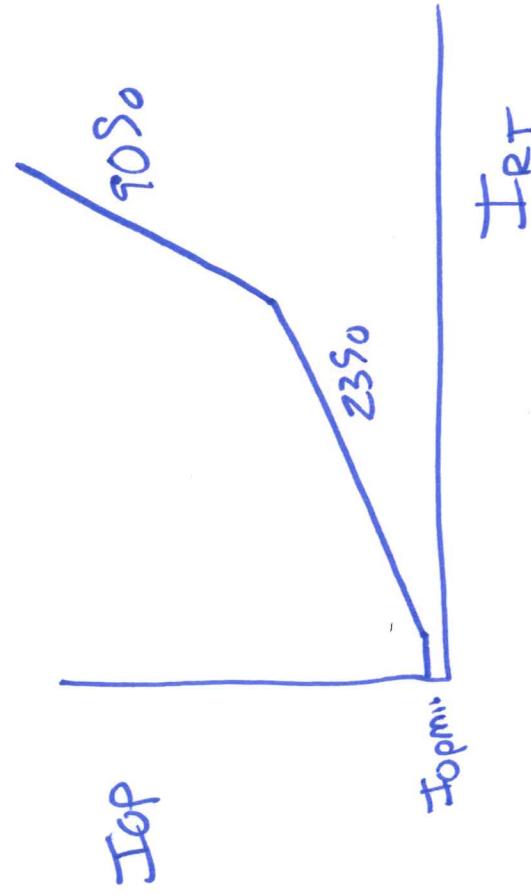

steeper slope  
for big currents  
(not great or  
DC offset)


2 saturates  
more slowly  
- other protection  
should act  
first

## ② Dynamic slope setting

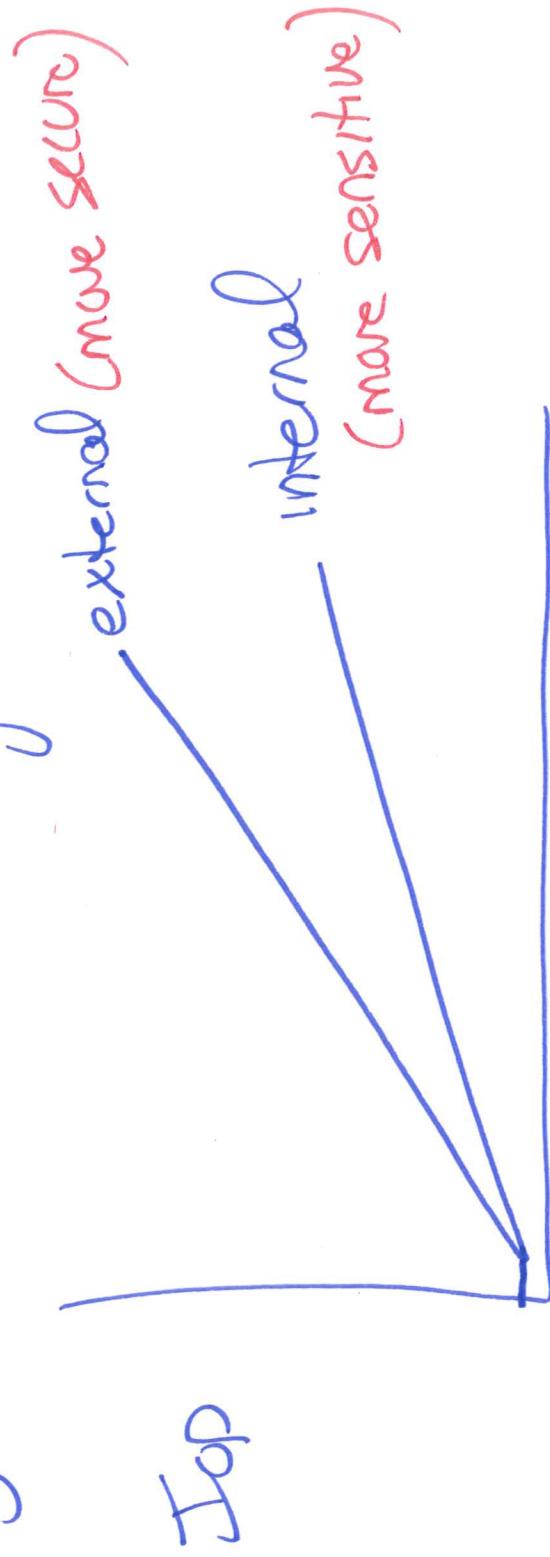

→ Make a fast determination if fault is internal or external  
- Before saturates

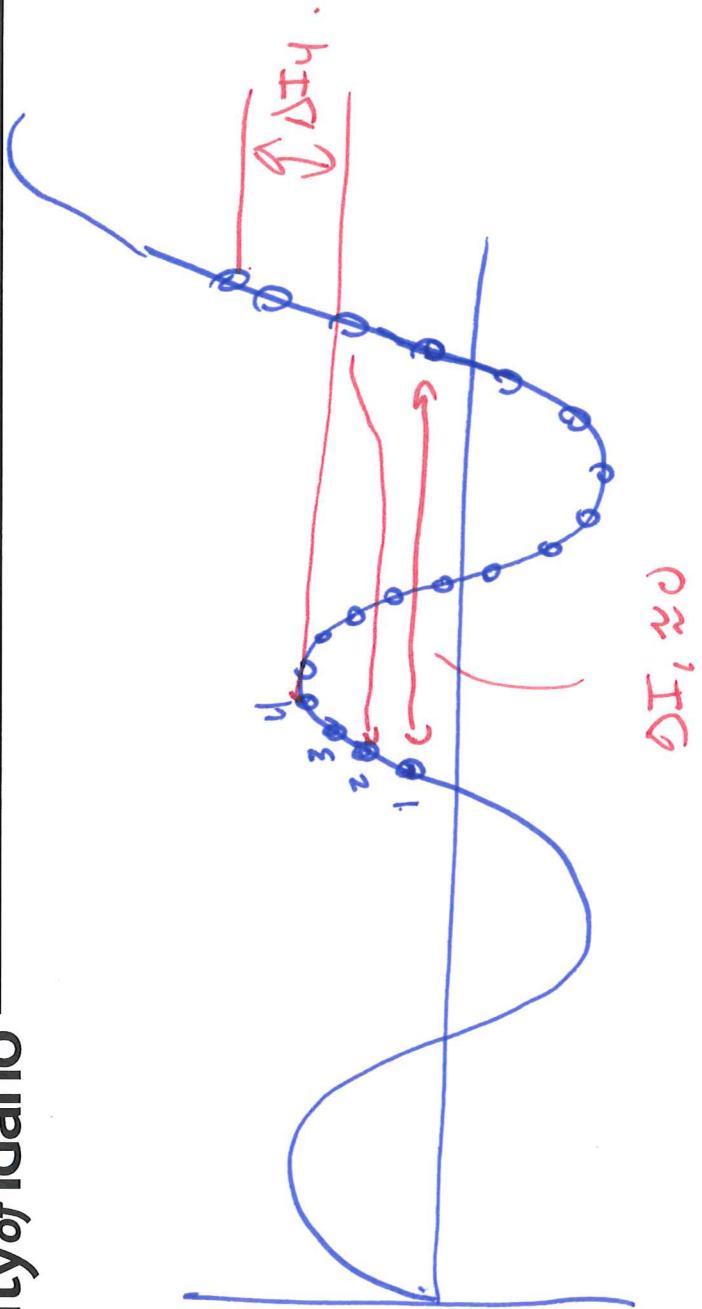- Use unfiltered quantities (raw)
- Superimposed quantities




$$\Delta I_k = I_k - I_{k-RS}$$

new cycle  
old

- Produce operate current based on these delta quantities

-  $\Delta I_{Top} >$  Threshold  
declare external

~~150 L<sup>-90</sup>~~

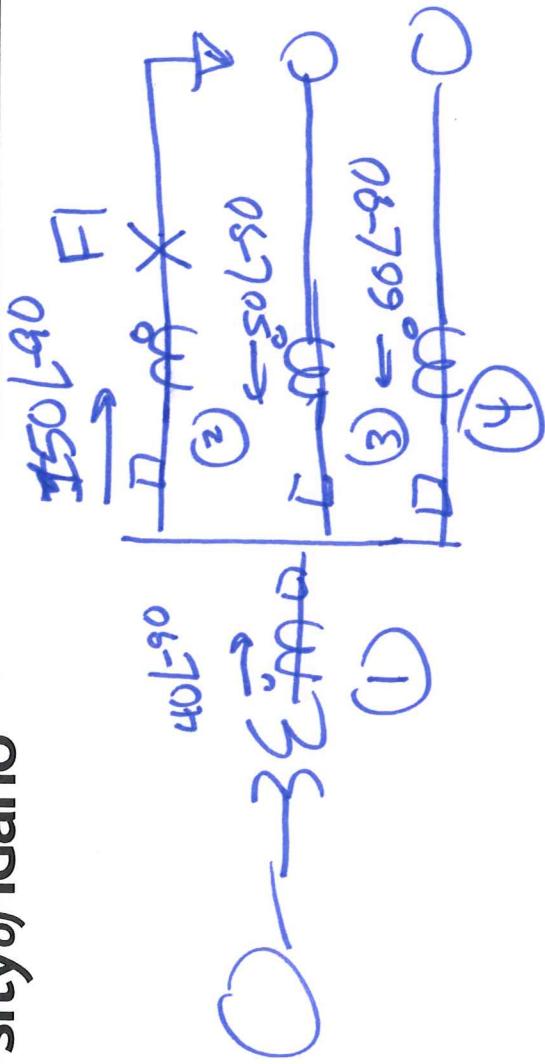

No saturation

$$\bar{I}_{op} = |\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4|$$

$$= |40 L^{-90} + 150 L^{-90} [+90^\circ + 50 L^{-90} + 60 L^{-90}]|$$

$$= 0 A$$

$$\bar{T}_{RT} = 300 A$$

Fault current causes CT to saturate  
→ relay sees  $\frac{2}{3}$  of current (no phase shift)


$$I_{op} = |40[-90^\circ] + (100[+50^\circ] + 50[-50^\circ] + 60[-90^\circ])|$$

$$= |50[-90^\circ]| = 50$$

$$I_{RT} = 250$$


$$\frac{I_{op}}{I_{RT}} = 0.2 \text{ (20\%)} \quad \checkmark$$

- would trip if  
slope  $< 20\%$

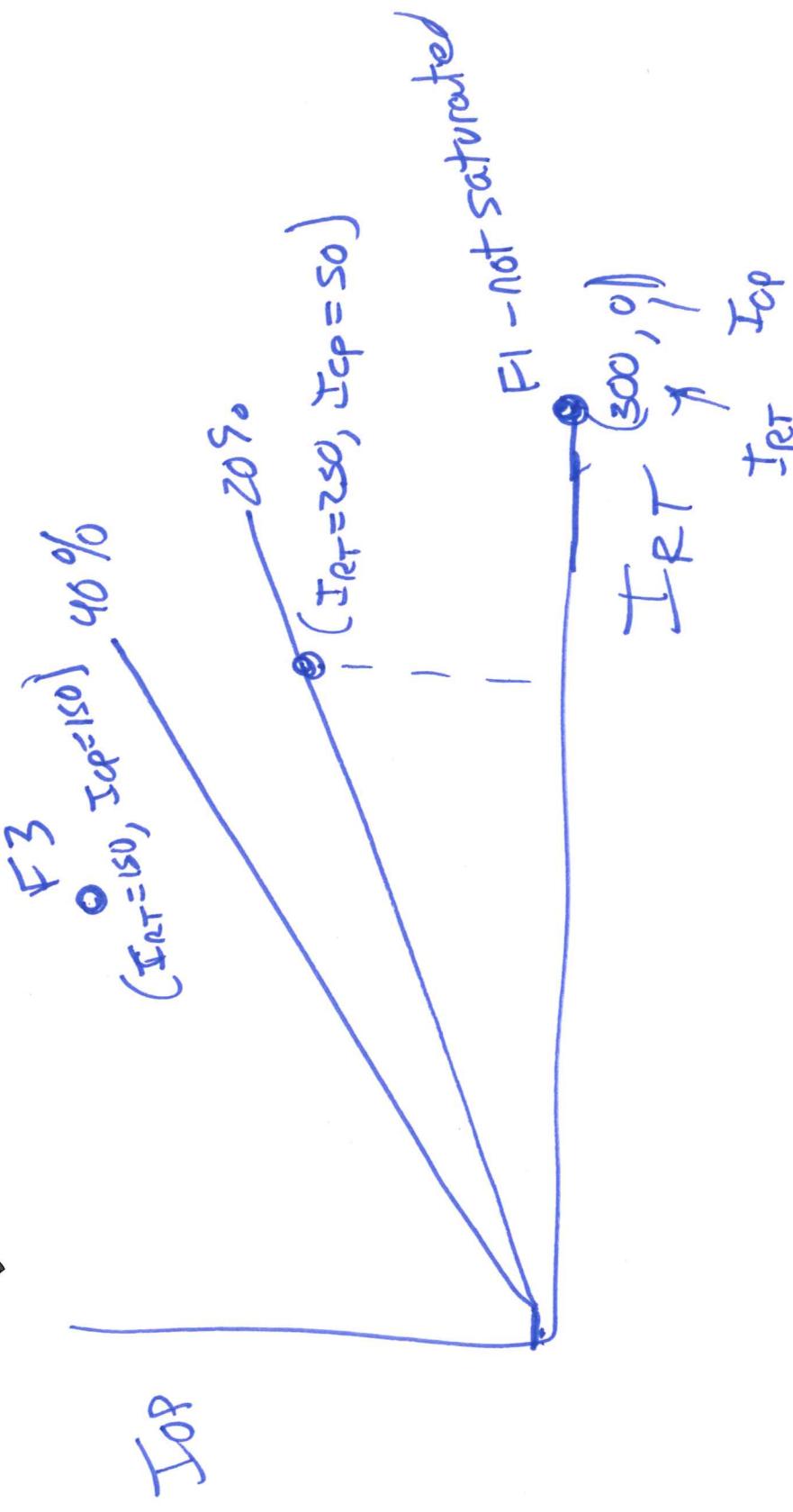

## Internal Fault

$\oplus A$

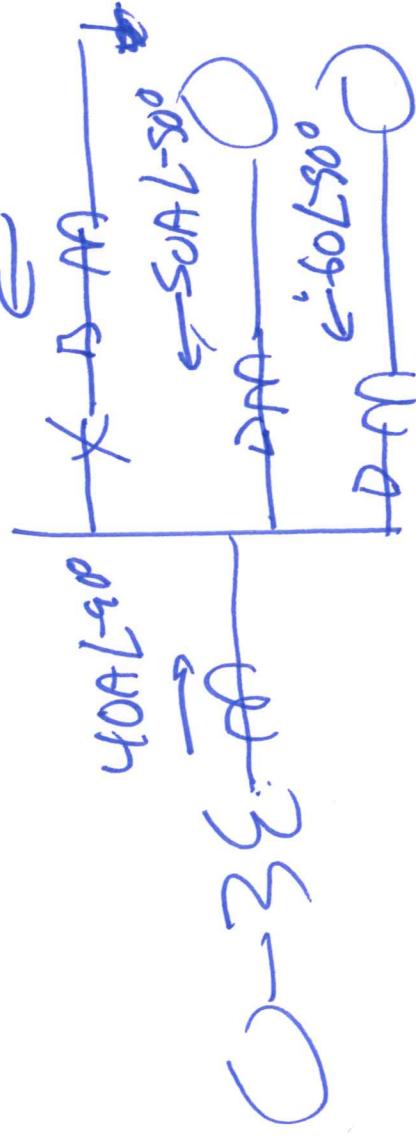

$$I_{\text{top}} = [40 \text{ L}90^\circ + 0 + \text{SCA L}90^\circ + 60 \text{ L}90^\circ]$$

$= 150A$

$I_{\text{DT}} = 150$

