

ECE 525

POWER SYSTEM PROTECTION
AND RELAYING


SESSION no. 27

Transformer Protection Example

L27 Y/13

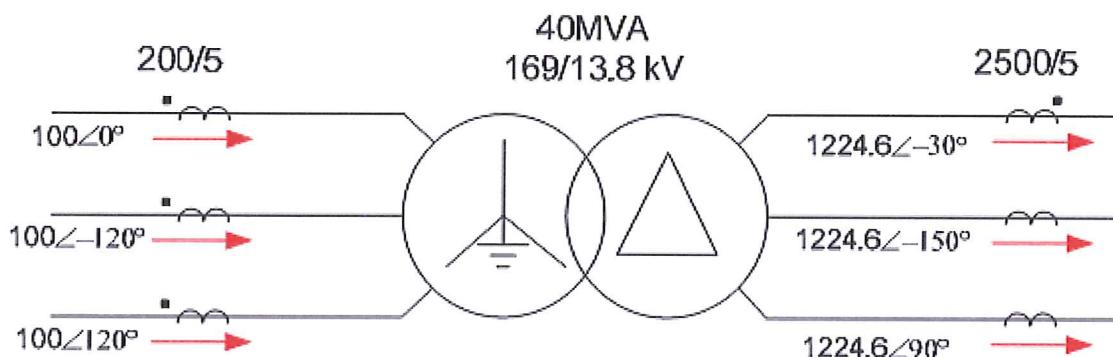- a) Consider the transformer shown. The transformer is protected by a digital current differential transformer relay. During routine maintenance a technician accidentally shorts out the C-phase CT on the HV side, determine whether the differential elements will operate and if so which “phase differential elements will operate.

Both set of CT are connected in wye (star). The matrix compensation is set so that correct phase correction is achieved. The TAP is set so that under full load conditions a one per unit “phase current” exists.



$$MVA := 1000 \text{ kW}$$

$$S_{\text{rated}} := 40 \text{ MVA}$$

$$V_{\text{HV}} := 169 \text{ kV}$$

$$V_{\text{LV}} := 13.8 \text{ kV}$$

$$\text{CTR}_{\text{HV}} := \frac{200}{5}$$

$$\text{CTR}_{\text{HV}} = 40$$

$$\text{CTR}_{\text{LV}} := \frac{2500}{5}$$

$$\text{CTR}_{\text{LV}} = 500$$

*Assumed
connected
CT*

$$\boxed{\text{Tap}_{\text{HV}} := \frac{S_{\text{rated}}}{\sqrt{3} \cdot V_{\text{HV}} \cdot \text{CTR}_{\text{HV}}}}$$

$$\text{Tap}_{\text{HV}} = 3.4163 \text{ A}$$

$$\boxed{\text{Tap}_{\text{LV}} := \frac{S_{\text{rated}}}{\sqrt{3} \cdot V_{\text{LV}} \cdot \text{CTR}_{\text{LV}}}}$$

$$\text{Tap}_{\text{LV}} = 3.347 \text{ A}$$

$$\text{MAT}_{11} := \frac{1}{\sqrt{3}} \cdot \begin{pmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{pmatrix}$$

$$\text{MAT}_0 := \begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{pmatrix}$$

$$\text{MAT}_{12} := \frac{1}{3} \begin{pmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{pmatrix}$$

$$\text{MAT}_1 := \frac{1}{\sqrt{3}} \begin{pmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{pmatrix}$$

- Primary Currents

$$I_{A_HV} := 100A \cdot e^{j \cdot 0\text{deg}}$$

$$I_{a_LV} := 1224.6A \cdot e^{-j \cdot 30\text{deg}}$$

$$I_{B_HV} := 100A \cdot e^{-j \cdot 120\text{deg}}$$

$$I_{b_LV} := 1224.6A \cdot e^{-j \cdot 150\text{deg}}$$

$$I_{C_HV} := 100A \cdot e^{j \cdot 120\text{deg}}$$

$$I_{c_LV} := 1224.6A \cdot e^{j \cdot 90\text{deg}}$$

- Uncorrected CT Secondary Currents


$$\begin{pmatrix} I_{A_{HV_sec}} \\ I_{B_{HV_sec}} \\ I_{C_{HV_sec}} \end{pmatrix} := \frac{1}{\text{CTR}_{HV}} \cdot \begin{pmatrix} I_{A_HV} \\ I_{B_HV} \\ I_{C_HV} \end{pmatrix}$$



$$\begin{pmatrix} I_{a_{LV_sec}} \\ I_{b_{LV_sec}} \\ I_{c_{LV_sec}} \end{pmatrix} := (-1) \cdot \left(\frac{1}{\text{CTR}_{LV}} \right) \cdot \begin{pmatrix} I_{a_LV} \\ I_{b_LV} \\ I_{c_LV} \end{pmatrix}$$

, correction for CT polarity

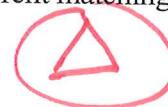- Note the (-1), the diagram doesn't have the LV side current matching the CT polarity



- Corrected currents for relay

$$\begin{pmatrix} I_{A_{HV_cor}} \\ I_{B_{HV_cor}} \\ I_{C_{HV_cor}} \end{pmatrix} := \frac{1}{\text{Tap}_{HV}} \cdot \text{MAT}_{11} \cdot \begin{pmatrix} I_{A_{HV_sec}} \\ I_{B_{HV_sec}} \\ I_{C_{HV_sec}} \end{pmatrix}$$

$$\begin{pmatrix} I_{a_{LV_cor}} \\ I_{b_{LV_cor}} \\ I_{c_{LV_cor}} \end{pmatrix} := \frac{1}{\text{Tap}_{LV}} \cdot \text{MAT}_0 \cdot \begin{pmatrix} I_{a_{LV_sec}} \\ I_{b_{LV_sec}} \\ I_{c_{LV_sec}} \end{pmatrix}$$

- Operate and Restraint Current

Phase A:

phasor sum

$$\text{IOP}_A := |I_{A_{HV_cor}} + I_{a_{LV_cor}}|$$

$$\text{IOP}_A = 2.252 \times 10^{-5}$$

sum of magnitudes

$$\text{IRTA}_A := |I_{A_{HV_cor}}| + |I_{a_{LV_cor}}|$$

$$\text{IRTA}_A = 1.464$$

Phase B:

$$IOP_B := |IB_{HV_cor} + IB_{LV_cor}|$$

$$IOP_B = 2.252 \times 10^{-5}$$

$$IRTA_B := |IB_{HV_cor}| + |IB_{LV_cor}|$$

$$IRTA_B = 1.464$$

Phase C:

$$IOP_C := |IC_{HV_cor} + IC_{LV_cor}|$$

$$IOP_C = 2.252 \times 10^{-5}$$

$$IRTA_C := |IC_{HV_cor}| + |IC_{LV_cor}|$$

$$IRTA_C = 1.464$$

- Alternate approach

$$\begin{pmatrix} IA_{HV_cor} \\ IB_{HV_cor} \\ IC_{HV_cor} \end{pmatrix} := \frac{1}{Tap_{HV}} \cdot MAT_{12} \cdot MAT_0 \cdot \begin{pmatrix} IA_{HV_sec} \\ IB_{HV_sec} \\ IC_{HV_sec} \end{pmatrix} \quad \begin{pmatrix} IA_{LV_cor} \\ IB_{LV_cor} \\ IC_{LV_cor} \end{pmatrix} := \frac{1}{Tap_{LV}} \cdot MAT_1 \cdot \begin{pmatrix} Ia_{LV_sec} \\ Ib_{LV_sec} \\ Ic_{LV_sec} \end{pmatrix}$$

zero sequence removal

- Operate and Restraint Current

Phase A:

$$IOP_A := |IA_{HV_cor} + IA_{LV_cor}|$$

$$IOP_A = 2.252 \times 10^{-5}$$

$$IRTA_A := |IA_{HV_cor}| + |IA_{LV_cor}|$$

$$IRTA_A = 1.464$$

Phase B:

$$IOP_B := |IB_{HV_cor} + IB_{LV_cor}|$$

$$IOP_B = 2.252 \times 10^{-5}$$

$$IRTA_B := |IB_{HV_cor}| + |IB_{LV_cor}|$$

$$IRTA_B = 1.464$$

Phase C:

$$IOP_C := |IC_{HV_cor} + IC_{LV_cor}|$$

$$IOP_C = 2.252 \times 10^{-5}$$

$$IRTA_C := |IC_{HV_cor}| + |IC_{LV_cor}|$$

$$IRTA_C = 1.464$$

L27 4/13
Repeat with the phase C CT shorted on the HV side:

- Uncorrected CT Secondary Currents

$$\begin{pmatrix} IA_{HV_sec} \\ IB_{HV_sec} \\ IC_{HV_sec} \end{pmatrix} := \frac{1}{CTR_{HV}} \cdot \begin{pmatrix} IA_{HV} \\ IB_{HV} \\ 0 \end{pmatrix}$$

due to shorted CT

$$\begin{pmatrix} Ia_{LV_sec} \\ Ib_{LV_sec} \\ Ic_{LV_sec} \end{pmatrix} := (-1) \cdot \left(\frac{1}{CTR_{LV}} \right) \cdot \begin{pmatrix} Ia_{LV} \\ Ib_{LV} \\ Ic_{LV} \end{pmatrix}$$

- Note the (-1), the diagram doesn't have the LV side current matching the CT polarity

- Corrected currents for relay

$$\begin{pmatrix} IA_{HV_cor} \\ IB_{HV_cor} \\ IC_{HV_cor} \end{pmatrix} := \frac{1}{Tap_{HV}} \cdot MAT_{11} \cdot \begin{pmatrix} IA_{HV_sec} \\ IB_{HV_sec} \\ IC_{HV_sec} \end{pmatrix}$$

$$\begin{pmatrix} IA_{LV_cor} \\ IB_{LV_cor} \\ IC_{LV_cor} \end{pmatrix} := \frac{1}{Tap_{LV}} \cdot MAT_0 \cdot \begin{pmatrix} Ia_{LV_sec} \\ Ib_{LV_sec} \\ Ic_{LV_sec} \end{pmatrix}$$

- Operate and Restraint Current, with shorted CT

Phase A:

$$IOP_A := |IA_{HV_cor} + IA_{LV_cor}|$$

$$\underline{IOP_A = 0.422}$$

$$IRTA_A := |IA_{HV_cor}| + |IA_{LV_cor}|$$

$$\underline{IRTA_A = 1.154}$$

Phase B:

$$IOP_B := |IB_{HV_cor} + IB_{LV_cor}|$$

$$\underline{IOP_B = 2.252 \times 10^{-5}}$$

$$IRTA_B := |IB_{HV_cor}| + |IB_{LV_cor}|$$

$$\underline{IRTA_B = 1.464}$$

Phase C:

$$IOP_C := |IC_{HV_cor} + IC_{LV_cor}|$$

$$\underline{IOP_C = 0.422}$$

$$IRTA_C := |IC_{HV_cor}| + |IC_{LV_cor}|$$

$$\underline{IRTA_C = 1.154}$$

- Due to the delta winding (and correction matrix) two of the differential elements respond.

Check the ratio of IOP to IRTA:

$$\frac{IOP_A}{IRTA_A} = 36.602\%$$

So if the relay slope is set larger than 36.602% the relay will not operate for this condition. Otherwise it will operate.

L27 5/3

- Alternate approach

$$\begin{pmatrix} IA_{HV_cor} \\ IB_{HV_cor} \\ IC_{HV_cor} \end{pmatrix} := \frac{1}{Tap_{HV}} \cdot MAT_{12} \cdot MAT_0 \cdot \begin{pmatrix} IA_{HV_sec} \\ IB_{HV_sec} \\ IC_{HV_sec} \end{pmatrix} \quad \begin{pmatrix} IA_{LV_cor} \\ IB_{LV_cor} \\ IC_{LV_cor} \end{pmatrix} := \frac{1}{Tap_{LV}} \cdot MAT_1 \cdot \begin{pmatrix} Ia_{LV_sec} \\ Ib_{LV_sec} \\ Ic_{LV_sec} \end{pmatrix}$$

- Operate and Restraint Current, with shorted CT

Phase A:

$$IOP_A := |IA_{HV_cor} + IA_{LV_cor}| \quad IRTA_A := |IA_{HV_cor}| + |IA_{LV_cor}|$$

. $IOP_A = 0.244 \quad IRTA_A = 1.377$

Phase B:

$$IOP_B := |IB_{HV_cor} + IB_{LV_cor}| \quad IRTA_B := |IB_{HV_cor}| + |IB_{LV_cor}|$$

. $IOP_B = 0.244 \quad IRTA_B = 1.377$

Phase C:

$$IOP_C := |IC_{HV_cor} + IC_{LV_cor}| \quad IRTA_C := |IC_{HV_cor}| + |IC_{LV_cor}|$$

$IOP_C = 0.488$

$\underline{IRTAC} = 0.976$

- Due to the delta winding (and correction matrix) two of the differential elements respond.


Check the ratio of IOPC to IRTC and IOPA to IRTA:

. $\frac{IOP_A}{IRTAA} = 17.712\%$

. $\frac{IOP_C}{IRTAC} = 49.999\%$

Note that the error is more significant in this case because the shorted CT was on HV side, and we are no longer scaling the current down as much.

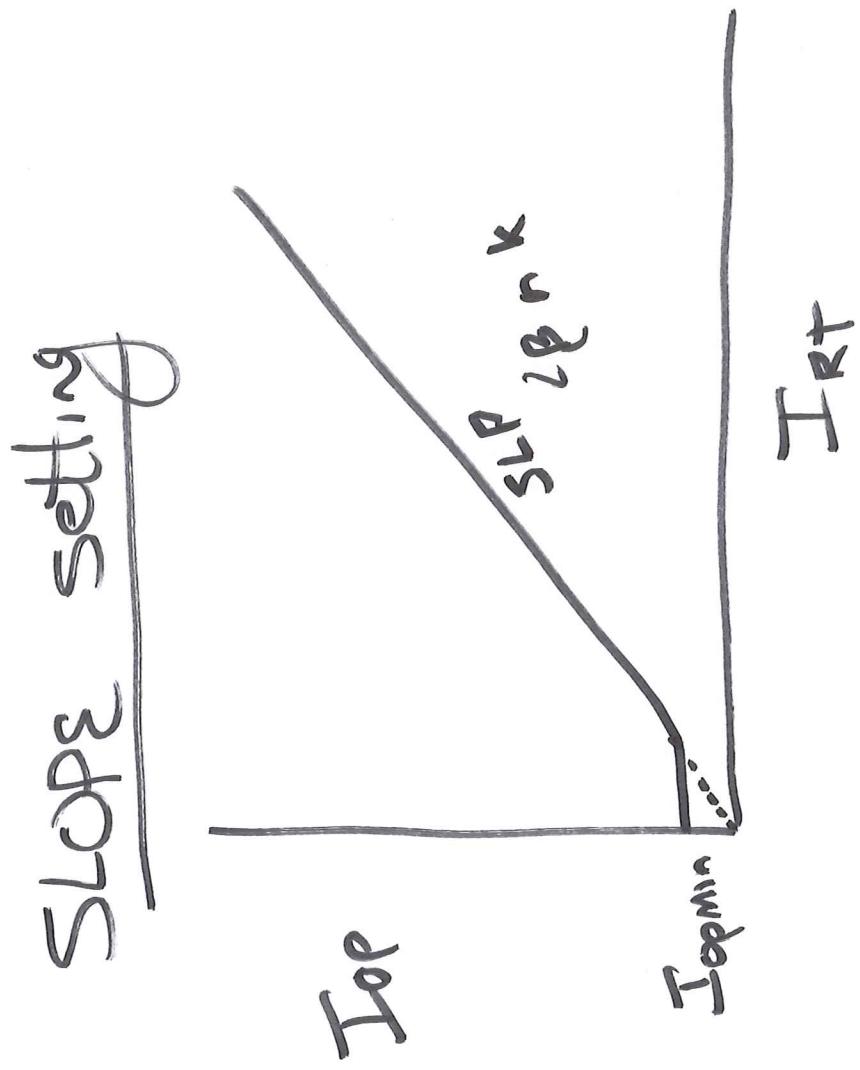So if these correction matrices are used, the relay slope need to be set larger than 50% the relay so the relay not operate for this condition. Otherwise it will operate.



$T_{RIP} = (I_{opt} > SLP \cdot I_{ext}) \text{ AND } I_{opt} > I_{optmin}$

Topmin considerations

→ C-Class CTs

- can have up to 3% error in nominal currents

→ 3% for even CT → consider 1% Base 5A or 1A


- minimum setting on relay

0.1 pu.

- Steady-state current
2-4% of rated current

→ Top min 0.2 pu - 1pu

Slope Setting

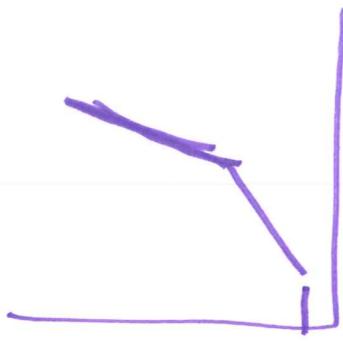

- ① CT error w/o saturation
 - (CT dual slope, the higher slope will handle saturation, IG single slope, handle it here)
- ② Add 10% for each CT input to differential element
- ③ Filter over each ~3-5% added to slope

Other considerations

- ③ Shorted CT / No current flow
CT due to single pole open. -

④ Tap Changer

- CT ratio, relay settings don't adapt

- Normalized voltage transformer Ratio

$$1 : (1 + \varepsilon)$$
$$1 : 1.05$$
$$1 : 1.025$$
$$1 : 1$$
$$1 : 0.975$$
$$1$$


Slope setting needs to be
secure for the extremes

$$\frac{1 + \varepsilon_{\max}}{1} \text{ or } \frac{1 - \varepsilon_{\max}}{1}$$

$$\left(\begin{array}{c} 0.9 \\ 1.1 \end{array} \right)$$

→ increase slope by this
go mismatch

Dual Slope --

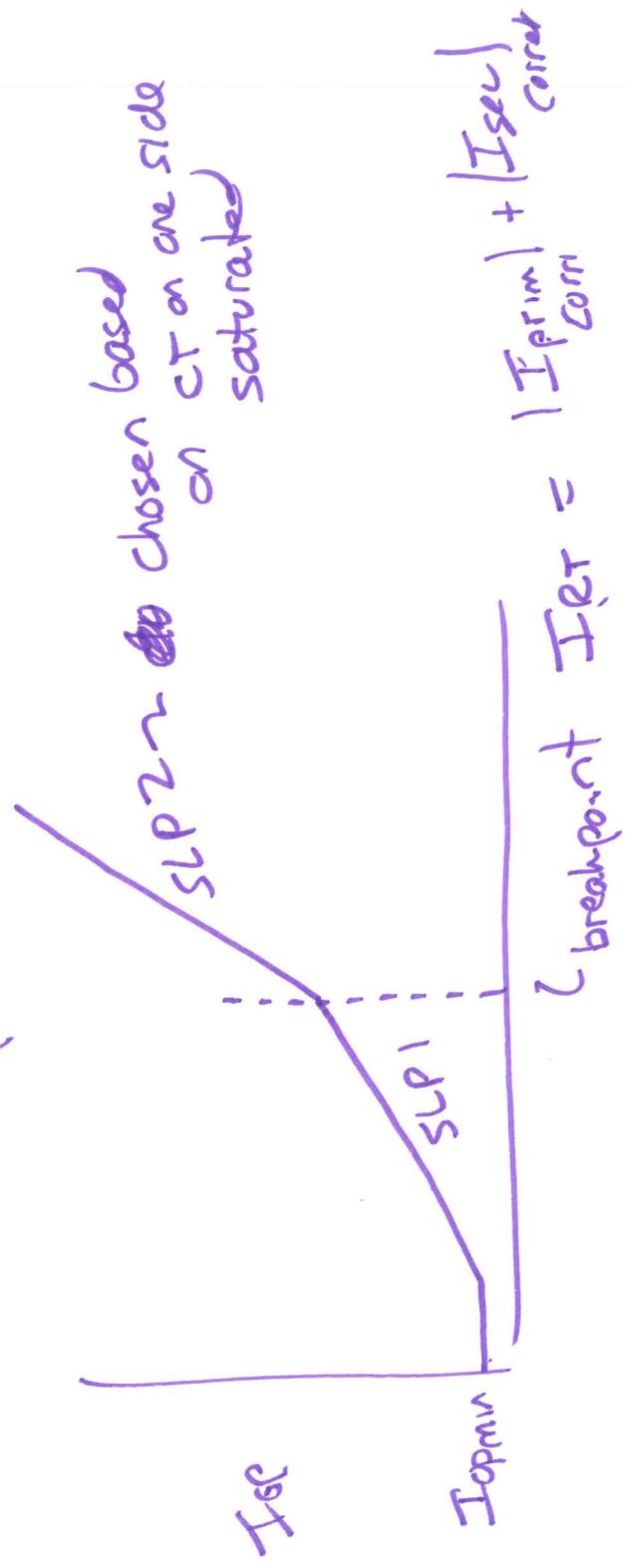

$$\text{breakpoint } I_{ZT} = |I_{\text{prim}}| + \left| I_{\text{sec}} \right|_{\text{corner}}$$

Recall formula to never saturate

$$\left(1 + \frac{X}{R} \right) \left(\frac{I_{\text{sec}}}{I_{\text{rate}}} \right) \left(\frac{Z_{\text{Burden}}}{Z_{\text{rated}}} \right) \leq 20$$


- break point is looking at I_{sec} for either CT

$$\left(1 + \frac{X}{R} \right) \left(\frac{I_{\text{sec}}}{I_{\text{rate}}} \right) \left(\frac{Z_B}{Z_{\text{rated}}} \right) \leq 50\%$$

- Other  Diode Element

Concerns for Transformers

Torus - large current possible

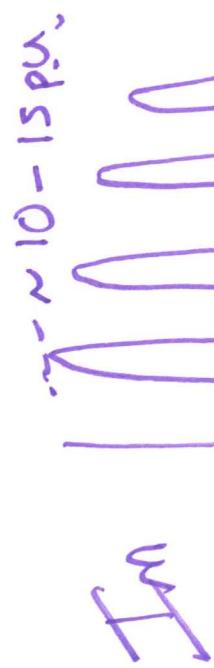

- Don't want to trip on inrush
- DC offset decaying
- Filters remove 1st harmonic terms
- Filters remove 1st harmonic terms
- Need filters to record at these frequencies
- 2nd harmonic
- Overexcitation detection

Solutions to avoid False trip on inrush

- Time delay - disable differential element while energizing
 \Rightarrow electromechanical solution
- Harmonic Blocking -
- Harmonic Restraint
- morphological Solutions - pattern matching