

## Comparing Primary and Secondary Ohms and Converting to Per Unit on Secondary When CTR and VTR Don't Cancel

- First look at a regular transformer

We know the following:

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad \text{which can be rearranged as:} \quad \frac{V_1}{V_2} = \frac{N_1}{N_2} = \text{VTR}$$

Similarly (using power transformer polarity)

$$I_1 \cdot N_1 - I_2 \cdot N_2 = 0 \quad \text{which can be rearranged as:} \quad \frac{I_1}{I_2} = \frac{N_2}{N_1} = \text{CTR}$$

- Now if we wanted to relate an impedance across the transformer

$$Z_2 = \frac{V_2}{I_2} = \frac{V_1 \cdot \left(\frac{N_2}{N_1}\right)}{I_1 \cdot \left(\frac{N_1}{N_2}\right)} = \frac{V_1}{I_1} \cdot \left(\frac{N_2}{N_1}\right)^2 = Z_1 \cdot \left(\frac{N_2}{N_1}\right)^2 \quad \text{This is how we usually view this...}$$

Alternate simplification

$$Z_2 = \frac{V_2}{I_2} = \left[ \frac{V_1 \cdot \left(\frac{N_2}{N_1}\right)}{I_1 \cdot \left(\frac{N_1}{N_2}\right)} \right] = \frac{V_1 \cdot \text{CTR}}{I_1 \cdot \text{VTR}} = Z_1 \cdot \frac{\text{CTR}}{\text{VTR}}$$

- In the case of the measurements seen at the protective relay, the voltages are stepped down through a set of voltage transformers with little current (which is not measured)
- And the currents are stepped down through a separate set of current transformers with the voltage not measured
- The measured voltage and current go into different inputs to the relay
- The relay "sees" an effective secondary impedance based on the voltages and currents stepped down by these separate VTs and CTs
- This will be more important when we look at distance relays, but it also matters for fault location calculations

### *Example*

$$Z_{\text{line\_primary}} := (5 + j \cdot 50) \text{ohm}$$

$$V_{\text{TR}} := \frac{345 \text{kV}}{120 \text{V}}$$

$$C_{\text{TR}} := \frac{800 \text{A}}{5 \text{A}}$$

- Now find the effective secondary line impedance.

$$Z_1 := Z_{\text{line\_primary}}$$

$$Z_2 := Z_1 \cdot \frac{C_{\text{TR}}}{V_{\text{TR}}} \quad Z_2 = (0.28 + 2.78i) \Omega \quad Z_{\text{line\_secondary}} := Z_2$$

If we had a three phase fault at the far end of the transmission line, then taking V/I

### *What does this do to per unit analysis?*

- Note that our conventional idea of per unit analysis is no longer accurate

$$Z_{\text{BLV}} := \frac{120 \text{V}}{\sqrt{3} \cdot 5 \text{A}} \quad Z_{\text{BLV}} = 13.86 \Omega$$

$$Z_{\text{BHV}} := \frac{345 \text{kV}}{\sqrt{3} \cdot 800 \text{A}} \quad Z_{\text{BHV}} = 248.98 \Omega$$

$$Z_{\text{pu}} := \frac{Z_{\text{line\_secondary}}}{Z_{\text{BLV}}} \quad Z_{\text{pu}} = 0.02 + 0.2i$$

$$Z_{\text{pu}} \cdot Z_{\text{BHV}} = (5 + 50i) \Omega$$

MVA := 1000kW

***Incorrect way:***

$$S_b := 100\text{MVA} \quad Z_{bLV} := \frac{(120\text{V})^2}{S_b} \quad Z_{bLV} = 1.44 \times 10^{-4} \Omega$$

$$Z_{bHV} := \frac{(345\text{kV})^2}{S_b} \quad Z_{bHV} = 1190.25 \Omega$$

$$Z_{\text{line\_secondary}} \cdot \frac{Z_{bHV}}{Z_{bLV}} = (2.3 \times 10^6 + 2.3i \times 10^7) \Omega$$

They are in secondary ohms. Because we have two different transformer ratios (that are determined independently based on primary voltage and current), the normal practice of finding impedance bases from a MVA base and a voltage base is not accurate.