

ECE 525


POWER SYSTEM PROTECTION  
AND RELAYING

SESSION no. 7

## ECE 525: Homework #1

### Solutions

1. Given the power system below:

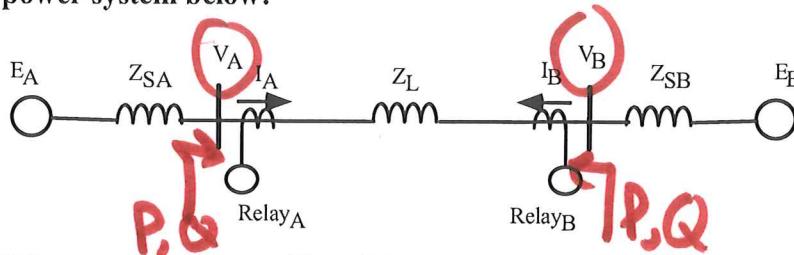

Where the following are given as CT and VT secondary quantities::

- $E_{SA} := 70V \cdot e^{j \cdot 0\text{deg}}$        $E_{SB} := 70V \cdot e^{-j \cdot 30\text{deg}}$
- $Z_{SA1} := 1.5\text{ohm} \cdot e^{j \cdot 87\text{deg}}$        $Z_{SA2} := Z_{SA1}$        $Z_{SA0} := 5\text{ohm} \cdot e^{j \cdot 87\text{deg}}$
- $Z_{SB1} := 0.8\text{ohm} \cdot e^{j \cdot 83\text{deg}}$        $Z_{SB2} := Z_{SB1}$        $Z_{SB0} := 2.5\text{ohm} \cdot e^{j \cdot 83\text{deg}}$

$$Z_{L1} := 5\text{ohm} \cdot e^{j \cdot 82\text{deg}} \quad Z_{L0} := 18\text{ohm} \cdot e^{j \cdot 82\text{deg}} \quad Z_{L2} := Z_{L1}$$

The current transformer ratios are:  $CTR := \frac{1200}{5}$

The voltage transformer ratios are:  $VTR := \frac{132.8\text{kV}}{70\text{V}}$  Line-to-neutral

A. Calculate the source voltages, line and source impedances and line current referred to primary values based on the information given above. Also find the line currents in secondary Amps accounting for CT polarity.

$$Z_{SA1\_prim} := \frac{VTR}{CTR} \cdot Z_{SA1} \quad |Z_{SA1\_prim}| = 11.86 \Omega \quad \arg(Z_{SA1\_prim}) = 87\text{-deg}$$

$$Z_{SA2\_prim} := \frac{VTR}{CTR} \cdot Z_{SA2} \quad |Z_{SA2\_prim}| = 11.86 \Omega \quad \arg(Z_{SA2\_prim}) = 87\text{-deg}$$

$$Z_{SA0\_prim} := \frac{VTR}{CTR} \cdot Z_{SA0} \quad |Z_{SA0\_prim}| = 39.52 \Omega \quad \arg(Z_{SA0\_prim}) = 87\text{-deg}$$

$$Z_{SB1\_prim} := \frac{VTR}{CTR} \cdot Z_{SB1} \quad |Z_{SB1\_prim}| = 6.32 \Omega \quad \arg(Z_{SB1\_prim}) = 83\text{-deg}$$

$$Z_{SB2\_prim} := \frac{VTR}{CTR} \cdot Z_{SB2} \quad |Z_{SB2\_prim}| = 6.32 \Omega \quad \arg(Z_{SB2\_prim}) = 83\text{-deg}$$

$$Z_{SB0\_prim} := \frac{VTR}{CTR} \cdot Z_{SB0} \quad |Z_{SB0\_prim}| = 19.76 \Omega \quad \arg(Z_{SB0\_prim}) = 83\text{-deg}$$

D. For the conditions of part A, calculate the effective impedance measured by Relay A and Relay B in terms of secondary values.

- Line to ground element:

- Assume balanced three phase:  $I_{0\_RA} := 0A$        $I_{0\_RB} := 0A$

$$k_0 := \frac{Z_{L0} - Z_{L1}}{Z_{L0}} \quad k_0 = 0.72$$

$$V_{AG\_sec\_relayA} := \frac{V_A\_BUSA\_LG}{VTR} \quad |V_{AG\_sec\_relayA}| = 68.95 V$$

$$\arg(V_{AG\_sec\_relayA}) = -6.09 \cdot \text{deg}$$

$$Z_{AG\_eff\_RelayA} := \frac{V_{AG\_sec\_relayA}}{I_{RelayA\_sec} + k_0 \cdot I_{0\_RA}}$$

$$|Z_{AG\_eff\_RelayA}| = 13.88 \Omega$$

$$\arg(Z_{AG\_eff\_RelayA}) = 2.05 \cdot \text{deg}$$

O<sub>2</sub> balanced

- Phase to phase element

$$I_{RelayA\_sec\_phaseB} := I_{RelayA\_sec} e^{-j \cdot 120\text{deg}}$$

$$V_{AG\_sec\_relayA\_phaseB} := V_{AG\_sec\_relayA} e^{-j \cdot 120\text{deg}}$$

$$Z_{AB\_relayA} := \frac{V_{AG\_sec\_relayA} - V_{AG\_sec\_relayA\_phaseB}}{I_{RelayA\_sec} - I_{RelayA\_sec\_phaseB}}$$

$$|Z_{AB\_relayA}| = 13.88 \Omega$$

$$\arg(Z_{AB\_relayA}) = 2.05 \cdot \text{deg}$$

Compare to line impedance  $|Z_L| = 5 \Omega$        $\arg(Z_L) = 82 \cdot \text{deg}$

- Line to ground element at relay B

$$V_{AG\_sec\_relayB} := \frac{V_A\_BUSB\_LG}{VTR} \quad |V_{AG\_sec\_relayB}| = 69.09 V$$

$$\arg(V_{AG\_sec\_relayB}) = -26.81 \cdot \text{deg}$$

$$Z_{AG\_eff\_RelayB} := \frac{V_{AG\_sec\_relayB}}{I_{RelayB\_sec} + k_0 \cdot I_{0\_RB}}$$

$$|Z_{AG\_eff\_RelayB}| = 13.91 \Omega$$

$$\arg(Z_{AG\_eff\_RelayB}) = 161.32 \cdot \text{deg}$$

$$I_{\text{RelayB\_sec\_phaseB}} := I_{\text{RelayB\_sec}} e^{-j \cdot 120\text{deg}}$$

$$V_{\text{AG\_sec\_relayB\_phaseB}} := V_{\text{AG\_sec\_relayB}} e^{-j \cdot 120\text{deg}}$$

L7 3/9

- Line to line element at Relay B

$$Z_{\text{AB\_relayB}} := \frac{V_{\text{AG\_sec\_relayB}} - V_{\text{AG\_sec\_relayB\_phaseB}}}{I_{\text{RelayB\_sec}} - I_{\text{RelayB\_sec\_phaseB}}}$$

$$|Z_{\text{AB\_relayB}}| = 13.91 \Omega$$

$$\arg(Z_{\text{AB\_relayB}}) = 161.32 \cdot \text{deg}$$

2. AB -

- Not required for assignment, but to help visualize this result, let's plot these in the impedance plane
- First draw a mho characteristic, and reason the problem out a bit. I'm using Zone 1, set to 80% of the line
- $k := 0, 1..719$      • 770 steps

$$\text{rad}_{\text{Mhozone1}} := 0.8 \cdot \frac{|Z_{L1}|}{2}$$

$$\text{offset}_{\text{Mhozone1}} := 0.8 \cdot \frac{Z_{L1}}{2}$$

- Create vector:


$$\text{LineZ} := \begin{pmatrix} 0 \\ Z_{L1} \end{pmatrix}$$

$$\text{Zone1}_k := \text{offset}_{\text{Mhozone1}} + \text{rad}_{\text{Mhozone1}} \cdot e^{j \cdot k \cdot 0.5\text{deg}}$$

center

phaser

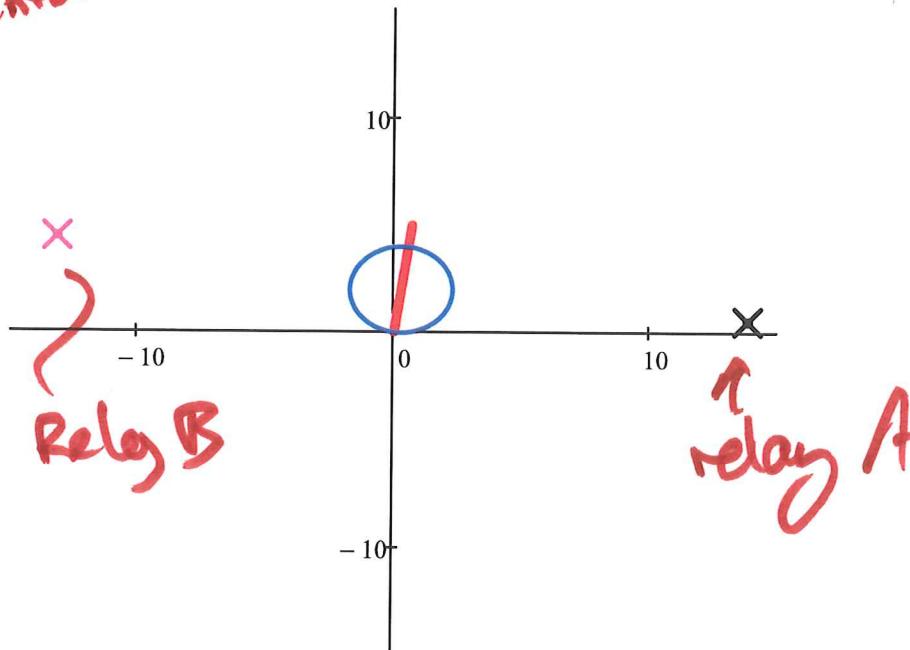- $\text{Im}(\text{LineZ})$
- $\text{Im}(\text{Zone1}_k)$
- $\text{Im}(Z_{\text{AG\_eff\_RelayA}})$
- $\text{Im}(Z_{\text{AG\_eff\_RelayB}})$



$$\text{Re}(\text{LineZ}), \text{Re}(\text{Zone1}_k), \text{Re}(Z_{\text{AG\_eff\_RelayA}}), \text{Re}(Z_{\text{AG\_eff\_RelayB}})$$

E. Suppose a 3 phase fault occurs 30% of the way from Bus A to Bus B, do the following:

- (1) Calculate the total fault current and the current seen at Relay A and Relay B in primary and secondary quantities.

$$Z_{\text{left}1} := Z_{SA1} + 0.3 \cdot Z_{L1}$$

$$Z_{\text{right}1} := (1 - 0.3) \cdot Z_{L1} + Z_{SB1}$$

$$Z_{\text{thev}1} := \left( \frac{1}{Z_{\text{left}1}} + \frac{1}{Z_{\text{right}1}} \right)^{-1} \quad Z_{\text{thev}1} = (0.2 + 1.76i) \Omega$$

$$\underline{Z_{\text{left}1}/Z_{\text{right}1}}$$

- Since we are assuming no load flow, the prefault voltage is the same everywhere in the system. Therefore:

- Total fault current

$$V_{\text{fault}} := E_{SA}$$

- Secondary Amps

$$I_{f\_3ph\_sec} := \frac{V_{\text{fault}}}{Z_{\text{thev}1}} \quad |I_{f\_3ph\_sec}| = 39.63 \text{ A} \quad \arg(I_{f\_3ph\_sec}) = -83.55 \cdot \text{deg}$$

- Primary Amps

$$I_{f\_3ph\_prim} := I_{f\_3ph\_sec} \cdot \text{CTR} \quad |I_{f\_3ph\_prim}| = 9510.52 \text{ A}$$

$$\arg(I_{f\_3ph\_prim}) = -83.55 \cdot \text{deg}$$

- Fault current at Relay A
  - Secondary Amps first:
    - Use current divider

$$I_{f\_RelayA\_3ph\_sec} := I_{f\_3ph\_sec} \cdot \frac{Z_{\text{right}1}}{Z_{\text{left}1} + Z_{\text{right}1}}$$



$$|I_{f\_RelayA\_3ph\_sec}| = 23.36 \text{ A}$$

$$\arg(I_{f\_RelayA\_3ph\_sec}) = -84.5 \cdot \text{deg}$$

$$I_{f\_RelayA\_3ph\_prim} := I_{f\_RelayA\_3ph\_sec} \cdot \text{CTR}$$

$$|I_{f\_RelayA\_3ph\_prim}| = 5605.34 \text{ A}$$
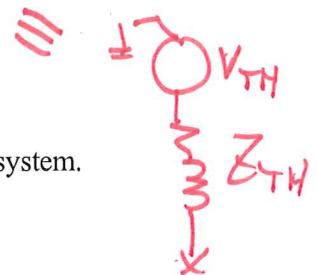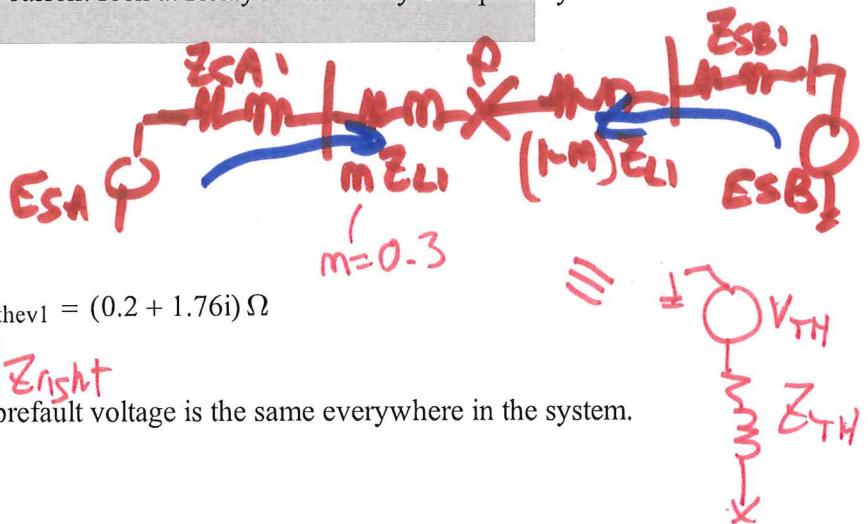
$$\arg(I_{f\_RelayA\_3ph\_prim}) = -84.5 \cdot \text{deg}$$



$$|V_{fA\_BUSA\_3ph}| = 66.46 \text{ kV} \quad \arg(V_{fA\_BUSA\_3ph}) = -2.5 \cdot \text{deg}$$

$$V_{fA\_BUSB\_3ph} := E_{SA\_prim} - I_{f\_RelayB\_3ph\_prim} \cdot Z_{SB1\_prim}$$

$$|V_{fA\_BUSB\_3ph}| = 108.1 \text{ kV} \quad \arg(V_{fA\_BUSB\_3ph}) = -0.19 \cdot \text{deg}$$

- Note that I used the same source voltage for each since I'm ignoring load flow
- Line to ground element at Relay A:

$$\bullet \text{ Assume balanced three phase fault: } I_{0\_RA} := 0A \quad I_{0\_RB} := 0A$$

$$V_{f\_AG\_3ph\_sec\_relayA} := \frac{V_{fA\_BUSA\_3ph}}{VTR} \quad |V_{f\_AG\_3ph\_sec\_relayA}| = 35.03 \text{ V}$$

$$\arg(V_{f\_AG\_3ph\_sec\_relayA}) = -2.5 \cdot \text{deg}$$

$$Z_{f\_3ph\_AG\_eff\_RelayA} := \frac{V_{f\_AG\_3ph\_sec\_relayA}}{I_{f\_RelayA\_3ph\_sec} + k_0 \cdot I_{0\_RA}}$$

$|Z_{f\_3ph\_AG\_eff\_RelayA}| = 1.5 \Omega$

$\arg(Z_{f\_3ph\_AG\_eff\_RelayA}) = 82 \cdot \text{deg}$

- Phase to phase element at Relay A

$$I_{f\_RelayA\_3ph\_sec\_ph\_B} := I_{f\_RelayA\_3ph\_sec} \cdot e^{-j \cdot 120\text{deg}}$$

$$V_{f\_AG\_3ph\_sec\_relayA\_phB} := V_{f\_AG\_3ph\_sec\_relayA} \cdot e^{-j \cdot 120\text{deg}}$$

$$Z_{f\_3ph\_AB\_relayA} := \frac{V_{f\_AG\_3ph\_sec\_relayA} - V_{f\_AG\_3ph\_sec\_relayA\_phB}}{I_{f\_RelayA\_3ph\_sec} - I_{f\_RelayA\_3ph\_sec\_ph\_B}}$$


$|Z_{f\_3ph\_AB\_relayA}| = 1.5 \Omega$

$\arg(Z_{f\_3ph\_AB\_relayA}) = 82 \cdot \text{deg}$

$$\text{Compare to line impedance} \quad 0.3 |Z_{L1}| = 1.5 \Omega \quad \arg(0.3 \cdot Z_{L1}) = 82 \cdot \text{deg}$$

So consistent results

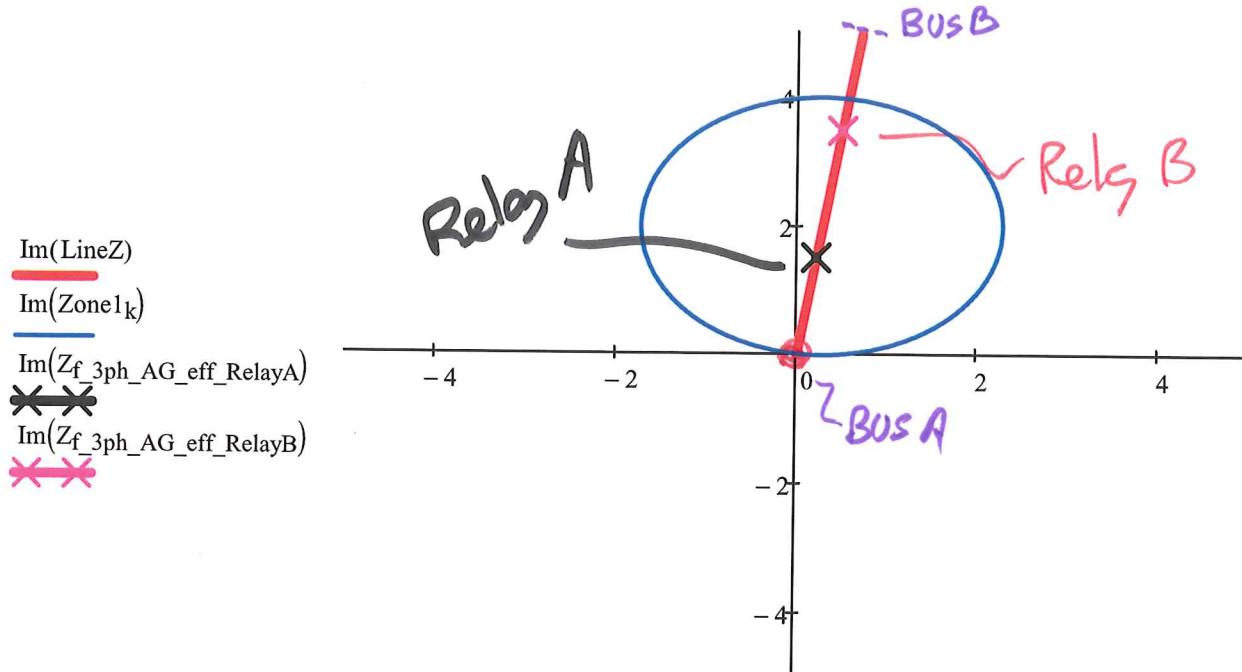
- Not required for assignment, but to help visualize this result, let's plot these in the impedance plane. Compare this figure to the one above with the load currents. Note also the change in scale



$$\text{Re}(\text{LineZ}), \text{Re}(\text{Zone1}_k), \text{Re}(\text{Z}_f\text{-3ph\_AG_eff_RelayA}), \text{Re}(\text{Z}_f\text{-3ph\_AG_eff_RelayB})$$

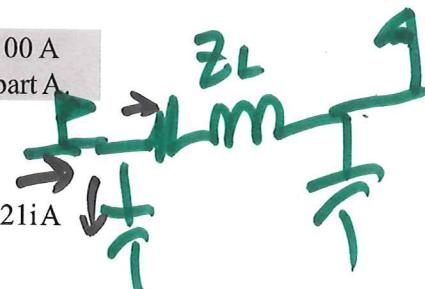(4) What  $I_{op}$  and  $I_{rt}$  be for a differential element (assume a charging current of 100 A capacitive divided equally between each end), for the fault and load flow of part A.

$$I_{cap\_secondary\_busA} := \frac{\frac{100}{2} \text{A} \cdot e^{j \cdot 90\text{deg}}}{\text{CTR}}$$



$$I_{cap\_secondary\_busA} = 0.21i\text{A}$$

$$I_{cap\_secondary\_busB} := \frac{\frac{100}{2} \text{A} \cdot e^{j \cdot 90\text{deg}}}{\text{CTR}}$$

$$I_{cap\_secondary\_busB} = 0.21i\text{A}$$

- Load flow case (only do for 1 phase since same for all three)

$$I_{OP\_loadflow} := \left| I_{RelayA\_sec} + I_{RelayB\_sec} + I_{cap\_secondary\_busA} + I_{cap\_secondary\_busB} \right|$$

$I_{OP\_loadflow} = 0.42 \text{ A}$

$\sum = 0$

$$C_{800} = 8 \cdot 20 = 160$$

Standard Twidler - (ed 8n C800)

(5A)

$20 \times$  nominal current

$I_{ther} < 10\%$

$\Rightarrow$  C-class

$\rightarrow$  Significant

at C-class CT

Guaranteed "not to saturate"  $\rightarrow z_B/z_{\text{standard}}$

$$I_f \left( 1 + \frac{R}{r} \right) \left( I_{T \text{ nominal}} \left( z_B \text{ standard} \right) \right) < 20$$

---

ECE 525  
Power Systems Protection and Relying

Power Systems Protection and Relying

Normalized

CT doesn't saturate

1

5

$$\rightarrow \left( 1 + \frac{X}{\lambda} \right) \cdot \frac{1}{1 - \frac{X}{\lambda}}$$

VRAT rated N

6.24.0

Simulation Time and Indexing

$\Delta t := .00001 \quad i := 1 .. \text{cell}$

1 sec

## I<sub>gate</sub> Primary Current Definition

$$\theta := \text{atan} \left( \frac{X}{R} \right) \quad \tau := \frac{X}{(r^2 + R^2)^{1/2}}$$

$$\theta = 86.987^\circ$$

$$I_i := \sqrt{2} \cdot I_{\text{mag}} \cdot \begin{pmatrix} -t_i \\ \sin(\omega \cdot t_i + \phi - \theta) - e^{\tau} \cdot \sin(\phi - \theta) \end{pmatrix}$$

卷之二

Magnetic Values

$$B_+ := 1.8$$

卷之三

$$\Delta = 4.912 \times 10^{-3}$$

Mean core length

L<sub>i</sub> := .75

