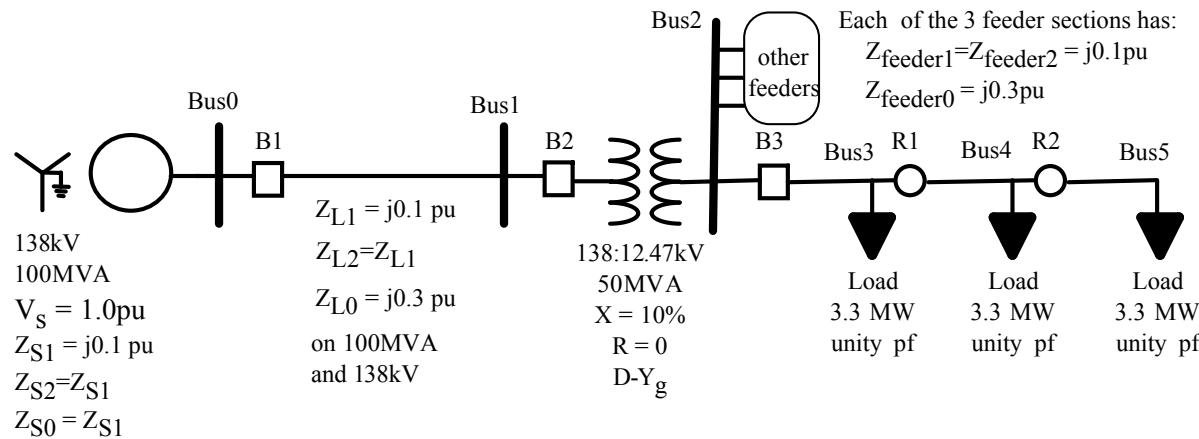


## ECE 525: Homework #4

### Fault Current Calculations

Calculate the fault currents for three-phase, phase-to-phase and single-phase-to-ground faults at the following locations: at the distribution station 138 kV bus, distribution station 12.47 kV bus, and the end of each of the three sections of the feeder.



- Define units and constants

$$\text{pu} := 1 \quad \text{MVA} := 1000\text{kW} \quad \text{MW} := \text{MVA}$$

$$a := e^{j \cdot 120\text{deg}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

- Define system bases

$$S_B := 100\text{MVA} \quad V_{BH} := 138\text{kV} \quad V_{BL} := V_{BH} \cdot \left( \frac{12.47\text{kV}}{138\text{kV}} \right) \quad V_{BL} = 12.47\text{kV}$$

$$I_{BH} := \frac{S_B}{\sqrt{3} \cdot V_{BH}} \quad I_{BH} = 418.37\text{A}$$

$$I_{BL} := \frac{S_B}{\sqrt{3} \cdot V_{BL}} \quad I_{BL} = 4629.91\text{A}$$

- Per unit impedances

- Source
- Line
- Feeder sections (per section)

$$Z_{S1} := j \cdot 0.1\text{pu} \quad Z_{L1} := j \cdot 0.1\text{pu} \quad Z_{feeder1} := j \cdot 0.1\text{pu}$$

$$Z_{S0} := j \cdot 0.1\text{pu} \quad Z_{L0} := j \cdot 0.3\text{pu} \quad Z_{feeder0} := j \cdot 0.3\text{pu}$$

- Transformer


$$S_{rated} := 50\text{MVA} \quad V_{HV} := 138\text{kV} \quad V_{LV} := 12.47\text{kV} \quad Z_r := j \cdot 10\%$$

- change of base calculation


$$Z_{T1} := Z_r \cdot \left( \frac{V_{HV}}{V_{BH}} \right)^2 \cdot \left( \frac{S_B}{S_{rated}} \right) \quad Z_{T1} = 0.2j\text{pu} \quad Z_{T0} := Z_{T1}$$

### Sequence Equivalent Circuits


- Positive sequence equivalent circuit:

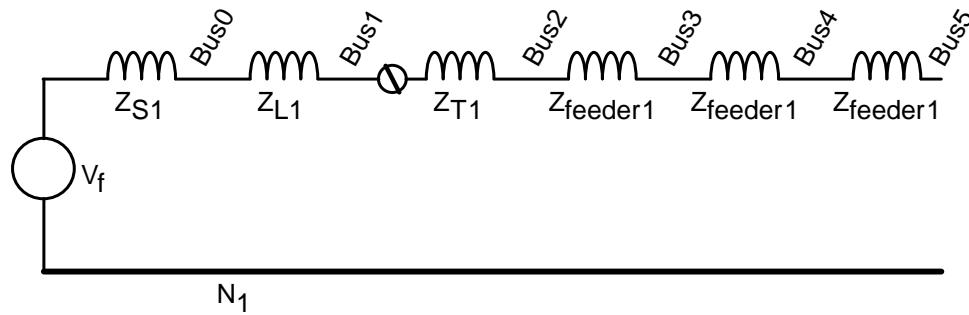

- Negative sequence equivalent circuit:

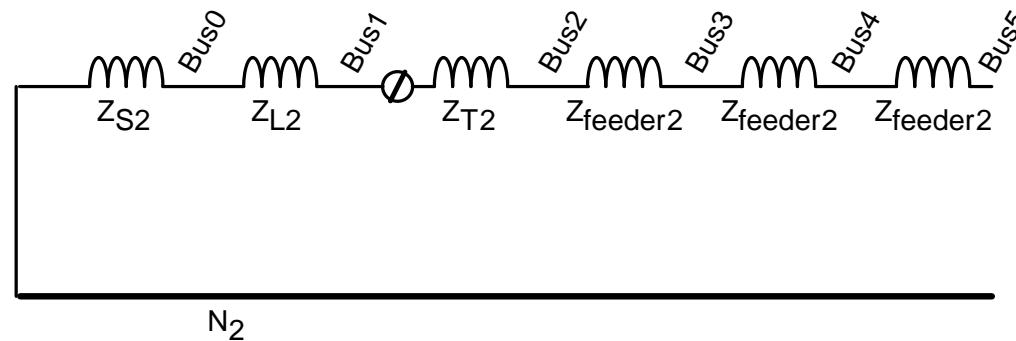

- Zero sequence equivalent circuit:

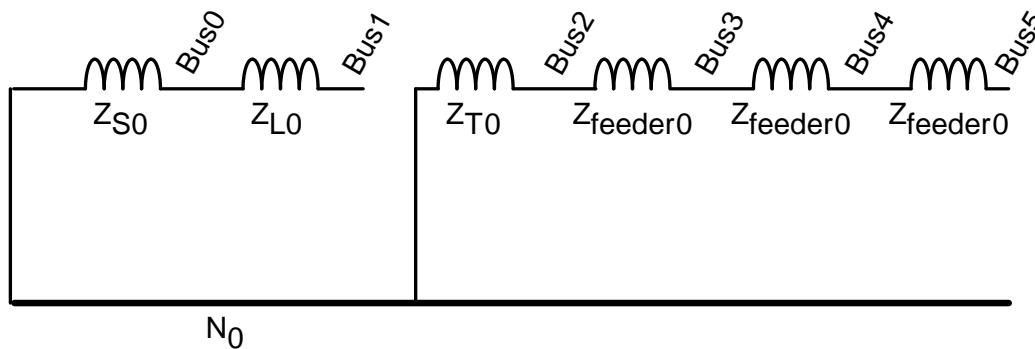

### Fault current calculations

- First form Ybus and then Zbus for each sequence. First the positive sequence

$$Y_1 := \begin{pmatrix} \frac{1}{Z_{S1}} + \frac{1}{Z_{L1}} & \frac{-1}{Z_{L1}} & 0 & 0 & 0 & 0 \\ \frac{-1}{Z_{L1}} & \frac{1}{Z_{L1}} + \frac{1}{Z_{T1}} & \frac{-1 \cdot e^{j \cdot 30\text{deg}}}{Z_{T1}} & 0 & 0 & 0 \\ 0 & \frac{-1 \cdot e^{-j \cdot 30\text{deg}}}{Z_{T1}} & \frac{1}{Z_{T1}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 & 0 \\ 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 \\ 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} \\ 0 & 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} \end{pmatrix}$$

$$Y_1 = \begin{pmatrix} -20i & 10i & 0 & 0 & 0 & 0 \\ 10i & -15i & -2.5 + 4.33i & 0 & 0 & 0 \\ 0 & 2.5 + 4.33i & -15i & 10i & 0 & 0 \\ 0 & 0 & 10i & -20i & 10i & 0 \\ 0 & 0 & 0 & 10i & -20i & 10i \\ 0 & 0 & 0 & 0 & 10i & -10i \end{pmatrix} \cdot \text{pu}$$

$$Z_1 := Y_1^{-1}$$

$$Z_1 = \begin{pmatrix} 0.1i & 0.1i & -0.05 + 0.09i & -0.05 + 0.09i & -0.05 + 0.09i & -0.05 + 0.09i \\ 0.1i & 0.2i & -0.1 + 0.17i & -0.1 + 0.17i & -0.1 + 0.17i & -0.1 + 0.17i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.4i & 0.4i & 0.4i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.5i & 0.5i & 0.5i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.5i & 0.6i & 0.6i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.5i & 0.6i & 0.7i \end{pmatrix}$$

- Now the negative sequence (note that the phase shift in the Y-Δ transformer reverses)

$$Y_2 := \begin{pmatrix} \frac{1}{Z_{S1}} + \frac{1}{Z_{L1}} & \frac{-1}{Z_{L1}} & 0 & 0 & 0 & 0 \\ \frac{-1}{Z_{L1}} & \frac{1}{Z_{L1}} + \frac{1}{Z_{T1}} & \frac{-1 \cdot e^{-j \cdot 30\text{deg}}}{Z_{T1}} & 0 & 0 & 0 \\ 0 & \frac{-1 \cdot e^{j \cdot 30\text{deg}}}{Z_{T1}} & \frac{1}{Z_{T1}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 & 0 \\ 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 \\ 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} \\ 0 & 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} \end{pmatrix}$$

$$Y_2 = \begin{pmatrix} -20i & 10i & 0 & 0 & 0 & 0 \\ 10i & -15i & 2.5 + 4.33i & 0 & 0 & 0 \\ 0 & -2.5 + 4.33i & -15i & 10i & 0 & 0 \\ 0 & 0 & 10i & -20i & 10i & 0 \\ 0 & 0 & 0 & 10i & -20i & 10i \\ 0 & 0 & 0 & 0 & 10i & -10i \end{pmatrix} \text{pu}$$

$$Z_2 := Y_2^{-1}$$

$$Z_2 = \begin{pmatrix} 0.1i & 0.1i & 0.05 + 0.09i & 0.05 + 0.09i & 0.05 + 0.09i & 0.05 + 0.09i \\ 0.1i & 0.2i & 0.1 + 0.17i & 0.1 + 0.17i & 0.1 + 0.17i & 0.1 + 0.17i \\ -0.05 + 0.09i & -0.1 + 0.17i & 0.4i & 0.4i & 0.4i & 0.4i \\ -0.05 + 0.09i & -0.1 + 0.17i & 0.4i & 0.5i & 0.5i & 0.5i \\ -0.05 + 0.09i & -0.1 + 0.17i & 0.4i & 0.5i & 0.6i & 0.6i \\ -0.05 + 0.09i & -0.1 + 0.17i & 0.4i & 0.5i & 0.6i & 0.7i \end{pmatrix}$$

- Now the zero sequence (no transformer phase shift, but now open circuit)

$$Y_0 := \begin{pmatrix} \frac{1}{Z_{S0}} + \frac{1}{Z_{L0}} & \frac{-1}{Z_{L0}} & 0 & 0 & 0 & 0 \\ \frac{-1}{Z_{L0}} & \frac{1}{Z_{L0}} & 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{Z_{T0}} + \frac{1}{Z_{\text{feeder}0}} & \frac{-1}{Z_{\text{feeder}0}} & 0 & 0 \\ 0 & 0 & \frac{-1}{Z_{\text{feeder}0}} & \frac{1}{Z_{\text{feeder}0}} + \frac{1}{Z_{\text{feeder}0}} & \frac{-1}{Z_{\text{feeder}0}} & 0 \\ 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder}0}} & \frac{1}{Z_{\text{feeder}0}} + \frac{1}{Z_{\text{feeder}0}} & \frac{-1}{Z_{\text{feeder}0}} \\ 0 & 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder}0}} & \frac{1}{Z_{\text{feeder}0}} \end{pmatrix}$$

$$Y_0 = \begin{pmatrix} -13.33i & 3.33i & 0 & 0 & 0 & 0 \\ 3.33i & -3.33i & 0 & 0 & 0 & 0 \\ 0 & 0 & -8.33i & 3.33i & 0 & 0 \\ 0 & 0 & 3.33i & -6.67i & 3.33i & 0 \\ 0 & 0 & 0 & 3.33i & -6.67i & 3.33i \\ 0 & 0 & 0 & 0 & 3.33i & -3.33i \end{pmatrix} \cdot \text{pu}$$

$$Z_0 := Y_0^{-1}$$

$$Z_0 = \begin{pmatrix} 0.1i & 0.1i & 0 & 0 & 0 & 0 \\ 0.1i & 0.4i & 0 & 0 & 0 & 0 \\ 0 & 0 & 0.2i & 0.2i & 0.2i & 0.2i \\ 0 & 0 & 0.2i & 0.5i & 0.5i & 0.5i \\ 0 & 0 & 0.2i & 0.5i & 0.8i & 0.8i \\ 0 & 0 & 0.2i & 0.5i & 0.8i & 1.1i \end{pmatrix}$$

- Three phase faults:

$$V_f := 1$$

#### - 138 kV Bus (Bus1):

$$I_{3ph\_Bus1} := \frac{V_f}{Z_{1,1}} \quad |I_{3ph\_Bus1}| = 5 \cdot pu \quad \arg(I_{3ph\_Bus1}) = -90 \cdot deg$$

$$I_{3ph\_Bus1\_Amps} := I_{3ph\_Bus1} \cdot I_{BH} \quad |I_{3ph\_Bus1\_Amps}| = 2091.85 \text{ A}$$

#### - 12.47 kV Bus (Bus2):

$$I_{3ph\_Bus2} := \frac{V_f}{Z_{1,2}} \quad |I_{3ph\_Bus2}| = 2.5 \cdot pu \quad \arg(I_{3ph\_Bus2}) = -90 \cdot deg$$

$$I_{3ph\_Bus2\_Amps} := I_{3ph\_Bus2} \cdot I_{BL} \quad |I_{3ph\_Bus2\_Amps}| = 11.575 \cdot kA$$

- As seen from the HV side of the transformer (B1 or B2)

$$\Delta V_1 := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ -I_{3ph\_Bus2} \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad \Delta V_1 = \begin{pmatrix} -0.22 - 0.13i \\ -0.43 - 0.25i \\ -1 \\ -1 \\ -1 \\ -1 \end{pmatrix} \cdot pu$$

$$V_1 := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V_1 \quad V_1 = \begin{pmatrix} 0.65 + 0.38i \\ 0.43 + 0.25i \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad \overrightarrow{|V_1|} = \begin{pmatrix} 0.75 \\ 0.5 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad \arg(V_{10}) = 30 \cdot \text{deg} \quad \arg(V_{11}) = 30 \cdot \text{deg}$$

$$I_{B2\_HV} := \frac{V_{10} - V_{11}}{Z_{L1}} \quad |I_{B2\_HV}| = 2.5 \cdot pu \quad \arg(I_{B2\_HV}) = -60 \cdot \text{deg}$$

$$I_{B2\_HV\_A} := I_{B2\_HV} \cdot I_{BH} \quad |I_{B2\_HV\_A}| = 1045.92 \cdot A$$

- We will see something similar for each of the three phase faults, with a +30 shift in the current

**- At end of first feeder section (just before recloser R1)**

$$I_{3ph\_Bus3} := \frac{V_f}{Z_{1_{3,3}}} \quad |I_{3ph\_Bus3}| = 2 \cdot pu \quad \arg(I_{3ph\_Bus3}) = -90 \cdot deg$$

$$I_{3ph\_Bus3\_Amps} := I_{3ph\_Bus3} \cdot I_{BL} \quad |I_{3ph\_Bus3\_Amps}| = 9259.83 \cdot A$$

**- At end of second feeder section (just before recloser R2)**

$$I_{3ph\_Bus4} := \frac{V_f}{Z_{1_{4,4}}} \quad |I_{3ph\_Bus4}| = 1.67 \cdot pu \quad \arg(I_{3ph\_Bus4}) = -90 \cdot deg$$

$$I_{3ph\_Bus4\_Amps} := I_{3ph\_Bus4} \cdot I_{BL} \quad |I_{3ph\_Bus4\_Amps}| = 7716.52 \cdot A$$

**- At end of third (and last) feeder section**

$$I_{3ph\_Bus5} := \frac{V_f}{Z_{1_{5,5}}} \quad |I_{3ph\_Bus5}| = 1.43 \cdot pu \quad \arg(I_{3ph\_Bus5}) = -90 \cdot deg$$

$$I_{3ph\_Bus5\_Amps} := I_{3ph\_Bus5} \cdot I_{BL} \quad |I_{3ph\_Bus5\_Amps}| = 6614.16 \cdot A$$

- Single line to ground faults:***

- 138 kV Bus (Bus1):

$$I_{0SLG\_Bus1} := \frac{V_f}{Z_{1_{1,1}} + Z_{2_{1,1}} + Z_{0_{1,1}}} \quad I_{1SLG\_Bus1} := I_{0SLG\_Bus1} \quad I_{2SLG\_Bus1} := I_{0SLG\_Bus1}$$

$$I_{ABC\_SLG\_Bus1} := A_{012} \cdot \begin{pmatrix} I_{0SLG\_Bus1} \\ I_{1SLG\_Bus1} \\ I_{2SLG\_Bus1} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_SLG\_Bus1}|} = \begin{pmatrix} 3.75 \\ 0 \\ 0 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_SLG\_Bus1})} = \begin{pmatrix} -90 \\ 26.57 \\ 26.57 \end{pmatrix} \cdot deg$$

$$I_{ABC\_SLG\_Bus1\_A} := I_{ABC\_SLG\_Bus1} \cdot I_{BH}$$

$$\overrightarrow{|I_{ABC\_SLG\_Bus1\_A}|} = \begin{pmatrix} 1568.89 \\ 0 \\ 0 \end{pmatrix} A$$

### - 12.47 kV Bus (Bus2):

$$I_{0SLG\_Bus2} := \frac{V_f}{Z_{1_{2,2}} + Z_{2_{2,2}} + Z_{0_{2,2}}} \quad I_{1SLG\_Bus2} := I_{0SLG\_Bus2} \quad I_{2SLG\_Bus2} := I_{0SLG\_Bus2}$$

$$I_{ABC\_SLG\_Bus2} := A_{012} \cdot \begin{pmatrix} I_{0SLG\_Bus2} \\ I_{1SLG\_Bus2} \\ I_{2SLG\_Bus2} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_SLG\_Bus2}|} = \begin{pmatrix} 3 \\ 0 \\ 0 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_SLG\_Bus2})} = \begin{pmatrix} -90 \\ 18.43 \\ 18.43 \end{pmatrix} \cdot deg$$

$$I_{ABC\_SLG\_Bus2\_A} := I_{ABC\_SLG\_Bus2} \cdot I_{BL}$$

$$\overrightarrow{|I_{ABC\_SLG\_Bus2\_A}|} = \begin{pmatrix} 13.8897 \\ 0 \\ 0 \end{pmatrix} \cdot kA$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$$I_{0\_HV\_SLG\_Bus2} := 0 \text{pu} \quad \text{no zero sequence current across the transformer}$$

$$\Delta V_{1\_SLGBus2} := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ -I_{1SLG\_Bus2} \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad \Delta V_{1\_SLGBus2} = \begin{pmatrix} -0.09 - 0.05i \\ -0.17 - 0.1i \\ -0.4 \\ -0.4 \\ -0.4 \\ -0.4 \end{pmatrix} \cdot \text{pu}$$

$$V_{1\_SLGBus2} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V_{1\_SLGBus2} \quad \overrightarrow{|V_{1\_SLGBus2}|} = \begin{pmatrix} 0.9 \\ 0.8 \\ 0.6 \\ 0.6 \\ 0.6 \\ 0.6 \end{pmatrix} \quad \overrightarrow{\arg(V_{1\_SLGBus2})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V2_{SLGBus2} := Z_2 \cdot \begin{pmatrix} 0 \\ 0 \\ -I_{2SLG\_Bus2} \\ 0 \\ 0 \\ 0 \end{pmatrix} \xrightarrow{|\Delta V2_{SLGBus2}|} = \begin{pmatrix} 0.1 \\ 0.2 \\ 0.4 \\ 0.4 \\ 0.4 \\ 0.4 \end{pmatrix} \cdot pu \quad \xrightarrow{\arg(\Delta V2_{SLGBus2})} = \begin{pmatrix} 150 \\ 150 \\ 180 \\ 180 \\ 180 \\ 180 \end{pmatrix} \cdot deg$$

$$V2_{SLGBus2} := \Delta V2_{SLGBus2}$$

$$I_{1\_HV\_SLG\_Bus2} := \frac{V1_{SLGBus2_0} - V1_{SLGBus2_1}}{Z_{L1}}$$

$$|I_{1\_HV\_SLG\_Bus2}| = 1 \cdot pu$$

$$\arg(I_{1\_HV\_SLG\_Bus2}) = -60 \cdot deg$$

$$I_{2\_HV\_SLG\_Bus2} := \frac{V2_{SLGBus2_0} - V2_{SLGBus2_1}}{Z_{L1}}$$

$$|I_{2\_HV\_SLG\_Bus2}| = 1 \cdot pu \quad \arg(I_{2\_HV\_SLG\_Bus2}) = -120 \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus2} := A_{012} \cdot \begin{pmatrix} I_{0\_HV\_SLG\_Bus2} \\ I_{1\_HV\_SLG\_Bus2} \\ I_{2\_HV\_SLG\_Bus2} \end{pmatrix}$$

$$|I_{ABC\_HV\_SLG\_Bus2}| = \begin{pmatrix} 1.73 \\ 0 \\ 1.73 \end{pmatrix} \cdot pu$$

$$\arg(I_{ABC\_HV\_SLG\_Bus2}) = \begin{pmatrix} -90 \\ 158.2 \\ 90 \end{pmatrix} \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus2\_A} := I_{ABC\_HV\_SLG\_Bus2} \cdot I_{BH}$$

$$|I_{ABC\_HV\_SLG\_Bus2\_A}| = \begin{pmatrix} 724.64 \\ 0 \\ 724.64 \end{pmatrix} \cdot A$$

- At end of first feeder section (just before recloser R1)

$$I_{0SLG\_Bus3} := \frac{V_f}{Z_{1,3} + Z_{2,3} + Z_{0,3}} \quad I_{1SLG\_Bus3} := I_{0SLG\_Bus3} \quad I_{2SLG\_Bus3} := I_{0SLG\_Bus3}$$

$$I_{ABC\_SLG\_Bus3} := A_{012} \cdot \begin{pmatrix} I_{0SLG\_Bus3} \\ I_{1SLG\_Bus3} \\ I_{2SLG\_Bus3} \end{pmatrix}$$

$$|I_{ABC\_SLG\_Bus3}| = \begin{pmatrix} 2 \\ 0 \\ 0 \end{pmatrix} \cdot pu$$

$$\arg(I_{ABC\_SLG\_Bus3}) = \begin{pmatrix} -90 \\ 14.04 \\ 14.04 \end{pmatrix} \cdot deg$$

$$I_{ABC\_SLG\_Bus3\_A} := I_{ABC\_SLG\_Bus3} \cdot I_{BL}$$

$$|I_{ABC\_SLG\_Bus3\_A}| = \begin{pmatrix} 9259.83 \\ 0 \\ 0 \end{pmatrix} \cdot A$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$$I_{0\_HV\_SLG\_Bus3} := 0 \text{pu} \quad \text{no zero sequence current across the transformer}$$

$$\Delta V1_{SLGBus3} := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ -I_{1SLG\_Bus3} \\ 0 \\ 0 \end{pmatrix} \quad \Delta V1_{SLGBus3} = \begin{pmatrix} -0.06 - 0.03i \\ -0.12 - 0.07i \\ -0.27 \\ -0.33 \\ -0.33 \\ -0.33 \end{pmatrix} \cdot \text{pu}$$

$$V1_{SLGBus3} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V1_{SLGBus3} \quad \overrightarrow{|V1_{SLGBus3}|} = \begin{pmatrix} 0.93 \\ 0.87 \\ 0.73 \\ 0.67 \\ 0.67 \\ 0.67 \end{pmatrix} \quad \overrightarrow{\arg(V1_{SLGBus3})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V2_{SLGBus3} := Z_2 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ -I_{2SLG\_Bus3} \\ 0 \\ 0 \end{pmatrix} \quad \overrightarrow{|\Delta V2_{SLGBus3}|} = \begin{pmatrix} 0.07 \\ 0.13 \\ 0.27 \\ 0.33 \\ 0.33 \\ 0.33 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(\Delta V2_{SLGBus3})} = \begin{pmatrix} 150 \\ 150 \\ 180 \\ 180 \\ 180 \\ 180 \end{pmatrix} \cdot \text{deg}$$

$$V2_{SLGBus3} := \Delta V2_{SLGBus3}$$

$$I_{1\_HV\_SLG\_Bus3} := \frac{V1_{SLGBus3}_0 - V1_{SLGBus3}_1}{Z_{L1}}$$

$$|I_{1\_HV\_SLG\_Bus3}| = 0.6667 \cdot pu \quad \arg(I_{1\_HV\_SLG\_Bus3}) = -60 \cdot deg$$

$$I_{2\_HV\_SLG\_Bus3} := \frac{V2_{SLGBus3}_0 - V2_{SLGBus3}_1}{Z_{L1}}$$

$$|I_{2\_HV\_SLG\_Bus3}| = 0.6667 \cdot pu \quad \arg(I_{2\_HV\_SLG\_Bus3}) = -120 \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus3} := A_{012} \cdot \begin{pmatrix} I_{0\_HV\_SLG\_Bus3} \\ I_{1\_HV\_SLG\_Bus3} \\ I_{2\_HV\_SLG\_Bus3} \end{pmatrix}$$

$$|I_{ABC\_HV\_SLG\_Bus3}| = \begin{pmatrix} 1.15 \\ 0 \\ 1.15 \end{pmatrix} \cdot pu$$

$$\arg(I_{ABC\_HV\_SLG\_Bus3}) = \begin{pmatrix} -90 \\ 40.6 \\ 90 \end{pmatrix} \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus3\_A} := I_{ABC\_HV\_SLG\_Bus3} \cdot I_{BH}$$

$$|I_{ABC\_HV\_SLG\_Bus3\_A}| = \begin{pmatrix} 483.09 \\ 0 \\ 483.09 \end{pmatrix} \cdot A$$

- At end of second feeder section (just before recloser R2)

$$I_{0SLG\_Bus4} := \frac{V_f}{Z_{1_{4,4}} + Z_{2_{4,4}} + Z_{0_{4,4}}} \quad I_{1SLG\_Bus4} := I_{0SLG\_Bus4} \quad I_{2SLG\_Bus4} := I_{0SLG\_Bus4}$$

$$I_{ABC\_SLG\_Bus4} := A_{012} \cdot \begin{pmatrix} I_{0SLG\_Bus4} \\ I_{1SLG\_Bus4} \\ I_{2SLG\_Bus4} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_SLG\_Bus4}|} = \begin{pmatrix} 1.5 \\ 0 \\ 0 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_SLG\_Bus4})} = \begin{pmatrix} -90 \\ 18.43 \\ 18.43 \end{pmatrix} \cdot deg$$

$$I_{ABC\_SLG\_Bus4\_A} := I_{ABC\_SLG\_Bus4} \cdot I_{BL}$$

$$\overrightarrow{|I_{ABC\_SLG\_Bus4\_A}|} = \begin{pmatrix} 6944.87 \\ 0 \\ 0 \end{pmatrix} \cdot A$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$$I_{0\_HV\_SLG\_Bus4} := 0pu \quad \text{no zero sequence current across the transformer}$$

$$\Delta V_{1SLGBus4} := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{1SLG\_Bus4} \\ 0 \end{pmatrix} \quad \Delta V_{1SLGBus4} = \begin{pmatrix} -0.04 - 0.03i \\ -0.09 - 0.05i \\ -0.2 \\ -0.25 \\ -0.3 \\ -0.3 \end{pmatrix} \cdot pu$$

$$V_{1\text{SLGBus4}} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V_{1\text{SLGBus4}} \quad \overrightarrow{|V_{1\text{SLGBus4}}|} = \begin{pmatrix} 0.95 \\ 0.9 \\ 0.8 \\ 0.75 \\ 0.7 \\ 0.7 \end{pmatrix}$$

$$\overrightarrow{\arg(V_{1\text{SLGBus4}})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{2\text{SLGBus4}} := Z_2 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{2\text{SLG_Bus4}} \\ 0 \end{pmatrix} \quad \overrightarrow{|\Delta V_{2\text{SLGBus4}}|} = \begin{pmatrix} 0.05 \\ 0.1 \\ 0.2 \\ 0.25 \\ 0.3 \\ 0.3 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(\Delta V_{2\text{SLGBus4}})} = \begin{pmatrix} 150 \\ 150 \\ 180 \\ 180 \\ 180 \\ 180 \end{pmatrix} \cdot \text{deg}$$

$$V_{2\text{SLGBus4}} := \Delta V_{2\text{SLGBus4}}$$

$$I_{1\text{HV_SLG_Bus4}} := \frac{V_{1\text{SLGBus4}_0} - V_{1\text{SLGBus4}_1}}{Z_{L1}}$$

$$|I_{1\text{HV_SLG_Bus4}}| = 0.5 \cdot \text{pu}$$

$$\overrightarrow{\arg(I_{1\text{HV_SLG_Bus4}})} = -60 \cdot \text{deg}$$

$$I_{2\text{HV_SLG_Bus4}} := \frac{V_{2\text{SLGBus4}_0} - V_{2\text{SLGBus4}_1}}{Z_{L1}}$$

$$|I_{2\_HV\_SLG\_Bus4}| = 0.5 \cdot pu$$

$$\arg(I_{2\_HV\_SLG\_Bus4}) = -120 \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus4} := A_{012} \cdot \begin{pmatrix} I_{0\_HV\_SLG\_Bus4} \\ I_{1\_HV\_SLG\_Bus4} \\ I_{2\_HV\_SLG\_Bus4} \end{pmatrix}$$

$$|I_{ABC\_HV\_SLG\_Bus4}| = \begin{pmatrix} 0.87 \\ 0 \\ 0.87 \end{pmatrix} \cdot pu$$

$$\arg(I_{ABC\_HV\_SLG\_Bus4}) = \begin{pmatrix} -90 \\ 0 \\ 90 \end{pmatrix} \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus4\_A} := I_{ABC\_HV\_SLG\_Bus4} \cdot I_{BH}$$

$$|I_{ABC\_HV\_SLG\_Bus4\_A}| = \begin{pmatrix} 362.32 \\ 0 \\ 362.32 \end{pmatrix} \cdot A$$

**- At end of third (and last) feeder section**

$$I_{0SLG\_Bus5} := \frac{V_f}{Z_{1_{5,5}} + Z_{2_{5,5}} + Z_{0_{5,5}}} \quad I_{1SLG\_Bus5} := I_{0SLG\_Bus5} \quad I_{2SLG\_Bus5} := I_{0SLG\_Bus5}$$

$$I_{ABC\_SLG\_Bus5} := A_{012} \cdot \begin{pmatrix} I_{0SLG\_Bus5} \\ I_{1SLG\_Bus5} \\ I_{2SLG\_Bus5} \end{pmatrix}$$

$$|I_{ABC\_SLG\_Bus5}| = \begin{pmatrix} 1.2 \\ 0 \\ 0 \end{pmatrix} \cdot pu$$

$$\arg(I_{ABC\_SLG\_Bus5}) = \begin{pmatrix} -90 \\ 18.43 \\ 18.43 \end{pmatrix} \cdot deg$$

$$I_{ABC\_SLG\_Bus5\_A} := I_{ABC\_SLG\_Bus5} \cdot I_{BL}$$

$$\overrightarrow{|I_{ABC\_SLG\_Bus5\_A}|} = \begin{pmatrix} 5555.9 \\ 0 \\ 0 \end{pmatrix} \cdot A$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$$I_{0\_HV\_SLG\_Bus5} := 0 \text{pu} \quad \text{no zero sequence current across the transformer}$$

$$\Delta V1_{SLGBus5} := Z_1 \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -I_{1SLG\_Bus5} \end{pmatrix} \quad \Delta V1_{SLGBus5} = \begin{pmatrix} -0.03 - 0.02i \\ -0.07 - 0.04i \\ -0.16 \\ -0.2 \\ -0.24 \\ -0.28 \end{pmatrix} \cdot \text{pu}$$

$$V1_{SLGBus5} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V1_{SLGBus5} \quad \overrightarrow{|V1_{SLGBus5}|} = \begin{pmatrix} 0.96 \\ 0.92 \\ 0.84 \\ 0.8 \\ 0.76 \\ 0.72 \end{pmatrix} \quad \overrightarrow{\arg(V1_{SLGBus5})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V2_{SLGBus5} := Z_2 \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -I_{2SLG\_Bus5} \end{pmatrix} \xrightarrow{|\Delta V2_{SLGBus5}|} = \begin{pmatrix} 0.04 \\ 0.08 \\ 0.16 \\ 0.2 \\ 0.24 \\ 0.28 \end{pmatrix} \cdot pu \quad \xrightarrow{\arg(\Delta V2_{SLGBus5})} = \begin{pmatrix} 150 \\ 150 \\ 180 \\ 180 \\ 180 \\ 180 \end{pmatrix} \cdot deg$$

$$V2_{SLGBus5} := \Delta V2_{SLGBus5}$$

$$I_{1\_HV\_SLG\_Bus5} := \frac{V1_{SLGBus5_0} - V1_{SLGBus5_1}}{Z_{L1}}$$

$$|I_{1\_HV\_SLG\_Bus5}| = 0.4 \cdot pu \quad \arg(I_{1\_HV\_SLG\_Bus5}) = -60 \cdot deg$$

$$I_{2\_HV\_SLG\_Bus5} := \frac{V2_{SLGBus5_0} - V2_{SLGBus5_1}}{Z_{L1}}$$

$$|I_{2\_HV\_SLG\_Bus5}| = 0.4 \cdot pu \quad \arg(I_{2\_HV\_SLG\_Bus5}) = -120 \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus5} := A_{012} \cdot \begin{pmatrix} I_{0\_HV\_SLG\_Bus5} \\ I_{1\_HV\_SLG\_Bus5} \\ I_{2\_HV\_SLG\_Bus5} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_HV\_SLG\_Bus5}|} = \begin{pmatrix} 0.69 \\ 0 \\ 0.69 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_HV\_SLG\_Bus5})} = \begin{pmatrix} -90 \\ 133.15 \\ 90 \end{pmatrix} \cdot deg$$

$$I_{ABC\_HV\_SLG\_Bus5\_A} := I_{ABC\_HV\_SLG\_Bus5} \cdot I_{BH}$$

$$\overrightarrow{|I_{ABC\_HV\_SLG\_Bus5\_A}|} = \begin{pmatrix} 289.86 \\ 0 \\ 289.86 \end{pmatrix} \cdot A$$

- Line to line faults:**

- **138 kV Bus (Bus1):**

$$I_{1LL\_Bus1} := \frac{V_f}{Z_{1,1,1} + Z_{2,1,1}} \quad I_{2LL\_Bus1} := -I_{1LL\_Bus1} \quad I_{0LL\_Bus1} := 1.0 \cdot 10^{-15} pu$$

$$I_{ABC\_LL\_Bus1} := A_{012} \cdot \begin{pmatrix} I_{0LL\_Bus1} \\ I_{1LL\_Bus1} \\ I_{2LL\_Bus1} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus1}|} = \begin{pmatrix} 0 \\ 4.33 \\ 4.33 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_LL\_Bus1})} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot deg$$

$$I_{ABC\_LL\_Bus1\_A} := I_{ABC\_LL\_Bus1} \cdot I_{BH}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus1\_A}|} = \begin{pmatrix} 0 \\ 1811.59 \\ 1811.59 \end{pmatrix} A$$

**- 12.47 kV Bus (Bus2):**

$$I_{1LL\_Bus2} := \frac{V_f}{Z_{1_{2,2}} + Z_{2_{2,2}}}$$

$$I_{2LL\_Bus2} := -I_{1LL\_Bus2}$$

$$I_{0LL\_Bus2} := 1.0 \cdot 10^{-15} \text{ pu}$$

$$I_{ABC\_LL\_Bus2} := A_{012} \cdot \begin{pmatrix} I_{0LL\_Bus2} \\ I_{1LL\_Bus2} \\ I_{2LL\_Bus2} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus2}|} = \begin{pmatrix} 0 \\ 2.17 \\ 2.17 \end{pmatrix} \text{ pu}$$

$$\arg(\overrightarrow{|I_{ABC\_LL\_Bus2}|}) = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC\_LL\_Bus2\_A} := I_{ABC\_LL\_Bus2} \cdot I_{BL}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus2\_A}|} = \begin{pmatrix} 0 \\ 10.0241 \\ 10.0241 \end{pmatrix} \cdot \text{kA}$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$$I_{0\_HV\_LL\_Bus2} := 0 \text{pu} \quad \text{no zero sequence current for this fault type}$$

$$\Delta V_{1LLBus2} := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ -I_{1LL\_Bus2} \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad \Delta V_{1LLBus2} = \begin{pmatrix} -0.11 - 0.06i \\ -0.22 - 0.13i \\ -0.5 \\ -0.5 \\ -0.5 \\ -0.5 \end{pmatrix} \cdot \text{pu}$$

$$V_{1LLBus2} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V_{1LLBus2} \quad \overrightarrow{|V_{1LLBus2}|} = \begin{pmatrix} 0.88 \\ 0.75 \\ 0.5 \\ 0.5 \\ 0.5 \\ 0.5 \end{pmatrix} \quad \overrightarrow{\arg(V_{1LLBus2})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{2LLBus2} := Z_2 \cdot \begin{pmatrix} 0 \\ 0 \\ -I_{2LL\_Bus2} \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad \overrightarrow{|\Delta V_{2LLBus2}|} = \begin{pmatrix} 0.13 \\ 0.25 \\ 0.5 \\ 0.5 \\ 0.5 \\ 0.5 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(\Delta V_{2LLBus2})} = \begin{pmatrix} -30 \\ -30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$V2_{LLBus2} := \Delta V2_{LLBus2}$$

$$I_{1\_HV\_LL\_Bus2} := \frac{V1_{LLBus2}_0 - V1_{LLBus2}_1}{Z_{L1}}$$

$$|I_{1\_HV\_LL\_Bus2}| = 1.25 \cdot \text{pu}$$

$$\arg(I_{1\_HV\_LL\_Bus2}) = -60 \cdot \text{deg}$$

$$I_{2\_HV\_LL\_Bus2} := \frac{V2_{LLBus2}_0 - V2_{LLBus2}_1}{Z_{L1}}$$

$$|I_{2\_HV\_LL\_Bus2}| = 1.25 \cdot \text{pu}$$

$$\arg(I_{2\_HV\_LL\_Bus2}) = 60 \cdot \text{deg}$$

$$I_{ABC\_HV\_LL\_Bus2} := A_{012} \cdot \begin{pmatrix} I_{0\_HV\_LL\_Bus2} \\ I_{1\_HV\_LL\_Bus2} \\ I_{2\_HV\_LL\_Bus2} \end{pmatrix}$$

$$|I_{ABC\_HV\_LL\_Bus2}| = \begin{pmatrix} 1.25 \\ 2.5 \\ 1.25 \end{pmatrix} \cdot \text{pu}$$

$$\arg(I_{ABC\_HV\_LL\_Bus2}) = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC\_HV\_LL\_Bus2\_A} := I_{ABC\_HV\_LL\_Bus2} \cdot I_{BH}$$

$$|I_{ABC\_HV\_LL\_Bus2\_A}| = \begin{pmatrix} 522.96 \\ 1045.92 \\ 522.96 \end{pmatrix} \cdot \text{A}$$

- At end of first feeder section (just before recloser R1)

$$I_{1LL\_Bus3} := \frac{V_f}{Z_{1_{3,3}} + Z_{2_{3,3}}} \quad I_{2LL\_Bus3} := -I_{1LL\_Bus3} \quad I_{0LL\_Bus3} := 1.0 \cdot 10^{-15} \text{ pu}$$

$$I_{ABC\_LL\_Bus3} := A_{012} \cdot \begin{pmatrix} I_{0LL\_Bus3} \\ I_{1LL\_Bus3} \\ I_{2LL\_Bus3} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus3}|} = \begin{pmatrix} 0 \\ 1.73 \\ 1.73 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(I_{ABC\_LL\_Bus3})} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC\_LL\_Bus3\_A} := I_{ABC\_LL\_Bus3} \cdot I_{BL}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus3\_A}|} = \begin{pmatrix} 0 \\ 8019.25 \\ 8019.25 \end{pmatrix} \cdot \text{A}$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$I_{0\_HV\_LL\_Bus3} := 0 \text{ pu}$  no zero sequence current for this fault type

$$\Delta V_{1LLBus3} := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ -I_{1LL\_Bus3} \\ 0 \\ 0 \end{pmatrix} \quad \Delta V_{1LLBus3} = \begin{pmatrix} -0.09 - 0.05i \\ -0.17 - 0.1i \\ -0.4 \\ -0.5 \\ -0.5 \\ -0.5 \end{pmatrix} \cdot pu$$

$$V_{1LLBus3} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V_{1LLBus3} \quad \overrightarrow{|V_{1LLBus3}|} = \begin{pmatrix} 0.9 \\ 0.8 \\ 0.6 \\ 0.5 \\ 0.5 \\ 0.5 \end{pmatrix} \quad \overrightarrow{\arg(V_{1LLBus3})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{2LLBus3} := Z_2 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ -I_{2LL\_Bus3} \\ 0 \\ 0 \end{pmatrix} \quad \overrightarrow{|\Delta V_{2LLBus3}|} = \begin{pmatrix} 0.1 \\ 0.2 \\ 0.4 \\ 0.5 \\ 0.5 \\ 0.5 \end{pmatrix} \cdot pu \quad \overrightarrow{\arg(\Delta V_{2LLBus3})} = \begin{pmatrix} -30 \\ -30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$V_{2LLBus3} := \Delta V_{2LLBus3}$$

$$I_{1\_HV\_LL\_Bus3} := \frac{V_{1LLBus3_0} - V_{1LLBus3_1}}{Z_{L1}}$$

$$|I_{1\_HV\_LL\_Bus3}| = 1\text{-pu}$$

$$\arg(I_{1\_HV\_LL\_Bus3}) = -60\text{-deg}$$

$$I_{2\_HV\_LL\_Bus3} := \frac{V_{2LLBus3_0} - V_{2LLBus3_1}}{Z_{L1}}$$

$$|I_{2\_HV\_LL\_Bus3}| = 1\text{-pu}$$

$$\arg(I_{2\_HV\_LL\_Bus3}) = 60\text{-deg}$$

$$I_{ABC\_HV\_LL\_Bus3} := A_{012} \cdot \begin{pmatrix} I_{0\_HV\_LL\_Bus3} \\ I_{1\_HV\_LL\_Bus3} \\ I_{2\_HV\_LL\_Bus3} \end{pmatrix}$$

$$|I_{ABC\_HV\_LL\_Bus3}| = \begin{pmatrix} 1 \\ 2 \\ 1 \end{pmatrix} \cdot \text{pu}$$

$$\arg(I_{ABC\_HV\_LL\_Bus3}) = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC\_HV\_LL\_Bus3\_A} := I_{ABC\_HV\_LL\_Bus3} \cdot I_{BH}$$

$$|I_{ABC\_HV\_LL\_Bus3\_A}| = \begin{pmatrix} 418.37 \\ 836.74 \\ 418.37 \end{pmatrix} \cdot \text{A}$$

- At end of second feeder section (just before recloser R2)

$$I_{1LL\_Bus4} := \frac{V_f}{Z_{14,4} + Z_{24,4}}$$

$$I_{2LL\_Bus4} := -I_{1LL\_Bus4}$$

$$I_{0LL\_Bus4} := 1.0 \cdot 10^{-15} \text{ pu}$$

$$I_{ABC\_LL\_Bus4} := A_{012} \cdot \begin{pmatrix} I_{0LL\_Bus4} \\ I_{1LL\_Bus4} \\ I_{2LL\_Bus4} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus4}|} = \begin{pmatrix} 0 \\ 1.44 \\ 1.44 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(I_{ABC\_LL\_Bus4})} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC\_LL\_Bus4\_A} := I_{ABC\_LL\_Bus4} \cdot I_{BL}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus4\_A}|} = \begin{pmatrix} 0 \\ 6682.71 \\ 6682.71 \end{pmatrix} \cdot \text{A}$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$$I_{0\_HV\_LL\_Bus4} := 0 \text{ pu} \quad \text{no zero sequence current for this fault type}$$

$$\Delta V_{1LLBus4} := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{1LL\_Bus4} \\ 0 \end{pmatrix} \quad \Delta V_{1LLBus4} = \begin{pmatrix} -0.07 - 0.04i \\ -0.14 - 0.08i \\ -0.33 \\ -0.42 \\ -0.5 \\ -0.5 \end{pmatrix} \cdot \text{pu}$$

$$V1_{LLBus4} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V1_{LLBus4} \quad \overrightarrow{|V1_{LLBus4}|} = \begin{pmatrix} 0.92 \\ 0.83 \\ 0.67 \\ 0.58 \\ 0.5 \\ 0.5 \end{pmatrix} \quad \overrightarrow{\arg(V1_{LLBus4})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V2_{LLBus4} := Z_2 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{2LL\_Bus4} \\ 0 \end{pmatrix} \quad \overrightarrow{|\Delta V2_{LLBus4}|} = \begin{pmatrix} 0.08 \\ 0.17 \\ 0.33 \\ 0.42 \\ 0.5 \\ 0.5 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(\Delta V2_{LLBus4})} = \begin{pmatrix} -30 \\ -30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$V2_{LLBus4} := \Delta V2_{LLBus4}$$

$$I_{1\_HV\_LL\_Bus4} := \frac{V1_{LLBus4}_0 - V1_{LLBus4}_1}{Z_{L1}}$$

$$|I_{1\_HV\_LL\_Bus4}| = 0.8333 \cdot \text{pu} \quad \arg(I_{1\_HV\_LL\_Bus4}) = -60 \cdot \text{deg}$$

$$I_{2\_HV\_LL\_Bus4} := \frac{V_{2LLBus4_0} - V_{2LLBus4_1}}{Z_{L1}}$$

$$|I_{2\_HV\_LL\_Bus4}| = 0.8333 \cdot pu \quad \arg(I_{2\_HV\_LL\_Bus4}) = 60 \cdot deg$$

$$I_{ABC\_HV\_LL\_Bus4} := A_{012} \begin{pmatrix} I_{0\_HV\_LL\_Bus4} \\ I_{1\_HV\_LL\_Bus4} \\ I_{2\_HV\_LL\_Bus4} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_HV\_LL\_Bus4}|} = \begin{pmatrix} 0.83 \\ 1.67 \\ 0.83 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_HV\_LL\_Bus4})} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot deg$$

$$I_{ABC\_HV\_LL\_Bus4\_A} := I_{ABC\_HV\_LL\_Bus4} \cdot I_{BH}$$

$$\overrightarrow{|I_{ABC\_HV\_LL\_Bus4\_A}|} = \begin{pmatrix} 348.64 \\ 697.28 \\ 348.64 \end{pmatrix} \cdot A$$

- At end of third feeder section (end of feeder)

$$I_{1LL\_Bus5} := \frac{V_f}{Z_{1,5,5} + Z_{2,5,5}}$$

$$I_{2LL\_Bus5} := -I_{1LL\_Bus5}$$

$$I_{0LL\_Bus5} := 1.0 \cdot 10^{-15} pu$$

$$I_{ABC\_LL\_Bus5} := A_{012} \cdot \begin{pmatrix} I_{0LL\_Bus5} \\ I_{1LL\_Bus5} \\ I_{2LL\_Bus5} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus5}|} = \begin{pmatrix} 0 \\ 1.24 \\ 1.24 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_LL\_Bus5})} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot deg$$

$$I_{ABC\_LL\_Bus5\_A} := I_{ABC\_LL\_Bus5} \cdot I_{BL}$$

$$\overrightarrow{|I_{ABC\_LL\_Bus5\_A}|} = \begin{pmatrix} 0 \\ 5728.03 \\ 5728.03 \end{pmatrix} \cdot A$$

- Fault current as seen on HV side of transformer by B2 (or B1)

$$I_{0\_HV\_LL\_Bus5} := 0pu \quad \text{no zero sequence current for this fault type}$$

$$\Delta V_{1LLBus5} := Z_1 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -I_{1LL\_Bus5} \end{pmatrix} \quad \Delta V_{1LLBus5} = \begin{pmatrix} -0.06 - 0.04i \\ -0.12 - 0.07i \\ -0.29 \\ -0.36 \\ -0.43 \\ -0.5 \end{pmatrix} \cdot pu$$

$$V_{1LLBus5} := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V_{1LLBus5} \quad \overrightarrow{|V_{1LLBus5}|} = \begin{pmatrix} 0.93 \\ 0.86 \\ 0.71 \\ 0.64 \\ 0.57 \\ 0.5 \end{pmatrix} \quad \overrightarrow{\arg(V_{1LLBus5})} = \begin{pmatrix} 30 \\ 30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{2LLBus5} := Z_2 \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -I_{2LL\_Bus5} \end{pmatrix} \quad \overrightarrow{|\Delta V_{2LLBus5}|} = \begin{pmatrix} 0.07 \\ 0.14 \\ 0.29 \\ 0.36 \\ 0.43 \\ 0.5 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(\Delta V_{2LLBus5})} = \begin{pmatrix} -30 \\ -30 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \cdot \text{deg}$$

$$V_{2LLBus5} := \Delta V_{2LLBus5}$$

$$I_{1\_HV\_LL\_Bus5} := \frac{V_{1LLBus5_0} - V_{1LLBus5_1}}{Z_{L1}}$$

$$|I_{1\_HV\_LL\_Bus5}| = 0.7143 \cdot \text{pu} \quad \arg(I_{1\_HV\_LL\_Bus5}) = -60 \cdot \text{deg}$$

$$I_{2\_HV\_LL\_Bus5} := \frac{V_{2LLBus5_0} - V_{2LLBus5_1}}{Z_{L1}}$$

$$|I_{2\_HV\_LL\_Bus5}| = 0.7143 \cdot pu \quad \arg(I_{2\_HV\_LL\_Bus5}) = 60 \cdot deg$$

$$I_{ABC\_HV\_LL\_Bus5} := A_{012} \begin{pmatrix} I_{0\_HV\_LL\_Bus5} \\ I_{1\_HV\_LL\_Bus5} \\ I_{2\_HV\_LL\_Bus5} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC\_HV\_LL\_Bus5}|} = \begin{pmatrix} 0.71 \\ 1.43 \\ 0.71 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC\_HV\_LL\_Bus5})} = \begin{pmatrix} 0 \\ -180 \\ 0 \end{pmatrix} \cdot deg$$

$$I_{ABC\_HV\_LL\_Bus5\_A} := I_{ABC\_HV\_LL\_Bus5} \cdot I_{BH}$$

$$\overrightarrow{|I_{ABC\_HV\_LL\_Bus5\_A}|} = \begin{pmatrix} 298.84 \\ 597.67 \\ 298.84 \end{pmatrix} \cdot A$$

### Mid-line Fault Between B3 and R1

- First form Ybus and then Zbus for each sequence. First the positive sequence

$$Y_1(m) := \begin{bmatrix} \frac{1}{Z_{S1}} + \frac{1}{Z_{L1}} & \frac{-1}{Z_{L1}} & 0 & 0 & 0 & 0 & 0 \\ \frac{-1}{Z_{L1}} & \frac{1}{Z_{L1}} + \frac{1}{Z_{T1}} & \frac{-1 \cdot e^{j \cdot 30\text{deg}}}{Z_{T1}} & 0 & 0 & 0 & 0 \\ 0 & \frac{-1 \cdot e^{-j \cdot 30\text{deg}}}{Z_{T1}} & \frac{1}{Z_{T1}} + \frac{1}{m \cdot Z_{\text{feeder1}}} & 0 & 0 & 0 & \frac{-1}{m \cdot Z_{\text{feeder1}}} \\ 0 & 0 & 0 & \frac{1}{(1-m) \cdot Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 & \frac{-1}{(1-m) \cdot Z_{\text{feeder1}}} \\ 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 \\ 0 & 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} & 0 \\ 0 & 0 & \frac{-1}{m \cdot Z_{\text{feeder1}}} & \frac{-1}{(1-m) \cdot Z_{\text{feeder1}}} & 0 & 0 & \frac{1}{m \cdot Z_{\text{feeder1}}} + \frac{1}{(1-m) \cdot Z_{\text{feeder1}}} \end{bmatrix}$$

$$Y_1(0.7) = \begin{pmatrix} -20i & 10i & 0 & 0 & 0 & 0 & 0 \\ 10i & -15i & -2.5 + 4.33i & 0 & 0 & 0 & 0 \\ 0 & 2.5 + 4.33i & -19.29i & 0 & 0 & 0 & 14.29i \\ 0 & 0 & 0 & -43.33i & 10i & 0 & 33.33i \\ 0 & 0 & 0 & 10i & -20i & 10i & 0 \\ 0 & 0 & 0 & 0 & 10i & -10i & 0 \\ 0 & 0 & 14.29i & 33.33i & 0 & 0 & -47.62i \end{pmatrix} \cdot \text{pu}$$

$$Z_1(m) := Y_1(m)^{-1}$$

$$Z_1(0.7) = \begin{pmatrix} 0.1i & 0.1i & -0.05 + 0.09i \\ 0.1i & 0.2i & -0.1 + 0.17i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.4i & 0.4i & 0.4i & 0.4i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.5i & 0.5i & 0.5i & 0.47i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.5i & 0.6i & 0.6i & 0.47i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.5i & 0.6i & 0.7i & 0.47i \\ 0.05 + 0.09i & 0.1 + 0.17i & 0.4i & 0.47i & 0.47i & 0.47i & 0.47i \end{pmatrix}$$

- Now the negative sequence (note that the phase shift in the Y-Δ transformer reverses)

- Assume ANSI phase shift (so HV leads LV by 30 degrees)
- Neglect load

$$Y_2(m) := \begin{bmatrix} \frac{1}{Z_{S1}} + \frac{1}{Z_{L1}} & \frac{-1}{Z_{L1}} & 0 & 0 & 0 & 0 & 0 \\ \frac{-1}{Z_{L1}} & \frac{1}{Z_{L1}} + \frac{1}{Z_{T1}} & \frac{-1 \cdot e^{-j \cdot 30\text{deg}}}{Z_{T1}} & 0 & 0 & 0 & 0 \\ 0 & \frac{-1 \cdot e^{j \cdot 30\text{deg}}}{Z_{T1}} & \frac{1}{Z_{T1}} + \frac{1}{m \cdot Z_{\text{feeder1}}} & 0 & 0 & 0 & \frac{-1}{m \cdot Z_{\text{feeder1}}} \\ 0 & 0 & 0 & \frac{1}{(1-m) \cdot Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 & \frac{-1}{(1-m) \cdot Z_{\text{feeder1}}} \\ 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} + \frac{1}{Z_{\text{feeder1}}} & \frac{-1}{Z_{\text{feeder1}}} & 0 \\ 0 & 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder1}}} & \frac{1}{Z_{\text{feeder1}}} & 0 \\ 0 & 0 & \frac{-1}{m \cdot Z_{\text{feeder1}}} & \frac{-1}{(1-m) \cdot Z_{\text{feeder1}}} & 0 & 0 & \frac{1}{m \cdot Z_{\text{feeder1}}} + \frac{1}{(1-m) \cdot Z_{\text{feeder1}}} \end{bmatrix}$$

$$Z_2(m) := Y_2(m)^{-1}$$

- Now the zero sequence (no transformer phase shift, but now open circuit)

$$Y_0(m) := \begin{bmatrix} \frac{1}{Z_{S0}} + \frac{1}{Z_{L0}} & \frac{-1}{Z_{L0}} & 0 & 0 & 0 & 0 \\ \frac{-1}{Z_{L0}} & \frac{1}{Z_{L0}} & 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{Z_{T0}} + \frac{1}{m \cdot Z_{\text{feeder}0}} & 0 & 0 & \frac{-1}{m \cdot Z_{\text{feeder}0}} \\ 0 & 0 & 0 & \frac{1}{(1-m) \cdot Z_{\text{feeder}0}} + \frac{1}{Z_{\text{feeder}0}} & \frac{-1}{Z_{\text{feeder}0}} & 0 \\ 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder}0}} & \frac{1}{Z_{\text{feeder}0}} + \frac{1}{Z_{\text{feeder}0}} & \frac{-1}{Z_{\text{feeder}0}} \\ 0 & 0 & 0 & 0 & \frac{-1}{Z_{\text{feeder}0}} & \frac{1}{Z_{\text{feeder}0}} \\ 0 & 0 & \frac{-1}{m \cdot Z_{\text{feeder}0}} & \frac{-1}{(1-m) \cdot Z_{\text{feeder}0}} & 0 & \frac{1}{m \cdot Z_{\text{feeder}0}} + \frac{1}{(1-m) \cdot Z_{\text{feeder}0}} \end{bmatrix}$$

$$Z_0(m) := Y_0(m)^{-1}$$

- Three phase faults at 70% of the feeder

$$V_f := 1$$

**- 138 kV Bus (Bus1):**

$$I_{3ph\_BusM}(m) := \frac{V_f}{Z_1(m)} \quad |I_{3ph\_BusM}(0.7)| = 2.13 \cdot pu \quad \arg(I_{3ph\_BusM}(0.7)) = -90 \cdot deg$$

$$I_{3ph\_BusM\_Amps} := I_{3ph\_BusM}(0.7) \cdot I_{BL} \quad |I_{3ph\_BusM\_Amps}| = 9.85 \cdot kA$$

- As seen from the HV side of the transformer (B1 or B2)

$$\Delta V_1(m) := Z_1(m) \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -I_{3ph\_BusM}(m) \end{pmatrix} \quad \Delta V_1(0.7) = \begin{pmatrix} -0.18 - 0.11i \\ -0.37 - 0.21i \\ -0.85 \\ -1 \\ -1 \\ -1 \\ -1 \end{pmatrix} \cdot pu$$

$$V1(m) := \begin{pmatrix} 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \cdot e^{j \cdot 30\text{deg}} \\ 1 \\ 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} + \Delta V1(m) \quad V1(0.7) = \begin{pmatrix} 0.68 + 0.39i \\ 0.5 + 0.29i \\ 0.15 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \xrightarrow{|V1(0.7)|} = \begin{pmatrix} 0.79 \\ 0.57 \\ 0.15 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$\arg(V1(0.7)_0) = 30 \cdot \text{deg}$   
 $\arg(V1(0.7)_1) = 30 \cdot \text{deg}$   
 $\arg(V1(0.7)_2) = 0 \cdot \text{deg}$

$$I_{BM\_HV}(m) := \frac{V1(m)_0 - V1(m)_1}{Z_{L1}}$$

$|I_{BM\_HV}(0.7)| = 2.1277 \cdot \text{pu}$        $\arg(I_{BM\_HV}(0.7)) = -60 \cdot \text{deg}$

$$I_{BM\_HV\_A}(m) := I_{BM\_HV}(m) \cdot I_{BH}$$

$|I_{BM\_HV\_A}(0.7)| = 890.15 \cdot \text{A}$

- We will see something similar for each of the three phase faults, with a +30 shift in the current

Similar procedure for the SLG, LL and DLG faults

### **Load current calculations**

- Positive sequence current for each load:

$$P_{\text{load}} := 3.3 \text{MW} \quad I_{\text{load}} := \frac{P_{\text{load}}}{\sqrt{3} \cdot V_{BL}} \quad I_{\text{load}} = 152.79 \text{ A} \quad \text{unity power factor}$$

- Worst case zero sequence current: assume a worst case of a 20% imbalance

$$I_{0\_load\_max} := 0.20 \cdot I_{\text{load}} \quad I_{0\_load\_max} = 30.56 \text{ A} \quad \text{Note this is } 3I_0$$

- This is also the load current seen by recloser R2

$$I_{\text{Load\_R2\_1}} := I_{\text{load}}$$

$$I_{\text{Load\_R2\_0max}} := I_{0\_load\_max}$$

- Load at recloser R1

$$I_{\text{load\_R1\_1}} := 2 \cdot I_{\text{load}} \quad I_{\text{load\_R1\_1}} = 305.57 \text{ A}$$

$$I_{\text{Load\_R1\_0max}} := 2I_{0\_load\_max} \quad I_{\text{Load\_R1\_0max}} = 61.11 \text{ A}$$

- Load current at 12.47kV breaker (B3)

$$I_{\text{load\_B3\_1}} := 3 \cdot I_{\text{load}} \quad I_{\text{load\_B3\_1}} = 458.36 \text{ A} \quad \sqrt{3} \cdot 12.47 \text{kV} \cdot 458.36 \text{ A} = 9.9 \times 10^6 \text{ W}$$

$$I_{\text{Load\_B3\_0max}} := 3I_{0\_load\_max} \quad I_{\text{Load\_B3\_0max}} = 91.67 \text{ A}$$

- Load current on 138kV system (B1 and B2): two approaches:

**A.** Assume that the only feeder supplied by the transformer is the one we're modeling:

$$I_{load\_B2\_a} := I_{load\_B3\_1} \cdot \left( \frac{V_{BL}}{V_{BH}} \right) \quad I_{load\_B2\_a} = 41.42 \text{ A}$$

**B.** Assume that there are other feeders too and the transformer is loaded to 80% of its MVA rating (so 40 MVA):

$$I_{load\_B2\_b} := 0.8 \cdot \left( \frac{50\text{MVA}}{\sqrt{3} \cdot V_{BH}} \right) \quad I_{load\_B2\_b} = 167.35 \text{ A}$$

*Note:* There won't be any zero sequence imbalance current on the HV side due to transformer connection.