

ECE 528 – Understanding Power Quality

<http://www.ece.uidaho.edu/ee/power/ECE528/>

Paul Ortmann
portmann@uidaho.edu
208-733-7972 (voice)

Lecture 4

1

Today...

- Power electronics review
- Common devices and topologies
- The Power Quality perspective on power electronics

Lecture 4

2

What are Power Electronics?

- Power electronics refers to devices employing semiconductors to convert and control electrical energy
- Types of conversions:
 - magnitude
 - Frequency
 - Number of phases


Why are power electronics important to PQ?

- They cause harmonic distortion
- The presence of harmonic distortion from power electronics can affect the power system and other loads
- Power electronic devices have particular vulnerabilities when it comes to PQ
- The use of power electronic devices is increasing

How power electronics create harmonics

Generally, a power electronic device draws current in "pulses" from the power system.


Current waveform for a desktop computer.

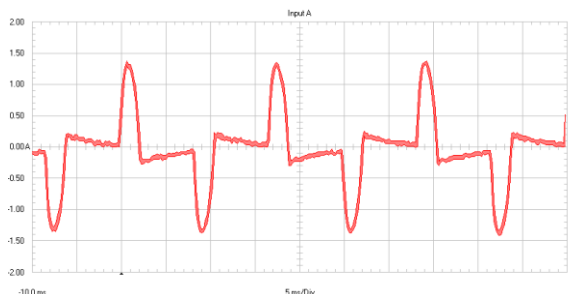

Non-linear current – harmonics



As we learned with the Fourier Series, the non-linear current can be "assembled" from sinusoids.

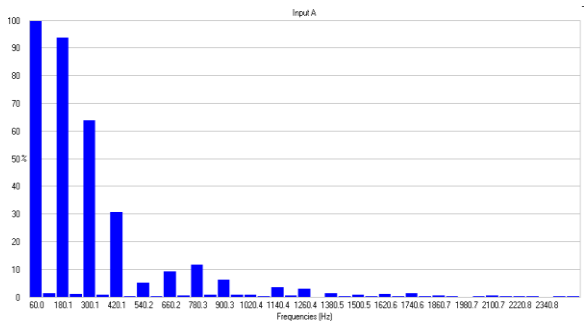Harmonic spectrum of the computer current. High 3rd, 5th, and 7th harmonics.




Why is the current drawn in "pulses"?

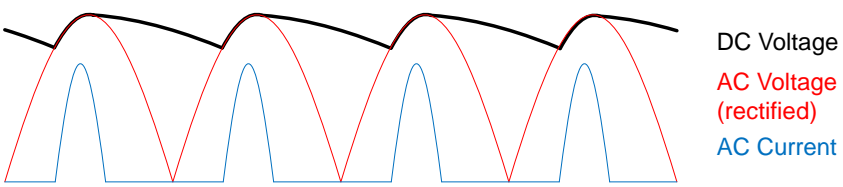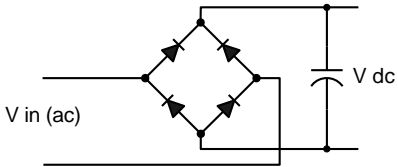The basic rectifier, filter-capacitor combination



Controlling the output: A regulated, linear DC power supply

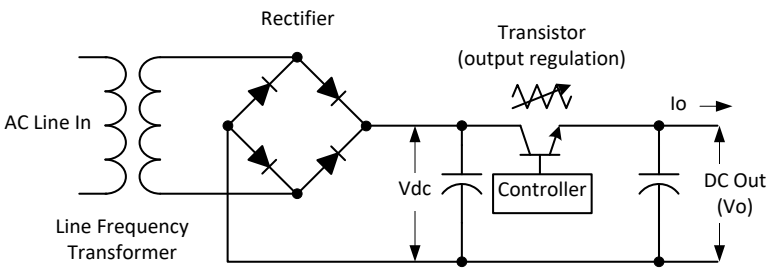We want the dc output voltage to be nearly constant despite load variations and supply voltage variations.




Transistor operated in active region as a variable resistor – varies voltage drop to regulate output voltage.

Losses in the linear dc supply

- $V_o < V_{dc}$ (output voltage < capacitor voltage)
- The power dissipated in the load is: $V_o \cdot I_o$
- The power dissipated in the transistor is: $P_{switch} = (V_{dc} - V_o) I_o$
- If $V_o = \frac{1}{2} V_{dc}$, then $P_{switch} = \frac{1}{2} (V_{dc}) I_o$
- The "switch mode" supply reduces losses significantly.

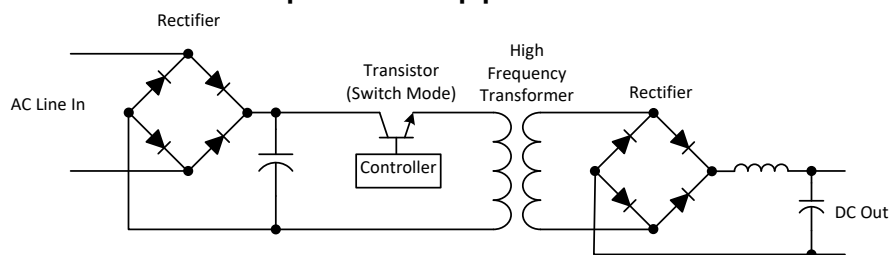Controlling the output: Switch mode power supplies



Transistor is operated as a **switch**; either on, or off.

Advantages:


Reduced losses and weight
More tolerant of input voltage variations

Disadvantages

High switching frequency – interference
Increased complexity

Topologies of converters

- The general switch mode power supply

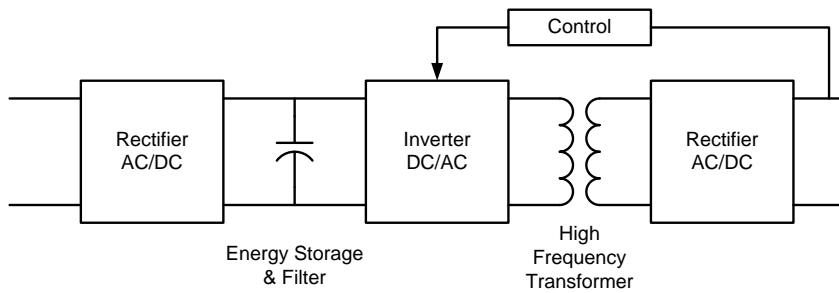


Lecture 4

11

Topologies of converters

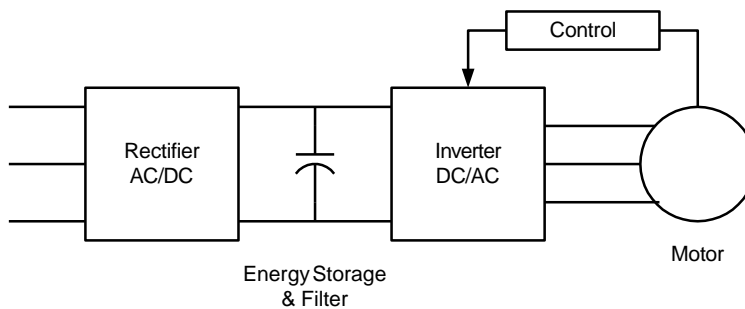- The variable frequency drive (VFD, ASD, VSD)



- See PSQ pages 214-223 or FPQ pages 201-205


Lecture 4

12

Where are power electronics?



- Almost everywhere...
 - Industrial systems
 - Motors (Drives)
 - Control systems
 - Lighting
 - Electronic ballasts in fluorescent lights
 - Dimming systems
 - Generation
 - Convert DC from solar, or AC from Wind to 60Hz AC.

Where are power electronics?

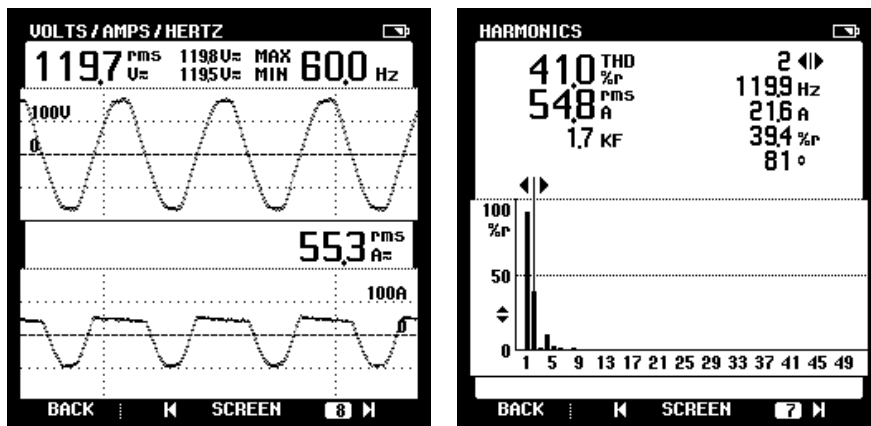

Some PQ issues with power electronics

- Impact on line voltage
 - “flat-topping” reduces ride through time of electronic loads during voltage sags
 - Distorted voltage results in distorted current, even in linear loads.

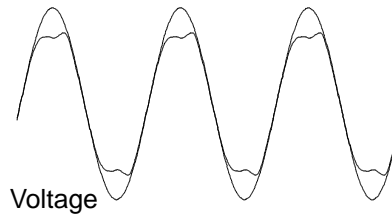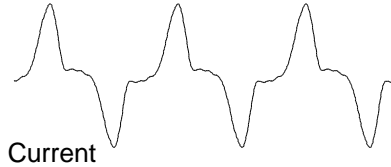


Lecture 4

15

Some PQ issues with power electronics

- Other line-side issues
 - Higher frequencies associated with harmonics and high switching frequencies can increase capacitive coupling.
 - Line voltage notching if rectifier uses thyristors

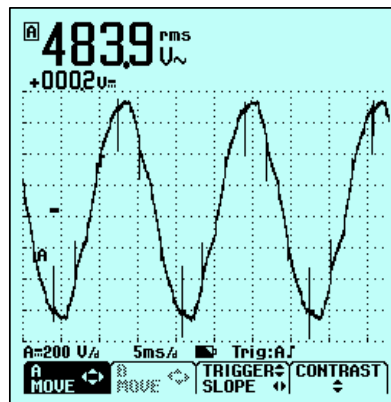


Lecture 4

16

Power electronics vulnerabilities

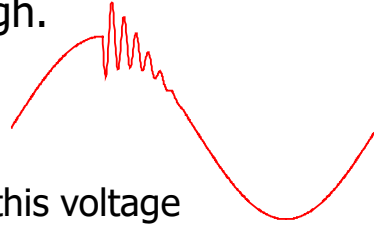
- Flat-topped voltage – reduces dc bus voltage, reducing stored energy for voltage sag ride-through.
- Capacitor switching.



What will happen when this voltage waveform passes through the rectifier and into the dc bus capacitor?


Load-side issues

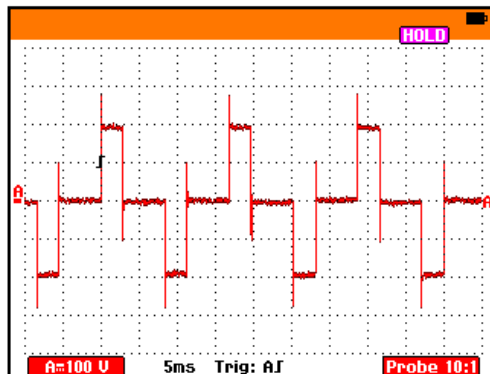- Primary issue is the fact that the "ac" output from a converter contains high frequency components.
- Voltage output of a small UPS.



Load side issues

Short rise time may affect load the same way a transient would. If the rise time here represents $\frac{1}{4}$ cycle, what would the frequency be?

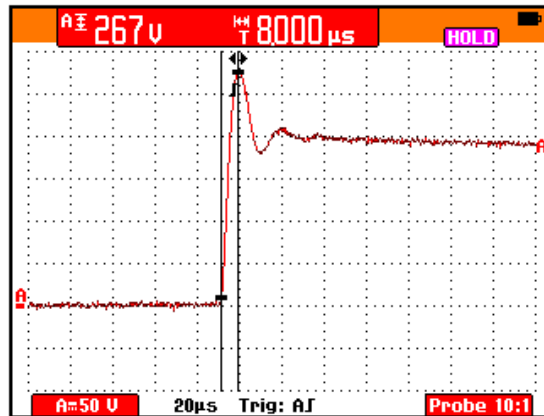

Lecture 4

19


Special problem with PWM drives

- A Pulse Width Modulated VFD can effectively vary both the voltage and frequency of its output signal.
- This is done by varying the width of output voltage pulses.
- Rise time can be 0.1 micro second.
- If the motor leads are "long," voltage reflections can lead to increased voltages at the motor terminals.


Lecture 4

20

Voltage reflections in PWM drives

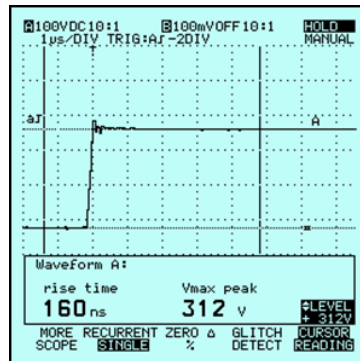

Normal leading edge
of PWM voltage pulse

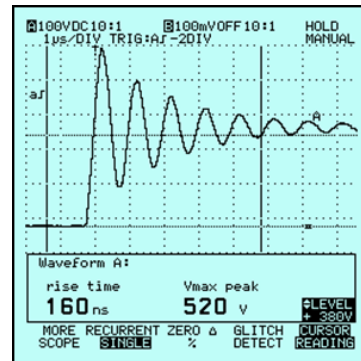

Leading edge of PWM
voltage pulse with
reflected voltage

Lecture 4

21

Problems for the investigator

- In some cases, handheld meters may give misleading readings.
- Average responding meters may read values significantly higher or lower than the True-RMS values of voltage and current, depending on the wave shape.
- Some problems, such as high frequency voltage reflections may require oscilloscopes or other more specialized monitoring equipment.

Lecture 4

22

Next time...

- Terminology
 - Read chapters 1 and 2 in FPQ and PSQ if you haven't
 - Skim both texts to familiarize yourself with them
- Investigation planning