

## ECE 528 – Understanding Power Quality

<http://www.ece.uidaho.edu/ee/power/ECE528/>

Paul Ortmann  
portmann@uidaho.edu  
208-733-7972 (voice)

### Lecture 17

1

## Today...

- Transient overvoltages
  - Ferroresonance
  - Capacitor switching transients
  - Switching capacitive and inductive loads

Lecture 17

2

## From lecture 16 - lightning detection

- A network of radio receivers in the US can help determine the precise time and location of lightning strikes.
- This can be used to rule-in or rule-out lightning damage.
- This system can also be used when planning new systems to determine the lightning environment in a particular area.

## Ferroresonance

- Symptoms
  - Audible noise
    - Due to "Magnetostriction" – the change in dimensions of the steel transformer core in the varying magnetic field
      - Described by witnesses as a "growling" sound
  - Overheating
    - Stray flux results in heating of the transformer and may lead to damage

## Ferroresonance


- Symptoms continued
  - Significant overvoltages
    - End-user equipment damage
    - Surge suppressor and lightning arrester damage
  - Flicker
    - Voltage may fluctuate over a wide range, resulting in noticeable light flicker.

Lecture 17

5

## Normal resonance

- The series RLC circuit:

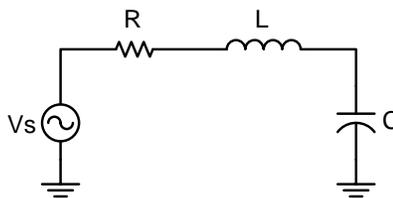


- In the series circuit, the current through the series elements must be the same
- The combined voltage across  $R$ ,  $L$ , and  $C$  must equal the applied voltage
- The voltage across individual elements is free to vary
- For ferroresonance to occur, there must be at least one point in the circuit where the voltage is not fixed

Lecture 17


6
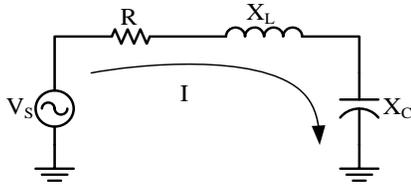
## Overvoltages in (nearly) resonant circuits



$$X_L = 2\pi fL \quad X_C = \frac{1}{2\pi fC}$$


$$V_S = I * (R + j(X_L - X_C))$$

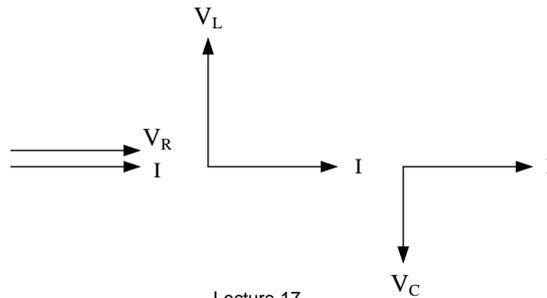


Lecture 17

7
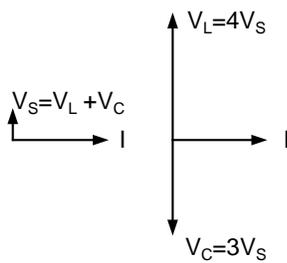
## Overvoltages in (nearly) resonant circuits



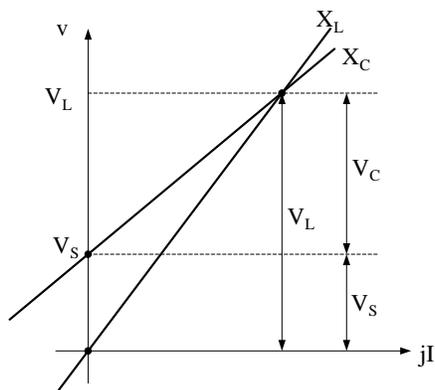Ignoring the resistance, the applied voltage is the difference between the voltage across the inductance and the voltage across the capacitance.




$X_L$  and  $X_C$  are described by the angles of the lines in the plot. Here each represents a fixed voltage/current relationship.

Lecture 17

8

## What's special about Ferroresonance

- Ferromagnetic materials (like steel transformer cores) exhibit hysteresis, and can saturate.
- The inductance is non-linear
- $X_L$  is no longer just a function of frequency, it is also a function of the applied voltage
- Circuit will have multiple stable and unstable operating points and may jump between points.

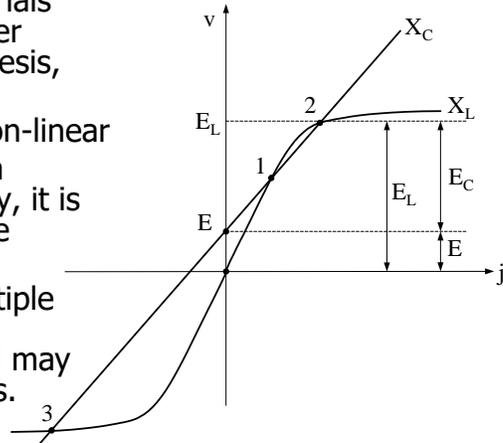

Lecture 17

9


## Necessary conditions for ferroresonance

- Capacitance with non-linear inductance
- At least one point where the voltage is not fixed by the external system
- Light loading – minimal damping

Lecture 17

10

## Example of ferroresonant condition

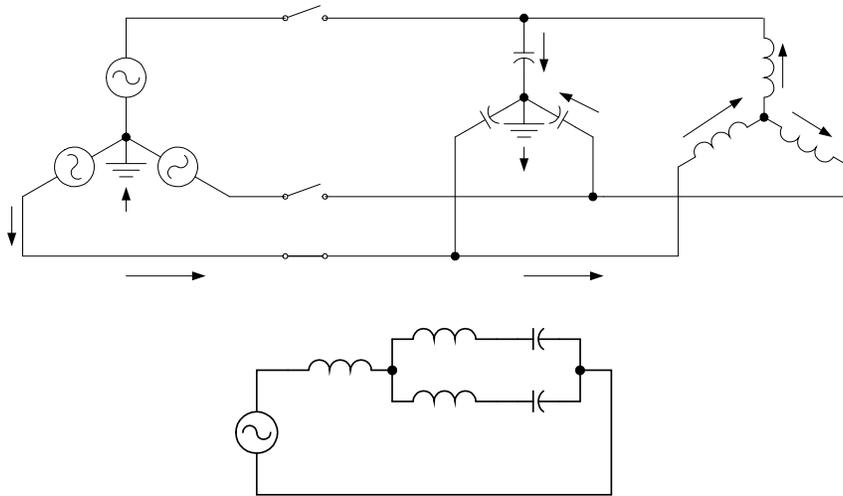

Lecture 17

11

## Preventing ferroresonance

- Use grounded-wye/grounded-wye systems
- Keep primary cable runs short
- Use three-phase switching and protection
- Place switch/protection directly upstream of the transformer
- Have some load on the transformer when switching
- Surge arrestors may be used to help suppress overvoltages

Lecture 17

12

## A real-world example


- Conditions:
  - Three-phase padmounted transformer
    - 75kVA, 34.5kV grounded-wye primary, 480Y/277V grounded-wye secondary
    - Intermittent fault inside transformer due to manufacturing defect
  - Padmounted vacuum fault interrupter immediately upstream
    - Set for single-phase tripping
  - Approximately 3500' of three-phase secondary cable underground to an irrigation panel (really!)
    - Irrigation system not operating

Lecture 17

13

## 36s after C phase opened on primary

### Event Details/Waveforms

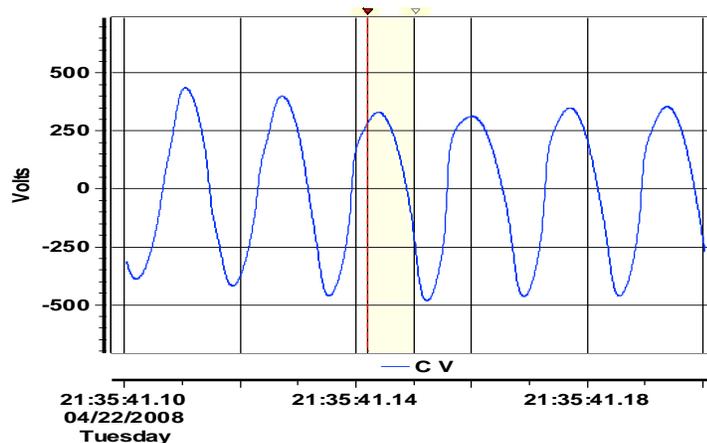


Lecture 17

14


### 3.5 minutes after C phase opened

#### Event Details/Waveforms

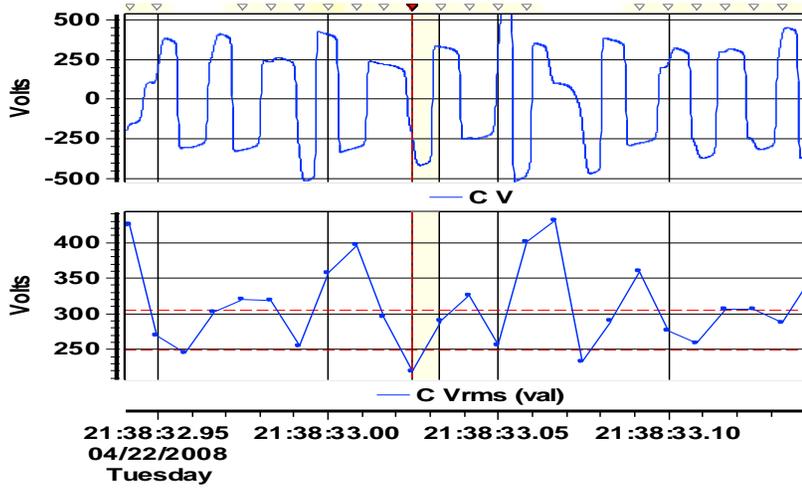

### Frequencies in the ferroresonant voltage


#### Waveform harmonics

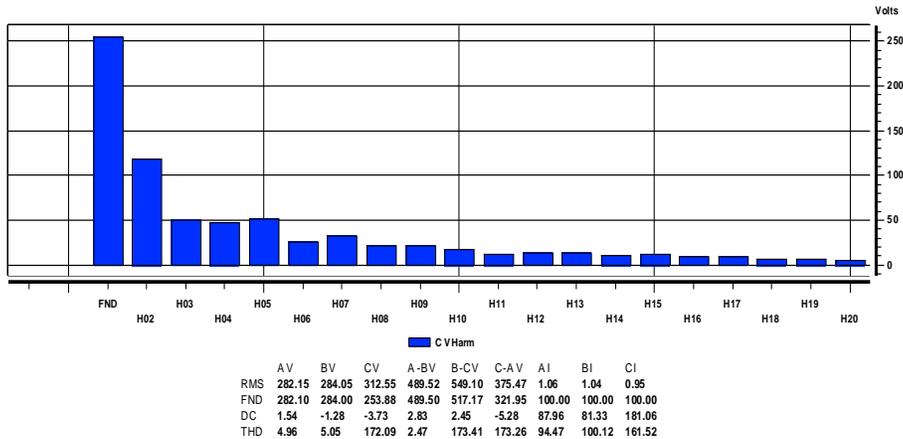

## Switching capacitive and inductive loads

- Capacitive loads:

- Voltage cannot change instantaneously
- **Closing the switch** when there is a large voltage across it can lead to a large current inrush transient
- The current transient results in an oscillatory voltage transient
- De-energizing capacitive loads is generally not an issue; voltage peaks at current zero, but voltage across switch can still be low

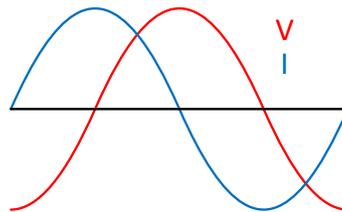


Lecture 17

17

## Switching capacitive and inductive loads

- Inductive loads:

- Current cannot change instantaneously
- **Opening the switch** when there is a large current through it can lead to a large voltage transient
- Voltage transient may cause switch to restrike and may impact other equipment
- Energizing inductive loads is generally not an issue

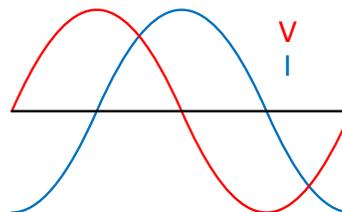

Lecture 17

18

## Capacitor switching transients


- Symptoms

- May follow a regular “schedule”
- Variable speed drives and other rectifier-based loads may trip
- Theoretical peak is 2 p.u. Damping normally results in transients with peaks of around 1.3 to 1.4 p.u.
- Over-currents accompany the voltage transients
- Voltage transient may be magnified at low-voltage capacitors in customer facilities

Lecture 17

19

## Capacitor switching transient

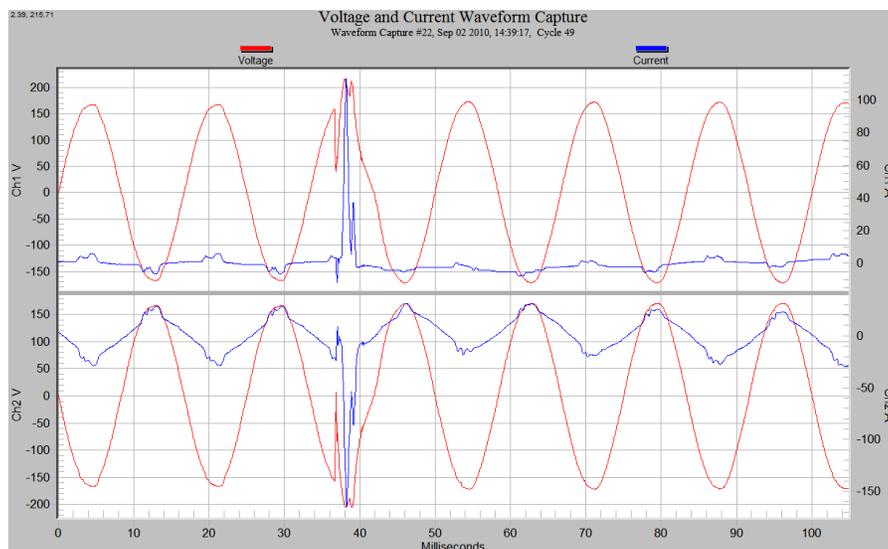

Lecture 17

20

## Capacitor switching transient magnification

Voltage magnification is generally most severe if:

- High voltage (HV) capacitor is much larger than low voltage (LV) capacitor
- Frequency of HV transient is close to resonant frequency of LV transformer in series with the LV capacitor
- Damping is low – LV system is lightly loaded

## Capacitor switch restrike

- When opening, a capacitor is left charged to nearly peak system voltage.
- Internal resistors dissipate this stored energy slowly
- If switch restrikes, voltage on capacitor is 180 degrees out of phase with applied voltage, and resulting voltage overshoot is doubled.
- Theoretical peak voltage transient is 3 p.u. on first restrike, 5 p.u. on second restrike.

## Mitigating capacitor switching transients – utility system

- Scheduling – switch at a different time
- Use pre-insertion resistors to damp the inrush and reduce the peak of the transient
- Synchronous switching – usually at voltage zero crossing
- Move the capacitor to provide some system impedance between it and loads

## Mitigating capacitor switching transients – customer system

- Address problem loads only – line reactors on variable speed drives (see PSQ p. 191)
- Use MOVs to clamp the transient peak
- Turn customer capacitors into harmonic filters – inductor in series with capacitors – similar to solution for variable speed drives

### Mitigating inductive load switching transients

- Mitigate Electrical fast transient (EFT) with electrical and physical separation (PSQ p. 192)
- Apply “snubbers” at switches to absorb transient energy
- Apply surge suppressors (MOVs).
- Apply a combination of snubbers and surge suppressors (see Littlefuse application note)

### Next time...

- Switching transients
- Transient protection summary