

## ECE 528 – Understanding Power Quality

<http://www.ece.uidaho.edu/ee/power/ECE528/>

Paul Ortmann  
portmann@uidaho.edu  
208-733-7972 (voice)

### Lecture 24

1

## Today...

- Harmonic control devices
  - In-line reactors (chokes)
  - Zigzag transformers
  - Passive filters
  - Active filters
  - Designing a harmonic filter

Lecture 24

2

## In-line reactors (chokes)

- Simply a series inductance
  - Presents a series impedance that is directly proportional to frequency
  - Forces DC bus capacitor to charge more slowly
  - Additional benefit:
    - Reduces DC bus overvoltages due to capacitor switching transients – reduced nuisance tripping



## In-line reactors (chokes)


- Sizing the in-line reactor
  - Line reactors are typically described as “a 3% reactor”, 3% to 5% are common
  - Size is based on the VA base of the drive

$$X_{L\_5\%} := 0.05 \frac{(V_{\text{base}})^2}{\text{VA}_{\text{base}}} \qquad L = \frac{X_L}{2\pi \cdot f}$$

- Inductance in Henrys is based on  $X_L$  at the fundamental frequency

## Zigzag transformers

- Used for zero-sequence currents
- Commercial facilities – single-phase non-linear loads
- Provides a path for zero-sequence currents between the phase and neutral conductors
- Useful in existing facilities

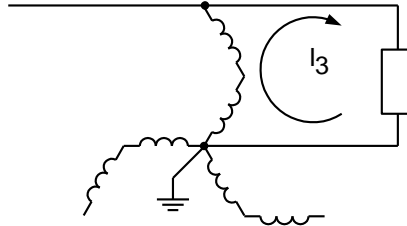

Lecture 24

5

## Passive filters



- Capacitors and inductors can be arranged to produce high or low impedances at certain frequencies
- Resistors can be added to provide damping
- Shunt passive filters – provide a low-impedance alternate path
- Series passive filters – increase the series impedance for certain frequencies

Lecture 24

6

## Passive filters

- Shunt passive filters
  - Notch filter is the most popular
  - May employ delta or wye connected capacitors connected to the line or neutral through inductors

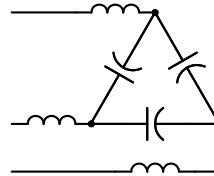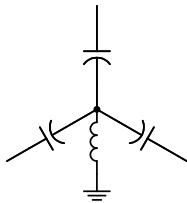

Lecture 24

7

## Passive filters

- Series passive filters
  - Provide a high impedance to the target harmonic
  - Must carry full load current
  - Not practical for multiple harmonics
  - Useful in single-phase applications

Lecture 24

8

## Low-pass broadband filter

- Combines shunt and series elements
  - Low impedance for low frequencies
  - Hi impedance for high frequencies
  - (See PSQ p.287)
  - Several basic “building blocks” of the low-pass filter can be placed in series to produce a steeper slope in the frequency response

## General approach with passive filters

- Start at the lowest harmonic of concern
- Tune filters slightly lower than the target harmonic
- Check for resonant points creating high impedances
- If system impedance changes, re-evaluate filter

## Active filters


- Use power-electronics to inject the missing current in the non-linear load's current waveform
- Results in minimal distortion on the source side
- No resonance concerns
- May also correct power factor and flicker

## Filter design example FPQ p. 259-266

- Goals – improve displacement power factor and filter 5<sup>th</sup> harmonic
  - Load is 480V, 3-ph., 1600kVA, DPF=0.75 lag.
  - Load current has 20% 5<sup>th</sup> harmonic
- We can address both the low power factor and the high 5<sup>th</sup> harmonic current with a shunt filter
- Note – both texts contain this example. Both texts contain errors. Underlined material on slides is corrected or clarified from texts. References are to the FPQ text.

## Filter design procedure

- Pick tuned frequency
- Calculate VAR requirements
- Calculate reactor size
- Determine filter duty requirements
  - Fundamental
  - Harmonic
  - RMS current and peak voltage
- Check capacitor ratings
- Calculate filter frequency response – check for resonance at other harmonics

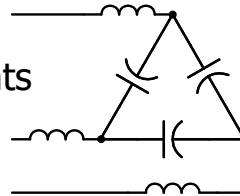

Lecture 24

13

## Filter design example

- Notch picked at 4.7<sup>th</sup> harmonic or 282Hz
- VAR requirement to improve DPF to 98% is 814.63kVAR
- Compute capacitive reactance (wye) of the FILTER based on VAR need: 0.2828 ohm. (eq. 7.21)
- Capacitive reactance of the filter's capacitors is higher because inductive reactance will cancel some (eq. 7.22)

Lecture 24

14

## Filter design example

- Capacitive reactance: 0.2962 ohms (eq. 7.24)
- Capacitive reactance and voltage rating determines kVAR rating:  
777.75kVAR at 480V (eq. 7.25)  
1215.2kVAR at 600V  
We'll use 750kVAR at 480V as a first try.
- Filter reactor's fundamental inductive reactance is calculated from capacitor size and harmonic number:

$$X_{\text{cap}} := \frac{(480\text{V})^2}{\text{kVAR}_{\text{cap}}} = 0.307 \Omega \quad (\text{eq. 7.26})$$

## Filter design example

- Inductance at fundamental:

$$X_L = \frac{X_{\text{cap}}}{h^2} \quad L = \frac{X_L}{2\pi 60\text{Hz}} \quad L = 0.0369\text{mH}$$

(for 480V capacitors)      (from eq. 7.29)

- Duty requirements
  - We compute the fundamental and harmonic voltage and current for the capacitors separately, then add these values to get the total RMS current and peak voltage.



## Filter design example

- Eq. 7.34 - Fundamental VARs produced by the capacitor

$$Q_{\text{cap\_fund}} = \sqrt{3} \cdot I_{\text{filt\_fund}} \cdot V_{\text{cap\_fund}}$$

- This is **not** the fundamental reactive power produced by the filter. Fundamental reactive power produced by the filter is: (**not in texts**)

$$\text{kVAR}_{\text{fund}} = \sqrt{3} \cdot I_{\text{filt\_fund}} \cdot V_{\text{LL\_Sys}} \quad \text{or} \quad \text{kVAR}_{\text{fund}} = 3 \cdot I_{\text{filt\_fund}}^2 \cdot X_{\text{filt}}$$

- Your filter design must produce enough reactive power at 60Hz to improve the power factor as required. PSQ's example does (it produces 565.6kVAR). FPQ's example doesn't (it produces 785kVAR).

## Filter design example

- Notes on duty calculations:
  - Fundamental duty is straightforward
    - Depends only on net filter reactance and the line voltage
  - Harmonic duty
    - Includes harmonic current from load AND source
    - Reactance calculations are at the harmonic frequency
  - "Total" duty
    - Sum of fundamental and harmonic duty

## Filter design example

- Check capacitor rating limits
  - Table 7.3 in FPQ or 6.4 in PSQ is based on IEEE standards (RMS current limit is 135%) PSQ lists 180%.
- Check parallel resonance below notch frequency
  - 3.95<sup>th</sup> harmonic – nearly the 4<sup>th</sup>, which is acceptable because 4<sup>th</sup> harmonic distortion is normally low
- Check effect of component variations.  
Parameters of real-world components vary.  
*(not required on midterm problem)*

## Next time

- Conclude Harmonics
  - Neutral loading
  - Interharmonics
  - Standards