

U_I

Voltage Sourced Converter Topologies

*ECE529**Lecture 19*

- Single phase bridge (H-bridge)
- Three phase bridge
 - » Called 6-pulse or 6-step converter
 - » Often connect several converters together with phase shifted inputs to improve voltage waveforms
 - Multipulse arrangements
 - Use magnet circuit configurations to improve waveform
 - Can reduce voltage ratings on devices too

Voltage Source Converter

1

Spring 2006

 U_I

Higher Voltage VSC Topologies

*ECE529**Lecture 19*

- Multilevel converter
 - » Originally called neutral point clamped
 - » Allows higher voltage ratings without series connected devices
 - » Smoother voltage waveforms without as many bridges (increased number devices)
- Chain Link Converters

Voltage Source Converter


2

Spring 2006

VSC Modeling in EMTP/ATP - Six Step

- VSC appears to ac system as controlled ac voltage source
- The equivalent source is able to vary voltage magnitude
- A conventional VSC bridge varies phase angle and not voltage magnitude

Basic VSC Relations

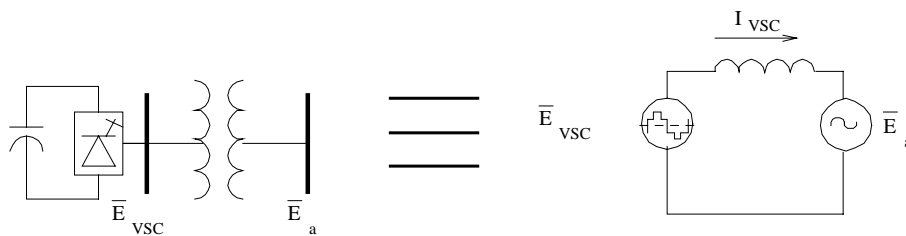

$$V_1 \angle \delta \quad \text{where } -\pi/2 < \delta < \pi/2$$

$$I_a \angle -\phi$$

$$V_1 = M_a E_{VSC}$$

U_I

Basic VSC Relationships

*ECE529**Lecture 19*

- Must have a capacitive ac source to operate in line-commutated mode
- Majority of VSC applications require self-commutating switches
- Bi-directional switch currents
- Switch voltage does not reverse
- Modules (connect in series or parallel) if no PWM

Voltage Source Converter

5

Spring 2006

 U_I

Fundamental Component Representation

*ECE529**Lecture 19*

- Only the fundamental component of voltage transfers useful power
- Approximate steady-state behavior with fundamental component equations
- AC equivalent is a controlled voltage source
- DC equivalent is a controlled current source in parallel with a capacitor

Voltage Source Converter

6


Spring 2006

U_I Fundamental Component Model

ECE529

Lecture 19

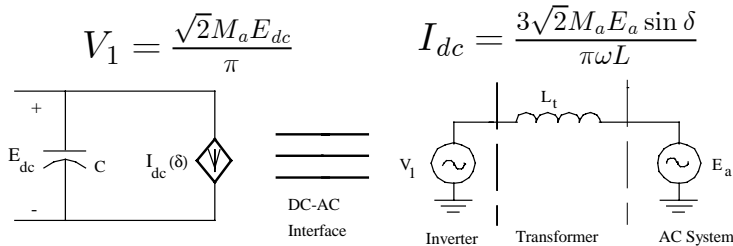- Based on power balance equations
- M_a is PWM Modulation Ratio
- E_{dc} varied with phase angle if no DC source



Voltage Source Converter

7

Spring 2006

U_I Device Models

ECE529

Lecture 19

- A VSC will require self-commutating switch
- Large applications will utilize GTO's or IGBT
- Requires representation of current reversal
- Detailed turn-on/turn-off not needed
- Several representations possible
- Paired with anti-parallel diodes to allow current reversal



Voltage Source Converter


8

Spring 2006


- Requires a TACS controlled switch to represent external gate pulses
- Options:
 - » EMTP Type 13 switch (with or without anti-parallel diode)
 - » EMTP Type 11 switch using OPEN/CLOSE input as GTO with a second Type 11 switch as the anti-parallel diode.

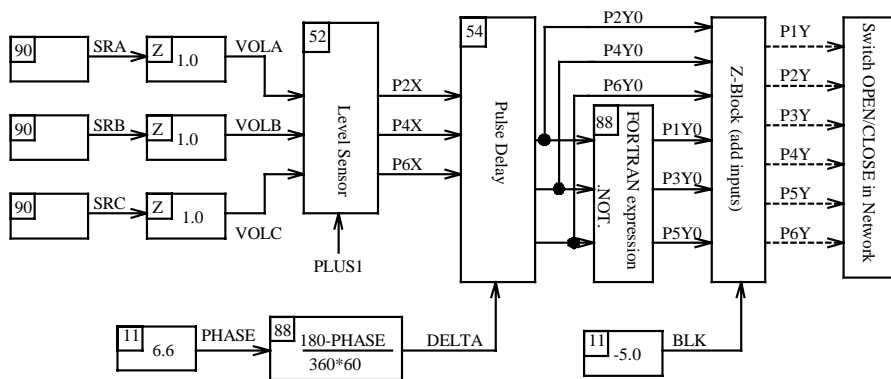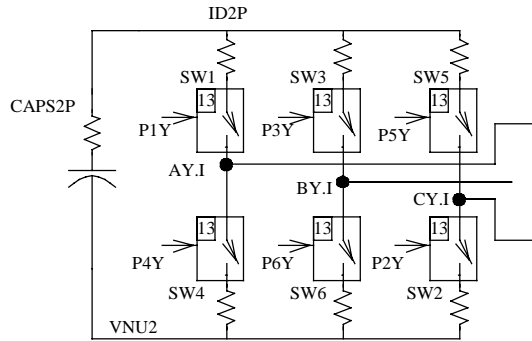- Allow to stay on for entire period
- Bidirectional current in switch, no need for added diode in normal operation
 - » Potential for errors, so better to add diode
- Send gate pulses to OPEN/CLOSE input
- OPEN > 0.0 ----> Close next time step
- OPEN <= 0.0 ----> Open next time step



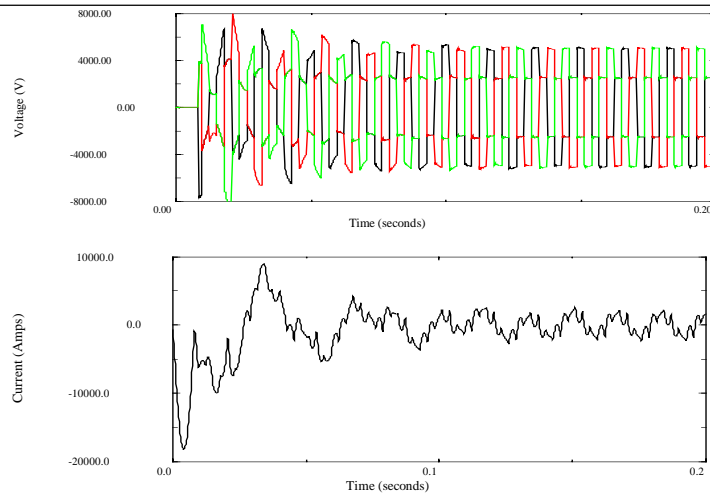

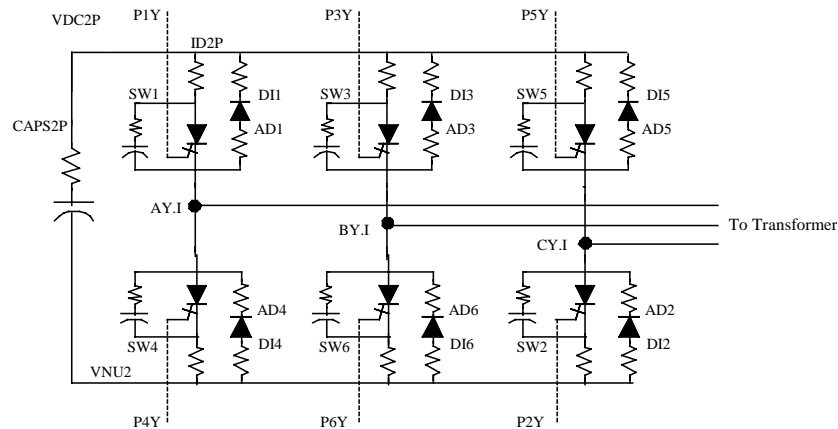- Use short GRID pulse to turn on as thyristor
 - » Negative OPEN/CLOSE to open switch
- Or can use the open/close signal as did with type 13
- Must add anti-parallel diodes (type 11 switch with no TACS Input)
- Requires RC turn-off snubbers




- In both cases can use ramp generator
- May want PLL due to voltage distortion
- Slightly different gate pulses

U_I

Simulation Results:

ECE529

Lecture 19

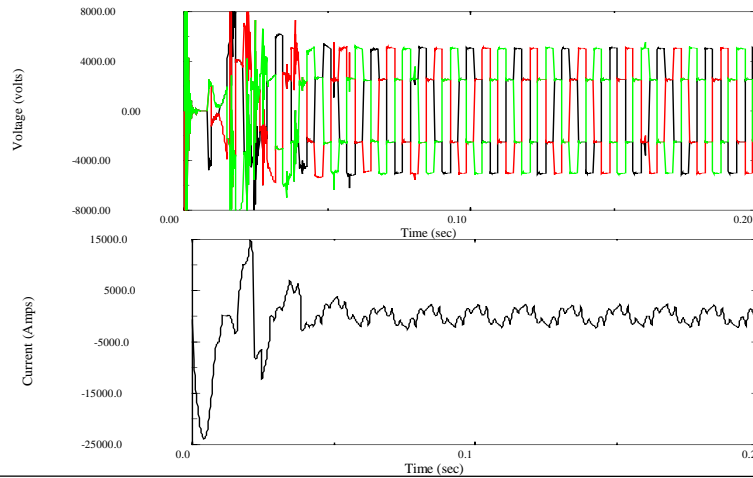

Voltage Source Converter

17

Spring 2006


U_I

Simulation Results: Gate Pulses


ECE529

Lecture 19

Type 13

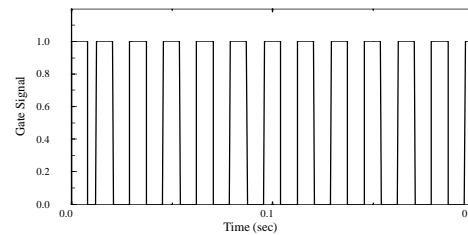

Type 11

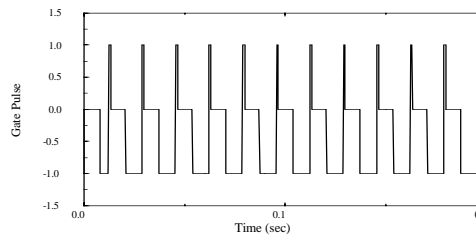

Voltage Source Converter

18

Spring 2006

Using 6-Step Converters

- Indirect control of V_q
 - » Can't easily go from capacitive to inductive series voltage injection
 - » Draw real power to increase V_q
 - » Discharge capacitor to decrease V_q
- Multipulse configuration to clean up voltage waveform
 - » Requires multiwinding transformer

PWM Converters


- Better to use type 13 switch with anti-parallel diode (type 11)
- Can use same circuit as earlier
- Gating for the type 11 case too difficult
- Generate carrier signal synchronized with power system

U_I

PWM Converters- Circuit Configuration

ECE529

Lecture 19

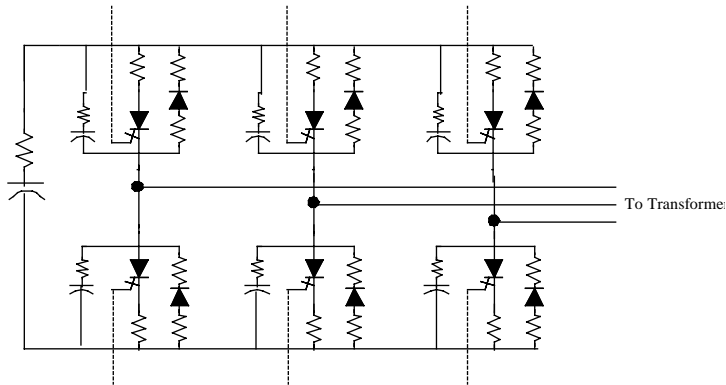

Voltage Source Converter

21

Spring 2006