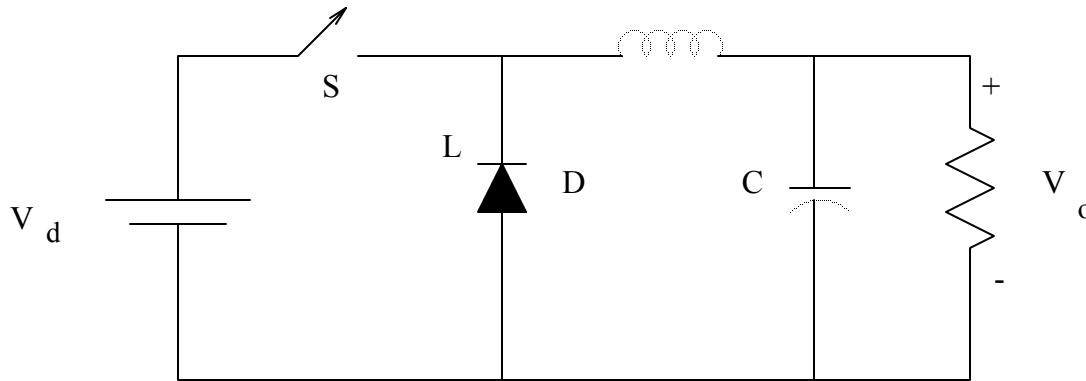


ECE 320: Lecture 39

Notes


Single Switch DC-DC Converter Configurations:

1. Buck Converter (or down converter). The output voltage is less than or equal to the input volta



$$\frac{V_o}{V_d} = D \qquad \frac{I_o}{I_d} = \frac{1}{D}$$

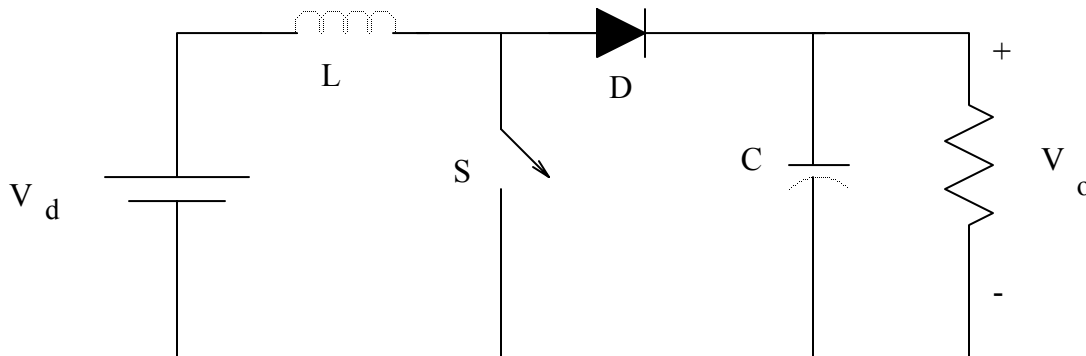
2. Boost Converter (up converter). The output voltage larger than the input voltage. The inductor current is on the input, and it is pumped up with the switch.



Ideal, steady-state continuous conduction:

$$\frac{V_o}{V_d} = \frac{1}{1 - D} \qquad \frac{I_o}{I_d} = 1 - D$$

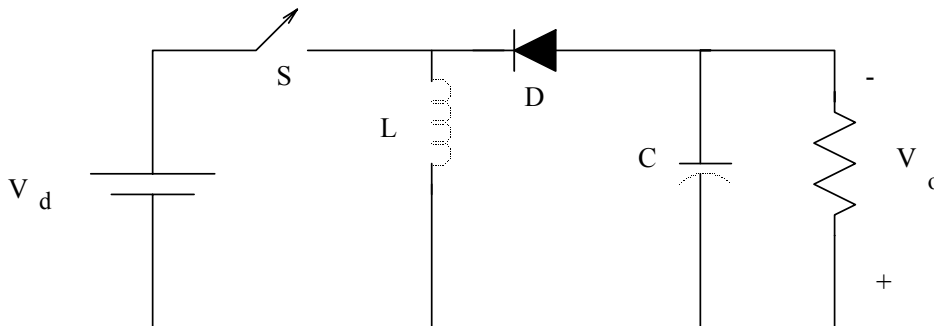3. Buck-Boost Converter (up/down converter). The output voltage can be smaller or larger than the input voltage. The inductor current is now an intermediate stage. Note output voltage polarity



Ideal, steady-state continuous conduction:

$$\frac{V_o}{V_d} = \frac{D}{1-D} \quad \frac{I_o}{I_d} = \frac{(1-D)}{D}$$

Polarity of the voltage and the current is reversed from the other two topologies.

Boundary of Discontinuous Conduction Through The Inductor:

- Boost Converter

When switch is closed, the slope of the inductor current is: :

$$\frac{\Delta i_L}{t} = \frac{V_d}{L}$$

When the switch is open, the slope is:

$$\frac{\Delta i_L}{t} = \frac{V_d - V_o}{L}$$

Since the current follows these slopes while the switch position is maintained, in continuous conduction the steady-state Current Ripple in inductor is:

$$\Delta i_L = \frac{V_d}{L} \cdot D \cdot T_s = \frac{(V_d - V_o)}{L} \cdot (1-D) \cdot T_s$$

The average input current is now the average current through the inductor

Power Balance:

$$P_o = \frac{V_o^2}{R} \quad \text{and} \quad \frac{V_o}{V_d} = \frac{1}{1-D}$$

So:

$$P_o = \frac{V_d^2}{(1-D)^2 \cdot R}$$

But: $P_o = P_i = V_d \cdot I_{Lave}$

Therefore: $\frac{V_d^2}{(1-D)^2 \cdot R} = V_d \cdot I_{Lave}$ or $I_{Lave} = \frac{V_d}{(1-D)^2 \cdot R}$

Adding on the current ripple, the minimum current through the inductor is:

$$I_{Lmin} = I_{Lave} - \frac{\Delta i_L}{2}$$

Adding on the current ripple, the maximum current through the inductor is:

$$I_{Lmax} = I_{Lave} + \frac{\Delta i_L}{2}$$

At the boundary of discontinuous conduction we see:

$$I_{Lmin} = 0 = \frac{V_d}{(1-D)^2 \cdot R} - \left(\frac{V_d}{2 \cdot L} \right) \cdot D \cdot T_s$$

So, we can determine L_{min} by solving this equation for L :

$$L_{min} = \frac{D \cdot (1-D)^2 \cdot R \cdot T_s}{2}$$

We can also state this in terms of voltages and currents using:

$$R = \frac{V_o}{I_o} \quad I_{oB} = (1 - D) \cdot I_d = (1 - D) \cdot I_{LB}$$

$$L_{min} = \frac{D \cdot (1 - D)^2 \cdot V_o \cdot T_s}{2 \cdot I_{oB}} = \frac{D \cdot (1 - D) \cdot V_o \cdot T_s}{2 \cdot I_{LB}}$$

or in terms of the output current at the boundary:

$$I_{oB} = \frac{D \cdot (1 - D)^2 \cdot V_o \cdot T_s}{2 \cdot L_{min}}$$

- Buck-Boost Converter

When switch is closed, the slope of the inductor current is :

$$\frac{\Delta i_L}{t} = \frac{V_d}{L}$$

When the switch is open, the slope is:

$$\frac{\Delta i_L}{t} = \frac{V_o}{L}$$

Since the current follows these slopes while the switch position is maintained, in continuous conduction the steady-state Current Ripple in inductor is:

$$\Delta i_L = \frac{V_d}{L} \cdot D \cdot T_s = \frac{(-V_o)}{L} \cdot (1 - D) \cdot T_s$$

Now the inductor current isn't the input current or the output current. It is only an intermediate step

- At the boundary between continuous and discontinuous conduction, we will have:

$$I_{LB} = \frac{1}{2} \cdot I_{Lpeak} = \frac{\Delta i_L}{2} = \left(\frac{1}{2 \cdot L} \right) \cdot D \cdot T_s \cdot V_d$$

or we could also write this in terms of V_o as:

$$I_{LB} = \left(\frac{1}{2 \cdot L}\right) \cdot D \cdot T_s \cdot \left(\frac{1-D}{D}\right) \cdot V_o = \left(\frac{1}{2 \cdot L}\right) \cdot T_s \cdot (1-D) \cdot V_o$$

or

$$L_{min} = \left(\frac{1}{2 \cdot I_{LB}}\right) \cdot T_s \cdot (1-D) \cdot V_o$$

However we usually want this in terms of the output current. If we write a node equation at the terminal of the inductor

$$I_o = I_L - I_d \quad \text{or}$$

$$I_L = I_o + I_d = I_o + I_o \cdot \left(\frac{D}{1-D}\right) = I_o \left(\frac{1-D+D}{1-D}\right) = \frac{I_o}{1-D}$$

$$I_{LB}(1-D) = \left[\left(\frac{1}{2 \cdot L}\right) \cdot T_s \cdot (1-D) \cdot V_o\right] \cdot (1-D)$$

$$I_{oB} = \left(\frac{V_o}{2 \cdot L}\right) \cdot T_s \cdot (1-D)^2$$

Uncontrolled Rectifier Circuits (Chapter 5)

- We have discussed the use of DC-DC converters to regulate a dc voltage to level different than the input dc voltage.
- But we haven't discussed where this dc voltage comes from.
- In most applications we start with the 120Vrms from a wall outlet
- Now we want to convert that ac with a rectifier circuit
- Next week we will combine the rectifier with a transformer and a dc-dc converter in one circuit