

## **ECE 320: Lecture 44**

### **Notes**

#### ***Misc Notes:***

- I have an ECE faculty meeting during office hours today
- Homework #9 due at 6:00pm instead of 5:00pm
- Hw 9 solutions will be posted this weekend.
- I will try to get missing lecture summaries on the web page, but I doubt that I will be get al them up before tuesday. The material that is missing is all covered in Mohan.

#### ***Final Exam***

- Tuesday, 10:00am - 12:00pm
- 1 sheet (both side) of 8.5in x 11in paper with notes
- Sample exam solutions will be posted this weekend

#### ***Topics***

Exam I material:

- Single phase AC circuits (time domain and phasors)
- Complex power, real power, reactive power, and power factor
- Hamonics analysis
  - \* Fourier series
  - \* Fundamental component RMS versus true RMS
  - \* Total Harmonic Distortion
  - \* Crest Factor
  - \* True power factor, displacement factor, distortion factor
- Transformers
  - \* Ideal transformer relationships
  - \* Transformer equivalent circuit with resistances and inductances
  - \* Short circuit/open circuit tests
  - \* Transforming impedances across the transformer
  - \* Voltage regulation
  - \* Efficiency
- Magnetic circuit analysis
  - \* Ampere's Law
  - \* Faraday's Law
  - \* Lenz's Law
  - \* Relationships between H, B,  $\phi$ , e
  - \* Reluctance
  - \* Magnetic saturation
  - \* Computing inductance
  - \* Detemining leakage and magnetizing inductances of transformers

## Exam 2 Material

- Speed Voltage
- Torque production
- Basic DC generator and DC motor operation
- Separately excited machine
- Determine speed if you know  $E_a$  and  $I_f$
- $E_a \cdot I_a = \tau \cdot \omega$
- Shunt Field machine
- Series excited
- Compound excited
- Motor starting behavior
- Speed control
- Fundamentals of power electronics
- Buck converter
- Basic relationships
- Determination of boundary of discontinuous conduction

## New Material Since Exam 2

The exam will be weighted a little more heavily on this material

- Boost and Buck-Boost Converters
- Input/output relationships for each type of dc-dc converter
- Determine boundary of discontinuous conduction for each
- Determine peak to peak voltage ripple for each dc-dc converter or size the capacitor to accomplish a specific ripple
- Closed loop current regulation-- why useful?
- Single phase diode rectifiers:
  - \* Basic circuit
  - \* Typical current waveforms for resistive, R-L and parallel R-C dc loads
  - \* Commutation overlap and impact on dc voltage in continuous conduction
  - \* Continuous versus discontinuous conduction
  - \* For a capacitor filtered converter determine peak dc current and initial conduction angle for the dc current
  - \* Determine true power factor given the current waveform.