

ECE 320: Lecture 28 Examples

1. For the shunt dc motor described below:

Prated := 30hp	ILrated := 110A
VT := 240V	N _F := 2700 turns/pole
n _{rated} := 1200M	N _{SE} := 12turns/pole
R _A := 0.19ohm	R _F := 75ohm
Rs := 0.02ohm	R _{adj} ranges from 100 to 400 ohm


(a) If the resistor, R_{adj} is adjusted to 175 ohms, what is the rotational speed of the motor at no load conditions?

$$R_{adj1} := 175\text{ohm}$$

$$E_{A1} := VT \quad \text{Therefore, } I_A=0 \text{ (as expected for no-load)}$$

$$I_{F1} := \frac{VT}{R_F + R_{adj1}} \quad I_{F1} = 0.96 \text{ A}$$

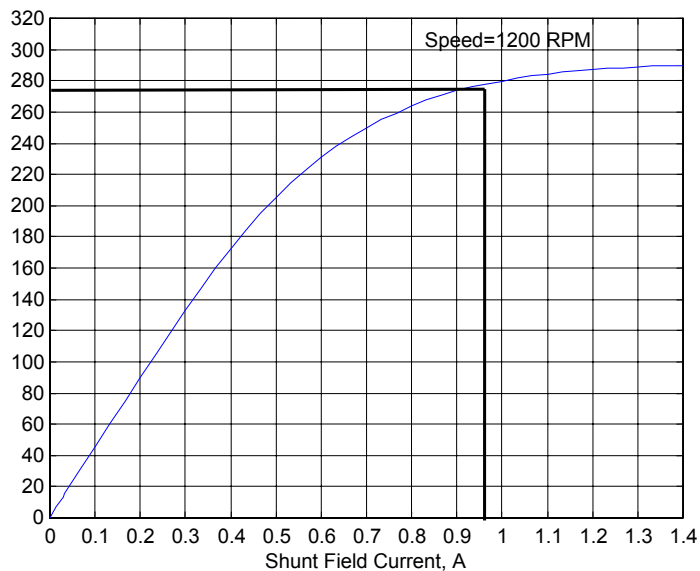Using the voltage characteristic below, determine the E_A resulting from I_{F1} at 1200 RPM



From the curve, we see that:

$$E_{a1200} := 277V$$

Find no-load speed for this case:

$$n_{\text{no load}} := 1200 \cdot \frac{E_{A1}}{E_{a1200}} \quad n_{\text{no load}} = 1040 \quad \text{RPM}$$

(b) For the shunt dc motor described in the last problem:

Assuming no armature reaction, what is the speed of the motor at full load? What is the speed regulation of the motor?

$$I_{Afl} := I_{Lrated} - I_{F1} \quad I_{Afl} = 109.04 \text{ A}$$

$$E_{Afl} := V_T - I_{Afl} \cdot R_A \quad E_{Afl} = 219.28 \text{ V}$$

Since the field current hasn't changed (same terminal voltage), $E_{a1200} = 277 \text{ V}$ as before

$$n_{fl} := 1200 \cdot \frac{E_{Afl}}{E_{a1200}} \quad n_{fl} = 950 \quad \text{RPM}$$

$$\text{SpeedRegulation} := \frac{n_{\text{no load}} - n_{fl}}{n_{fl}} \quad \text{SpeedRegulation} = 9.448 \%$$

2. Series motor:

$$R_{tot} := 0.08 \text{ ohm} \quad \text{this is } R_a + R_{se}$$

$$V_t := 250 \text{ V} \quad n_{\text{base}} := \frac{1200}{1 \text{ sec}} \text{ RPM} \quad \omega_{\text{base}} := n_{\text{base}} \cdot \left(\frac{2\pi}{60} \right)$$

$$N_{se} := 25 \quad \text{turns} \quad \omega_{\text{base}} = 125.66 \frac{\text{rad}}{\text{sec}}$$

(a) Find torque if $I_a = 50 \text{ A}$

$$I_a := 50 \text{ A}$$

$$E_a := V_t - I_a \cdot R_{tot} \quad E_a = 246 \text{ V}$$

$$\text{MMF} := N_{se} \cdot I_a \quad \text{MMF} = 1250 \text{ A} \cdot \text{turns}$$

From the magnetization characteristic, determined at 1200 RPM, 1250 A-turns corresponds

$$E_{a\text{eff}} := 80 \text{ V}$$

$$n_{\text{actual}} := n_{\text{base}} \cdot \frac{E_a}{E_{a\text{eff}}} \quad n_{\text{actual}} = 3690 \text{ Hz RPM}$$

$$\omega_{\text{actual}} := n_{\text{actual}} \cdot \left(\frac{2 \cdot \pi}{60} \right) \quad \omega_{\text{actual}} = 386.42 \frac{\text{rad}}{\text{sec}}$$

$$\tau := \frac{E_a \cdot I_a}{\omega_{\text{actual}}} \quad \tau = 31.83 \text{ N}\cdot\text{m}$$

We can repeat this for additional operating points and get a torque-speed characteristic.

3. The machine below is connected as a shunt generator. The shunt field resistor R_{adj} is adjusted to 10 ohm, and the generator's speed is 1800 RPM.

$$R_a := 0.18 \text{ ohm} \quad V_f := 120 \text{ V} \quad R_f := 24 \text{ ohm}$$

$$N_f := 1000 \text{ turns/pole}$$


R_{adj} ranges from 0 to 30 Ohm

(a) What is the no-load terminal voltage of the generator?

Add the plot of V_T vs I_f on the no-load magnetization curve.

$$R_{\text{adj}} := 10 \text{ ohm} \quad R_{\text{shunt}} := R_f + R_{\text{adj}} \quad R_{\text{shunt}} = 34 \text{ ohm}$$

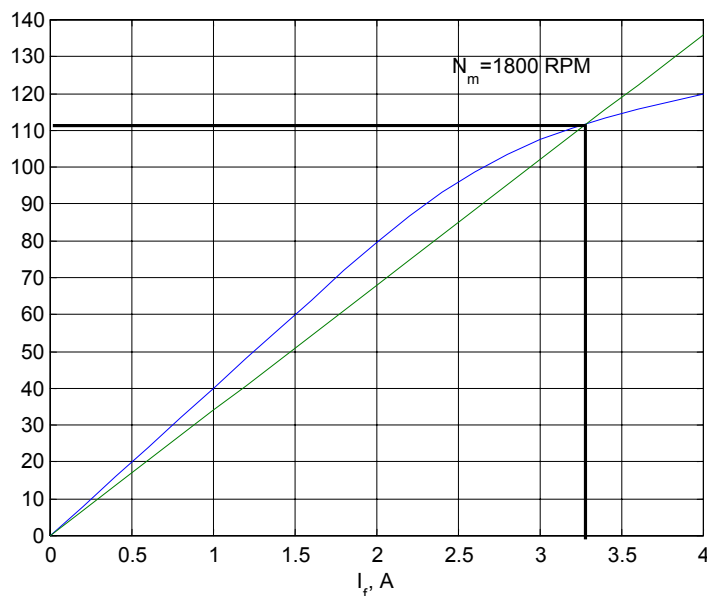The generator is operating at no-load, so the intersection between the V_T line and the magnetization curve is the no load voltage.



$$T_{\text{no-load}} := 112 \text{ V}$$

(b) Assuming no armature reaction, what is the terminal voltage of the generator with an armature current of 20A? 40A?


$$IA1 := 20A$$

$$\text{Voltage Drop: } V_{ra1} := IA1 \cdot Ra \quad V_{ra1} = 3.6V$$

$$IA2 := 40A$$

$$\text{Voltage Drop: } V_{ra2} := IA2 \cdot Ra \quad V_{ra2} = 7.2V$$

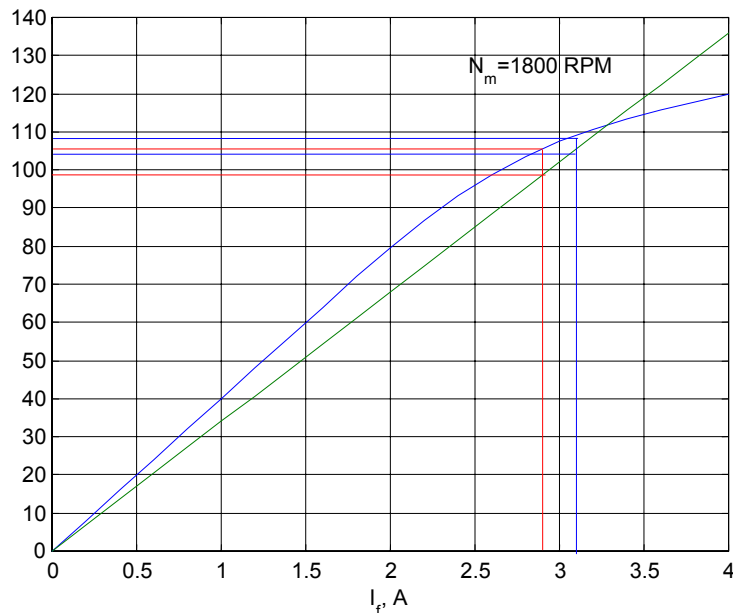Find the point on the characteristic where the difference between E_a and V_t is equal to the voltage drop



The answer will depend on your reading of the graph.


A voltage difference of 3.6V occurs when $E_a=110V$ and $V_t=106.4V$, as shown with the blue lines.

A voltage difference of 7.2V occurs when $E_a=106V$ and $V_t=98.8V$, as shown with the red lines.

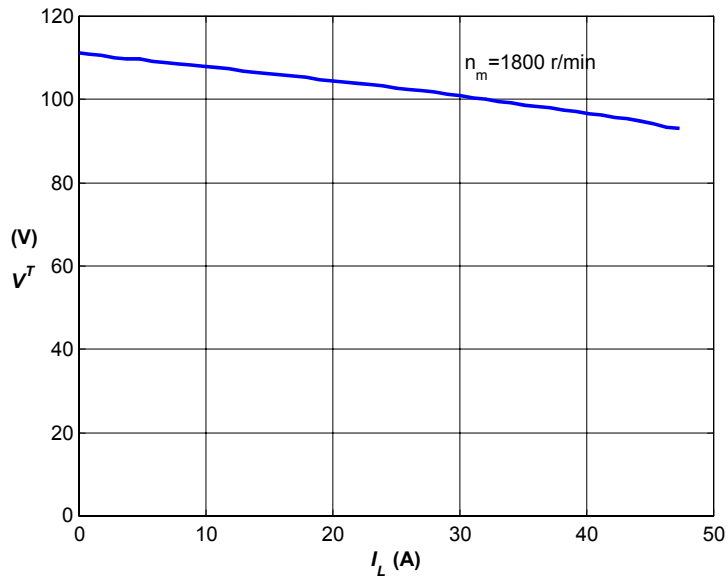(d) Calculate and plot the terminal characteristics of this generator with and without armature reaction

Basically repeat this process of part b over the full range of desired currents. The resulting plot is shown below.


Terminal Characteristic of a Shunt DC Generator, without Armature Reaction



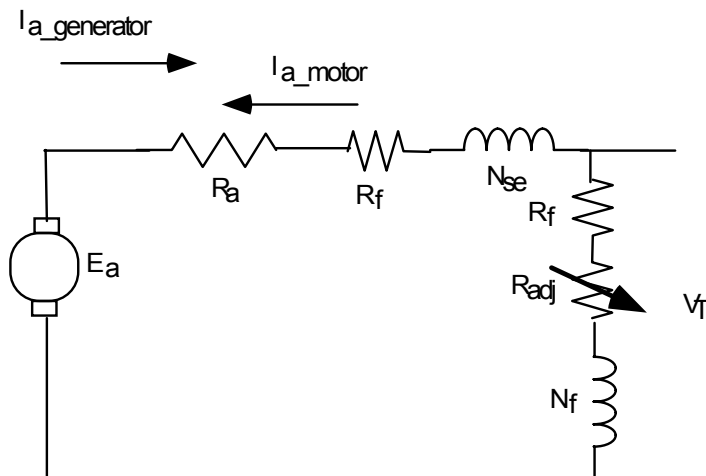4. A 120-V, 50-A cumulatively compounded dc generator has the following characteristics:


- $R_{series} := 0.20\text{ohm}$ $R_a + R_{se}$ $N_{se} := 15$ turns
- $R_{f_27} := 20\text{ohm}$ $N_{f_27} := 1000$ turns
- $R_{adj_27} := 10\text{ohm}$ Ranges from 0 to 30 ohms
- $n_m := 1800$ RPM

The machine has the magnetization curve shown in below. Its equivalent circuit is below. Answer the following questions about this machine assuming no armature reaction.



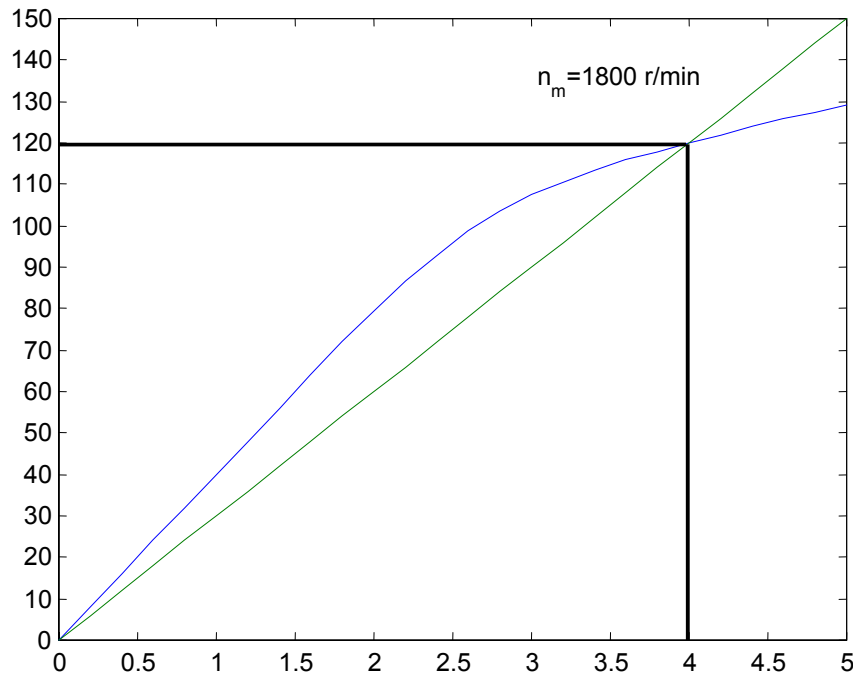(a) If the generator is operating at no load, what is its terminal voltage?

$$V_t = I_f \cdot (R_f + R_{adj}) = I_f \cdot 30$$



From the graph, $V_{t_noload} = E_{A_noload} = 120V$

(b) If the generator has an armature current of 20A, what is its terminal voltage?

$$I_{a_27} := 20A$$

Determine MMF from series winding, and then find the equivalent field current


$$MMF_{se} := N_{se} \cdot I_{a_27} \quad MMF_{se} = 300 \text{ Aturns}$$

$$I_{f_se} := \frac{MMF_{se}}{N_{f_27}} \quad I_{f_se} = 0.3 \text{ A}$$

Voltage drop, due to $I_a \cdot (R_a + R_{se})$

$$V_{ra20} := I_{a_27} \cdot (R_{series}) \quad V_{ra20} = 4 \text{ V}$$

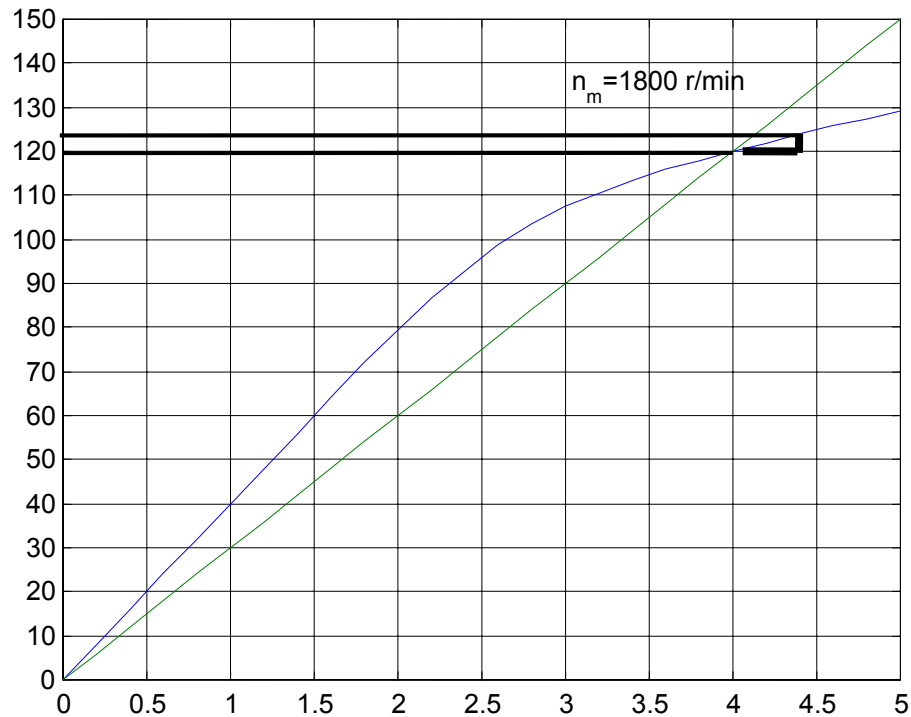Find a triangle that has sides with voltage equal to voltage drop and current equal to I_{f_se} . Notice that the I_{f_se} extends from the V_t line, not the E_a line. In this case the triangle will have a plus sign, I_{f_se} since cumulative compounded.



From the figure we see: $V_t=119V$ and $E_a= 123V$

(c) If the generator has an armature current of 40A, what is its terminal voltage?

$$I_{a_27c} := 40A$$

Determine MMF from series winding, and then find the equivalent field current


$$MMF_sec := N_{se} \cdot I_{a_27c} \quad MMF_sec = 600 \text{ Aurns}$$

$$I_{f_sec} := \frac{MMF_sec}{N_{f_27}} \quad I_{f_sec} = 0.6 A$$

Voltage drop, due to $I_a \cdot (R_a + R_{se})$

$$V_{ra20c} := I_{a_27c} \cdot (R_{series}) \quad V_{ra20c} = 8 V$$

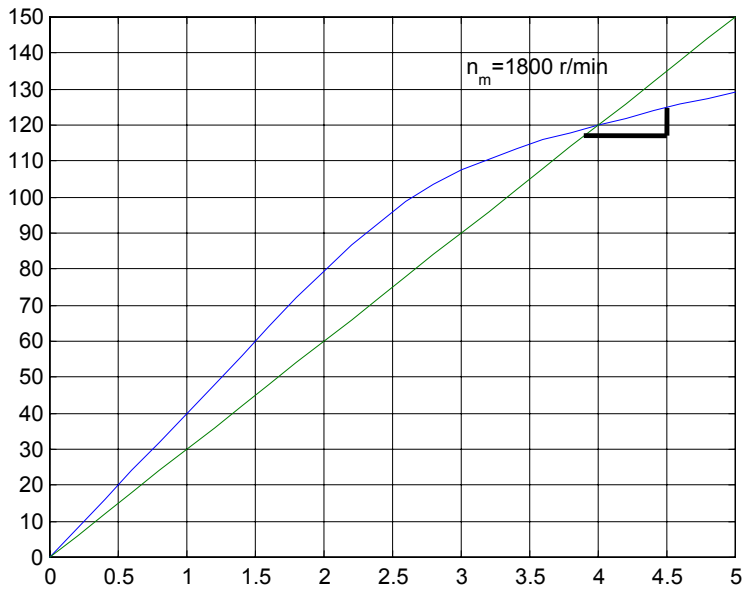Find a triangle that has sides with voltage equal to voltage drop and current equal to I_{f_se} . Notice that the I_{f_se} extends from the V_t line, not the E_a line. In this case the triangle will have a plus I_{f_se} since cumulative compounded.



From the figure we see: $V_t = 117$ V and $E_a = 125$ V

(d) Calculate and plot the terminal characteristics of this machine.

Basically repeat this process over the full range of desired currents. The resulting plot is shown below.

