

ECE 320: Homework #1

DUE DATE: By 5:00pm on Friday September 5.

Hand in to my mailbox, my office, or the homework collection box on the second floor of GJL (slot marked EE320).

1. Given a sinusoidal voltage source:

$$v_s = 170\cos(377t + 30\text{deg}) \text{ V}$$

Find the following:

- Maximum amplitude
- RMS magnitude
- Phase angle in radians
- Phase angle in milliseconds
- Period in milliseconds
- Frequency in Hertz

2. Express the following sums in Phasor form:

a. $v_1 = 170\cos(377t - 30\text{deg}) \text{ V} + 170\cos(377t + 30\text{deg}) \text{ V}$

b. $v_2 = 170\cos(377t - 30\text{deg}) \text{ V} + 155\cos(377t + 45\text{deg}) \text{ V}$

3. In each of the following, the 60Hz voltage appears across a black box, and the 60Hz current is entering the black box.

Calculate: P, Q, power factor, and state whether the black box is supplying or sinking real power.

a. $v_a = 300\cos(\omega t + 60\text{deg}) \text{ V}$ and $i_a = 20\cos(\omega t + 15\text{deg}) \text{ A}$

b. $v_a = 75\cos(\omega t - 15\text{deg}) \text{ V}$ and $i_a = 75\cos(\omega t + 60\text{deg}) \text{ A}$

c. $v_a = 200\cos(\omega t + 240\text{deg}) \text{ V}$ and $i_a = 10\cos(\omega t + 40\text{deg}) \text{ A}$

4. A 60Hz voltage source with a RMS magnitude to 500V, and an angle of 0 degrees, supplies 7500W. It is connected to a load that draws 2500W, and supplies 5000VARs through a line with a resistance of 20 Ohm.

- Determine the line current.
- Determine the inductive reactance X of the line such that the source neither delivers nor absorbs reactive power.

5. A 60Hz voltage source with a RMS magnitude to 7200V, and an angle of 0 degrees is connected to a series RL load with $R = 140 \text{ Ohm}$ and $jX = j500\text{Ohm}$ by a line with $R = 2 \text{ Ohm}$ and $jX = j20 \text{ Ohm}$.
- Calculate the voltage across the load
 - Calculate P and Q drawn by the load
 - Calculate P and Q supplied by the source
 - Now we want to connect a capacitor in parallel with the R-L load. Determine the capacitive reactance and the capacitance (in microFarads) such parallel combination has a unity power factor
 - Calculate the voltage across the load in part d.
 - Calculate P delivered to the load in part d. (compare this to P in part b).
 - Calculate P and Q supplied by the source in part d.