

## ECE 320: Homework #3

**DUE DATE:** By 5:00pm on Wednesday September 24.

1. A 20 kVA 8000/277-V distribution transformer has the following resistances and reactances:

$$\begin{aligned} R_p &:= 32\text{ohm} & R_s &:= 0.05\text{ohm} \\ X_p &:= 45\text{ohm} & X_s &:= 0.06\text{ohm} \\ R_c &:= 250\text{k}\Omega & X_m &:= 40\text{k}\Omega \end{aligned}$$

The excitation branch impedances are given referred to the high-voltage side of the transformer.

- Find the equivalent circuit of this transformer referred to the high-voltage side
  - Assume that this transformer is supplying rated load at 277V and 0.8 PF lagging. What is this transformer's input voltage? What is its voltage regulation?
  - What is the transformer's efficiency under the conditions of part (b)?
2. A 1000VA 230/115-V transformer has been tested to determine its equivalent circuit. The results of the test are shown below.

Open Circuit Test	Short Circuit Test
$V_{oc} := 230\text{V}$	$V_{sc} := 13.2\text{V}$
$I_{oc} := 0.45\text{A}$	$I_{sc} := 6.0\text{A}$
$P_{oc} := 30\text{W}$	$P_{sc} := 20.1\text{W}$

All data given were taken on the primary side of the transformer

- Find the equivalent circuit for the transformer referred to the low voltage side of the transformer.
  - Find the transformer's voltage regulation at rated conditions and (1) 0.8 PF lagging, (2) 1.0 PF and (3) 0.8 PF leading.
  - Determine the transformer's efficiency at rated conditions and unity power factor. Repeat at 0.8 PF lagging.
3. A 15kVA 8000/230-V distribution transformer has an impedance referred to the primary of  $80 + j300 \Omega$ . The components of the excitation branch referred to the primary side are  $R_c=350\text{k}\Omega$  and  $X_m=70\text{k}\Omega$
- If the primary voltage is 7967V and the load impedance is  $Z_L=3.2+j1.5 \Omega$ , what is the secondary voltage of the transformer? What is the voltage regulation of the transformer?
  - If the load is disconnected and a capacitor of  $-j3.5\Omega$  is connected in its place, what is the secondary voltage of the transformer? What is its voltage regulation under these conditions?
4. Why does the short-circuit test essentially show only  $i^2R$  losses and not excitation losses in a transformer?
5. Why does the open circuit test essentially show only excitation losses and not  $i^2R$  losses?