

Energy Systems I

Homework 8

Due by 5:00pm on Wednesday, December 3

1. Problem 7-2 in Mohan.
2. Problem 7-7 in Mohan.
3. Problem 7-8 in Mohan with I_o set at 1.0A instead of the value given in the problem. Plot the inductor current.
4. Problem 7-12 in Mohan.
5. Problem 7-13 in Mohan with I_o set at 1.0A instead of the value given in the problem. Plot the inductor current.