

EE/CompE 243
Examples (from Hw #1 and #2 in Spring 99)

1. Simplify each of the expression using one of the theorems

2.4(a) $A'B'C + (A'B'C)'$

Let $X = A'B'C$

$X + X' = 1$ Theorem (5)

Solution: 1

2.4(b) $A(B+C'D) + B + C'D$

$= A(B+C'D) + (B + C'D)$

Let $X = B+C'D$

Let $Y = A$

$XY + X = X$ Theorem (10)

Solution:

$B + C'D$

2. Multiply to obtain a Sum of Products

2.6(c) $(A + B'C + D')(B'C + D' + E)(A + E')(AD + E')$

$= (AB'C + AD' + AE + B'C + B'CD' + B'CE + B'CD' + D' + D'E)$
 $(AD + AE' + ADE' + E')$

$= (B'C + AD' + AE + B'CD' + B'CE + D')(AD + E')$

$= (B'C + D' + AE + B'CE)(AD + E')$

$= (B'C + D' + AE)(AD + E')$

$= AB'CD + B'CE' + D'E' + ADE$

Solution:

$AB'CD + B'CE' + D'E' + ADE$

2.6(d) $(A' + BE')(BE' + C + D)(E + C')$

$= (A'BE' + A'C + A'D + BE' + BCE' + BDE')(E + C')$

$= A'CE + A'DE + A'BC'E' + A'C'D + BC'E' + BC'DE'$

$= BC'E' + A'CE + A'DE + A'C'D$

Solution:

$BC'E' + A'CE + A'DE + A'C'D$

3. Factor each of the expression to obtain a Product of Sums

$$\begin{aligned} 2.9(b) \quad & WX' + WY'Z' + WYZ \\ &= W(X' + Y'Z' + YZ) \\ \text{Let } X &= X' + Y'Z' \\ &YZ = YZ \end{aligned}$$

Second Distributive Law

$$\begin{aligned} X + YZ &= (X + Y)(X + Z) \\ W[(X' + Y'Z') + Y] &= [(X' + Y'Z') + Z] \end{aligned}$$

Second Distributive Law

$$\begin{aligned} W[(Y + X' + Z')(Y + X' + Y')] &= [(Z + X' + Z')(Z + X' + Y')] \\ &= W(X' + Y + Z')(X' + Y' + Z) \end{aligned}$$

Solution:

$$W(X' + Y + Z')(X' + Y' + Z)$$


$$\begin{aligned} 2.9(e) \quad & AC'D + C'D' + A'D' \\ &= C'(AD + D') + A'D' \\ &= C'(D + D')(A + D') + A'D' && \text{2nd Distributive Law} \\ &= C'(A + D') + A'D' \\ &= [C'(A + D') + A'] [C'(A + D') + D'] && \text{2nd Distributive Law} \\ &= (A' + C')(A' + A + D')(C' + D')(A + D' + D') && \text{2nd Distributive Law} \\ &= (A + D')(C' + D')(A' + C') \end{aligned}$$

Solution:

$$(A + D')(C' + D')(A' + C')$$

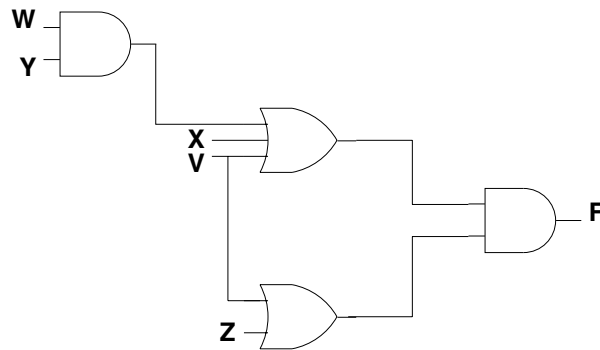4. Realize the function and draw the network using two OR gates and two AND gates

$$\begin{aligned}
 2.13 \quad F &= (V + W + X)(V + X + Y)(V + Z) \\
 &= (V + VX + VY + WV + WX + WY + VX + X + XY)(V + Z) \\
 &= (V + X + WY)(V + Z)
 \end{aligned}$$



5. Finding the complement of each expression

$$\begin{aligned}
 3.4(a) \quad &(a'b + 1)(cd + e') + f(g' + 0) + h \\
 &= [(a'b + 1)(cd + e') + f(g' + 0) + h]' \\
 &= [(a'b + 1)' + (cd + e')'] [f' + (g' + 0)'h'] \\
 &= [(a + b') \cdot 0 + (c' + d')e] [f' + (g \cdot 1)]h'
 \end{aligned}$$

Solution:

$$[(a + b') \cdot 0 + (c' + d')e] [f' + (g \cdot 1)]h'$$

$$\begin{aligned}
 3.4(b) \quad &[a'b'(c + d')(c' + d) + ab(c'd + cd')] \\
 &= [(a'b')' + (c + d')' + (c' + d)'] [(ab)' + (c'd)'(cd)'] \\
 &= [a + b + (c'd) + cd'] [a' + b' + (c + d')(c' + d)]
 \end{aligned}$$

Solution:

$$[a + b + (c'd) + cd'] [a' + b' + (c + d')(c' + d)]$$

6. Finding the dual of each expression

$$3.6(a) \quad (a'b + 1)(cd + e') + f(g' + 0) + h$$

The dual is found by replacing AND by OR, OR by AND, 0 by 1 and 1 by 0

Solution:

$$[(a' + b)0 + (c + d)e'] [f + (g' \cdot 1)]h$$

$$3.6(b) \quad = a'b'(c + d')(c' + d) + ab(c'd + cd')$$

Solution:

$$[a' + b' + cd' + c'd][a + b + (c' + d)(c + d)']$$

7. Multiplying to obtain a sum of four terms

$$\begin{aligned} 3.10(a) \quad & (A' + B' + C')(A + C + D')(A + B)(A' + D)(A' + C + D) \\ & = (A'C + A'D' + AB' + B'C + B'D' + AC' + C'D')(AD + A'B + BD)(A' + C + D) \\ & = (A'C + A'D' + AB' + B'C + B'D' + AC' + C'D') \\ & \quad (ADC + AD + A'B + A'BC + A'BD + A'BD + BCD + BD') \\ & = (A'C + A'D' + AB' + B'C + B'D' + AC' + C'D')(AD + A'B + BD) \\ & = A'BC + A'BCD + A'BD' + AB'D + AB'CD + AC'D + ABC'D + A'BC'D' \\ & = AB'D + AC'D + A'BC + A'BD' \end{aligned}$$

Solution:

$$AB'D + AC'D + A'BC + A'BD'$$

8. 3.21(a) Show that $x \oplus y = (x \equiv y)'$

$$\begin{aligned} x \oplus y &= x'y + xy' \\ &= (x'y + x)(x'y + y') \\ &= (x' + x)(y + x)(x' + y')(y + y') \\ &= (x + y)(x' + y') \\ &= (xy + x'y')' \\ &= (x \equiv y)' \end{aligned}$$

$$\text{Since } X + YZ = (X + Y)(X + Z)$$

Solution:

$$x \oplus y = (x \equiv y)'$$

3.21(b) Realize $a'b'c' + a'bc + ab'c + abc'$ using only two input equivalence gates

$$\begin{aligned} & a'b'c' + a'bc + ab'c + abc' \\ & c'(a'b' + ab) + c(a'b + ab') \\ & c'(a \equiv b) + c(a \oplus b) \\ & c'(a \equiv b) + c(a \equiv b)' \\ & c \oplus (a \equiv b) \end{aligned}$$

$$\text{Since } X \oplus Y = (X \equiv Y)'$$

Solution:

$$[(a \equiv b) \equiv c]'$$

9. Express f as a minterm and maxterm expansion using m and M notation.

$$f(a, b, c) = a'(b + c')$$

a	b	c	f	f'
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$$a'(b + c') = a'b + a'c'$$

(a) Expressing f as a minterm expansion

$$f = \sum m(0, 2, 3)$$

Form a summation of the input combinations when $f = 1$

(b) Expressing f as a maxterm expansion

$$f = \prod M(1, 4, 5, 6, 7)$$

Form a product of the input combinations when $f = 0$

(c) Expressing f' as a minterm expansion

$$f' = \sum m(1, 4, 5, 6, 7)$$

Form a summation of the input combinations when $f' = 1$

(d) Expressing f' as a maxterm expansion

$$f' = \prod M(0, 2, 3)$$

Form a product of the input combinations when $f' = 0$

10. Express each of the following as minterm and maxterm expansions using algebraic and m (or M) notation.

(a) $f(a, b, c) = (b + c)(a' + b + c')(a + c)$

a	b	c	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$f = \sum m(1, 3, 6, 7)$$

$$= a'b'c + a'bc + abc' + abc$$

$$= a'c + ab$$

$$f = \prod M(0, 2, 4, 5)$$

$$= (a + b + c)(a + b' + c)(a' + b + c)(a' + b + c')$$

$$= (a + c)(a' + b)$$

(b) $f(x, y, z) = \sum m(0, 3, 4, 7)$

a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$f = \sum m(0, 3, 4, 7)$$

$$= x'y'c' + x'yz + xy'z' + xyz$$

$$= y'z' + yz$$

$$= y \equiv z$$

$$f = \prod M(1, 2, 5, 6)$$

$$= (x + y + z')(x + y' + z)(x' + y + z')(x' + y' + z)$$

$$= (y + z')(y' + z)$$

$$= y \equiv z$$

11. Express the minterm and maxterm expansions for the following: (use m and M notation). (a)

$$f(a, b, c, d) = c(a' + b) + b'd$$

a	b	c	d	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

$$f = \sum m(1, 2, 3, 6, 7, 9, 11, 14, 15)$$

$$f = a'b'c'd' + a'b'cd' + a'b'cd + a'bcd' + a'bcd + ab'c'd + ab'cd + abcd' + abcd$$

$$= a'b'c'd' + a'b'c + a'bc + ab'd + abc$$

$$= a'b'c'd' + a'c + ab'd + abc$$

$$= b'd(a'c' + a) + a'c + abc$$

$$f = \prod M(0, 4, 5, 8, 10, 12, 13)$$

$$f = (a + b + c + d)(a + b' + c + d)(a + b' + c + d')(a' + b + c + d)$$

$$(a' + b + c' + d)(a' + b' + c + d)(a' + b' + c + d)$$

$$= (a + c + d)(b' + c + d')(a' + b + d)(a' + b' + c + d)$$

(b) $g(w, x, y, z) = xy'z + w'xy' + yz' + w'x'z$

w	x	y	z	g
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$g = \sum m(1, 2, 3, 4, 5, 6, 10, 13, 14)$$

$$g = w'x'y'z' + w'x'yz' + w'x'yz + w'xyz + w'xy'z + w'xyz' + wx'y'z' + wxy'z + wxyz$$

$$g = \prod M(0, 7, 8, 9, 11, 12, 15)$$

$$g = (w + x + y + z)(w + x' + y' + z')(w' + x + y + z)(w' + x + y + z')(w' + x + y' + z')$$

$$= (x + y + z)(x' + y' + z')(w' + x + z')(w' + x' + y + z)$$

12. Express f from the table below, as a minterm expansion (use m) and as a maxterm expansion (use M).

a	b	c	d	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

$$f = \sum m(0, 2, 4, 5, 7, 8, 9, 11, 12, 14)$$

$$\begin{aligned} f &= a'b'c'd' + a'b'cd' + a'bc'd' + a'bc'd + a'bcd + ab'c'd' + ab'c'd \\ &\quad + ab'cd + abc'd' + abcd' \\ &= a'b'd' + a'bc' + ab'c' + abd' + a'bcd + ab'cd \end{aligned}$$

$$f = \prod M(1, 3, 6, 10, 13, 15)$$

$$\begin{aligned} f &= (a+b+c+d')(a+b+c'+d')(a+b'+c'+d)(a'+b+c'+d) \\ &\quad (a'+b'+c+d')(a'+b'+c'+d') \\ &= (a+b+d')(a+b'+c'+d)(a'+b+c'+d)(a'+b'+d') \end{aligned}$$