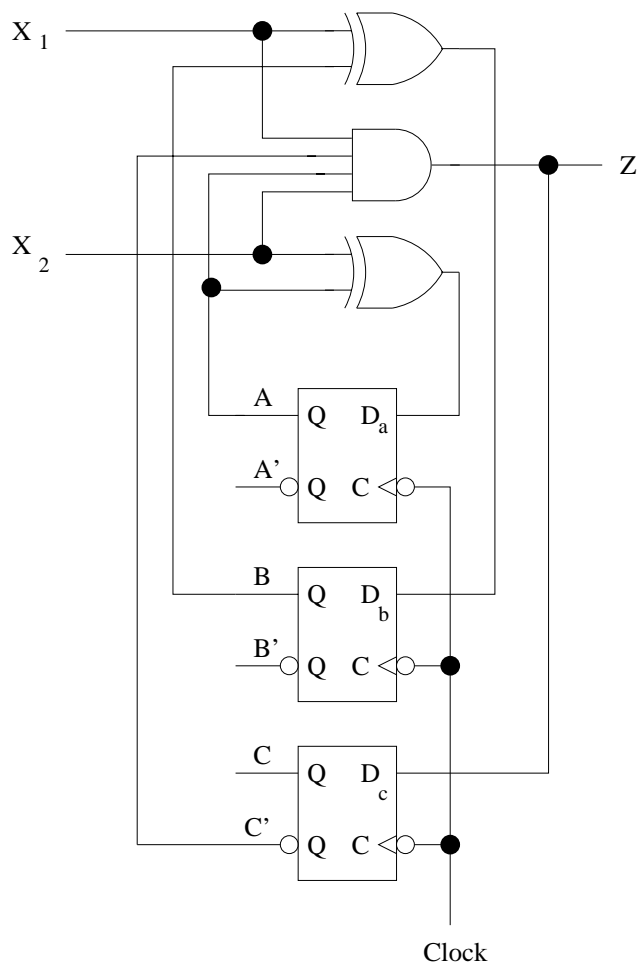


COE/EE 243

Sample Exam #4 Solution

1. (16 pts) Find the transition table and the state table for the Mealy sequential circuit below.




$$D_C = Z = X_1 \cdot X_2 \cdot A \cdot C'$$

$$D_A = X_2 \oplus A$$

$$D_B = X_1 \oplus B$$

ABC	A + B + C +				Z				ABC	A + B + C +			
	X <sub>1</sub> X <sub>2</sub> = 00	01	11	10	00	01	11	10		00	01	11	10
000	000	100	110	010	0	0	0	0	S <sub>0</sub>	S <sub>0</sub>	S <sub>4</sub>	S <sub>6</sub>	S <sub>2</sub>
001	000	100	110	010	0	0	0	0	S <sub>1</sub>	S <sub>0</sub>	S <sub>4</sub>	S <sub>6</sub>	S <sub>2</sub>
010	010	110	100	000	0	0	0	0	S <sub>2</sub>	S <sub>2</sub>	S <sub>6</sub>	S <sub>4</sub>	S <sub>0</sub>
011	010	110	100	000	0	0	0	0	S <sub>3</sub>	S <sub>2</sub>	S <sub>6</sub>	S <sub>4</sub>	S <sub>0</sub>
100	100	000	011	110	0	0	1	0	S <sub>4</sub>	S <sub>4</sub>	S <sub>0</sub>	S <sub>3</sub>	S <sub>6</sub>
101	100	000	010	110	0	0	0	0	S <sub>5</sub>	S <sub>4</sub>	S <sub>0</sub>	S <sub>2</sub>	S <sub>6</sub>
110	110	010	001	100	0	0	1	0	S <sub>6</sub>	S <sub>6</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>4</sub>
111	110	010	000	100	0	0	0	0	S <sub>7</sub>	S <sub>6</sub>	S <sub>2</sub>	S <sub>0</sub>	S <sub>4</sub>

 2. (8 pts) The sequential circuit below yields an output sequence of  $Z = 11011111$  when you apply the input sequence  $X = 01101010$ . What is the starting state  $A$ ?



Since  $X = 0$  initially and  $Z = 1$ , the  $A \oplus X = Z = 1$  requires that  $A=1$  initially.

3. (16 pts) Determine the D flip-flop realization of the sequential circuit specified by the following transition table. Write the combinational logic expressions for the flip-flop inputs and draw the logic circuit diagram.

ABC	A+B+C+		Z	
	X=0	X=1	X=0	X=1
000	001	100	0	0
001	000	010	1	1
010	001	010	0	1
011	010	100	0	0
100	011	000	1	0
101	---	---	-	-
110	---	---	-	-
111	---	---	-	-

Da

AB	00	01	11	10
CX	00	01	11	10
00	0	0	X	0
01	1	0	X	0
11	0	1	X	X
10	0	0	X	X

Dc

AB	00	01	11	10
CX	00	01	11	10
00	1	1	X	1
01	0	0	X	0
11	0	0	X	X
10	0	0	X	X

Db

AB	00	01	11	10
CX	00	01	11	10
00	0	0	X	1
01	0	1	X	0
11	1	0	X	X
10	0	1	X	X

Z


AB	00	01	11	10
CX	00	01	11	10
00	0	0	X	1
01	0	1	X	0
11	1	0	X	X
10	1	0	X	X

$$A+ = D_A = BCX + A'B'C'X$$


$$B+ = D_B = AX' + BCX' + BC'X + B'CX$$

$$C+ = D_C = C'X'$$

$$Z = AX' + B'C + BC'X$$

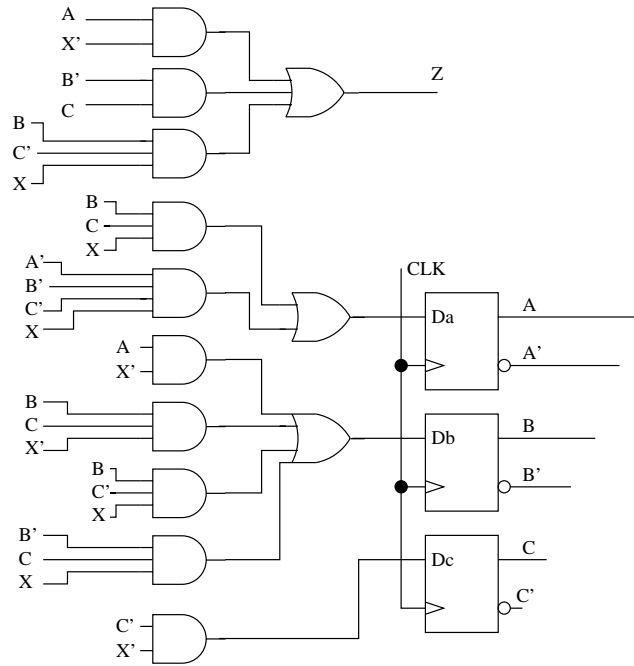

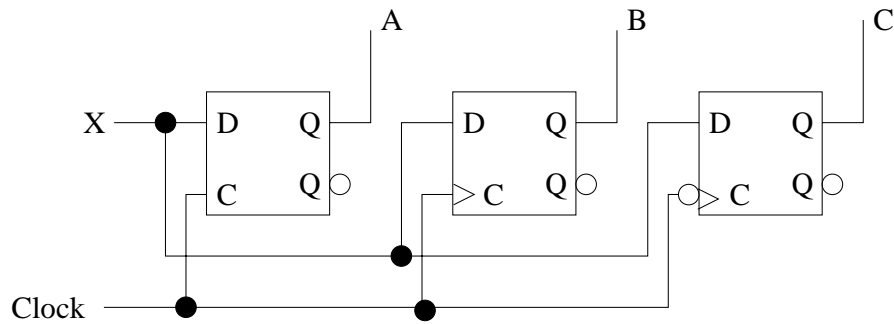4. (10 pts) The circuit below has three D flip-flops, one is level triggered (i.e. triggers based on the level of the clock). The other two are edge triggered, one on the positive-edge and the other on the negative-edge. Complete the timing diagram by filling in the waveforms for A, B, and C.



Propagation delay is assumed to be 1/2 division

