

## Open Stator Circuit Voltage Build-up

### I. Define the Situation

A synchronous generator is rotating at a constant angular velocity,  $\omega$ .

The rotor angle,  $\theta_r$ , is given by the following.  $\theta_r = \omega \cdot t + \theta_{r0}$

The three stator windings are open-circuited; i.e.,  $i_a = i_b = i_c = 0$

A DC voltage is applied to the field voltage at time equal to zero; i.e.,

$$v_f = V_{fdc} \quad \text{for time greater or equal to zero}$$

Initial field current is zero.

### II. Determine $i_f(t)$ .

$$V_{fdc} = R_{fd} \cdot i_f(t) + \frac{d}{dt} \psi_f(t) \quad (1)$$

$$\psi_f(t) = L_{ff} \cdot i_f(t) \quad (2)$$

Substitute Eq. 2 in to Eq. 1.

$$V_{fdc} = R_{fd} \cdot i_f(t) + \frac{d}{dt} (L_{ff} \cdot i_f(t)) \quad (3)$$

$L_{ff}$  is a constant w.r.t. time.

$$V_{fdc} = R_{fd} \cdot i_f(t) + L_{ff} \cdot \frac{d}{dt} i_f(t) \quad (4)$$

The solution of Eq. 4 is given below.

$$i_f(t) = \frac{V_{fdc}}{R_f} \cdot \left( 1 - e^{-\frac{t}{\tau_f}} \right) \quad (5)$$

where  $\tau_f = \frac{L_{ff}}{R_f}$

III. Determine  $v_a(t)$ .

$$v_a(t) = \frac{d}{dt}\psi_a(t) \quad (6)$$

$$\psi_a(t) = L_{af}(t) \cdot i_f(t) \quad (7)$$

$$L_{af}(t) = L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0}) \quad (8)$$

Substitute Eq. 8 in to Eq. 7.

$$\psi_a(t) = L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0}) \cdot i_f(t) \quad (9)$$

Substitute Eq. 9 in to Eq. 6.

$$v_a(t) = \frac{d}{dt}(L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0}) \cdot i_f(t)) \quad (10)$$

Using the product rule of differentiating yields:

$$v_a(t) = i_f(t) \cdot \frac{d}{dt}(L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0})) \dots \\ + L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0}) \cdot \left( \frac{d}{dt} i_f(t) \right) \quad (11)$$

$$v_a(t) = -i_f(t) \cdot \omega \cdot L_{sf} \cdot \sin(\omega \cdot t + \theta_{r0}) \dots \\ + L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0}) \cdot \frac{d}{dt} \left[ \frac{V_{fdc}}{R_f} \cdot \left( 1 - e^{-\frac{t}{\tau_f}} \right) \right] \quad (12)$$

$$v_a(t) = - \left[ \frac{V_{fdc}}{R_f} \cdot \left( 1 - e^{-\frac{t}{\tau_f}} \right) \right] \cdot \omega \cdot L_{sf} \cdot \sin(\omega \cdot t + \theta_{r0}) \dots \\ + L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0}) \cdot \frac{V_{fdc}}{\tau_f \cdot R_f} \cdot e^{-\frac{t}{\tau_f}} \quad (13)$$

$$v_a(t) = -\frac{V_{fdc}}{R_f} \cdot \left(1 - e^{-\frac{t}{\tau_f}}\right) \cdot \omega \cdot L_{sf} \cdot \sin(\omega \cdot t + \theta_{r0}) \dots$$

$$+ L_{sf} \cdot \cos(\omega \cdot t + \theta_{r0}) \cdot \frac{V_{fdc}}{L_f} \cdot e^{-\frac{t}{\tau_f}} \quad (14)$$

$$v_a(t) = -\frac{V_{fdc}}{R_f} \cdot \left(1 - e^{-\frac{t}{\tau_f}}\right) \cdot \omega \cdot L_{sf} \cdot \sin(\omega \cdot t + \theta_{r0}) \dots$$

$$+ V_{fdc} \cdot \frac{L_{sf}}{L_f} \cdot e^{-\frac{t}{\tau_f}} \cdot \cos(\omega \cdot t + \theta_{r0}) \quad (15)$$

or

$$v_a(t) = -\frac{V_{fdc}}{R_f} \cdot \omega \cdot L_{sf} \cdot \sin(\omega \cdot t + \theta_{r0}) \dots$$

$$+ V_{fdc} \cdot e^{-\frac{t}{\tau_f}} \cdot \left( \frac{\omega \cdot L_{sf}}{R_f} \cdot \sin(\omega \cdot t + \theta_{r0}) + \frac{L_{sf}}{L_f} \cdot \cos(\omega \cdot t + \theta_{r0}) \right) \quad (16)$$

## IV. Graph to Visualize

$$V_{fdc} := 140 \cdot \text{V} \quad R_f := 0.20 \cdot \Omega \quad L_f := 1.4 \cdot \text{H} \quad L_{sf} := 0.0743 \cdot \text{H} \quad \omega := 377 \cdot \frac{\text{rad}}{\text{sec}}$$

$$\frac{V_{fdc}}{R_f} = 700 \text{ A} \quad \frac{\sqrt{3}}{\sqrt{2}} \cdot \frac{V_{fdc}}{R_f} \cdot \omega \cdot L_{sf} = 24.015 \text{ kV} \quad \text{A 24 kV machine.}$$

$$\tau_f := \frac{L_f}{R_f} \quad \tau_f = 7 \text{ s} \quad \theta_{r0} := \frac{-\pi}{2}$$

$$v_{a1}(t) := - \left[ \frac{V_{fdc}}{R_f} \cdot \left( 1 - e^{-\frac{t}{\tau_f}} \right) \right] \cdot \omega \cdot L_{sf} \cdot \sin(\omega \cdot t + \theta_{r0})$$

$$\frac{V_{fdc}}{R_f} \cdot \omega \cdot L_{sf} = 19.608 \text{ kV}$$

$$v_{a2}(t) := V_{fdc} \cdot \frac{L_{sf}}{L_f} \cdot e^{-\frac{t}{\tau_f}} \cdot \cos(\omega \cdot t + \theta_{r0})$$

$$V_{fdc} \cdot \frac{L_{sf}}{L_f} = 7.43 \text{ V}$$

$$v_a(t) := v_{a1}(t) + v_{a2}(t)$$

The transformer voltage term is negligible compared to the speed voltage term.





