
ECE 320 & ECE 329

BACKGROUND STUDY IN ENERGY SYSTEMS **ENERGY SYSTEMS I**

SESSION no. 4

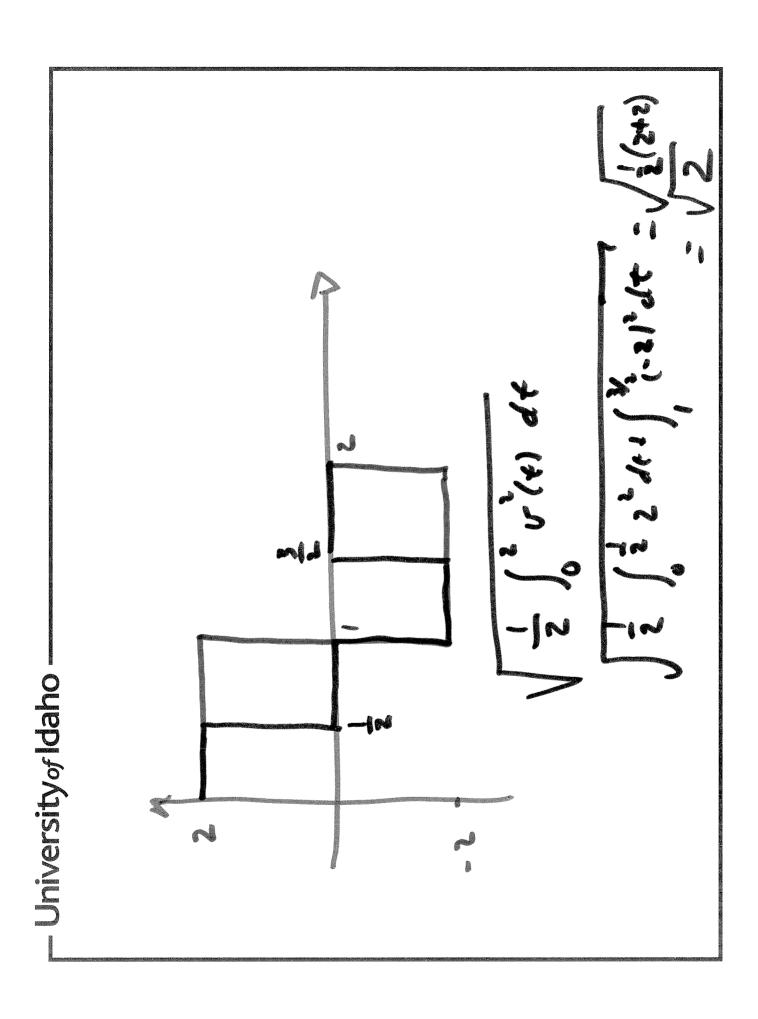

University of Idaho -


(20) (24) (6.6)


- University of Idaho -

(97)(32)(99)

3


— University₀fIdaho —

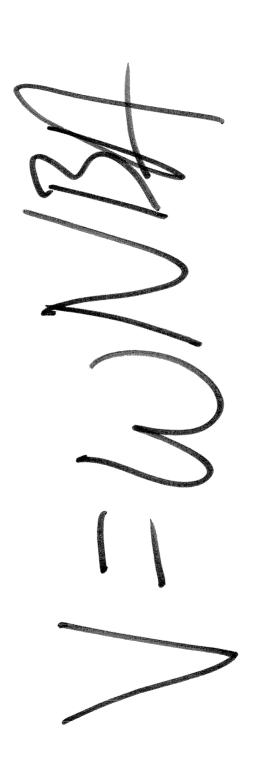


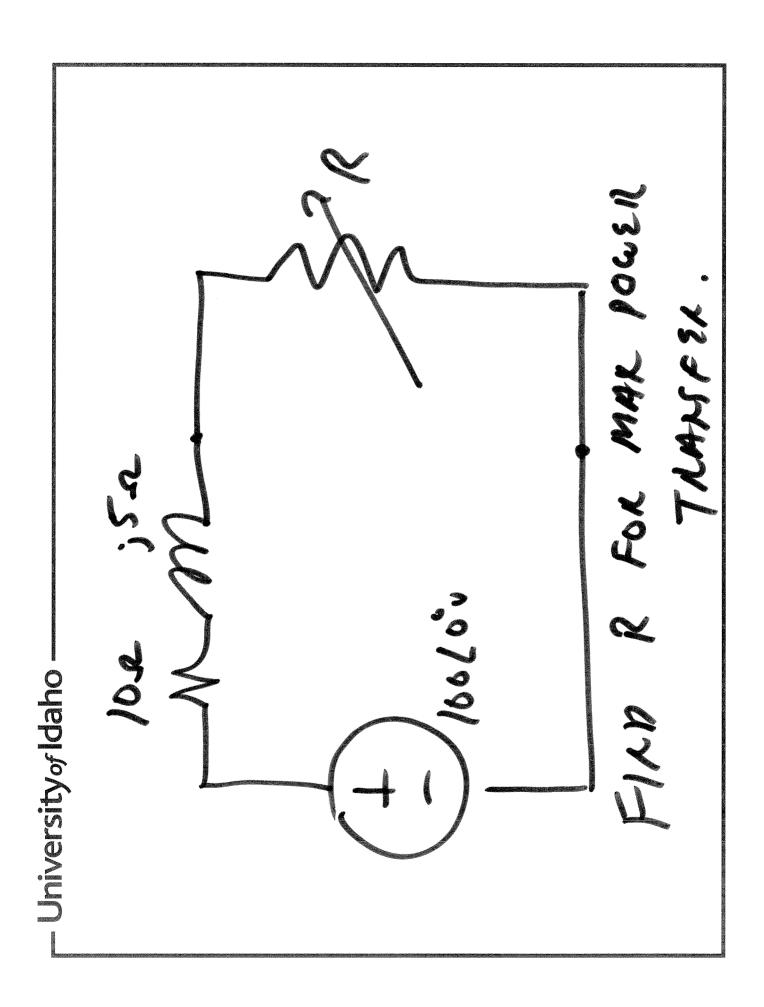

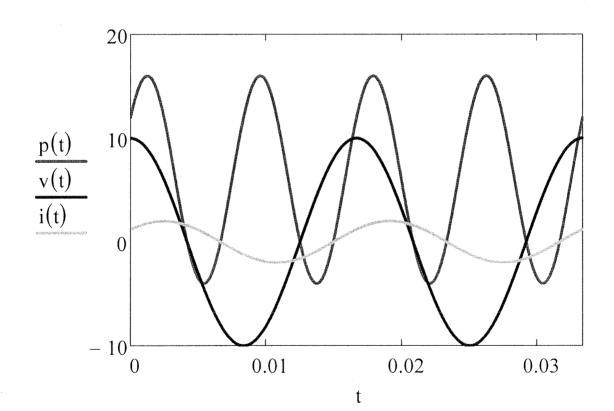Example Double Frequency Power Term. For a voltage of $10 \cos(\omega t)$ Volts and a current of $2\cos(\omega t - \theta)$ Amps, find the power as a function of time. Vary the power factor over its range to see if there is any effect on the power output.


$$\begin{aligned} \text{pf} &:= 0.6 & \theta &:= a\cos(\text{pf}) \\ v(t) &:= 10 \cdot \cos(\omega \cdot t) \cdot V \\ i(t) &:= 2 \cdot \cos(\omega \cdot t - \theta) \cdot A & \omega &= 376.991 \frac{\text{rad}}{\text{sec}} \\ p(t) &:= v(t) \cdot i(t) & \text{sec} \end{aligned}$$




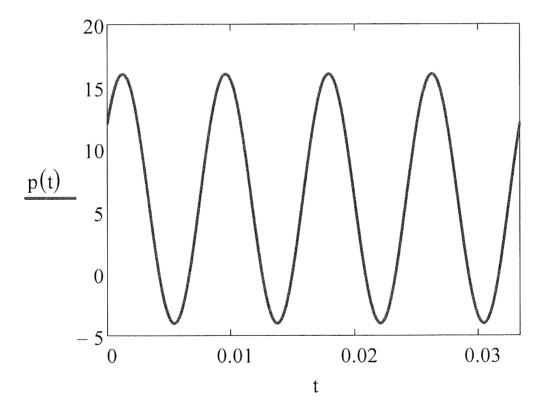

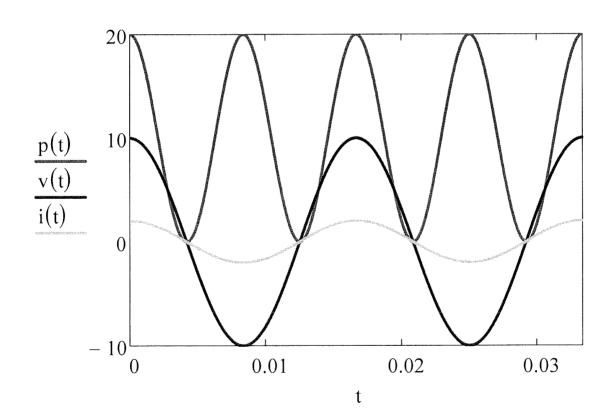Example Double Frequency Power Term. For a voltage of 10 $cos(\omega t)$ Volts and a current of $2cos(\omega t-\theta)$ Amps, find the power as a function of time. Vary the power factor over its range to see if there is any effect on the power output.


$$\begin{aligned} \text{pf} &:= 1.0 & \theta &:= a\cos(\text{pf}) \\ v(t) &:= 10 \cdot \cos(\omega \cdot t) \cdot V \\ i(t) &:= 2 \cdot \cos(\omega \cdot t - \theta) \cdot A & \omega &= 376.991 \frac{\text{rad}}{\text{sec}} \\ p(t) &:= v(t) \cdot i(t) & \text{sec} \end{aligned}$$




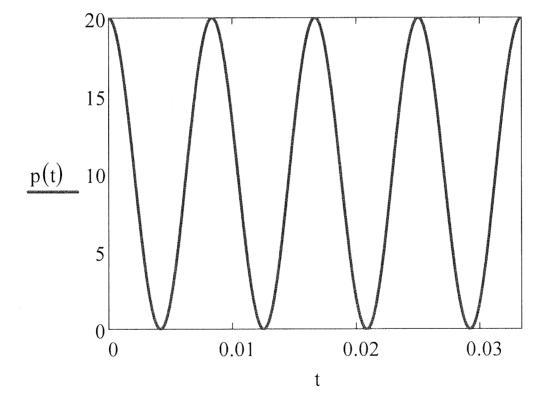

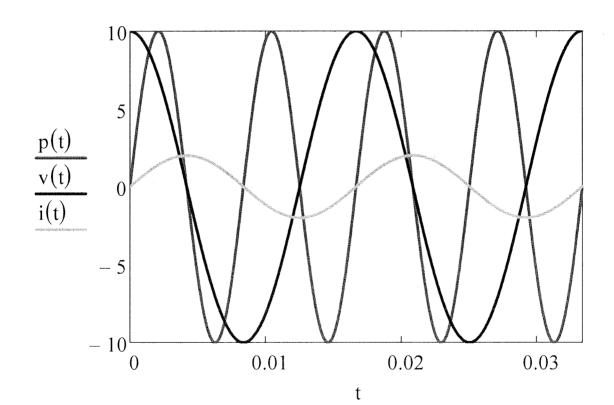Example Double Frequency Power Term. For a voltage of 10 $cos(\omega t)$ Volts and a current of $2cos(\omega t - \theta)$ Amps, find the power as a function of time. Vary the power factor over its range to see if there is any effect on the power output.


$$\begin{aligned} \text{pf} &:= 0 & \theta := a\cos(\text{pf}) \\ v(t) &:= 10 \cdot \cos(\omega \cdot t) \cdot V \\ i(t) &:= 2 \cdot \cos(\omega \cdot t - \theta) \cdot A & \omega &= 376.991 \frac{\text{rad}}{\text{sec}} \\ p(t) &:= v(t) \cdot i(t) & \text{sec} \end{aligned}$$




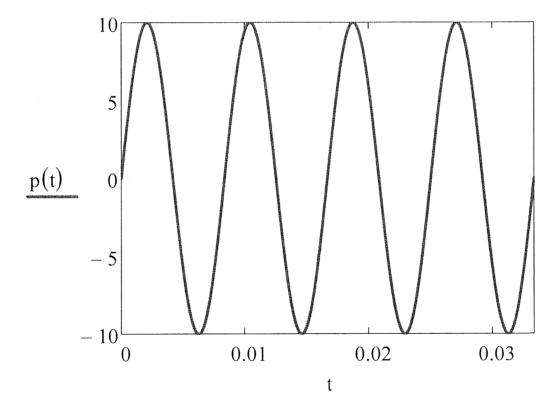

Example Double Frequency Power Term. For a voltage of 10 $cos(\omega t)$ Volts and a current of $2cos(\omega t-\theta)$ Amps, find the power as a function of time. Vary the power factor over its range to see if there is any effect on the power output.

$$\begin{aligned} \text{pf} &:= 0.6 & \theta &:= -\text{acos}(\text{pf}) \\ v(t) &:= 10 \cdot \text{cos}(\omega \cdot t) \cdot \text{V} \\ i(t) &:= 2 \cdot \text{cos}(\omega \cdot t - \theta) \cdot \text{A} \\ p(t) &:= v(t) \cdot i(t) \end{aligned} \qquad \begin{aligned} \omega &:= 2 \cdot \pi \cdot 60 \cdot \frac{\text{rad}}{\text{sec}} \\ \omega &= 376.991 \frac{\text{rad}}{\text{sec}} \end{aligned}$$

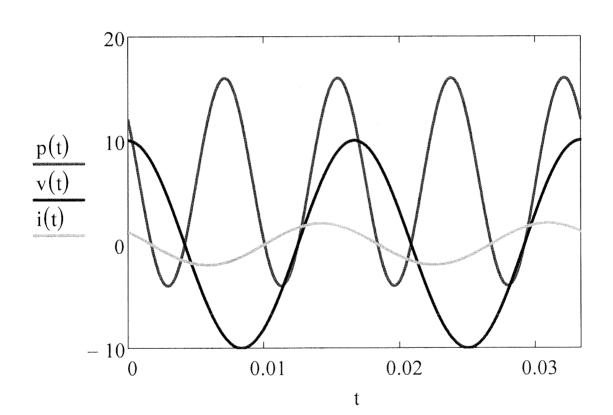

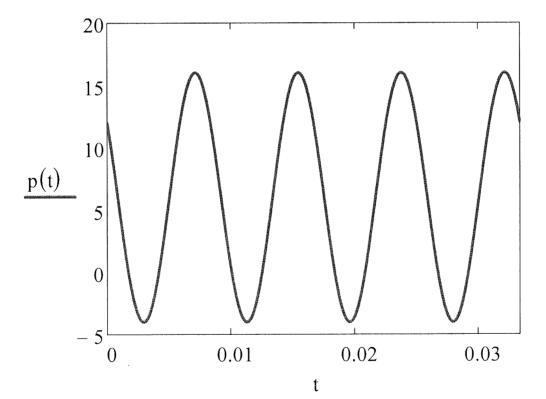

ECE 320

Energy Systems I

Lesson 4

AC Power Examples